


# Real Diode Analysis

Wednesday, March 20, 2024

4:09 PM




Exam II is on Friday March 29 in class.

→ Section 4 & 5

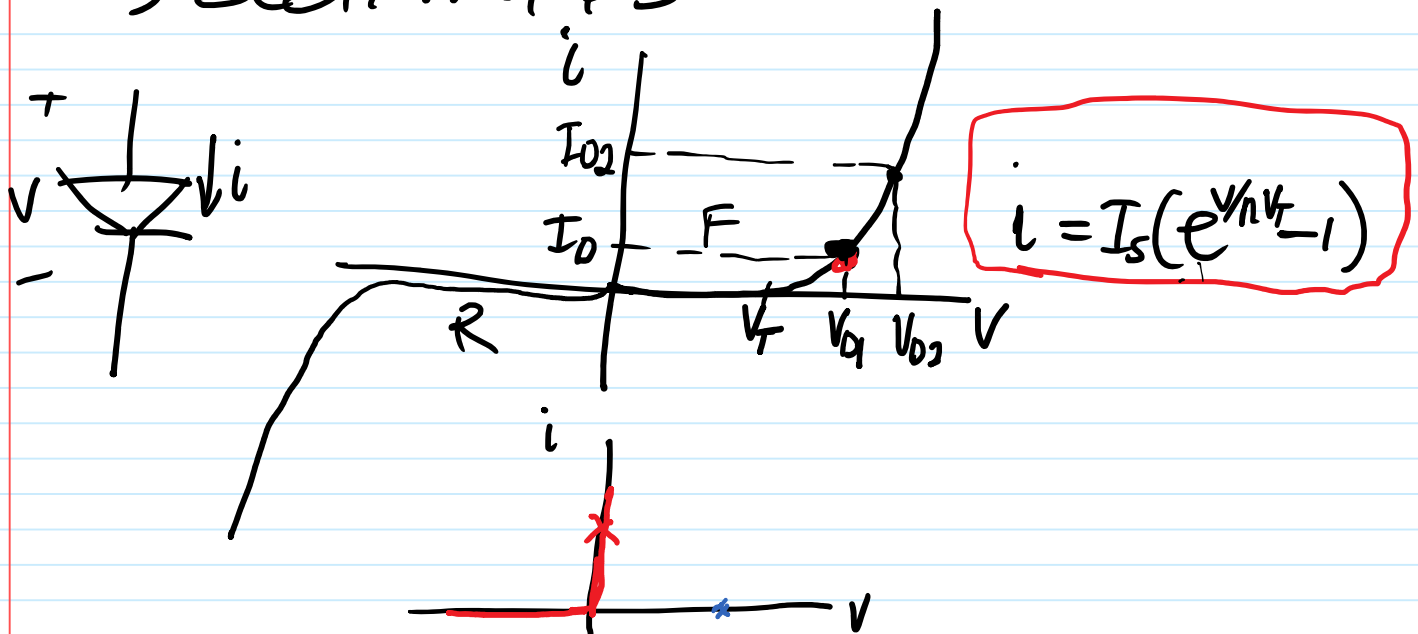

$$V_2 - V_1 = nV_T \ln(I_2/I_1)$$

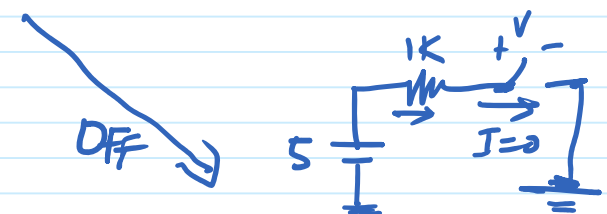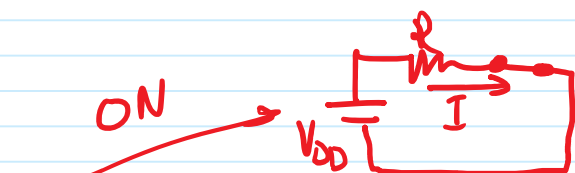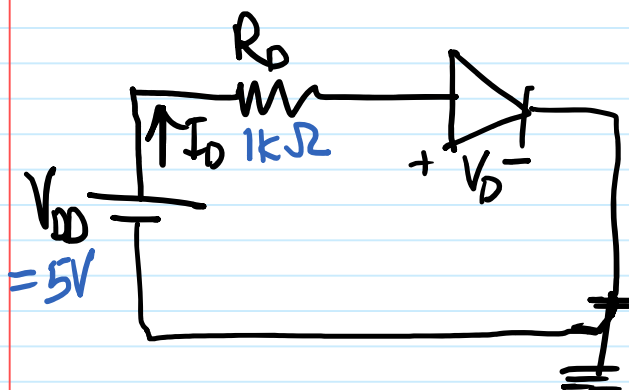
$$I = \frac{5-0}{1K} = 5mA \quad \checkmark OK$$



$$I_0 = \frac{V_{DD} - V_{D1}}{R_0} \quad \text{--- (1)}$$

$$V = 5 - 0 = 5V \quad \checkmark OK$$
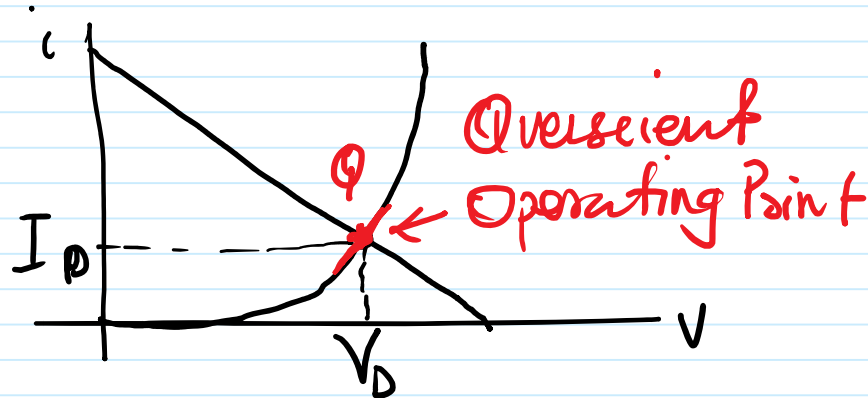
$$V_{D2} - V_{D1} = nV_T \ln(I_{D2}/I_{D1})$$



### Iterative analysis

- Start with a point on the I-V curve
- Iterate through  $I_D$  and  $V_D$  solutions
- Stop when  $I_D, V_D$  stop changing
- Always use 3 decimal places.

• Apply

$$I_{D1}, V_{D1} = 1\text{mA}, 0.7\text{V} \quad (1\text{mA diode})$$

$$I_{D1} = \frac{V_{DD} - V_{D1}}{R_D} = \frac{5 - 0.7}{1\text{K}} = 4.300\text{mA}$$

$$V_{D2} = V_{D1} + V_T \ln\left(\frac{I_{D2}}{I_{D1}}\right) = 0.7 + 0.025 \ln\left(\frac{4.3\text{mA}}{1\text{mA}}\right)$$

$$V_{D2} = 0.7 + 0.036 = \underline{0.736\text{V}}$$


$$I_{D2} = \frac{5 - 0.736}{1\text{K}} = 4.264\text{mA}$$

$$I_{D2} = \frac{5 - 0.736}{1k} = 4.264 \text{ mA}$$

$$V_{D3} = 0.7 + 0.025 \ln\left(\frac{4.264}{1}\right) = \underline{\underline{0.736 \text{ V}}} \text{ stop!}$$

$$I_0, V_0 \equiv 4.264 \text{ mA}, 0.736 \text{ V}$$

Another Example (1mA, 0.7V)

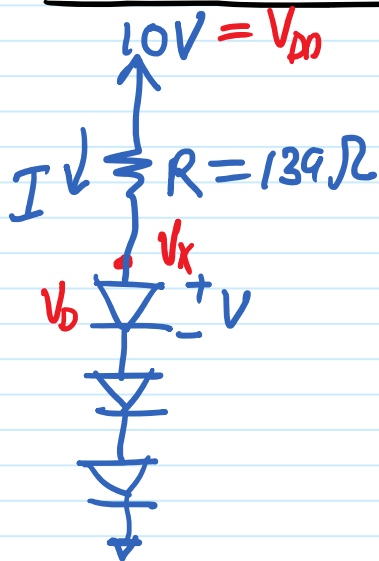

$$V_2 - V_1 = nV_T \ln\left(\frac{I_2}{I_1}\right) \quad \text{--- (1)}$$

$$I = \frac{V_{DD} - V_x}{R} = \frac{V_{DD} - 3V_0}{R}$$

$$I = \frac{10 - 3 \times 0.7}{139} = 56.830 \text{ mA}$$

$$V_2 = 0.7 + 0.025 \ln\left(\frac{56.830}{1}\right) = \underline{\underline{0.801 \text{ V}}}$$

$$I_2 = \frac{10 - 3 \times 0.801}{139} = \underline{\underline{54.650 \text{ mA}}}$$

$$V_3 = 0.7 + 0.025 \ln\left(\frac{54.65}{1}\right) = 0.800 \text{ V}$$

$$I_3 = \frac{10 - 3 \times 0.8}{139} = 54.680 \text{ mA}$$

$$V_4 = 0.7 + 0.025 \ln(54.28) = 0.700 \text{ V} = \text{stop}$$

## Linearization

