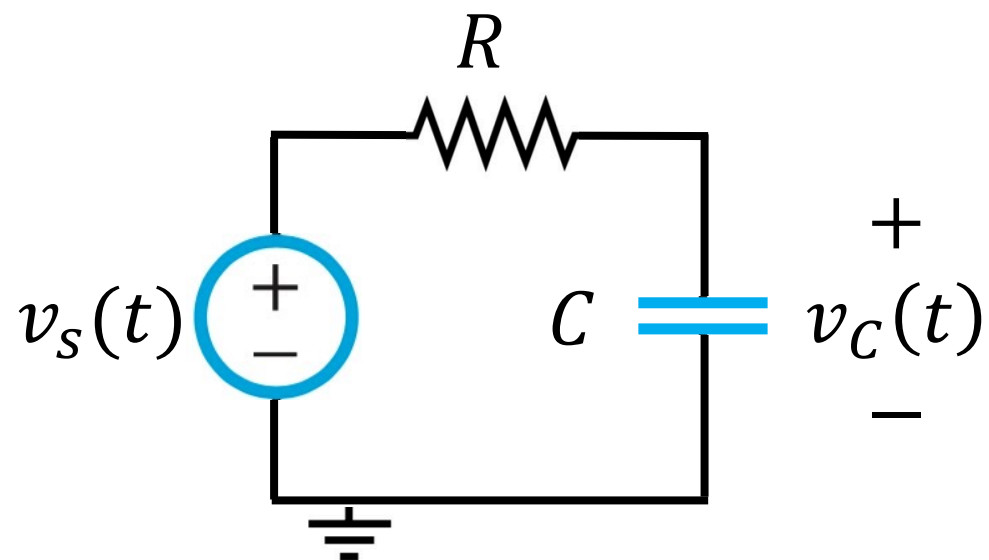




Find $V_c(j\omega)$





THE OHIO STATE UNIVERSITY


COLLEGE OF ENGINEERING

Transfer Functions




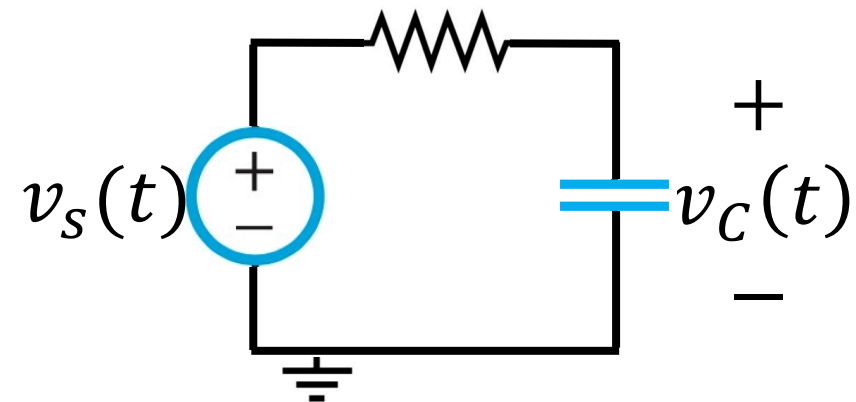- Learning Objectives:
 - Derive the transfer function of an AC Circuit.






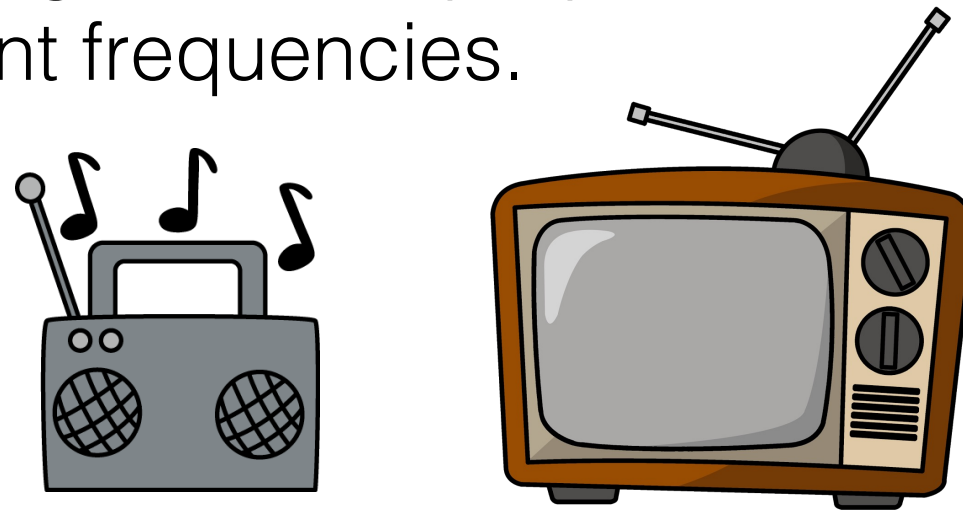- Often, the input signal is a superposition of many sinusoidal signals at different frequencies.



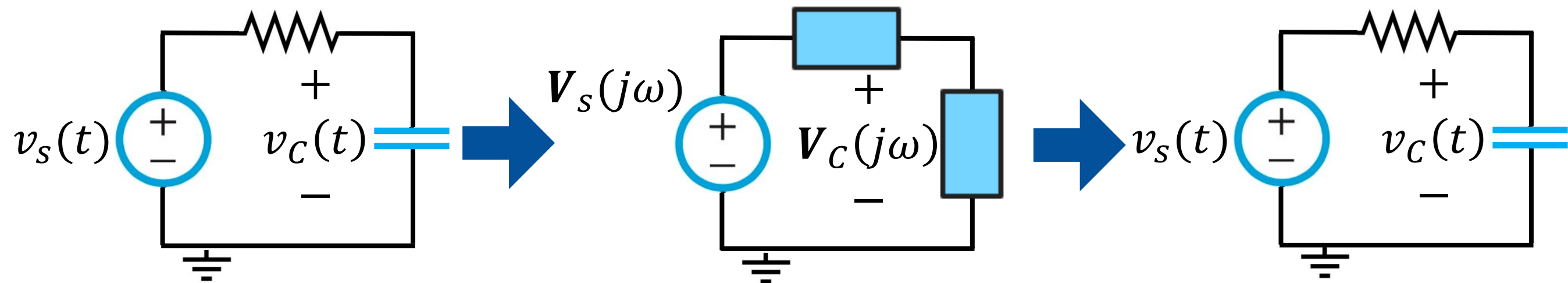- How to design RLC circuits that can **filter in** (pass through) the range of frequencies of interest and **filter out** (reject) the range of frequencies of signals that are either problematic or not of interest.



- At a given angular frequency ω :
 - Load voltage is a sinusoid with the same frequency as the source voltage.
- $V_C(j\omega)$ is a phase-shifted and amplitude-scaled version of $V(j\omega)$.



- **Frequency Response:** Measures how circuit responds to sinusoidal inputs of arbitrary frequency.



- **Transfer function:** describes the output response to an input excitation as a function of the angular frequency ω .



Voltage Gain:

Transfer Impedance:

Current Gain:

Transfer Admittance:

- V_{in} and I_{in} are often chosen to be independent voltage and current sources.
- Outputs V_{out} and I_{out} are freely chosen and represent the load in a circuit.

