



## Reminders to self:

- ☐ Turn on lecture recording to Cloud
- ☐ Turn on Zoom microphone

- Last Lecture
  - Foundations for K-Maps (Minterms & Maxterms)
  - Started K-Maps(2-variable introduction so far)
- Today's Lecture
  - Continue K-Maps
    - 3-variable
    - 4-variable
  - Start binary adders and subtractors



# Handouts and Announcements

---

- Announcements
  - Homework Problems 5-1, 5-2
    - Posted on Carmen yesterday
    - Due in Carmen 11:25am, Monday 2/6
  - Homework Problems 2-4 and 4-1 reminder
    - Both due: 11:59pm Thursday 2/2
  - Participation Quiz 3
    - Based on this lecture. 15min limit after you start.
    - Available 12:25pm today, due 12:25pm tomorrow, but also available 24hrs more with late penalty
  - Read for Wednesday: No new reading assignment



# 3-Variable Karnaugh Maps

- Three-variable K-Map plotted in a similar manner
- The value of one variable,  $a$ , is listed on the top and the values of the other two,  $b$  and  $c$ , are listed on the side
  - Order of variables in the minterms shown here is  $abc$
  - Note: alternative layout with one variable on the side and two on the top is equally valid

**FIGURE 5-3**

Location of Minterms on a Three-Variable Karnaugh Map

© Cengage Learning 2014

- Note “Gray-code-like” order
- Only one variable changes from row-to-row

		$a$	
		$bc$	
$bc$	00	000	100
	01	001	101
	11	011	111
	10	010	110

100 is adjacent to 110

(a) Binary notation

		$a$	
		$bc$	
$bc$	00	0	4
	01	1	5
	11	3	7
	10	2	6

(b) Decimal notation



# 3-Variable Karnaugh Maps

- Minterms in adjacent squares of map differ in only one variable and therefore can be combined using uniting theorem  $XY + XY' = X$
- Do this as an example. Formal algorithm next lecture

from Truth Table:  $F(A, B, C) = A'BC' + A'BC + AB'C' + ABC'$

From k-map:  $F = A'B + AC'$

Values of  $F$  come from first equation  
\* just because \*  
- equation can be changed to whatever we want

A B C	F
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	1
1 0 1	0
1 1 0	1
1 1 1	0


(a)

$ABC = 001, F = 0$

$A = 0, 0 \rightarrow A'$

$B = 1, 1 \rightarrow B$

$C = 1, 0 \rightarrow C'$

 

(b)



## 4-Variable Karnaugh Maps

A	B	C	D	F
0	0	0	0	$m_0$
0	0	0	1	$m_1$
0	0	1	0	$m_2$
0	0	1	1	$m_3$
0	1	0	0	$m_4$
0	1	0	1	$m_5$
0	1	1	0	$m_6$
0	1	1	1	$m_7$
1	0	0	0	$m_8$
1	0	0	1	$m_9$
1	0	1	0	$m_{10}$
1	0	1	1	$m_{11}$
1	1	0	0	$m_{12}$
1	1	0	1	$m_{13}$
1	1	1	0	$m_{14}$
1	1	1	1	$m_{15}$

Map with  $AB$  on *top*  
and  $CD$  on *side*

Remember that the map wraps

- Left edge is adjacent to right edge ( *Only one bit changes* )
- Top edge is adjacent to bottom edge ( *only one bit changes* )

$C = 1$

$CD \backslash AB$	00	01	11	10
00	$m_0$	$m_1$	$m_3$	$m_2$
01	$m_4$	$m_5$	$m_7$	$m_6$
11	$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
10	$m_8$	$m_9$	$m_{11}$	$m_{10}$

$AB \backslash CD$	00	01	11	10
00	$m_0$	$m_4$	$m_{12}$	$m_8$
01	$m_1$	$m_5$	$m_{13}$	$m_9$
11	$m_3$	$m_7$	$m_{15}$	$m_{11}$
10	$m_2$	$m_6$	$m_{14}$	$m_{10}$

$B = 1$  (grouping columns 01 and 11)

$D = 1$  (grouping rows 01 and 11)

$A = 1$  (grouping columns 11 and 10)

Map with  $AB$  on *side*  
and  $CD$  on *top*



# K-Map Minimal SOP Algorithm

---

1. Draw the largest rectangular box (squares are a special case of rectangular) that:
  - A. Does not include any 0s
  - B. Has height (# of rows ) that is a power of 2 ( 1, 2, 4, 8, .... )
  - C. Has width ( # of columns ) that is a power of 2
2. Make sure that every 1 on the map is in the **largest possible box** *Larger boxes do more reduction*
3. Reduce the products by looking at boxes
  - A. The reduced expression will be SOP
  - B. The result may not be unique, but will be maximally reduced




# K-Map Example

a	b	c	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

$$f(a, b, c) = \sum m(1, 3, 4, 5, 7)$$
 
$$f = a'b'c + a'bc + ab'c' + ab'c + abc$$



$$F = AB' + C$$




# K-Map Example

w	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	1

$$f(w, y, z) = \sum m(1, 3, 4, 5, 7)$$

$$+ \sum d(6)$$

 

w \ yz	00	01	11	10
0	0	1	1	0
1	1	1	1	X

Handwritten annotations on the K-map:

- Red box around the column where  $w=1$  (cells 11, 10).
- Green box around the rows where  $y=1$  (cells 01, 11, 10).
- Purple box around the cells where  $z=1$  (cells 01, 11).

$$F = W + Z$$

## Don't Cares in K-maps

- All 1s must be covered
- Xs are used only if they will simplify the resulting expression

Note: Still SOP form





# K-Map Amount of Reduction

---

K-map Boxes that are Groups of:

- 2  $\rightarrow$  reduce minterm by 1 variable
- 4  $\rightarrow$  reduce minterm by 2 variables
- 8  $\rightarrow$  reduce minterm by 3 variables
- 1  $\rightarrow$  reduce minterm by 0 variables (full-length minterm)



# K-Map Example


$$f(a, b, c) = \sum m(0, 2, 4)$$

*Handwritten notes:*  
 $a=0$   
 $c=0$   
 $b=0, c=0$

$a \backslash bc$	00	01	11	10
0	1	0	0	1
1	1	0	0	0

$$F = A'C' + B'C'$$


Sketch circuit

 

Later in semester will implement logic using hardware that assume 2-level AND-OR  $\rightarrow$  SOP

Note:  $f = c'(a' + b')$  is algebraically correct, but it is POS.

Sketch circuit

 


Not correct for SOP  
But uses fewer gates

# K-Map Example

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>F</i>
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	X
1	0	0	1	X
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0
 
$$f(A, B, C, D) = \sum m(0, 2, 10) + \sum d(8, 9)$$






## K-Map Example

A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

$$f(A, B, C, D) = \sum m(0, 5, 10, 15)$$

 I copied the truth table from the previous slide and pasted it here. I was supposed to edit it for the function of this example, but apparently neglected to do so before lecture. I corrected it after lecture.



$$f(A, B, C, D) = A'B'C'D' + A'BC'D + ABCD + AB'CD'$$


equation already minimal



## K-Map Example

$$f(A, B, C, D) = \sum m(0, 3, 4, 5, 9, 11, 13, 15)$$

$$+ \sum d(2, 6, 14)$$

 


$$f(A, B, C, D) = AD + A'D' + BC'D + B'CD$$

Note that this solution is not unique. There are other ways to pick up those last two ones:

- $A'BC'$  for the first one
- $A'B'C$  for the second one



# Summary of K-Maps

- Method to reduce SOP expression into another SOP expression:
  - Minimal in # of gates
  - Minimal in # of inputs/gate
- Map minterms next to each other such that they vary by only one bit
- Group in rectangles whose dimensions are power of 2
  - Variables whose values change within rectangles can be eliminated
  - $AB'C + A'B'C = B'C(A + A') = B'C$
  - Group of 1, no reduction
  - Group of 2, eliminate 1 variable
  - Group of 4, eliminate 2 variables
  - Group of 8, eliminate 3 variables
- K-Map edges are connectable ( *wrap around* )  $\leftrightarrow$   $\updownarrow$   *corners too*
- Five variable K-map (think 3-D: layers) section not assigned reading
  - You are not responsible for (not on HW or exams)
  - But we will do an example that uses them late in semester




# Half Adder

- Add two binary bits,  $A$  and  $B$ . Need two outputs
  - A sum bit,  $S$
  - A carry bit,  $C$
- $A + B = S, C$  (regular addition here, not an OR)
- $S = A'B + AB' = A \oplus B$
- $C = AB$
- This works for adding two 1-bit numbers, but what if each number has more than one bit?
- Need to be able to add in the carry from the previous bit
- Circuit for that is known as a Full Adder

$A$	$B$	$S$	$C$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

XOR  
AND

 



## Full Adder

- Add two binary bits,  $X_i$  and  $Y_i$ ; *and carry bit  $C_i$*
- $X_i + Y_i + C_i = S_i, C_{i+1}$  (regular addition here)
- $S_i = \sum m(1,2,4,7)$
- $C_{i+1} = \sum m(3,5,6,7)$
- K-map for  $S_i$

		$Y_i C_i$			
		00	01	11	10
$X_i$	0		1		1
	1	1		1	

$X_i$	$Y_i$	$C_i$	$S_i$	$C_{i+1}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- No reduction possible*
- For  $S_i$  *each minterm has an odd number of 1s*
- $S_i = X_i \oplus Y_i \oplus C_i$





# Full Adder

- Add two binary bits,  $X_i$  and  $Y_i$ ; and carry bit  $C_i$
- $X_i + Y_i + C_i = S_i, C_{i+1}$  (regular addition here)
- $S_i = \sum m(1,2,4,7)$
- $C_{i+1} = \sum m(3,5,6,7)$
- K-map for  $C_{i+1}$

		$Y_i C_i$			
		00	01	11	10
$X_i$	0				
	1				

$X_i$	$Y_i$	$C_i$	$S_i$	$C_{i+1}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


•

- $C_{i+1} = X_i Y_i + X_i C_i + Y_i C_i$



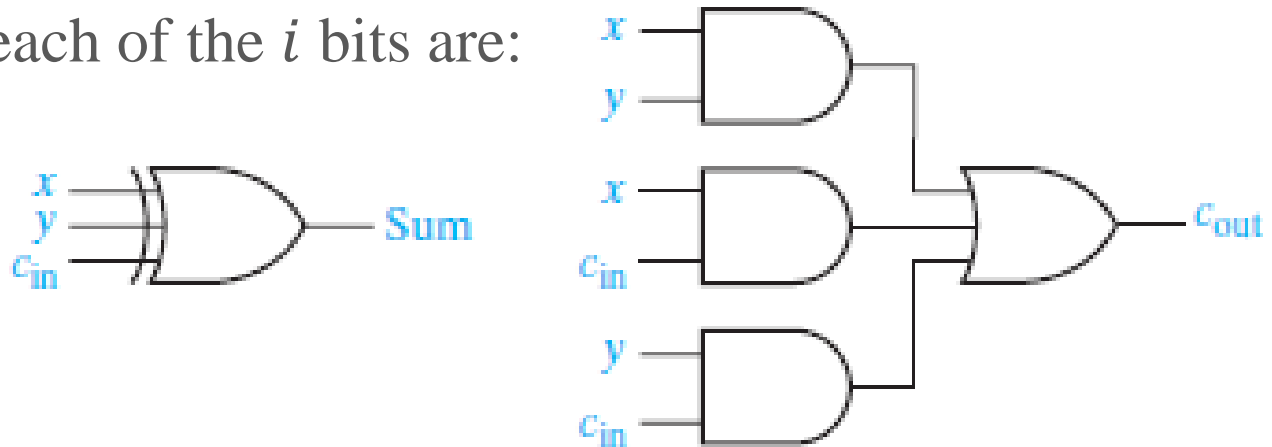
# Ripple Carry Adder

- $S_i = X_i \oplus Y_i \oplus C_i$
- $C_{i+1} = X_i Y_i + X_i C_i + Y_i C_i$
- The circuits for each of the  $i$  bits are:



 - The Carry-out circuit has two levels of logic
  - Two gate-delays for the  $C_{out}$  signal to be stable after  $x$ ,  $y$  and  $c_{in}$  are applied
- In block diagram form, each Full Adder block contains both the Sum and Carry-out circuits





# Four-bit Adder


---

- In principle, one could make a four-bit adder directly from a truth table using a brute force approach
  - Add  $B_3B_2B_1B_0$  to  $A_3A_2A_1A_0$
  - Need to allow for a carry-in bit,  $C_0$ 
    - Nine inputs
    - Five outputs:  $S_3S_2S_1S_0$  and  $C_4$  ( )
  - Truth table will have
  - This approach very difficult, and logic circuit to implement very complex
- Alternate approach
  - Use multiple instances of the full-adder block
  - This type of approach - using multiple instances of smaller functional blocks - is standard in digital design
  - Allows reliable design of complex systems to perform complex tasks


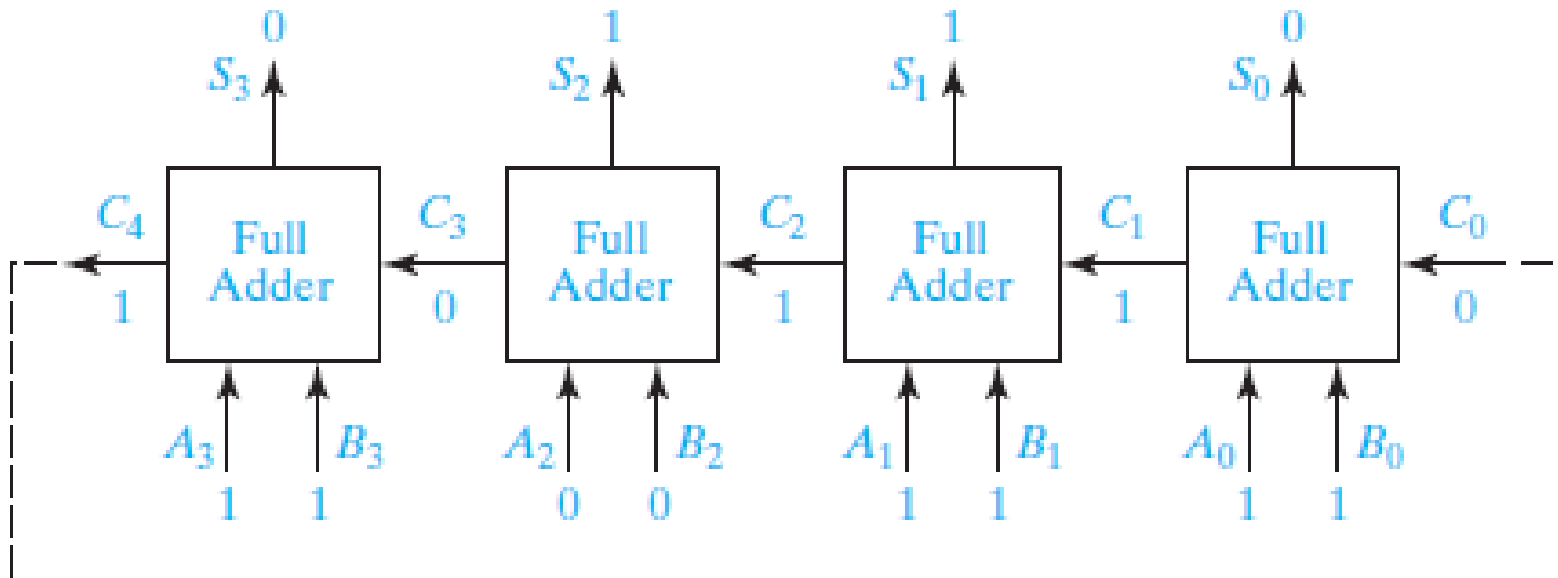
# Ripple Carry Adder

- To make a four-bit adder use four full adders
    - Add  $B_3B_2B_1B_0$  to  $A_3A_2A_1A_0$ , bit-by-bit
    - With the carry-out from the  $i$ -th bit becoming the carry-in of the  $i + 1$  bit
    - Figure shows addition of      and      and
    -
- Question:** What can you say about the result if this is 1's or 2's complement addition?




- Dashed line wire is only needed for: **end-around carry for 1's complement**
- For 2's complement the carry out of bit 4 is discarded, so wire not needed


 
# Ripple Carry Adder


- For 2s complement addition
  - Since each there is a delay of 2 gate-delays to generate each carry, and
  - the carry from one bit ripples into the next bit ( )
  - there is a total delay of 8 gate-delays to generate the final carry




 
# Ripple Carry Adder


- For 2s complement addition
  - The final carry is discarded ( )
  - Note that  $C_0 = 0$ , giving simplifications  $S_0 = A_0 \oplus B_0$  and  $C_1 = A_0 B_0$




 
# Ripple Carry Adder

- For 1s complement addition
  - The final carry is used for the end-around carry
  - Fed back as  $C_0$ , as shown by the dashed line
  - Have to wait an additional 7 gate delays for certainty its effects rippled to  $S_3$





# Ripple Carry Adder

- Overflow detection
  - Adding two positive numbers and getting a negative result
  - Adding two negative numbers and getting a positive result
  - Use the sign bits of  $A$ ,  $B$  and  $S$
  - Overflow  $V = A'_3B'_3S_3 + A_3B_3S'_3$

