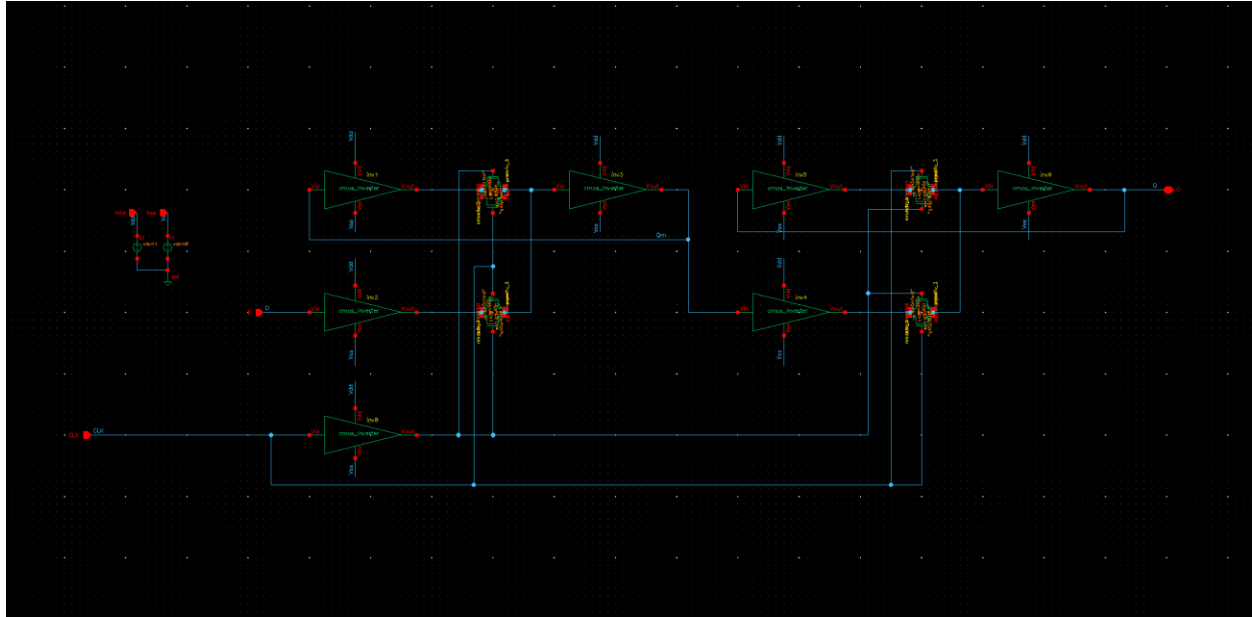



Homework 6

Flip Flop




1.92um PMOS, 0.96um NMOS

Flip Flop Test Bench

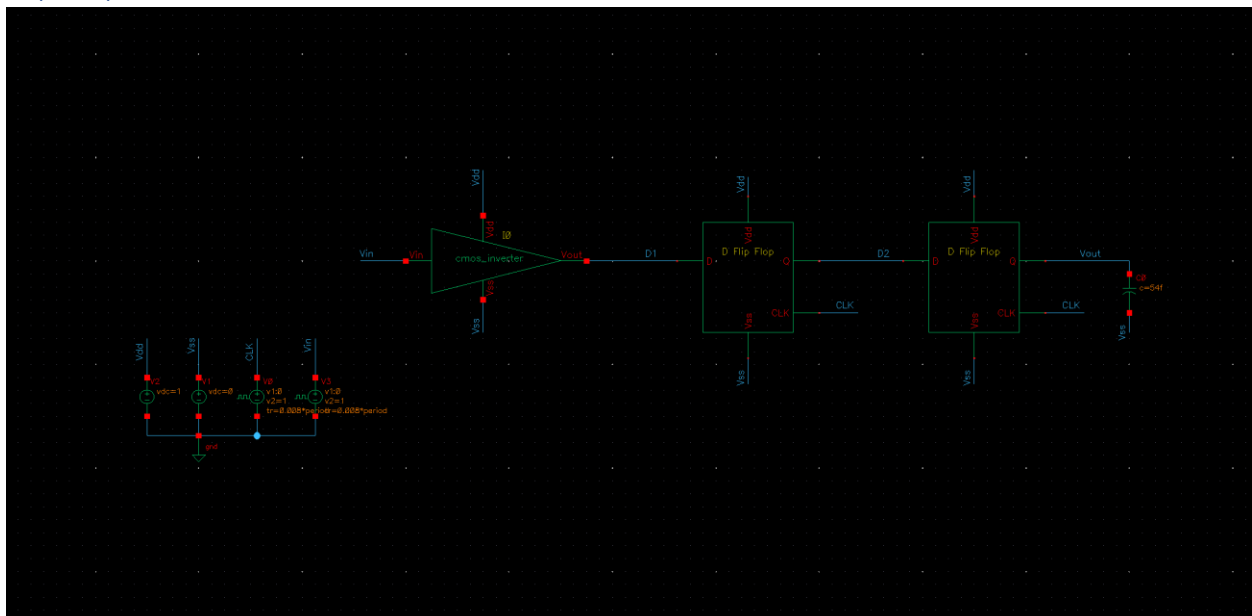

54fF Capacitor on Vout

Setup Time & Hold Time

 

$$t_{su} = 79.7ps, \quad t_h = 15.8ps$$

CLK to Q time (Falling and Rising Q)



$$t_{cqf} = 40.4ps, \quad t_{cqr} = 32.6ps$$