



Lecture Outline

Reminders to self:

- ☐ Turn on lecture recording to Cloud
- ☐ Turn on Zoom microphone

- Last Lecture

- Hazards in combinatorial logic
- Started Multiplexers

- Today's Lecture

- Continue Multiplexers
- Brief look at CMOS gates at transistor level
- Three-state buffers / Tri-state outputs



Handouts and Announcements

- Announcements
 - Homework: No new assignment today
 - Homework Reminder:
 - HW 8-1 and 8-2 Due: 11:59pm Thursday 2/16
 - Participation Quiz 7 available starting 12:25pm today
 - Due 12:25pm Thursday 2/16
 - Available until 12:25pm Friday 2/17 with late penalty
 - Read for Friday: pages 271-275



Handouts and Announcements

- Announcements

- Mini-Exam 3 Reminder

- Available 5pm Monday 2/20 through 5:00pm Tuesday 2/21
- Due in Carmen PROMPTLY at 5:00pm on 2/21
- Designed to be completed in ~36 min, but you may use more
- When planning your schedule:
 - I recommend building in 10-15 min extra
 - To allow for downloading exam, signing and dating honor pledge, saving solution as pdf, and uploading to Carmen
- I also recommend not procrastinating


- Exam review topics available on Carmen

- Sample Mini-Exams 3 and 4 from Au20 also available



Multiplexers

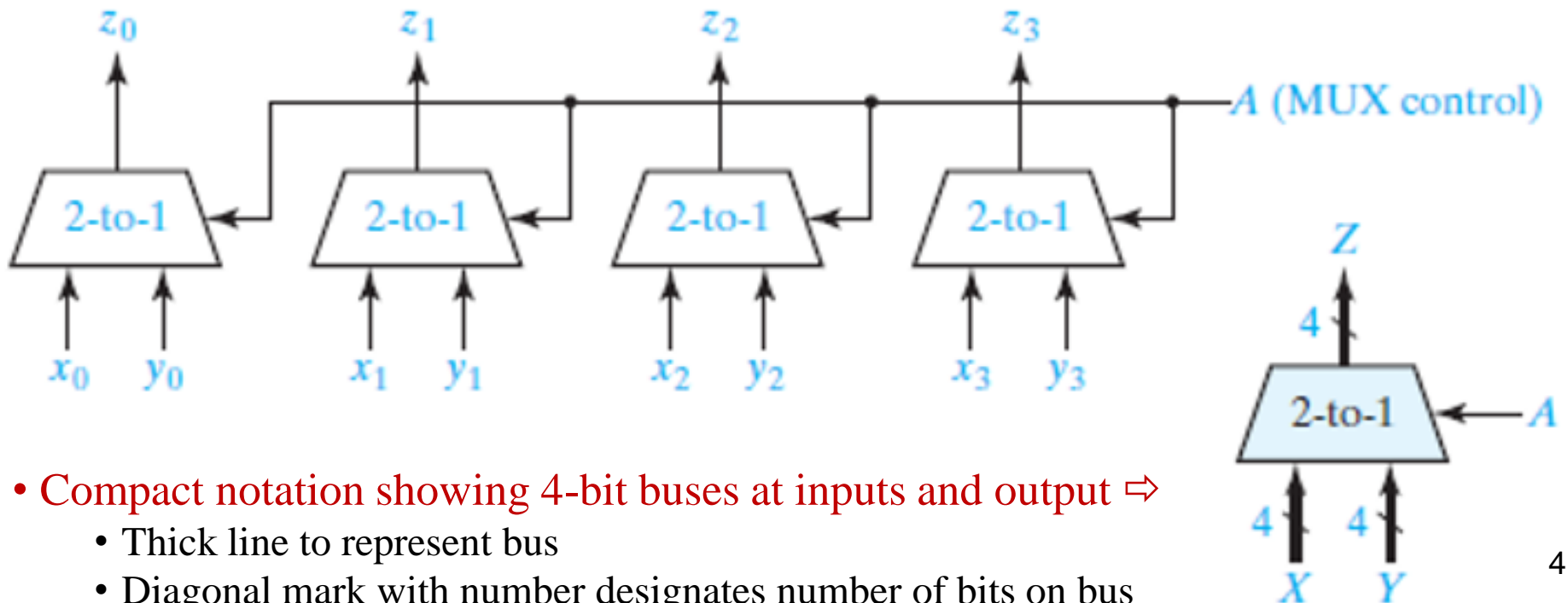- Multiplexers often used to select data which is to be processed or stored in digital system design
- N identical MUX connected in parallel, with shared control, can be used to select between N -bit data words
- A 4-bit example:
 - (x_3, x_2, x_1, x_0) and (y_3, y_2, y_1, y_0) are the two 4-bit data words to select between
 - (z_3, z_2, z_1, z_0) is the output data word




- Compact notation showing 4-bit buses at inputs and output \Rightarrow
 - Thick line to represent bus
 - Diagonal mark with number designates number of bits on bus




Digital MOSFET circuit symbols

 - MOSFET is a type of transistor, dominant in modern digital ICs
- Two varieties: NMOS and PMOS
- Three terminal device: Gate, Drain, Source (arrow in symbol)
- Digital-circuit designers often use a different circuit symbol for the MOSFET when it is used for implementing logic
- Which terminal is source and which is drain inferred from circuit:



NMOS

(a)

 


PMOS

(b)

Circle incorporated into symbol at gate of PMOS FET to indicate "active low" input




PMOS + NMOS = CMOS

 

PMOS

$A = 0$: 5 V gets through (Short)

$A = 1$: Nothing gets through (Open)

 

NMOS

$A = 1$: 0 V gets through (Short)

$A = 0$: Nothing gets through (Open)



PMOS + NMOS = CMOS

C stands for “complimentary”



CMOS Inverter

Sketch in wires for input and output

  

$v_A = 0 \text{ V}$:
PMOS = On (*short*)
NMOS = Off (*open*)
Output = 5 V
“Pulled up” to 5 V

$v_A = 5 \text{ V}$:
PMOS = Off (*open*)
NMOS = On (*short*)
Output = 0 V
“Pulled down” to ground

If you were to turn on both FETs

- Tries to short power supply to ground
- Large current flow and power dissipation
- Heat and damage




CMOS Logic-Gate Circuits

- Derived from CMOS inverter, but individual transistors replaced by networks of transistors

- PU FET replaced by a *Pull-Up Network* (PUN) of PMOS FETs
- PD FET replaced by a *Pull-Down Network* (PDN) of NMOS FETs

- Both networks operated by input variables, in complementary way *similar to PMOS and NMOS*

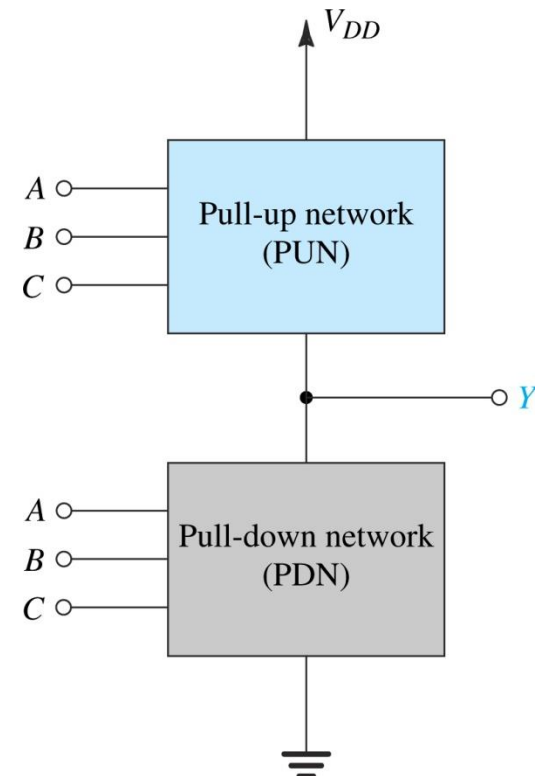-
- PDN network establishes path to *ground* for input combinations that require low output ($Y=0, V_Y=0$)
 - At same time, PUN does **not** establish path to V_{DD}
-
- PUN network establishes path to V_{DD} for input combinations that require high output ($Y=1, V_Y=V_{DD}$)
 - At same time, PDN does **not** establish path to ground







CMOS Logic-Gate Circuits

NOR and NAND

- A or $B = 1$: At least one active low PMOS off, no output connection to V_{DD}
- A and $B = 0$: Both PMOS on, output connected to V_{DD}

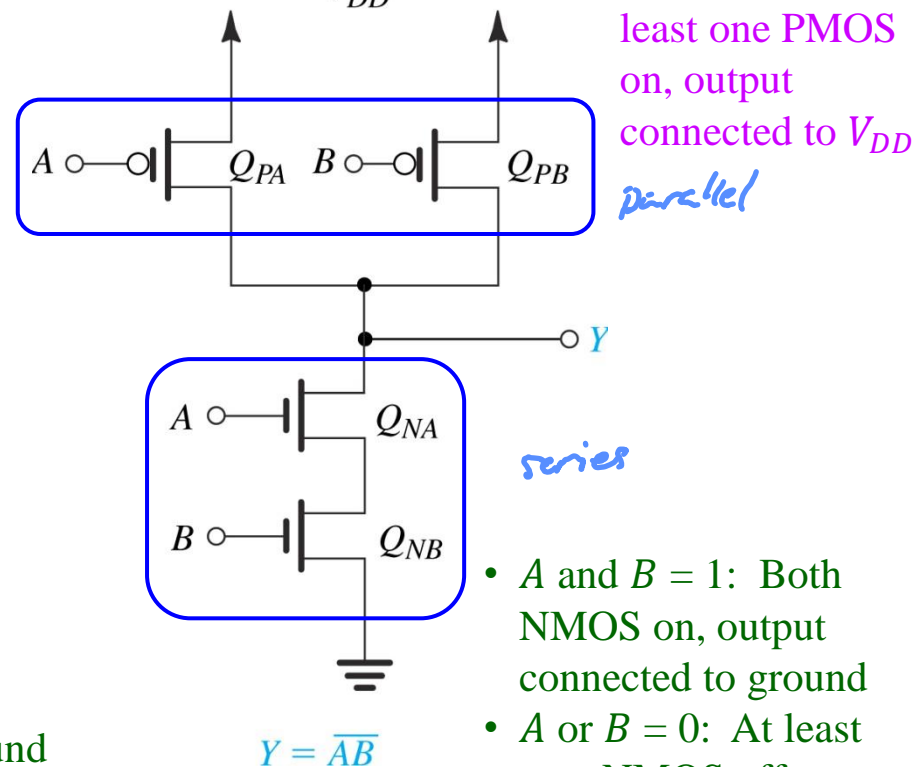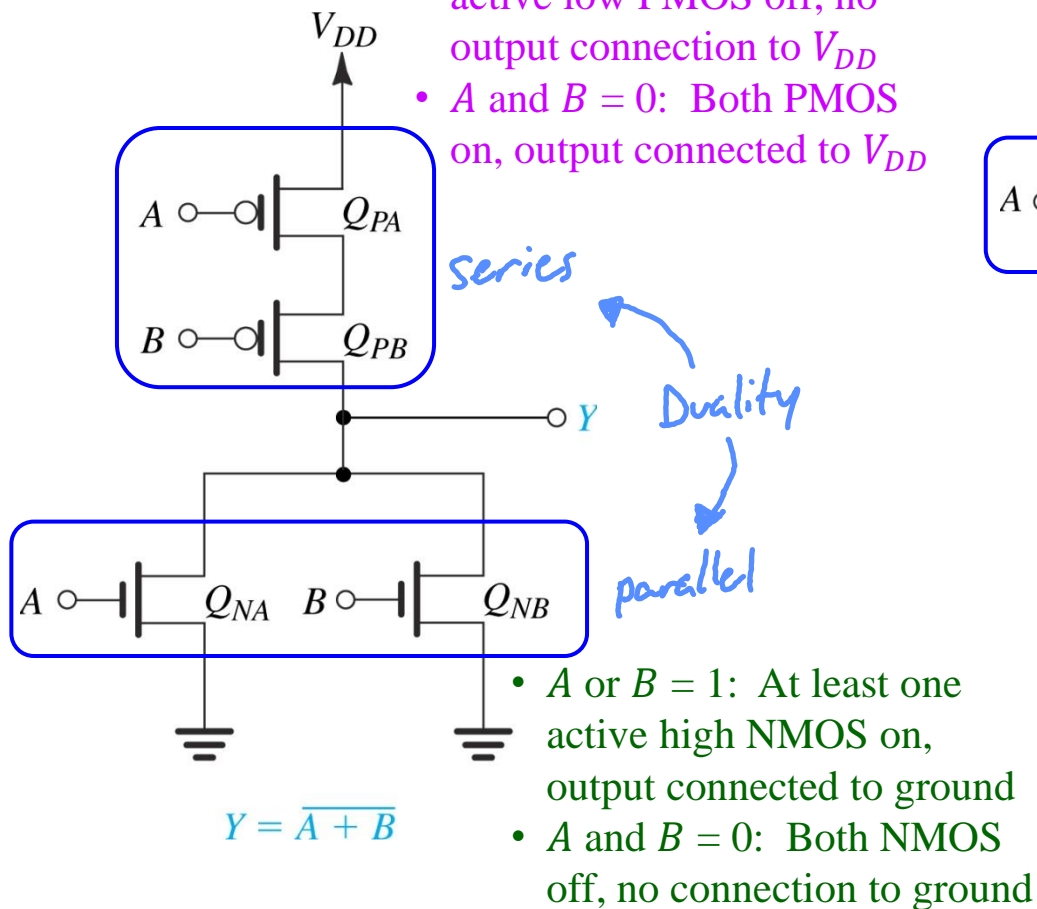- A and $B = 1$: Both PMOS off, no output connection to V_{DD}
- A or $B = 0$: At least one PMOS on, output connected to V_{DD}



To make an OR, follow this
with 2-FET inverter: *6 transistors*


To make an AND, follow
this with 2-FET inverter: *6 transistors*



CMOS Logic-Gate Circuits

XOR

$$A \oplus B = AB' + A'B$$

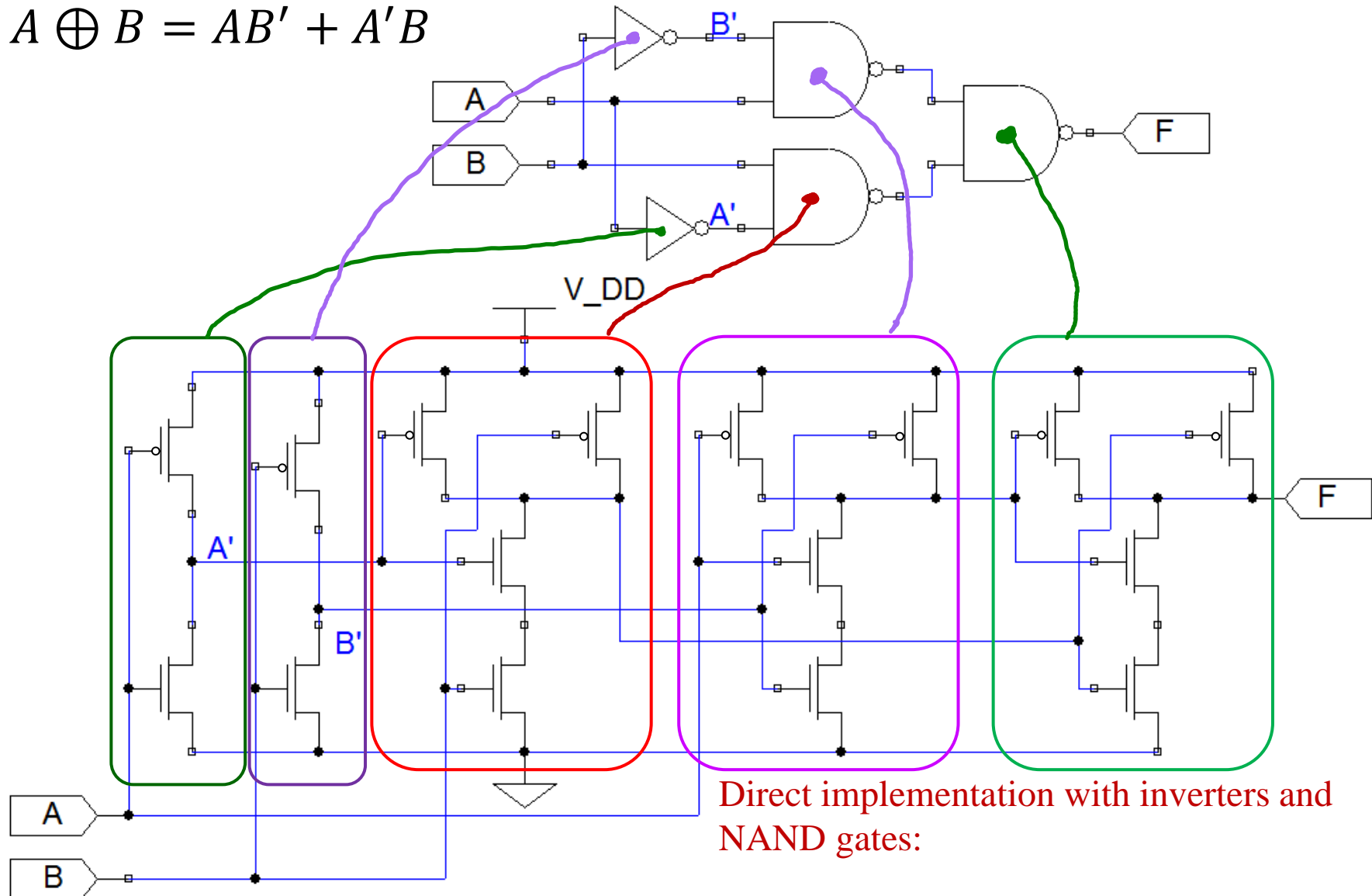




CMOS Logic-Gate Circuits

- But can do better by directly applying these PUN and PDN concepts
- *Transistor-Level Design*

-
- PDN network establishes path to ground for input combinations that require low output ($Y = 0, v_Y = 0$)
 - At same time, PUN does **not** establish path to V_{DD}
-
- PUN network establishes path to V_{DD} for input combinations that require high output ($Y = 1, v_Y = V_{DD}$)
 - At same time, PDN does **not** establish path to ground

Generic 3-input example

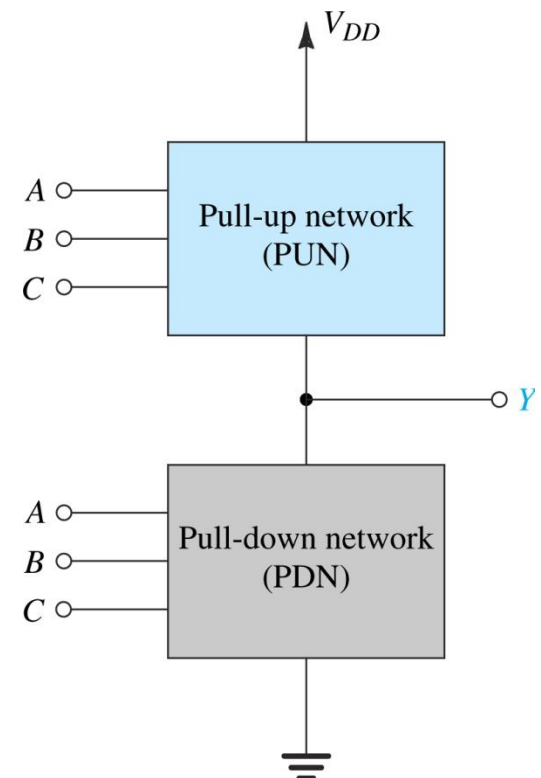




CMOS Logic-Gate Circuits

XOR – by direct synthesis of PUN and PDN

PUN synthesis: $Y = A\bar{B} + \bar{A}B$

 

Complement of variables from equation applied at PMOS inputs, since they are active-low


Including the two inverters: 12 transistors

Inverter delay + 1 gate-delay

PDN synthesis: $\bar{Y} = \overline{A\bar{B} + \bar{A}B} = \overline{A\bar{B}}\overline{\bar{A}B} = (\bar{A} + B)(A + \bar{B})$

$$\bar{Y} = (\bar{A} + B)(A + \bar{B})$$


$$\bar{Y} = AB + \bar{A}\bar{B}$$

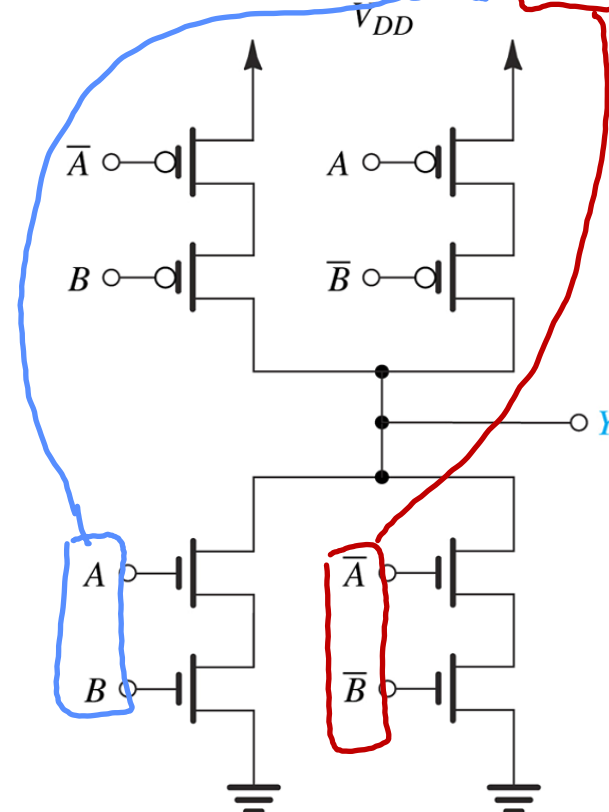



Adder/Subtractor

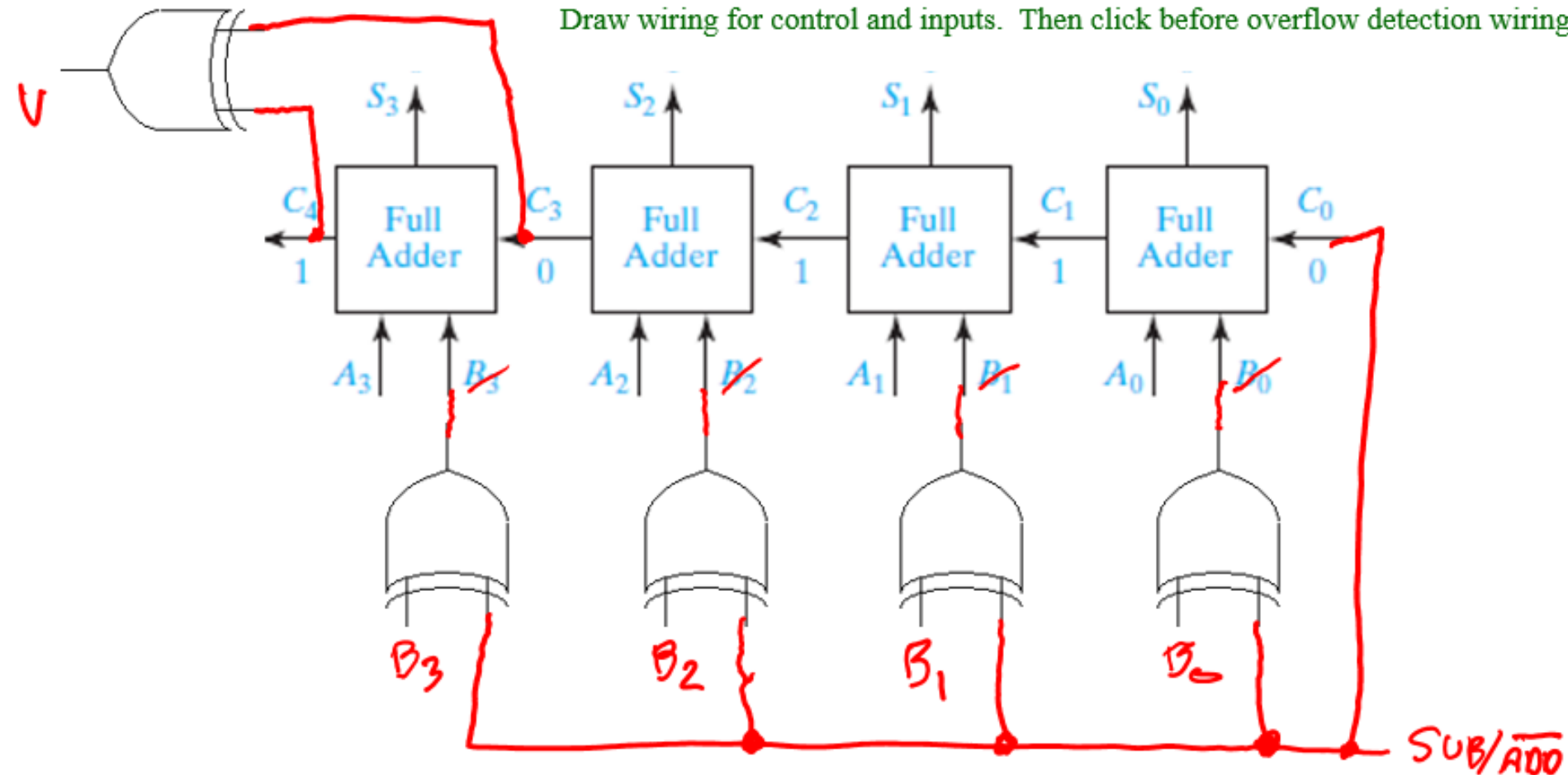Draw wiring for control and inputs. Then click before overflow detection wiring




In a previous lecture saw an adder/subtractor circuit in which XOR gates were used to

- invert the bits of B when $SUB = 1$ (subtraction), and
- not invert them when $SUB = 0$ (addition)



Adder/Subtractor

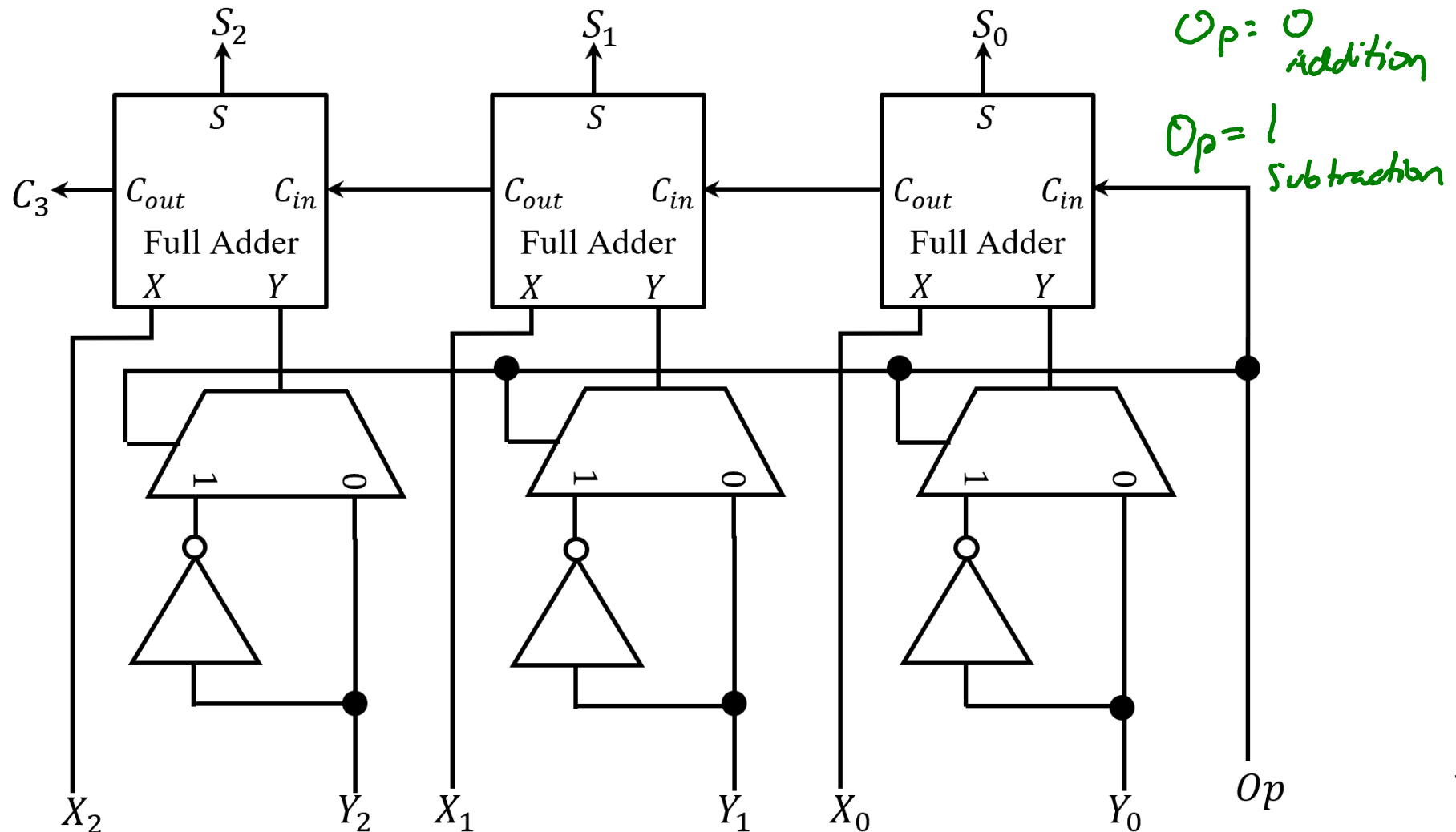Here is a 3-bit version, implemented using multiplexers





Three-State Buffers


Buffers

- A gate output can only be connected to a limited number of other device inputs without degrading the digital system's performance
(fan-out)
- A simple buffer may be used to increase the driving capability of a gate output
- Figure 9-10 shows a buffer connected between a gate output and several gate inputs

FIGURE 9-10

Gate Circuit with
Added Buffer

© Cengage Learning 2014

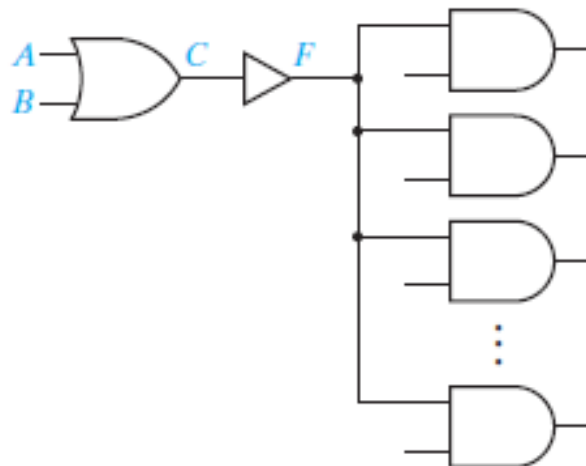




Three-State Buffers

- Tying the outputs of two gates together is **BAD**
- Tying gate outputs \neq OR
- Gates FORCE a wire to 1 or 0
- Gates FORCE the voltage on a wire to High (e.g. 3 V) or Low (e.g. 0 V)
- Three-state logic permits two or more outputs to be wired together
- In the third state the output of the gate is “high impedance”
 - Hi-Z
 - It is effectively disconnected from the logic circuit inside the gate
- Also known as “Tri-state” Buffers

FIGURE 9-11
Three-State Buffer
© Cengage Learning 2014

 




Three-State Buffers

- Other reasons for adding a buffer (even if not tri-state)
 - Add a delay (for example: to keep two-level logic in *time-step* with three-level logic)
 - Increase output current driving capability (*fan-out*)
- Three-state buffer logic symbol & logical equivalent:

FIGURE 9-11**Three-State Buffer**

© Cengage Learning 2014

 

- Four types of three-state buffer
- All have same three output states:
 -
 -
 - “High Impedance”




Three-State Buffers

- Four types of three-state buffer

FIGURE 9-12
Four Kinds of
Three-State Buffers

© Cengage Learning 2014

 

B is an “enable”
control bit

not
enabled

$C=A$

Inverter w/
tri-state output

Non-inverting and
inverting tri-state buffers
with active-low enable

B	A	C
0	0	Z
0	1	Z
1	0	0
1	1	1

(a)

B	A	C
0	0	Z
0	1	Z
1	0	1
1	1	0

(b)

B	A	C
0	0	0
0	1	1
1	0	Z
1	1	Z

(c)

B	A	C
0	0	1
0	1	0
1	0	Z
1	1	Z

(d)




Three-State Buffers

• Data selection using three-state buffers

FIGURE 9-13

Data Selection
Using Three-State
Buffers

© Cengage Learning 2014

 

• Logically equivalent to 2-to-1 MUX introduced last lecture:

- $B = 0 \rightarrow D = A$, lower buffer in high-Z state
- $B = 1 \rightarrow D = C$, upper buffer in high-Z state

• Can be implemented with 6 transistors, vs 14 before


- Inverter (2) + two “pass-transistor” PMOS/NMOS pairs (2x2)
- Inverter (2) + three NAND gates (3x4 /gate) = 14



Three-State Buffers

- Data selection using 3-state buffers

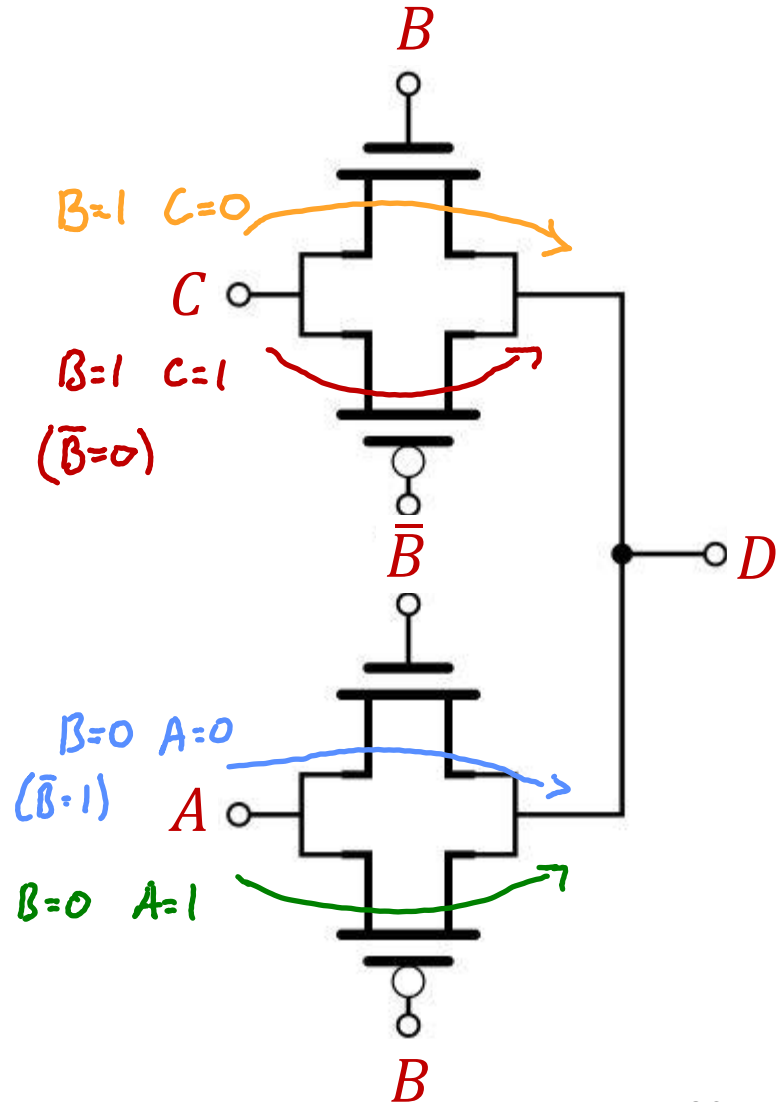- CMOS multiplexer
- Note NMOS and PMOS in “pass-transistor” pairs
 - NMOS active-high
 - PMOS active-low
- Need both to confidently pass signal for both high and low states of A or C
 - NMOS does good job of passing logic 0
 - PMOS does good job of passing logic 1
- Inverter also needed, from B









Three-State Buffers

• Straight-through/Cross-through MUX

-
-
-
-

    

- Two outputs tied together
- But only one active at a time
- Other in high-Z state




Three-State Buffers

- Three-state bus as alternative to MUX data selector
- Example: 4-bit adder with one operand sourced from four different locations

FIGURE 9-15

4-Bit Adder with
Four Sources for
One Operand

© Cengage Learning 2014

 

- A bus controller is needed to ensure that only one of EnA , EnB , EnC , and EnD are true at any time
- Outputs of the other buffers must be in
- Device known as can be used for bus control