

### Homework 3: Counters and Sequential Circuit Analysis

Solve the **four** following problems. Show all your work/process. Please neatly write or type your answers, and please scan or upload your answers in a single PDF file to the assignment submission on Carmen. Answers may be graded for correctness, thoroughness, completion, or some combination.

**3.1** Consider a 4-bit counter which counts in the following sequence:

0000, 0001, 0010, 0011, 0100, 0110, 1000, 1001, 1010, 1100, 1110, 1111, 0000, ...

- Design the counter using D flip-flops. Derive the excitation equations and draw the circuit.
- Design the counter using J-K flip-flops. Derive the excitation equations and draw the circuit.
- Design the counter using the LS163A (74x163) 4-bit binary counter shown below in Figure 1. Derive the excitation equations for  $CLR$ ,  $LD$ ,  $D$ ,  $C$ ,  $B$ , and  $A$ , and draw the circuit. Assume both  $ENP$  and  $ENT$  are connected to power (set to high level). Assume  $CLR$  has precedence over  $LD$ . Draw a clock signal into the  $CLK$  input and the connection to power for  $ENP$  and  $ENT$ .


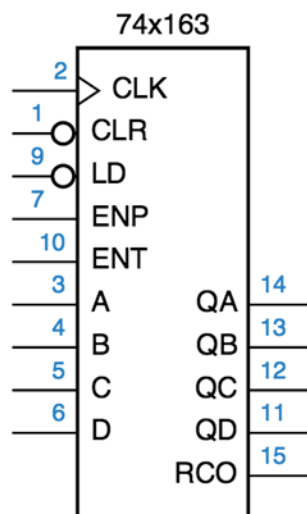


Figure 1: LS163A 4-bit synchronous counter block diagram.

**3.2** A sequential circuit contains a register of four flip-flops. Initially a binary number  $N$  is stored in the flip-flops ( $0000 \leq N \leq 1011$ ). After a single clock pulse is applied to the circuit, the register should contain  $N + 0100$ . In other words, the function of the sequential circuit is to add 4 to the contents of a 4-bit register. Design the circuit using T flip-flops. Derive the excitation equations and draw the circuit.

**3.3** Consider the sequential circuit shown in Figure 2.

 

**Figure 2:** Sequential circuit for problem 3.3.

- Is this a Mealy machine or a Moore machine? Explain how you know.
- Derive the excitation equations, characteristic equations, and output equation for this circuit.
- Construct a state/output table for this circuit.
- Construct a state diagram for this circuit.
- Construct a timing diagram for this circuit for the input sequence  $X = 10011$ . Show the clock,  $X$ ,  $Q_1$ ,  $Q_2$ , and  $Z$  signals. Assume that  $X$  changes midway between falling and rising clock edges. Initially,  $Q_1 = Q_2 = 0$  and  $X = 1$ .

For parts (f) through (i), use the timing data shown in the tables at the end of this document.

- Compute the maximum clock frequency  $f_{max}$  for this circuit. Show all paths which need to be considered and their associated delays.
- Compute the setup time  $t_{su}^X$  for the input  $X$  for this circuit. Show all paths which need to be considered and their associated delays.
- Compute the hold time  $t_h^X$  for the input  $X$  for this circuit. Show all paths which need to be considered and their associated delays.
- Compute the maximum propagation delay to the output  $t_{pd}^{X \rightarrow Z}$  for the input  $X$  for this circuit. Show all paths which need to be considered and their associated delays.



**Combinational Parts**

Chip	$t_{pLH}$ (ns)	$t_{pHL}$ (ns)	Comments
'LS04, 'LS00, 'LS10, 'LS20	15	15	Inverter, 2-, 3-, 4-input NAND
'LS08, 'LS11	15	20	2-, 3-input AND
'LS02, 'LS27	15	15	2-, 3-input NOR
'LS32	22	22	2-input OR
'LS86			2-input XOR
2 levels	23	17	Other input low
3 levels	30	22	Other input high
'LS138			3-to-8 Decoder
$A, B, C \rightarrow Y$ (2 levels)	20	41	$A \rightarrow Y_0, Y_2, Y_4, Y_6$ or $B \rightarrow Y_0, Y_1, Y_4, Y_6$ or $C \rightarrow Y_0, Y_1, Y_2, Y_3$
$A, B, C \rightarrow Y$ (3 levels)	27	39	Other cases
$G2A, G2B \rightarrow Y$	18	32	
$G1 \rightarrow Y$	26	38	
'LS139			2-to-4 Decoder
$A, B \rightarrow Y$ (2 levels)	20	33	$A \rightarrow Y_0, Y_2$ or $B \rightarrow Y_0, Y_1$
$A, B \rightarrow Y$ (3 levels)	29	38	Other cases
$G \rightarrow Y$	24	32	

**'LS74 - D Type Positive-Edge-Triggered Flip-Flops**

Data	$t_{pLH}$	$t_{pHL}$	$t_s$	$t_h$
$CLR, PR, CLK \rightarrow Q$	25	40		
$D$			20	5
$f_{max} = 25$ Mhz				

**'LS109 - J -  $\bar{K}$  Type Positive-Edge-Triggered Flip-Flops**

Data	$t_{pLH}$	$t_{pHL}$	$t_s$	$t_h$
$CLR, PR, CLK \rightarrow Q$	25	40		
$J, K$			35	5
$f_{max} = 25$ Mhz				