
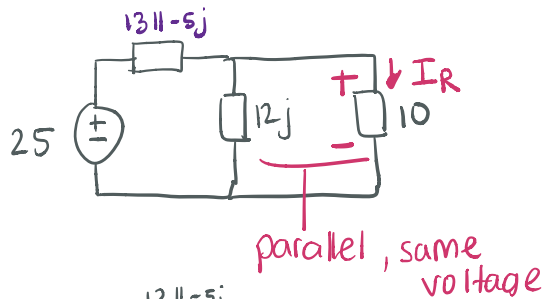



- Find I_R , given that $V_s = 25V$.

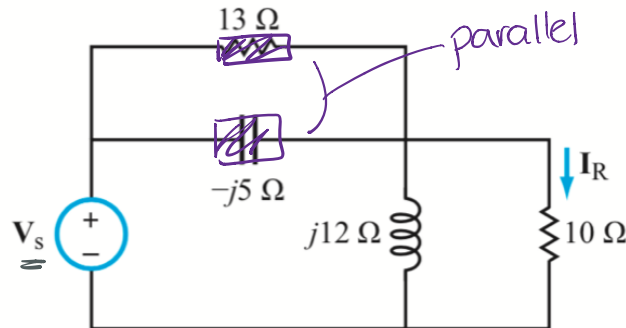

$$13 || -5j = \frac{13(-5j)}{13 - 5j}$$

$$= 1.67 - 4.35j$$

$$= 4.67 \angle -68.96^\circ$$

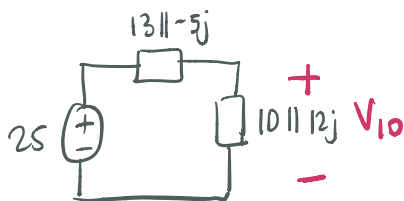

$$10 || 12j = \frac{10(12j)}{10 + 12j}$$

$$= 5.9 + 4.91j$$

$$= 7.68 \angle 39.8^\circ$$

voltage division

$$V_{10} = 25 \cdot \frac{7.68 \angle 39.8^\circ}{7.57 + 0.56j} = 20.57 + 14.71j$$


$$= 25.29 \angle 35.57^\circ$$

$$I_R = \frac{V_{10}}{10} = \frac{25.29 \angle 35.57^\circ}{10} = 2.53 \angle 35.57^\circ$$

$$i_R(t) = 2.53 \cos(\omega t + 35.57^\circ)$$

Your objective is to obtain a Thevenin, given that $i_s(t) = 3\cos(4 \times 10^4 t)$, then:

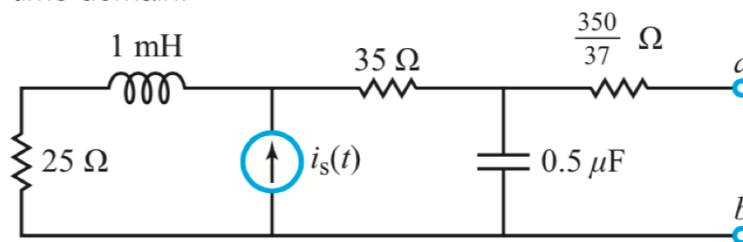
- Transform the circuit to the phasor domain. ✓
- Apply the ~~source transformation~~ technique to obtain the Thevenin equivalent circuit at terminals (a, b).
- Transform the phasor-domain Thevenin ~~circuit~~ ^{voltage} back to the time domain.





$$I(j40k) = 3 \angle 0^\circ \quad \omega = 40k$$

$$Z_C = \frac{-j}{40k(0.5 \times 10^{-6})} = -50j$$


$$Z_L = j(40k)(1m) = 40j$$

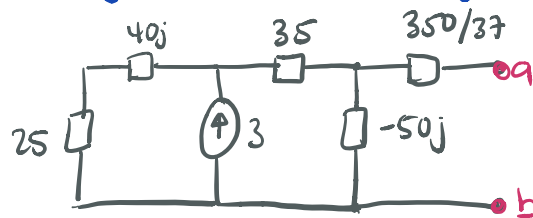

Thevenin equivalent

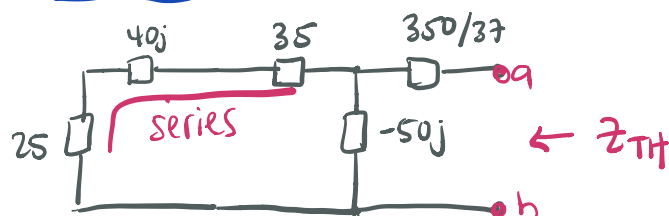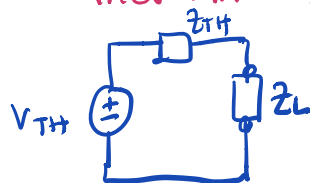


$$25 + 35 + 40j = 60 + 40j$$

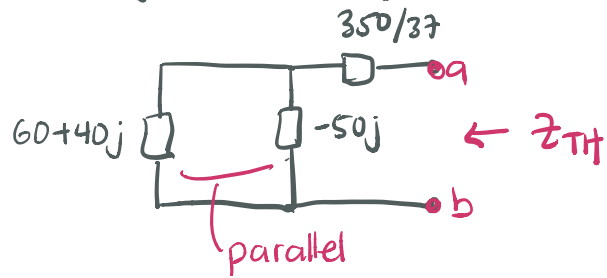

$$(60 + 40j) \parallel -50j = \frac{(60 + 40j)(-50j)}{60 - 10j}$$

$$= 40.54 - 43.24j$$



$$= 59.27 \angle -46.85^\circ$$

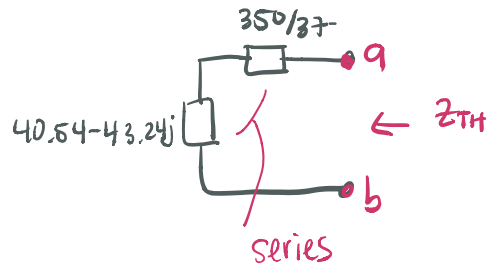


$$Z_{TH} = 50 - 43.24j$$

$$= 66.1 \angle -40.85^\circ$$

V_{TH}

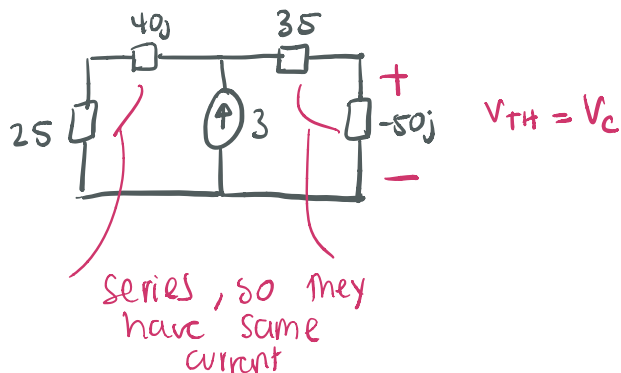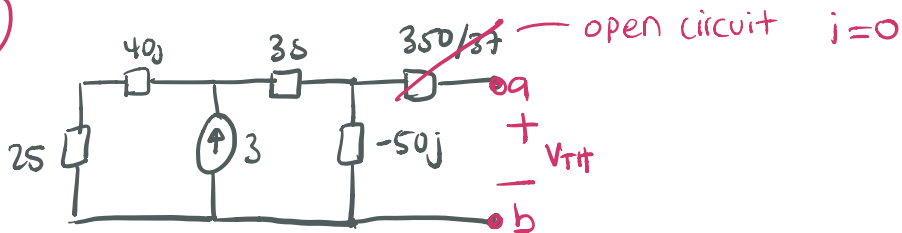

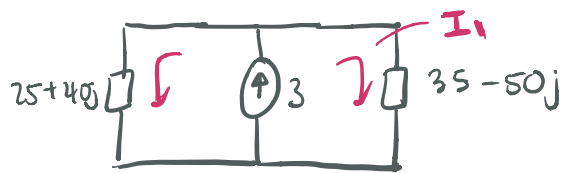

current division

$$V_{TH} = (-50j) I_1$$

$$\begin{aligned} I_1 &= \frac{z_{eq}}{(35 - 50j)} \cdot 3 \\ &= \frac{25 + 40j}{60 - 10j} \cdot 3 \\ &= 0.89 + 2.15j \\ &= 2.33 \angle 67.46^\circ \end{aligned}$$

$$z_{eq} = \frac{(35 - 50j)(25 + 40j)}{60 - 10j}$$

$$\begin{aligned} V_{TH} &= (-50j)(2.33 \angle 67.46^\circ) \\ &= 107.43 - 44.59j \\ &= 116.32 \angle -22.54^\circ \end{aligned}$$

$$v_{th}(t) = 116.32 \cos(40\text{K}t - 22.54^\circ) \checkmark$$



- Determine the complex power, apparent power, average power absorbed, reactive power, and power factor for a load circuit whose voltage and current at its input terminals are given by:

1. $v(t) = 100\cos(377t - 30^\circ) \text{ V}$, $i(t) = 2.5\cos(377t - 60^\circ) \text{ A}$.

2. $v(t) = 25 \cos(2\pi \times 10^3 t + 40^\circ) \text{ V}$,
 $i(t) = 0.2 \cos(2\pi \times 10^3 t - 10^\circ) \text{ A}$.

3. $V = 110 \angle 60^\circ \text{ V}$, $I = 3 \angle 45^\circ \text{ A}$.

4. $V = 440 \angle 0^\circ \text{ V}$, $I = 0.5 \angle 75^\circ \text{ A}$.

$$S = \frac{V \cdot I^*}{2}$$

1. $V = 100 \angle -30^\circ$ $I = 2.5 \angle -60^\circ$

$$S = \frac{(100 \angle -30^\circ)(2.5 \angle 60^\circ)}{2}$$

$$= 125 \angle 30^\circ$$

$$= 125 \cos(30^\circ) + j125 \sin(30^\circ)$$

$$= 108.25 + j62.5$$

$$P = 108.25 \text{ W}$$

$$Q = 62.5 \text{ VA}$$

$$|S| = 125$$

$$\text{PF} = \cos(30^\circ) = 0.86$$

2. $V = 25 \angle 40^\circ$ $I = 0.2 \angle -10^\circ$

$$S = \frac{(25 \angle 40^\circ)(0.2 \angle 10^\circ)}{2}$$

$$= 2.5 \angle 50^\circ$$

$$= 2.5 \cos(50^\circ) + j 2.5 \sin(50^\circ)$$

$$= 1.61 + j1.91$$

$$P = 1.61$$

$$Q = 1.91$$

$$|S| = 2.5$$

$$PF = \cos(50) = 0.64$$

$$3. \quad \mathbf{V} = 110 \angle 60$$

$$\mathbf{I} = 3 \angle 45$$

$$S = \frac{(110 \angle 60)(3 \angle -45)}{2}$$

$$= 165 \angle 15$$

$$= 165 \cos(15) + j 165 \sin(15)$$

$$= 159.38 + 42.7j$$

$$P = 159.38$$

$$Q = 42.7$$

$$|S| = 165$$

$$PF = \cos(15) = 0.96$$

$$4. \quad \mathbf{V} = 440 \angle 0^\circ$$

$$\mathbf{I} = 0.5 \angle -75^\circ$$

$$S = \frac{(440)(0.5 \angle -75)}{2}$$

$$= 110 \angle -75$$

$$= 110 \cos(-75) + j 110 \sin(-75)$$

$$= 28.47 - 106.25j$$


$$P = 28.47$$

$$Q = -106.25$$

$$|S| = 110$$

$$PF = \cos(-75) = 0.26$$

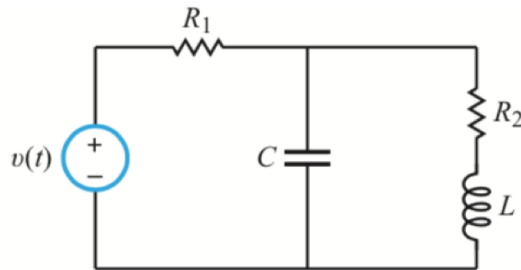- In the circuit below, $v(t) = 40 \cos(10^5 t) V$, $R_1 = 100 \Omega$, $R_2 = 500 \Omega$, $C = 0.1 \mu F$, and $L = 0.5 mH$. Determine the complex power for each passive element, and verify that conservation of energy is satisfied.




$$V = 40 \angle 0^\circ$$


$$\omega = 10^5$$

$$Z_C = \frac{-j}{10^5 (0.1 \times 10^{-6})} = -100j$$
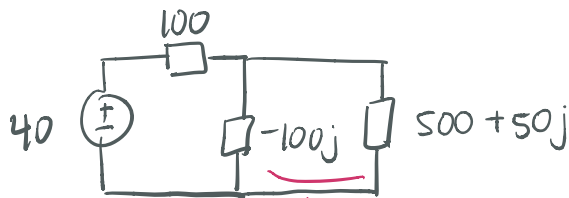
$$Z_L = j(10^5)(0.5 \times 10^{-3}) = 50j$$



parallel, same voltage

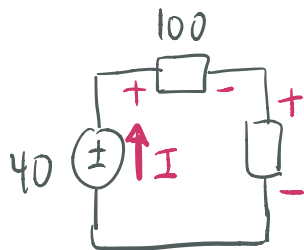

$$Z = \frac{(-100j)(500 + 50j)}{500 - 50j}$$

$$= 19.8 - 98.02j$$


$$= 100 \angle -78.58^\circ$$

voltage division

$$V_{100} = \frac{40 \cdot 100}{19.8 - 98.02j} = 25.84 \angle 39.29^\circ$$

$$V_{\perp} = V_c = \frac{40 \cdot 100 \angle -78.58^\circ}{119.8 - 98.02j} = 25.84 \angle -39.29^\circ$$
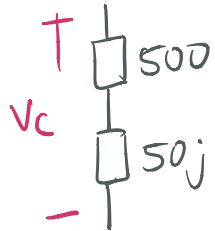
$$I = \frac{40}{119.8 - 98.02j} = 0.26 \angle 39.29^\circ$$



$$I_{500} = I_L = \frac{V_c}{500 + 50j} = 0.05 \angle -45^\circ$$

$$S_c = \frac{(25.84)^2}{2(100j)} = -3.34j$$

$$S_L = \frac{(0.05)^2 (50j)}{2} = 0.06j$$

$$S_{100} = \frac{(25.84)^2}{2 \cdot 100} = 3.34$$

$$S_{500} = \frac{(0.05)^2 (500)}{2} = 0.625$$

$$\underline{\underline{3.97 - 3.28j}}$$

$$S = \frac{V \cdot I^*}{2} \quad \begin{aligned} &= \frac{V_m^2}{2 \cdot Z^*} \\ &= \frac{I_m^2 \cdot Z}{2} \end{aligned}$$

$$I = \frac{V}{Z}$$

$$I^* = \frac{V^*}{Z^*}$$

$$V = I \cdot Z$$

$$S_{Vs} = \frac{40 (0.26 \angle -39.29^\circ)}{2} = 5.2 \angle -39.29^\circ$$

$$\underline{\underline{= 4.02 - 3.29j}}$$