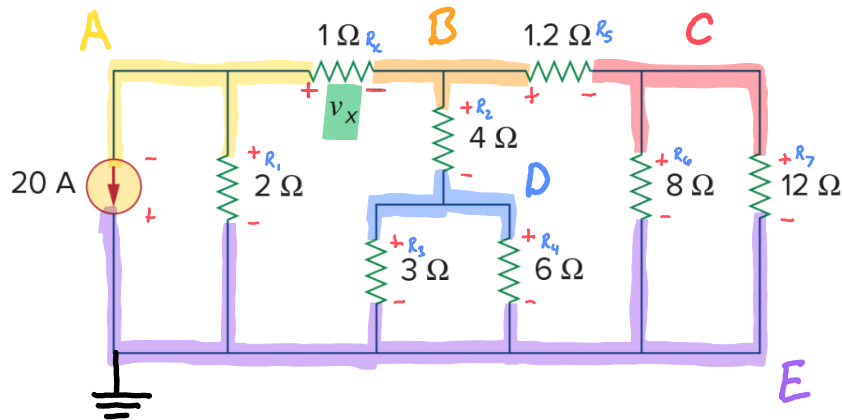


Homework 2

Due: Friday, February 3rd, 2023 by 7PM.

Note: In order to receive full credit, you must show your work and carefully justify your answers. The correct answer without any work will receive little or no credit.


- Using equivalent resistance, current division, voltage division, and Ohm's Law only, find the voltage v_x in the circuit below.



$$i_A = 20A$$



$$V_E = 0V$$

$$V_B = V_A - V_C - V_D$$

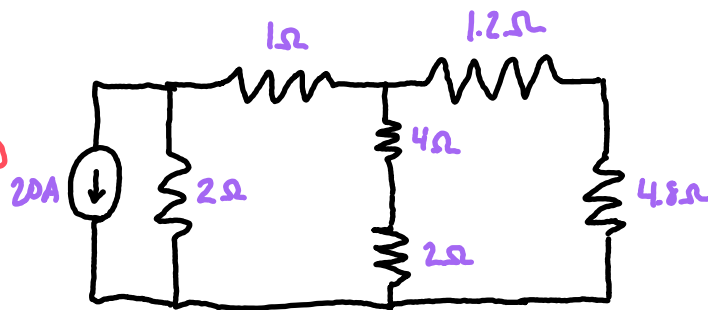


$$\frac{1}{\frac{1}{8} + \frac{1}{12}} = 4.8$$
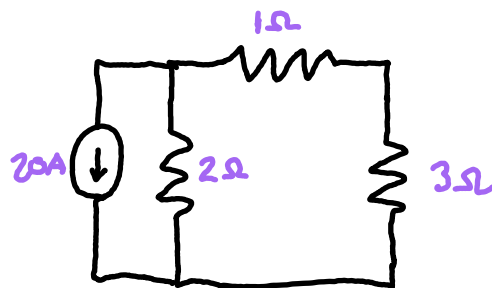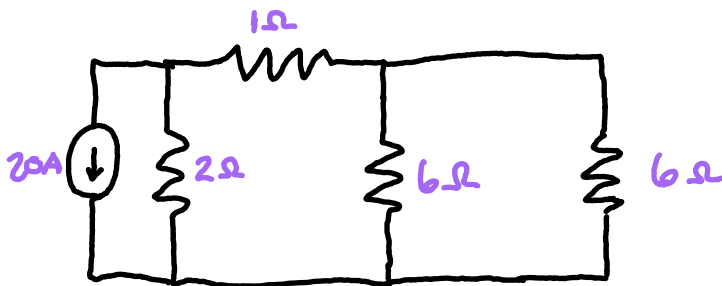
$$\frac{1}{\frac{1}{3} + \frac{1}{6}} = 2$$


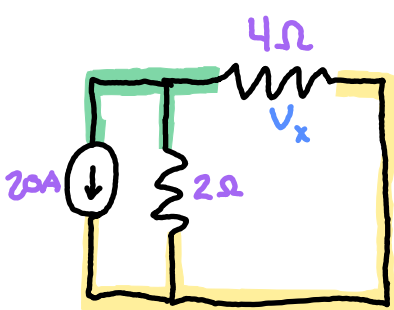
$$\frac{1}{\frac{1}{6} + \frac{1}{6}} = 3$$



$$I_x = \frac{R_T}{R_x + R_T} I_T$$

$$= \frac{2}{2+4} =$$

$$6.67A \cdot 1\Omega = 6.67V$$


$$I_x = \frac{2}{4+2} 20 = 6.67A$$

$$V_x = 6.67V$$


2. For the circuit below:

A. Find R_{eq} from node a and b.







B. Find R_{eq} from node b and c.

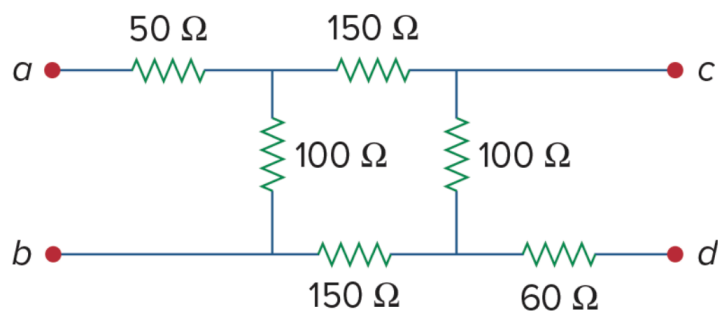

A.

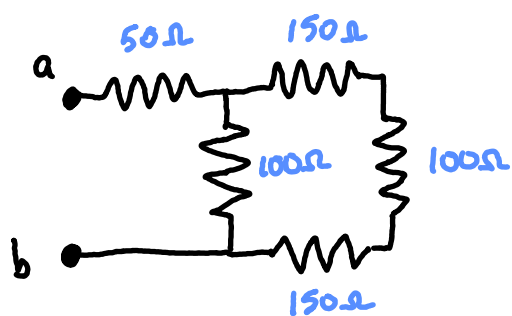


B

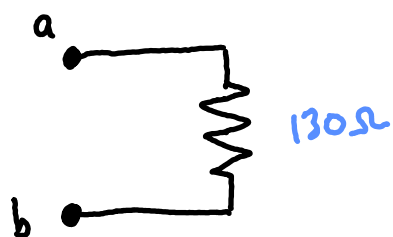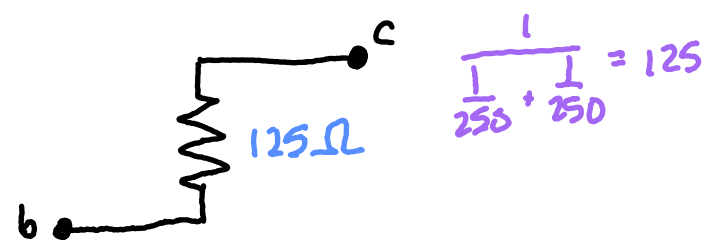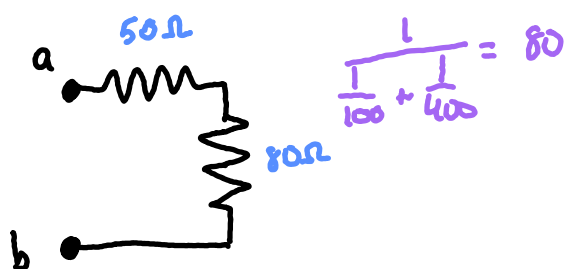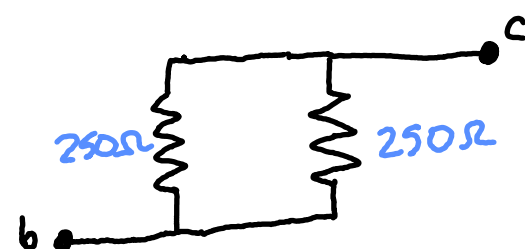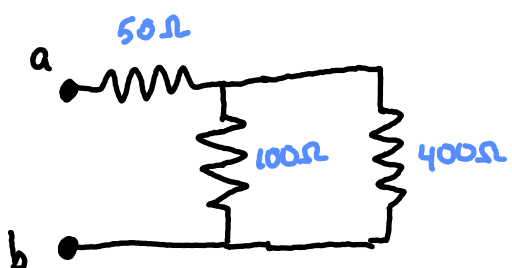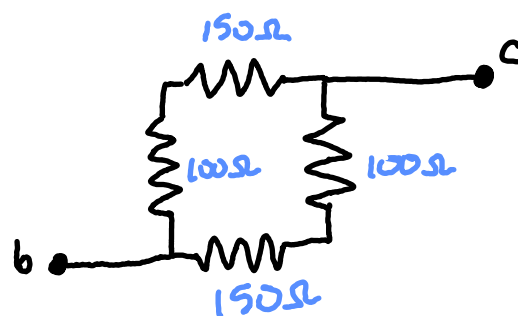

$$R_{eq} = 125 \Omega$$

$$R_{eq} = 130 \Omega$$

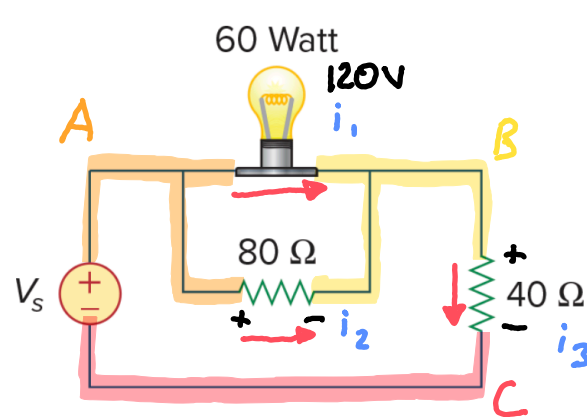3. The 60 W light bulb is rated at 120 V. Calculate the value of V_s to make the light bulb operate at its rated conditions.



$$P = VI$$

$$P = \frac{V^2}{R}$$

$$R = \frac{V^2}{P}$$

$$I = \frac{P}{V}$$

KCL@ B.

$$i_3 = i_1 + i_2$$

Ohm's Law $I = \frac{V}{R}$

$$\frac{V_3}{R_3} = \frac{1}{2} + \frac{V_2}{R_2}$$

$$\frac{V_3}{40} = \frac{1}{2} + \frac{120}{80} = \frac{1}{2} + \frac{3}{2}$$

$$\underline{V_3 = 2 \cdot 40 = 80V}$$


KVL@ C:

$$V_s = V_1 + V_3$$

$$V_s = 120 + 80 = 200V$$

$$V_s = 200V$$

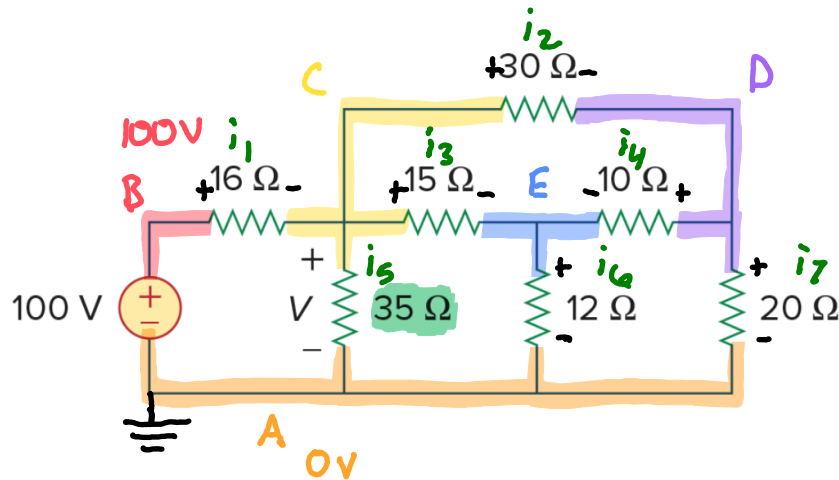4. Using node voltage analysis to find voltage V across the 35Ω resistor.



KCL @ A:

$$i_5 + i_6 + i_7 = 0$$

KCL @ C:

$$i_1 = i_2 + i_3 + i_5$$

$$\frac{V_1}{16} = \frac{V_2}{30} + \frac{V_3}{15} + \frac{V_5}{35}$$

$$65V_1 = 35V_2 + 70V_3 + 30V_5$$

$$65(V_B - V_C) = 35(V_C - V_D) + 70(V_C - V_E) + 30(V_C)$$

$$0 = 70V_C - 35V_D - 70V_E + 65V_B$$

$$V_C = \frac{1}{2}V_D + V_E - \frac{13}{14}V_B$$

KCL @ D:

$$i_7 = i_2 + i_4$$

$$\frac{V_7}{20} = \frac{V_2}{30} + \frac{V_4}{10}$$

$$3V_7 = 2V_2 + 6V_4$$

$$3V_D = 2(V_C - V_D) + 6(V_E - V_D)$$

$$0 = 2V_C - 11V_D + 6V_E$$

$$V_C = \frac{11}{2}V_D - 3V_E$$

KCL @ E:

$$i_6 = i_3 + i_4$$

$$\frac{V_6}{12} = \frac{V_3}{15} + \frac{V_4}{10}$$

$$5V_6 = 4V_3 + 6V_4$$

$$5V_E = 4(V_C - V_E) + 6(V_E - V_D)$$

$$0 = 4V_C - 6V_D - 3V_E$$

$$V_C = \frac{3}{2}V_D + \frac{3}{4}V_E$$

$$i_1 = 100$$

$$V_1 = V_B - V_C$$

$$V_2 = V_C - V_D$$

$$V_3 = V_C - V_E$$

$$V_4 = V_E - V_D$$

$$V_5 = V_C$$

$$V_6 = V_E$$

$$V_7 = V_D$$

$$V = 42V$$