




Autumn 2024 – ECE 5020

Homework 3

Due: 09/25/2024

   
1. For the following schematics

- Write Y in terms of the inputs (What logic function does it perform?)
- Size the schematics to have same drive strength as a 2/1 inverter.
- Show how they could be constructed with just INV, NAND and NOR gates (logic construction before you took ECE 5020).



 2. Consider the pulldown network.

- What logic function does it perform?
- Construct its pull up (dual) network.
- Size it to have same drive strength as a 2/1 inverter.



3. Construct a static complementary CMOS logic for the following expressions.

(a) $Y = \bar{A} + B + (S + C)D + R(\bar{C} + \bar{D})$

(b) $Y = \overline{A(B + C) + BAC}$

(c) $Y = \overline{ABC(D + E) + C(B + A)}$