
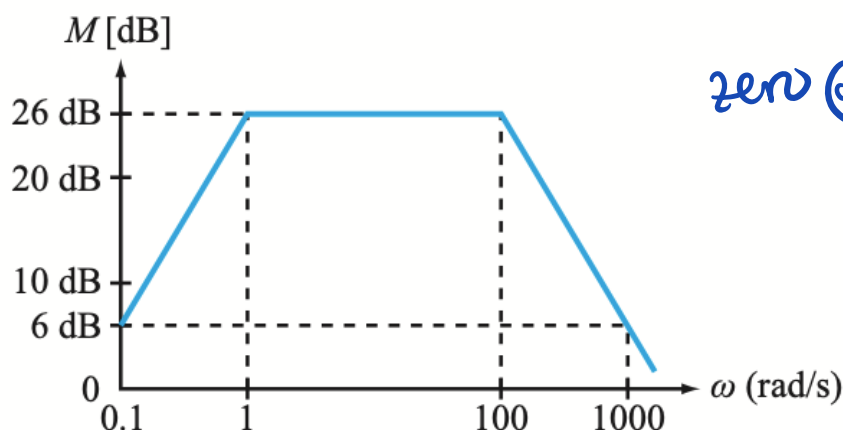


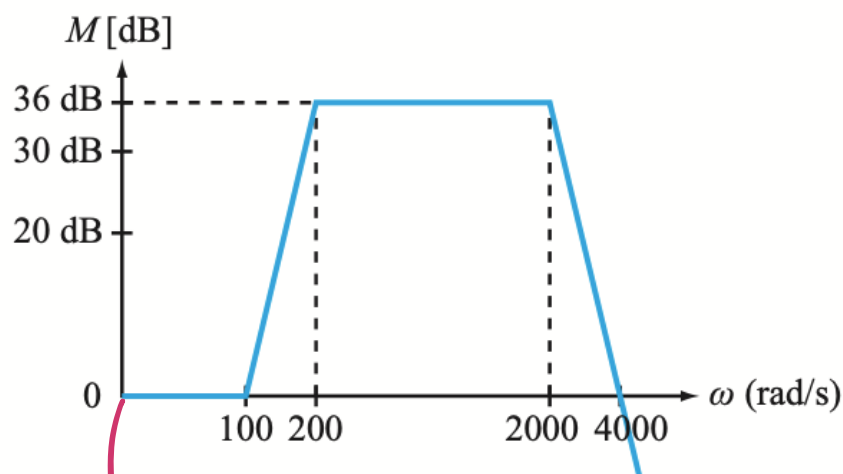

What is the gain K for the bode plots below



start with slope  
zero @ 0  
pole @ 0  
 $\omega = 1 \Rightarrow 0 \text{ dB}$



$0 \text{ dB} = 20 \log_{10}(K) \Rightarrow K = 1$

$$26 \text{ dB} = 20 \log_{10}(K)$$

$$\frac{26}{20} = \log_{10}(K)$$

$$K = 10^{26/20} = 19.95$$





THE OHIO STATE UNIVERSITY

---

COLLEGE OF ENGINEERING

# Intro to Operational Amplifiers




- Learning Objectives:
  - Describe the basic properties of an op amp and state the constraints of the ideal op-amp model.







- Amplifier:

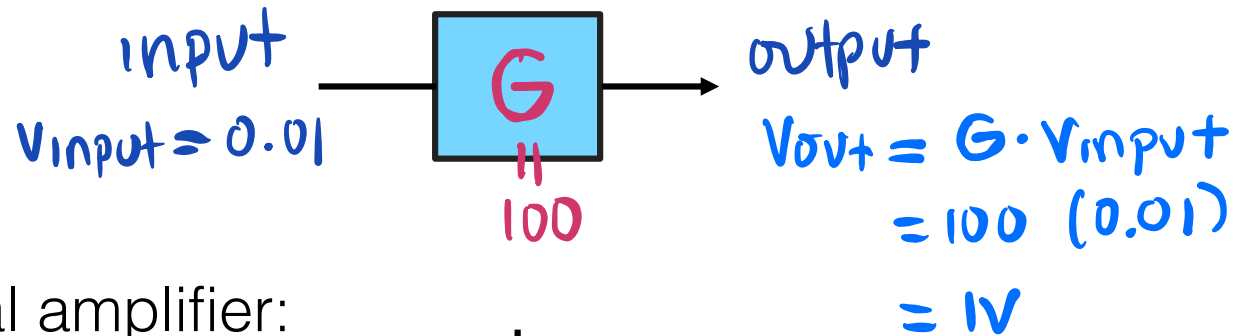

- Operational amplifier:

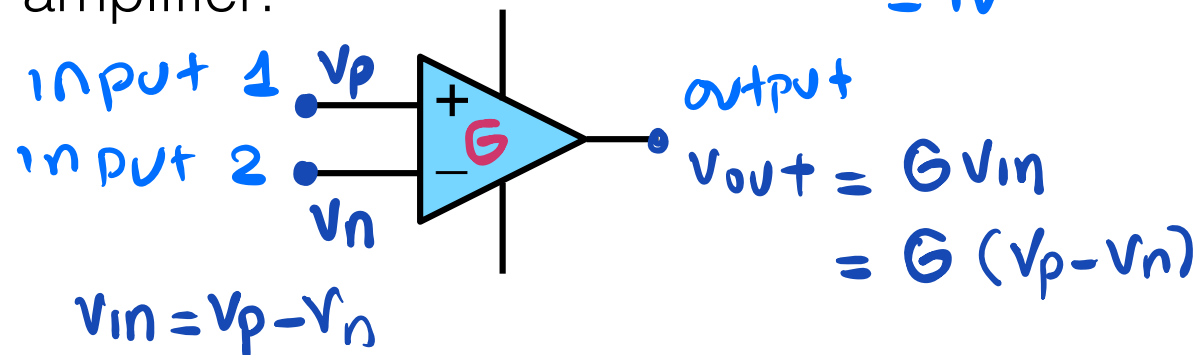


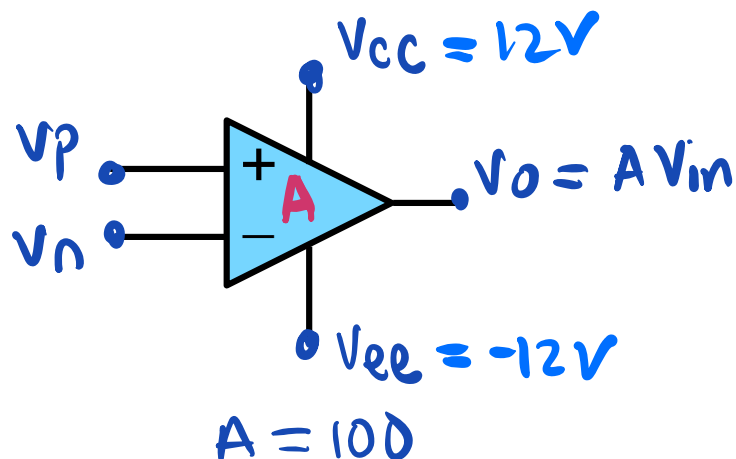- It acquired the adjective operational because it is a versatile device capable not only of amplifying a signal but also inverting it (reversing its polarity), integrating it, or differentiating it.




Properties:

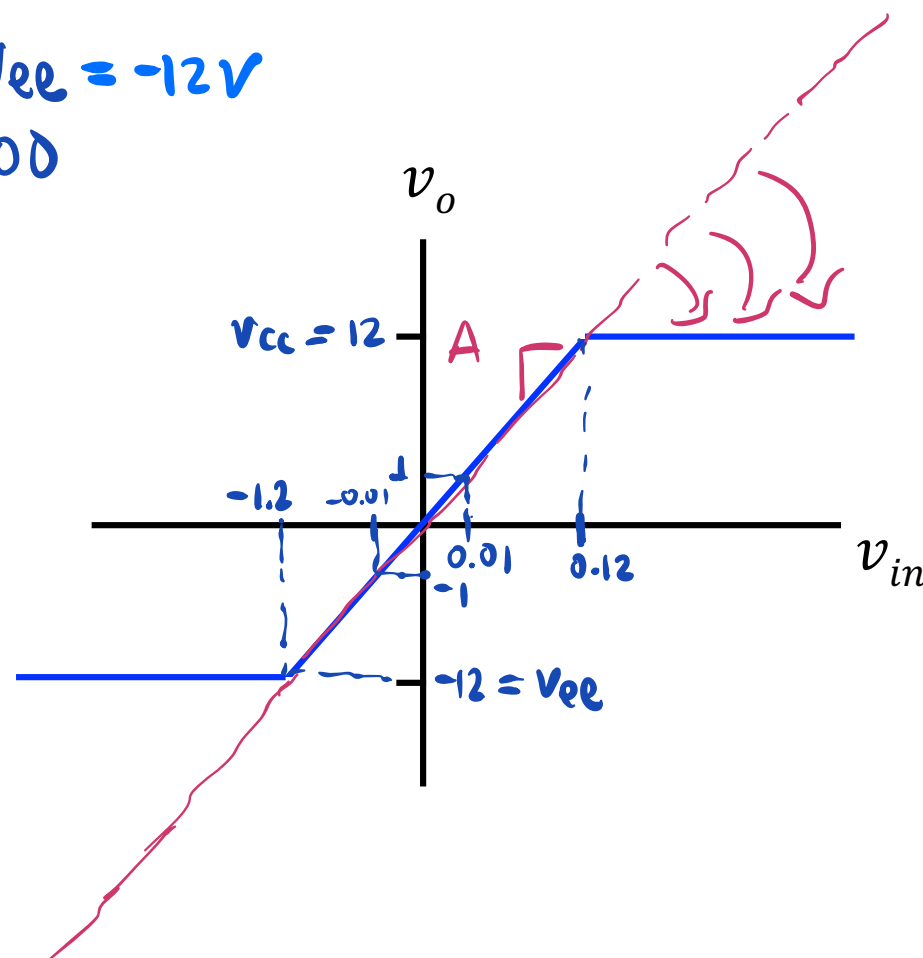- High Gain:  $A = 10^5 - 10^6$
- ✓ • Differential input:  $v_{in} = v_p - v_n$
- Linear operating range:
- Saturated by  $+v_{cc}$  and  $-v_{ee}$
- Usually  $v_{ee} = -v_{cc}$






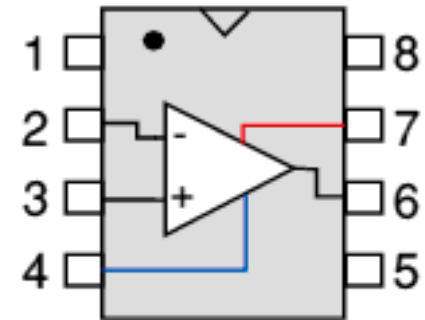
- Amplifier functions:
  - Signal Amplification.
  - Filtering.
  - Add, Subtract, Integrate, Differentiate.
- Example amplifier applications:
  - Digital audio player.
  - Measurement sensors.
  - Feedback.





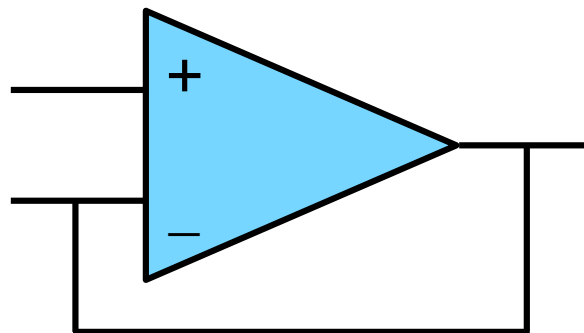- Process of using the output to reinforce (positive feedback) or inhibit (negative feedback) its input.
  - Open-loop mode if feedback is not used.
  - Closed-loop if feedback is used.
- Key benefits:
  - Decreased sensitivity to signal variations.
  - Increased bandwidth and linearity.
  - Increased signal-to-noise ratio.



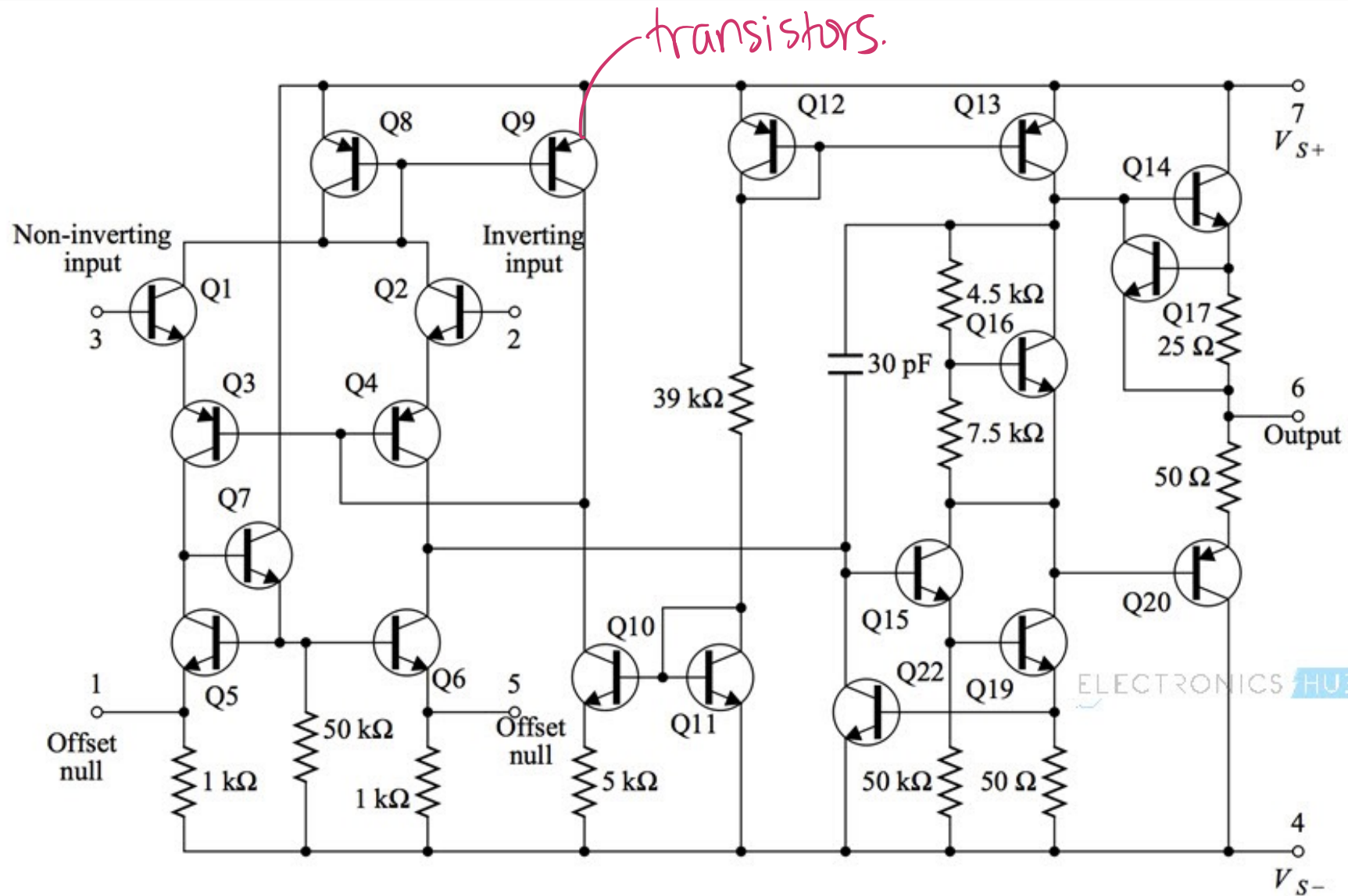


Internal Circuitry of 741 Op-Amp IC





# Amplifier Behavioral Model

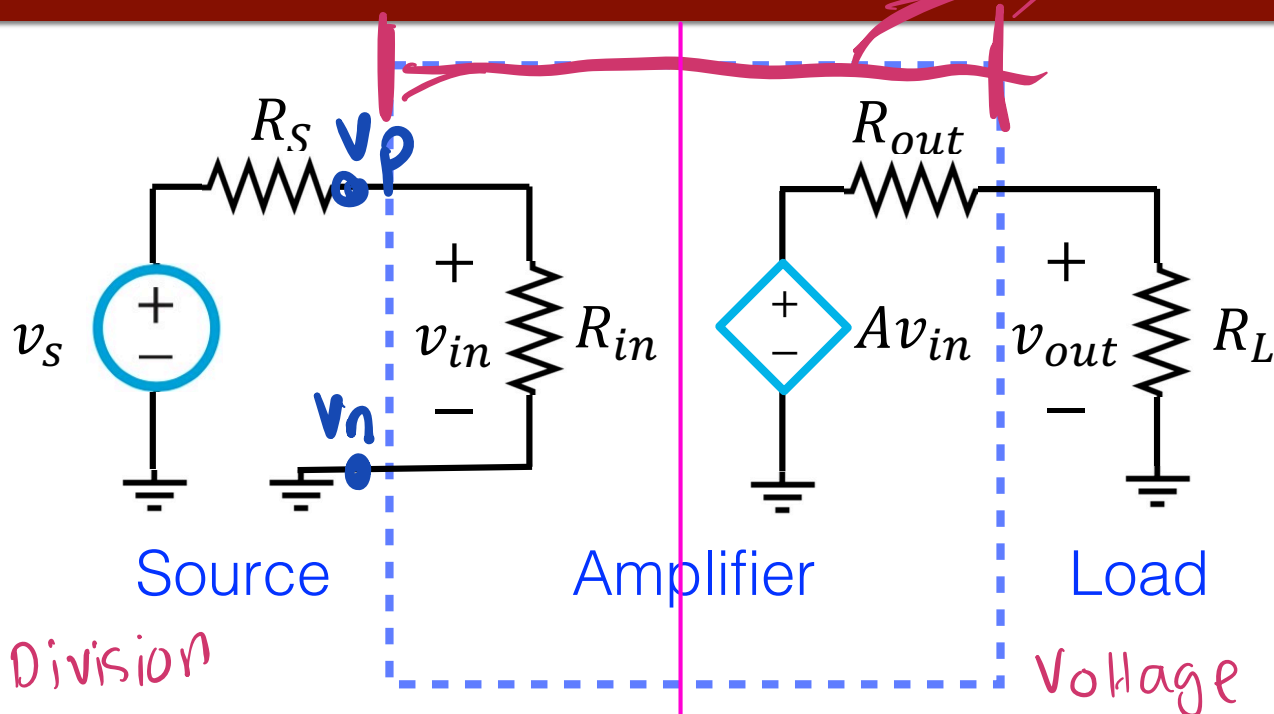

Voltage Division

$$v_{in} = \frac{R_{in}}{R_s + R_{in}} v_s$$

Voltage Division:

$$v_{out} = \frac{R_L}{R_{out} + R_L} \cdot A v_{in}$$


Ideally I want

$$v_{out} = G \cdot v_{in}$$

$$R_{out} = 0 \Omega \quad R_{in} = \infty$$

$$v_{out} = \frac{R_L}{R_{out} + R_L} \cdot A \cdot \frac{R_{in}}{R_s + R_{in}} v_s$$
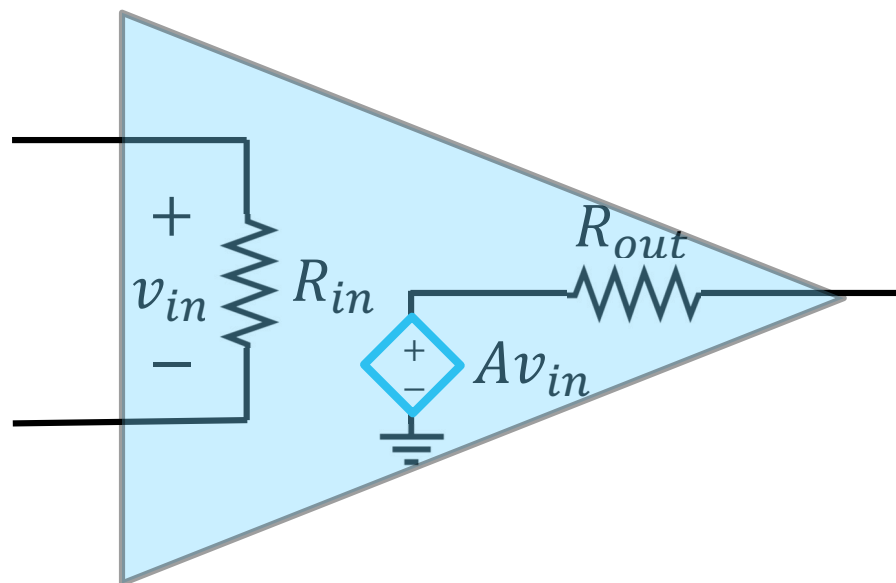
$$v_{out} = A v_s \frac{R_L}{R_{out} + R_L} \cdot \frac{R_{in}}{R_s + R_{in}}$$



Ideally

$$R_{out} = 0 \Omega$$

$$R_{in} = \infty$$


$$A = \infty$$

Realistically

$$R_{out} = 10 - 100$$

$$R_{in} = 10^6 - 10^{13}$$

$$A = 10^6$$

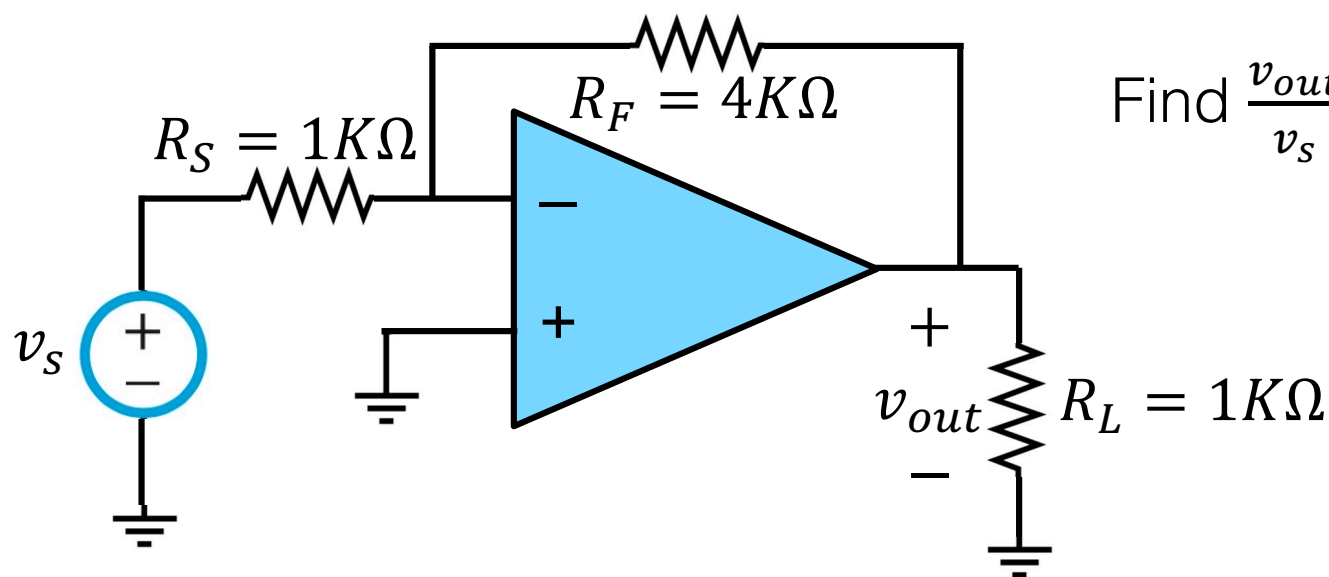


Find  $\frac{v_{out}}{v_s}$  given that:

$$R_{in} = 10^6 \Omega$$

$$R_{out} = 100 \Omega$$

$$A_{vol} = 10^6$$

Behavioral Model

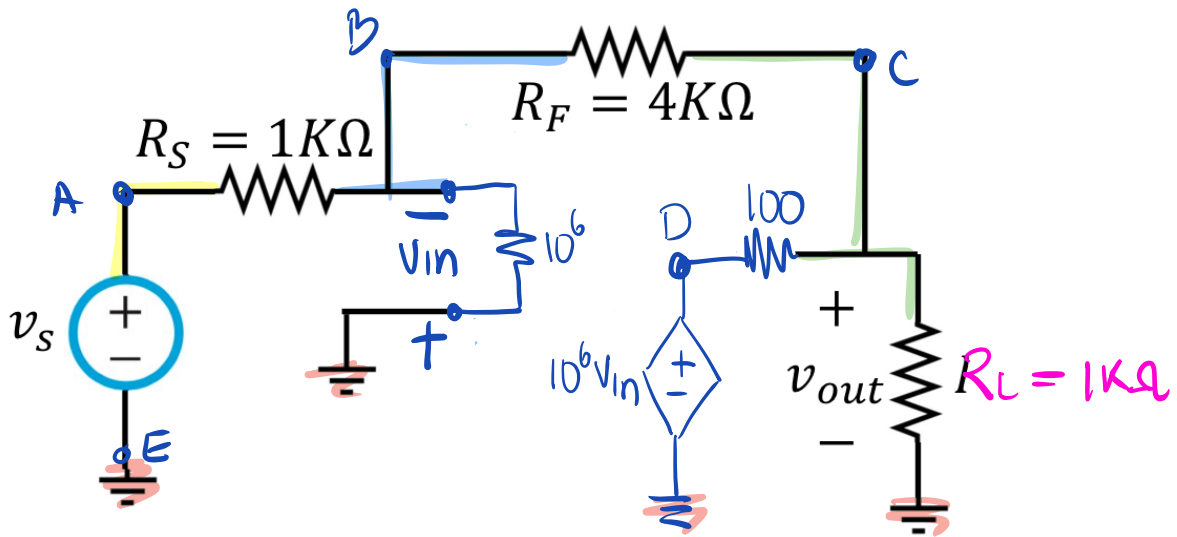

Node Voltage Analysis 5 nodes

$$V_E = 0V$$

$$V_D = 10^6 V_{in} = 10^6 (V_E - V_B) = -10^6 V_B$$

$$V_A = V_S$$

KCL @ B:

KCL @ C

we will finish on Wednesday.