
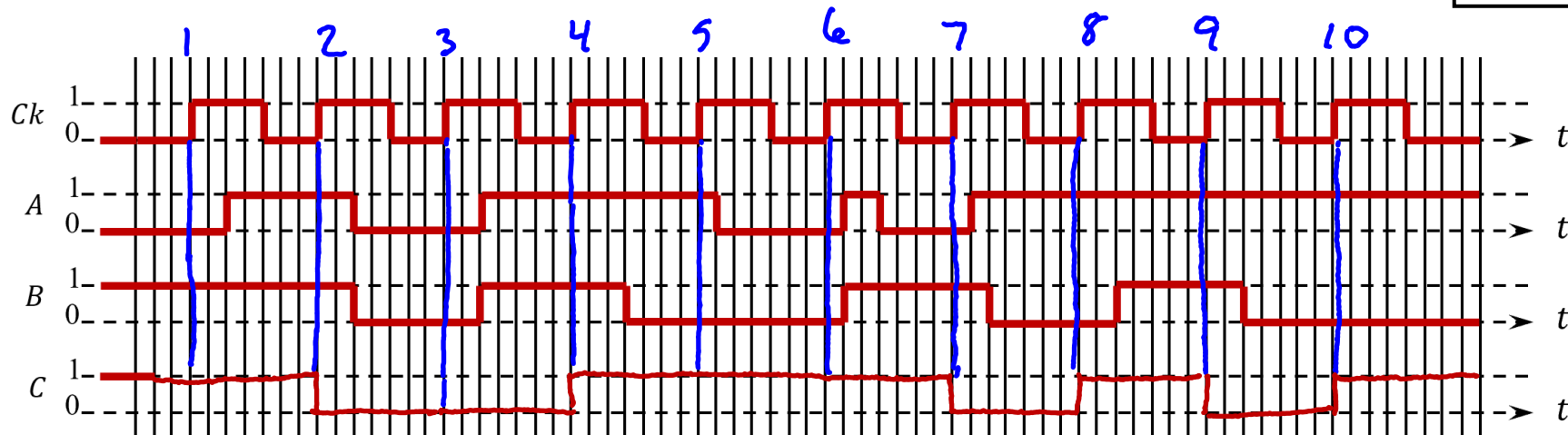


Complete the timing diagram below for the adjacent flip-flop.

For this problem the clock frequency is so low, and hence the clock period is so long, that the delay between the active clock edge and the new flip-flop output is negligible on the time-scale of this diagram.

 The thick bar on the left of the timing diagram shows the starting state of the flip-flop.



$$Q^+ = A Q' + B Q$$

Ck	A	A'	B	B'	Q	Q'	C (Q <sup>+</sup> )
1	0	1	1	0	1	0	1
2	1	0	1	0	1	0	0
3	0	1	0	1	0	1	0
4	1	0	1	0	0	1	1
5	1	0	0	1	1	0	1
6	0	1	0	1	1	0	1
7	0	1	1	0	1	0	0
8	1	0	0	1	0	1	1
9	1	0	1	0	1	0	0
10	1	0	0	1	0	1	1