
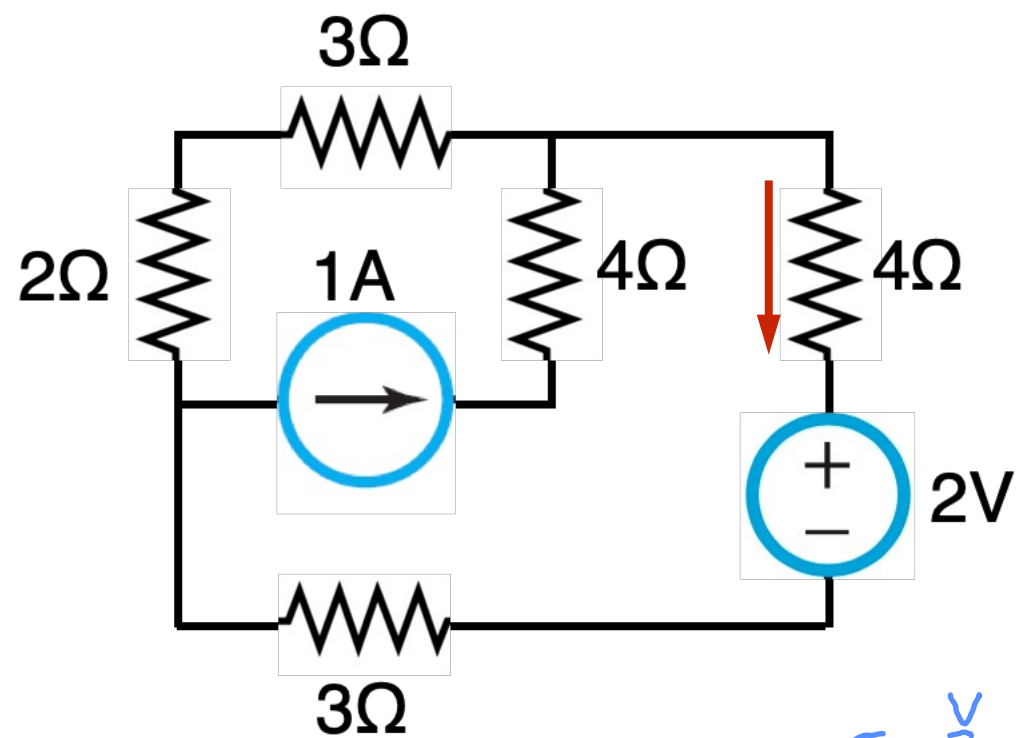


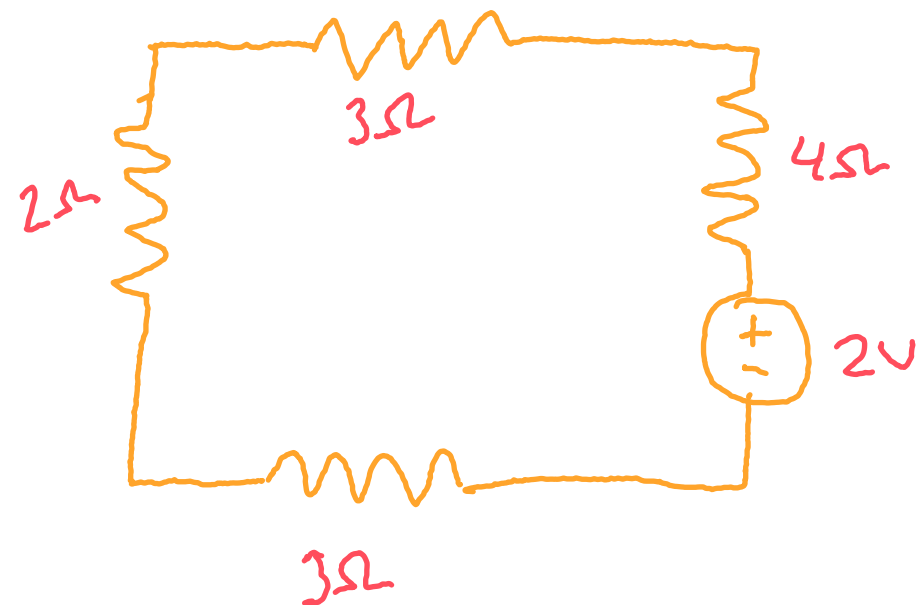

Use the principle of superposition to find the current i .



$$I = \frac{V}{R}$$



$$I = \frac{2}{12}$$

$$I = \frac{1}{6} A$$






THE OHIO STATE UNIVERSITY

COLLEGE OF ENGINEERING

Equivalent Circuits




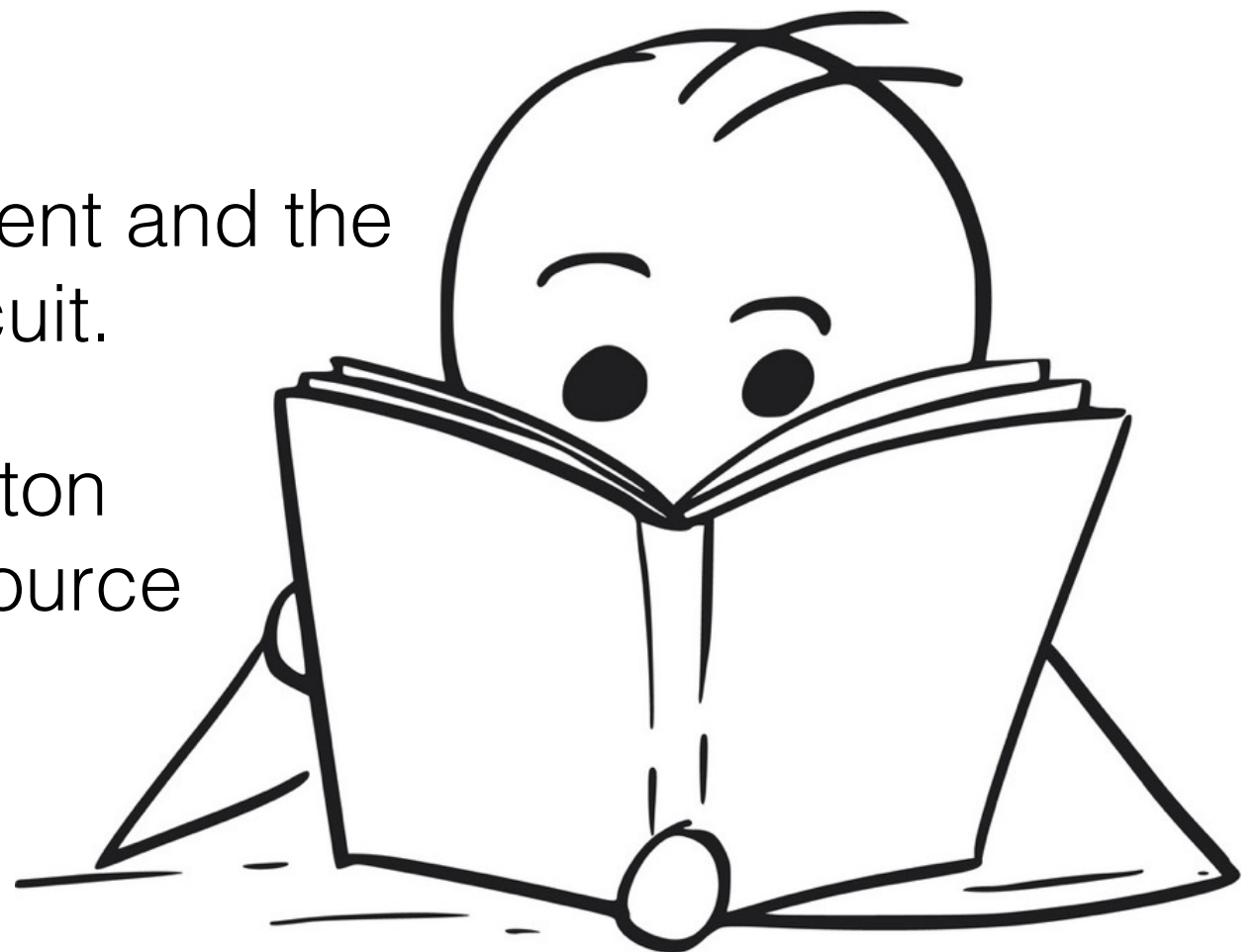- Learning Objectives:
 - Understand the importance and application of equivalent circuits.
 - Determine the Thévenin voltage and the Thevenin resistance of a circuit.
 - Determine the Norton current and the Norton resistance of a circuit.
 - Given the Thévenin or Norton equivalent circuit, apply source transformation.





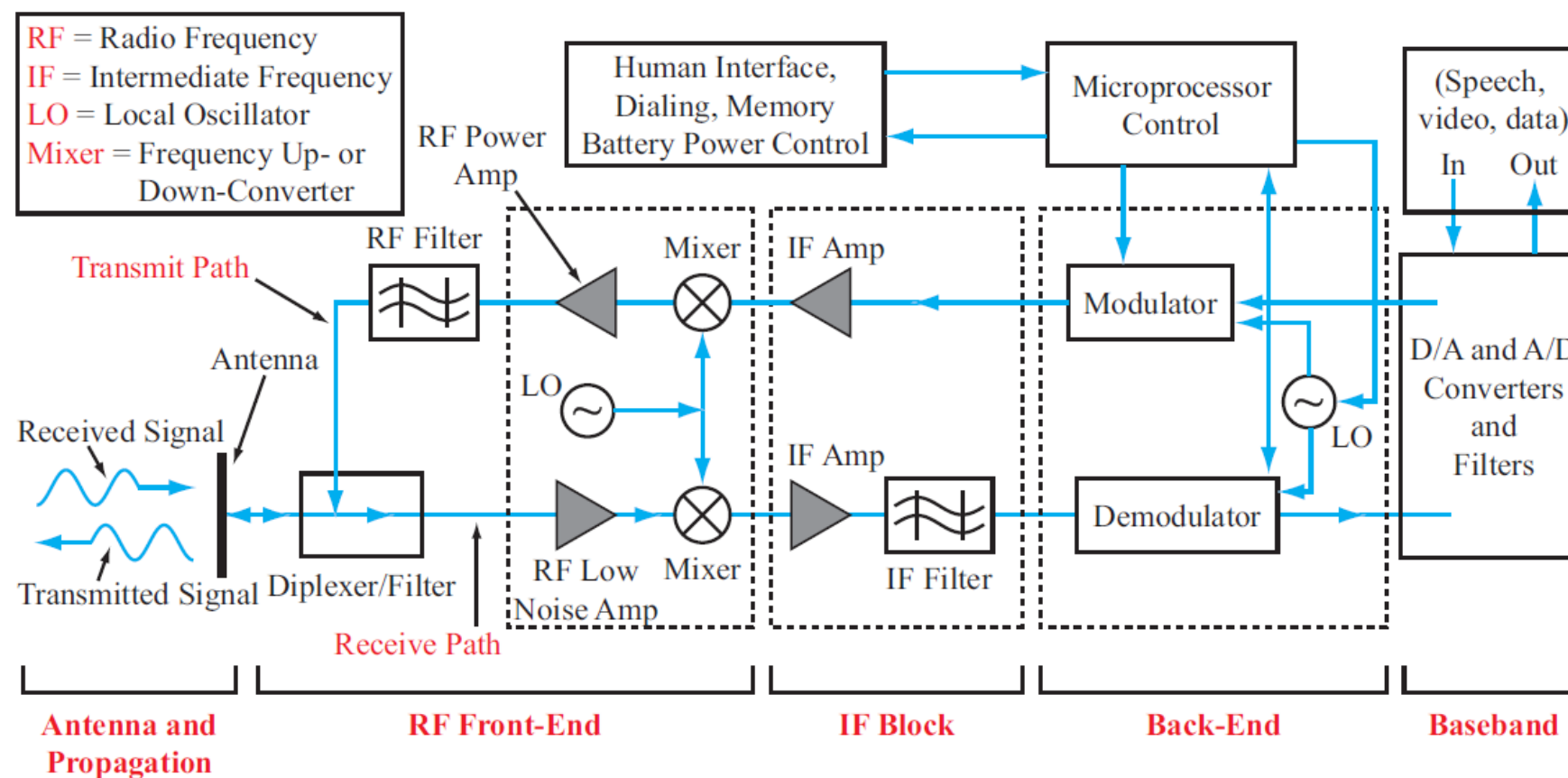
- Today's systems are complex. We use a block diagram approach to represent circuit sections.





Recall that:

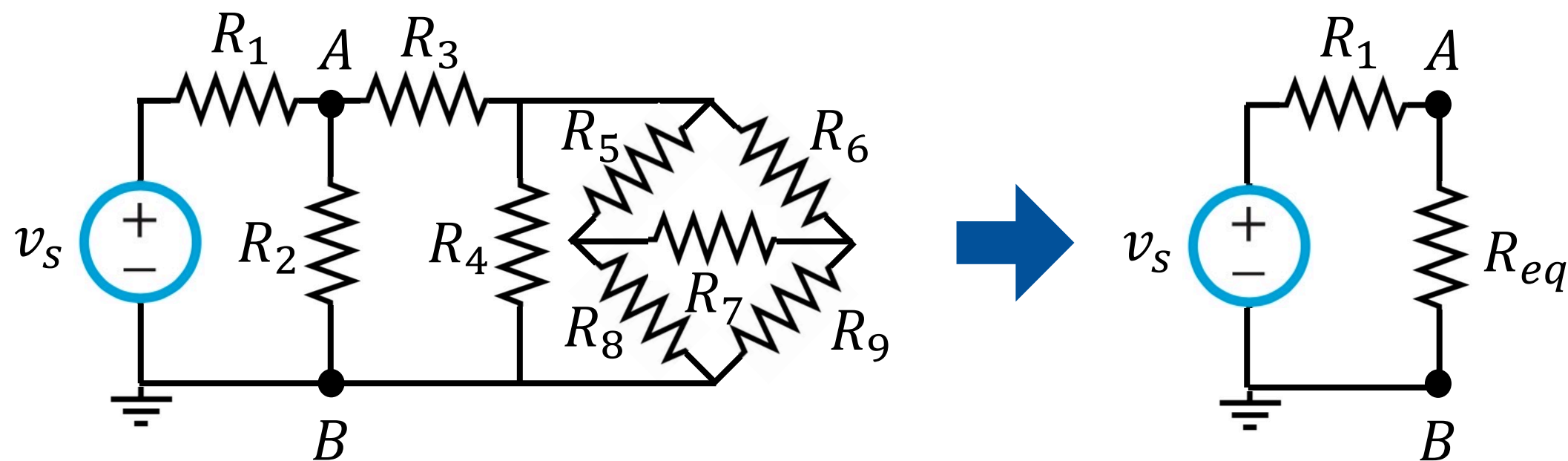
- Simplify analysis.
- Voltage and Current between A and B do not change.





Recall that:

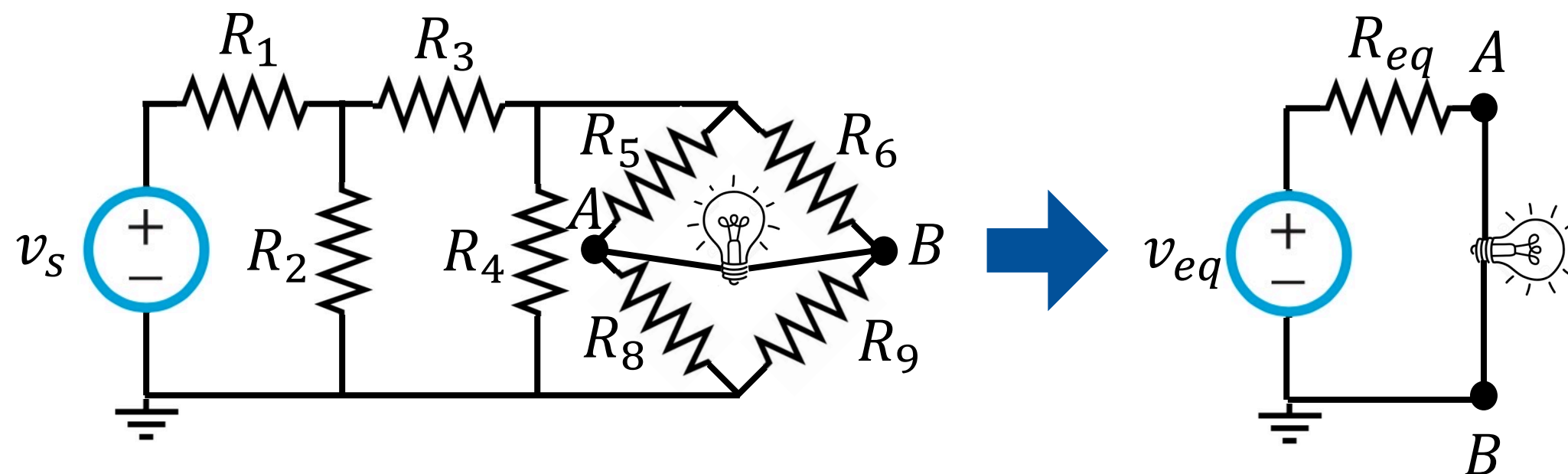
- Simplify analysis.
- Voltage and Current between A and B do not change.



Our ability to develop equivalent-circuit representations is made possible (in part) by a pair of theorems of fundamental significance known as Thévenin's and Norton's theorems.





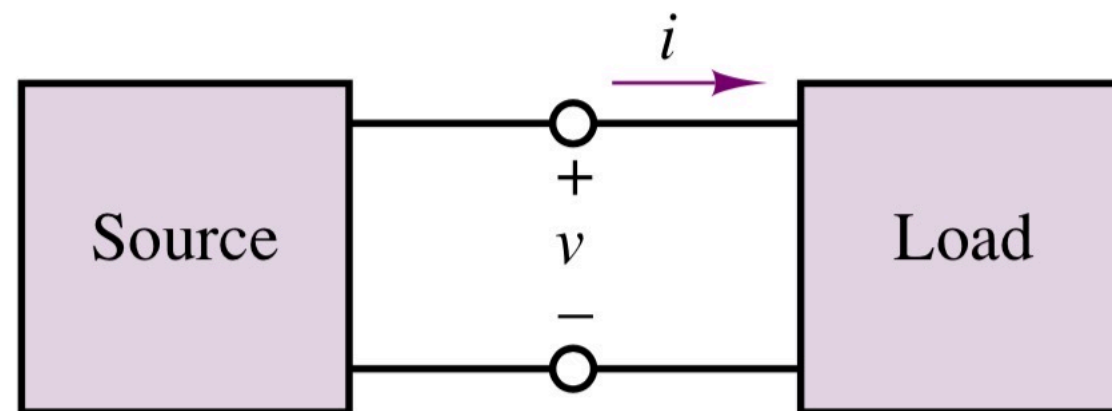- Linear two-terminal circuit can be replaced by an equivalent circuit:



Thévenin equivalent

Norton equivalent

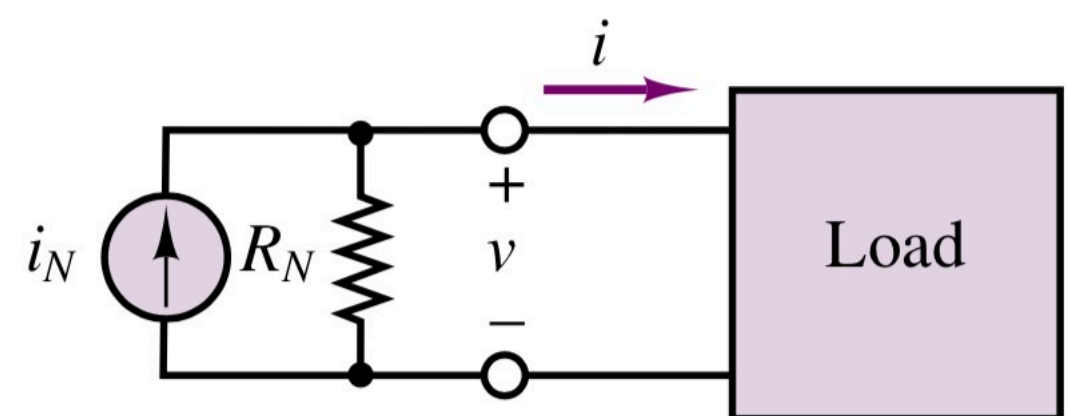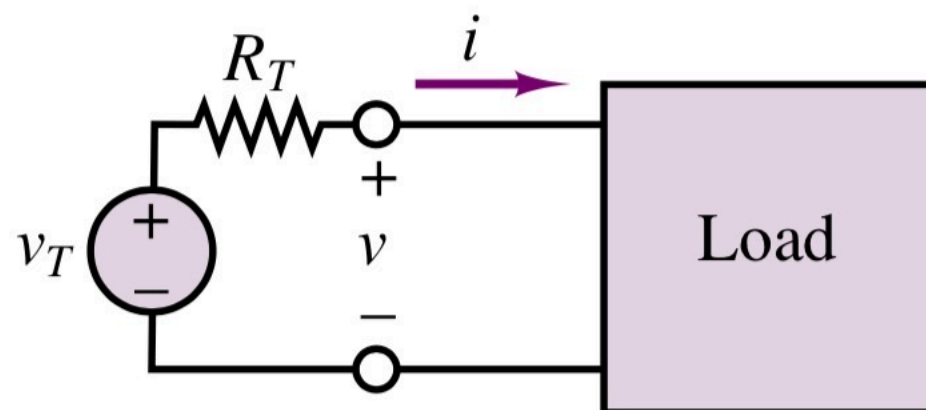


Composed of a voltage source and a series resistor.

Composed of a current source and parallel resistor.




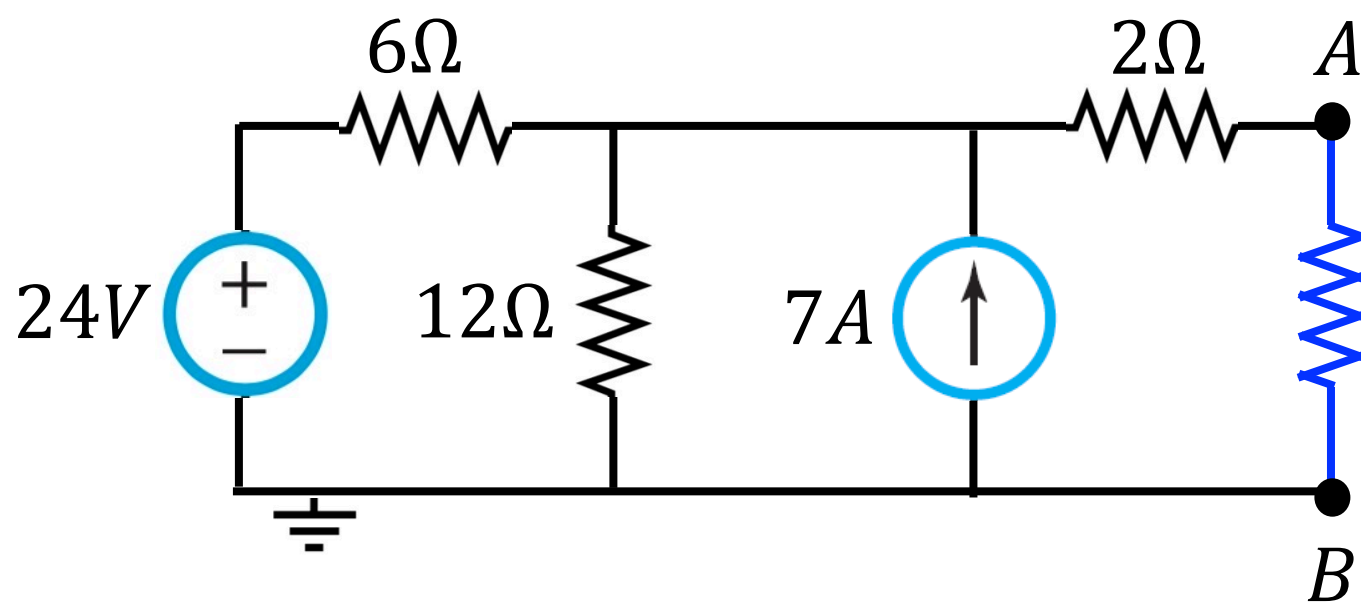1. Remove the load and set all independent sources to zero.






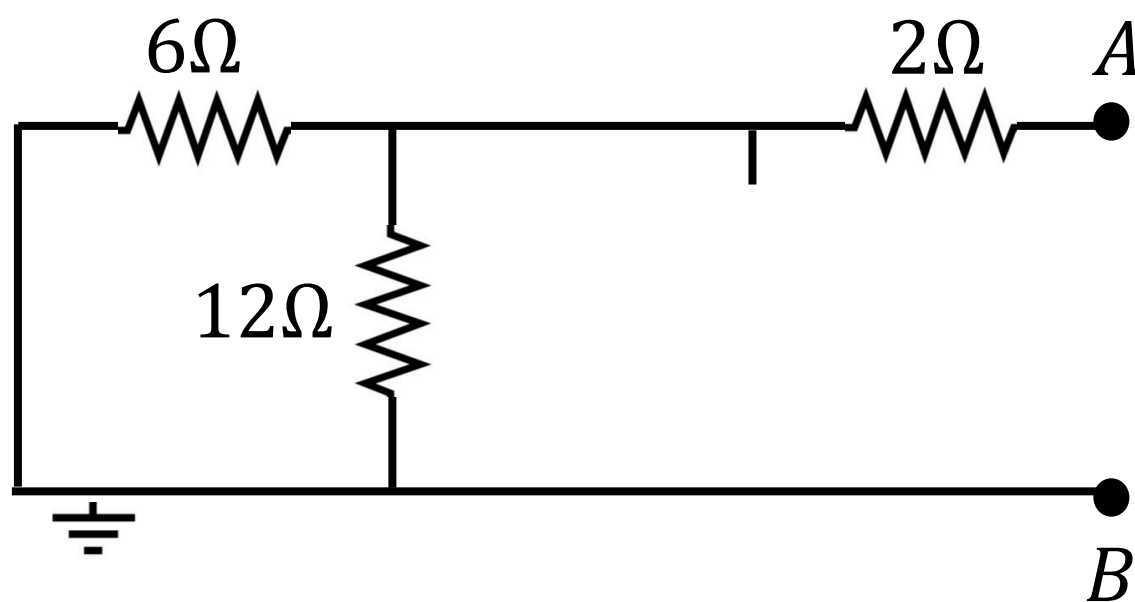1. Remove the load and set all independent sources to zero.
2. Apply series and parallel equivalent resistance substitutions to find effective equivalent resistance.
 - Sometimes may need to attach independent voltage source to the terminals (e.g., when there is a dependent source).






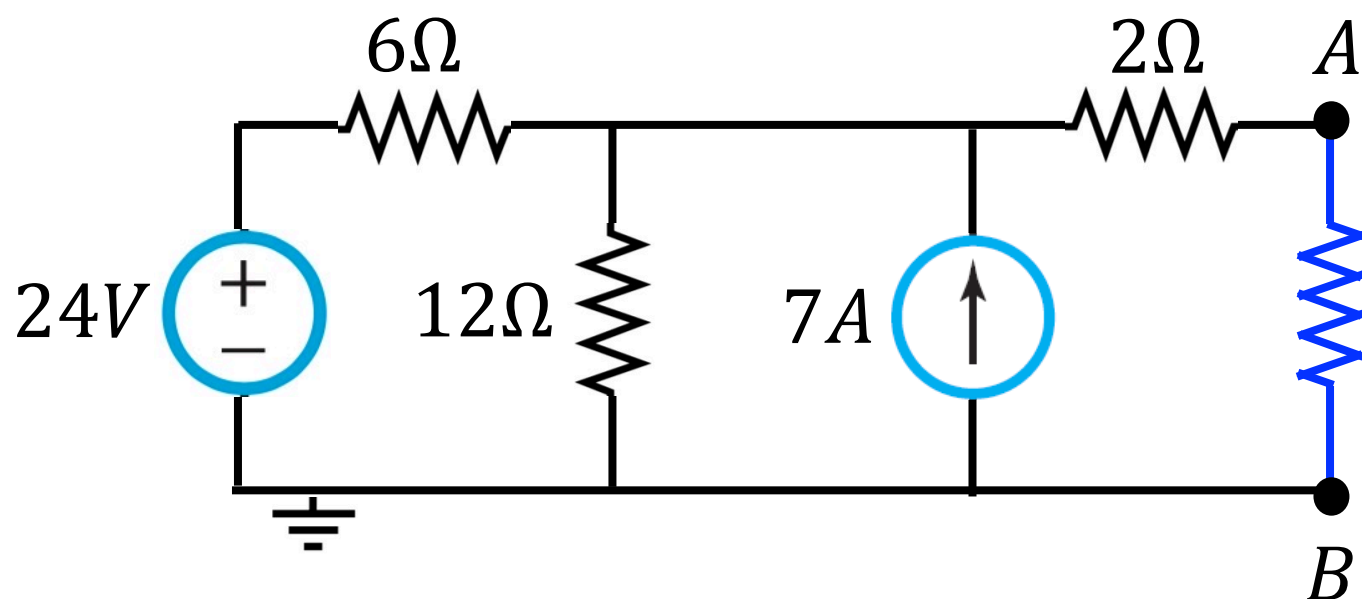1. Remove the load, leaving the load terminals open-circuited.






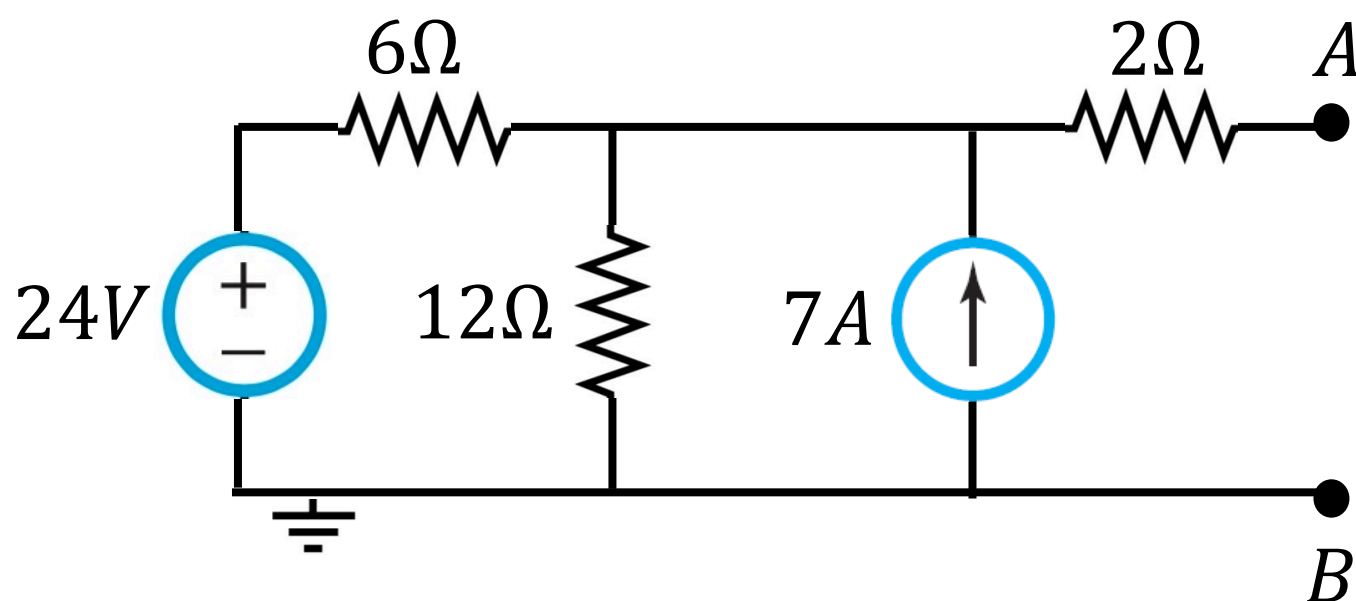1. Remove the load, leaving the load terminals open-circuited.
2. Define the open-circuit voltage v_{TH} across the open load terminals.
3. Apply any preferred method (e.g., nodal analysis, mesh analysis) to solve for v_{TH} .





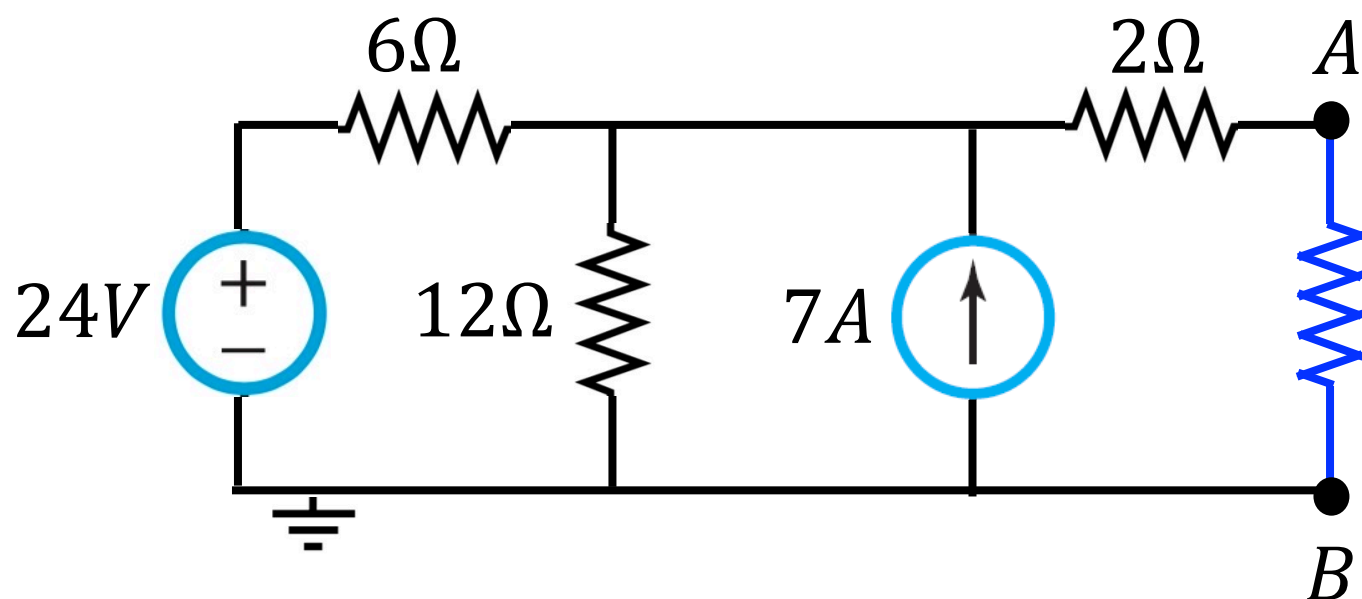1. Replace the load with a short circuit.





1. Replace the load with a short circuit.
2. Define the short circuit current, i_N , to be the Norton equivalent current.
3. Apply any preferred method (e.g., nodal analysis) to solve for i_N .

