

This is a Mealy machine design problem. Note that difference from Homework Problem 13-3.


For this problem you are to design another sequence detector. Design constraints:

1. It must be a Mealy machine.
2. The sequence it must detect in a serial string of 1s and 0s at input Y is "100".
3. You may assume that the values arriving at input Y are properly synchronized with the clock.
4. The output must be $Z = 1$ when the prescribed sequence is detected, and 0 otherwise.
5. The circuit does not have to automatically reset when a 1 output occurs. (Return to initial state only when appropriate for sequence detection.)
6. You MUST not use more than two flip-flops in your design.
7. Name the flip-flops A and B. One of the objectives of this problem is for you to see, through comparison with HW 13-3, that the same operation can be completed with fewer states in a Mealy machine than in a Moore machine. Thus, you may not use more than three states for your design. However, since two flip-flops can realize four states you may use S_0 and any two of the other three, with these state-name definitions: S_0 ($AB = 00$), S_1 ($AB = 01$), S_2 ($AB = 10$), S_3 ($AB = 11$)
8. Use S_0 for the initial state. It is up to you to decide what each of the other state-names mean with respect to the input sequence. Since you have some freedom of choice it is up to you to clearly articulate what each state-name means. See slide 6 of the 3/29 lecture, for example.
9. Logic must be implemented with no more than two levels and use only AND gates and OR gates (and a single inverter if you need to generate Y' from the Y input).

Please submit:

- a) Your design for the State Graph, with documentation of what each State means (see item 8 above).
- b) Corresponding State Table
- c) Corresponding Transition Table
- d) Corresponding flip-flop Next-State Maps and expressions derived therefrom.
- e) Circuit diagram

a)

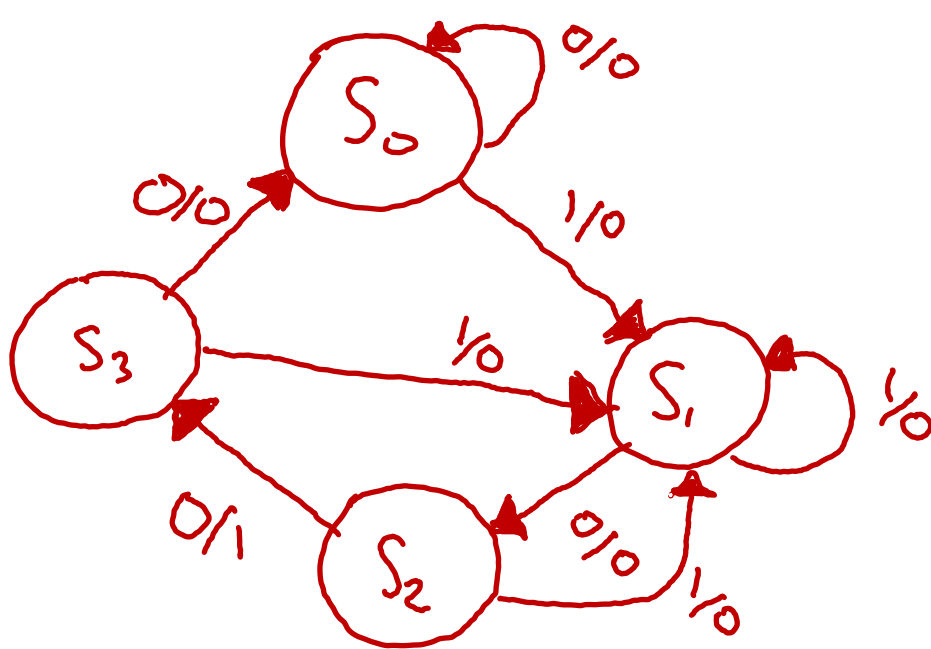

Realized my mistake in 13-3

b)

Present state	Next state		Present output	
	X=0	X=1	X=0	X=1
S ₀	S ₀	S ₁	0	0
S ₁	S ₂	S ₁	0	0
S ₂	S ₃	S ₁	1	0
S ₃	S ₀	S ₁	0	0

c)

AB	A ⁺ B ⁺		Z	
	X=0	X=1	X=0	X=1
01	01	00	0	0
00	10	00	0	0
10	11	00	1	0
11	01	00	0	0

d)

Hand-drawn truth table for the XOR operation:

Z	0	1
00	0	0
01	1	0
11	1	0
10	0	0

$$A^+ = BZ'$$

	0	1
00	1	0
01	0	0
11	1	0
10	1	0

$$B^+ = AZ' + B'Z$$

Hand-drawn Karnaugh map for the function $Z = A \oplus B \oplus C$. The map is a 4x2 grid with columns labeled 0 and 1, and rows labeled 00, 01, 11, and 10. The cell at row 11, column 0 contains a red '1' and is highlighted with a purple box.

	0	1
00	0	0
01	0	0
11	1	0
10	0	0

$$Z^+ = ABZ'$$

e)

