KCL @ N_1 :

$$i_{4K} = i_{24K}$$

$$\frac{v_{S1} - v_{S2}}{4K} = \frac{v_{S2} - v_{O1}}{24K}$$

$$6v_{S1} - 6v_{S2} = v_{S2} - v_{O1}$$

$$v_{O1} = 7v_{S2} - 6v_{S1}$$

KCL @ N_2 :


$$i_{20K} = i_{400K}$$

$$\frac{v_{O1} - v_{S3}}{20K} = \frac{v_{S3} - v_O}{400K}$$

$$20v_{O1} - 20v_{S3} = v_{S3} - v_O$$

$$v_O = 21v_{S3} - 20v_{O1}$$
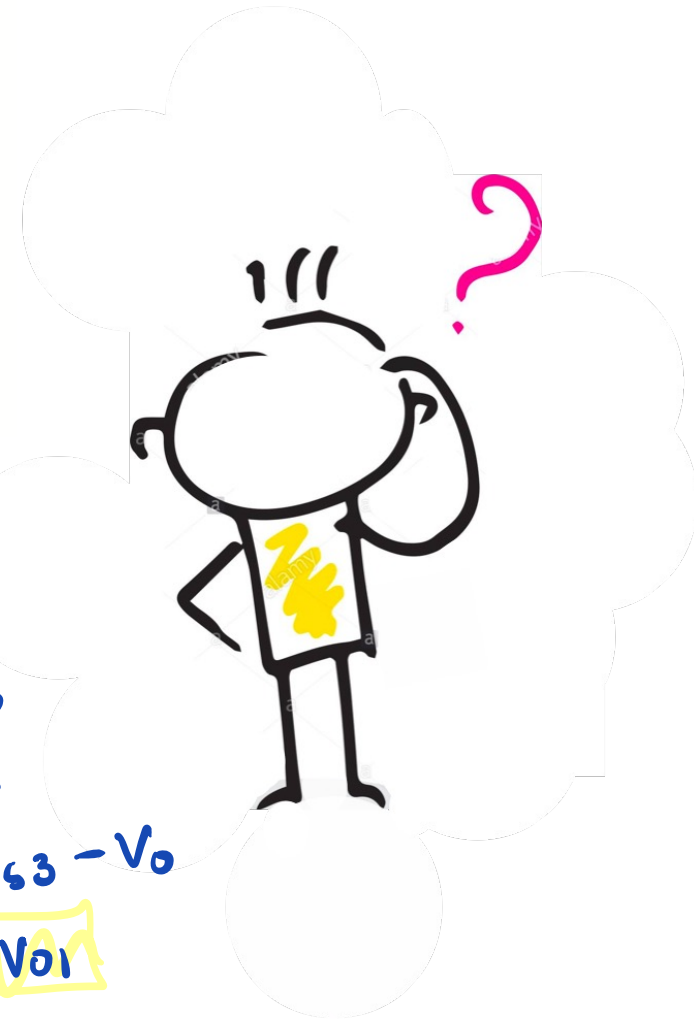
$$v_O = 21v_{S3} - 20(7v_{S2} - 6v_{S1}) = 21v_{S3} - 140v_{S2} + 120v_{S1}$$





THE OHIO STATE UNIVERSITY

COLLEGE OF ENGINEERING

Op-amp models

Active Filters



- Learning Objectives:
 - Combine multiple op-amp circuits together to perform signal processing operations.
 - Analyze and design simple active filters.





Table 4-3: Summary of op-amp circuits.

Op-Amp Circuit	Block Diagram
(a)	 Noninverting Amp (v_o independent of R_s)
(b)	 Inverting Amp
(c)	 Inverting Summing Amp
(d)	 Subtracting Amp
(e)	 Voltage Follower / Buffer (v_o independent of R_s and R_L)
(f)	 Noninverting Summing Amp

$$TF = \frac{\text{output}}{\text{input}}$$

inputs \rightarrow \rightarrow output


$$\text{output} = TF \cdot \text{input}$$



- A filter that contains an active component (op-amps).
- Op-amps can provide amplification (gain) in addition to the filtering effects.


Passive

Review on LPF:



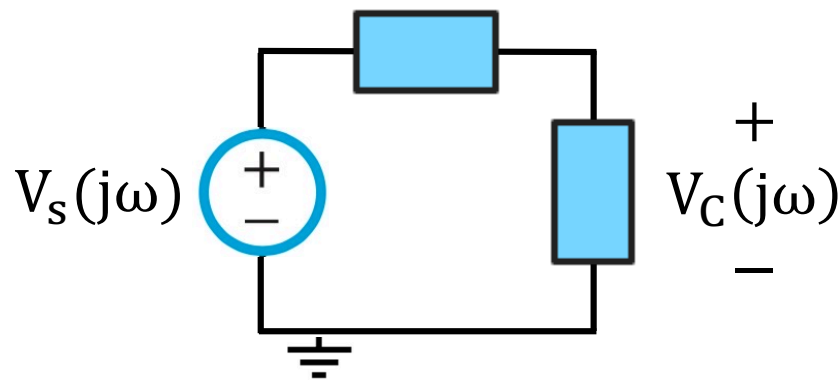


$$\frac{V_C}{V_S} = \frac{1}{1 + j\omega CR}$$

Review on Inverting Amplifier:

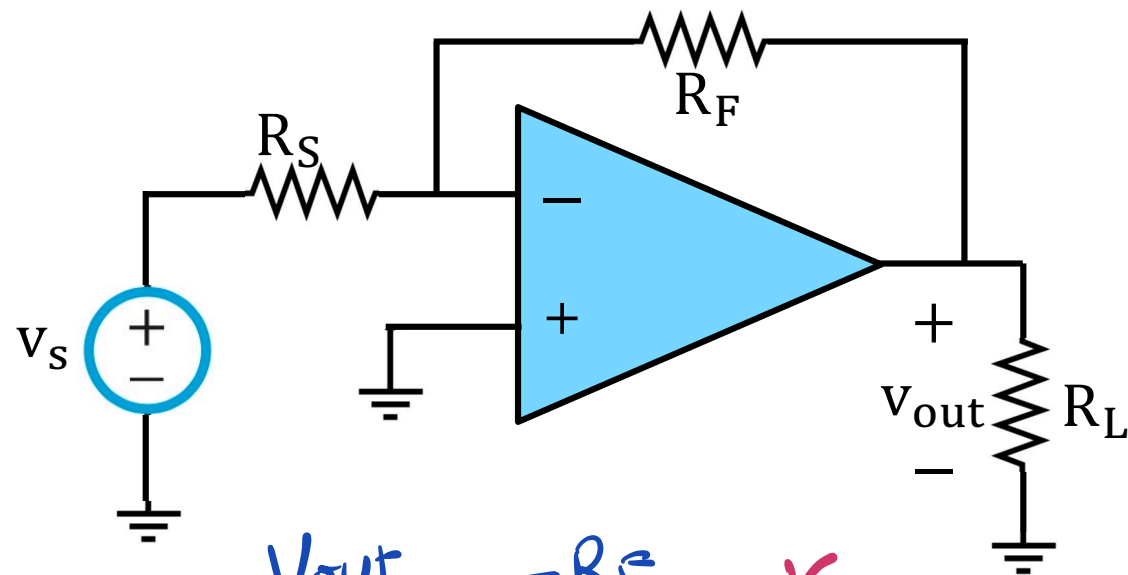
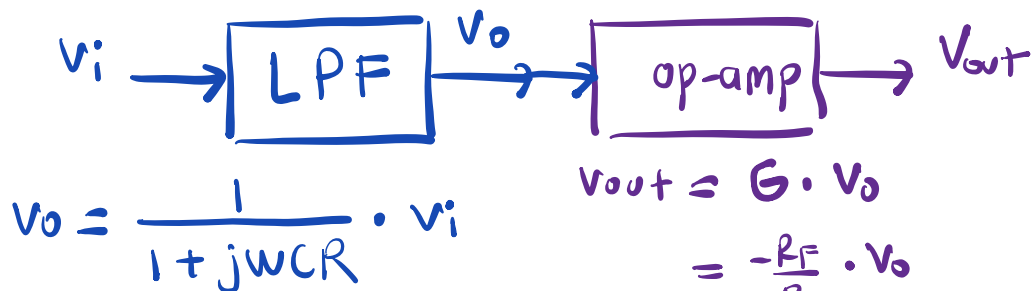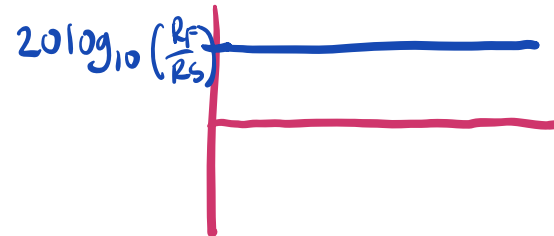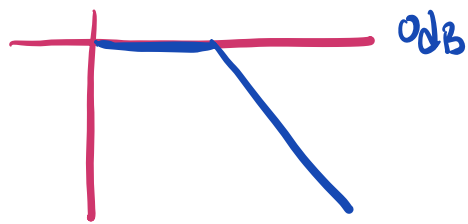
$$\frac{V_{out}}{V_S} = -\frac{R_F}{R_S} = K$$




$$V_{out} = G \cdot V_o$$

$$= -\frac{R_F}{R_S} \cdot V_o$$


$$V_{out} = -\frac{R_F}{R_S} \cdot \frac{1}{1 + j\omega CR} \cdot V_i$$
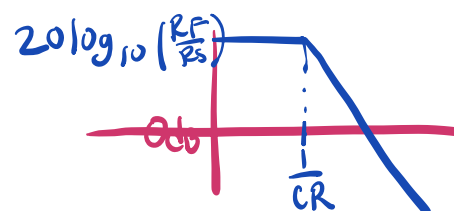
$$\frac{V_{out}}{V_i} = \underbrace{-\frac{R_F}{R_S}}_{\text{gain}} \cdot \underbrace{\frac{1}{1 + j\omega CR}}_{\text{LPF}}$$






Find $\frac{v_{out}}{v_s}$

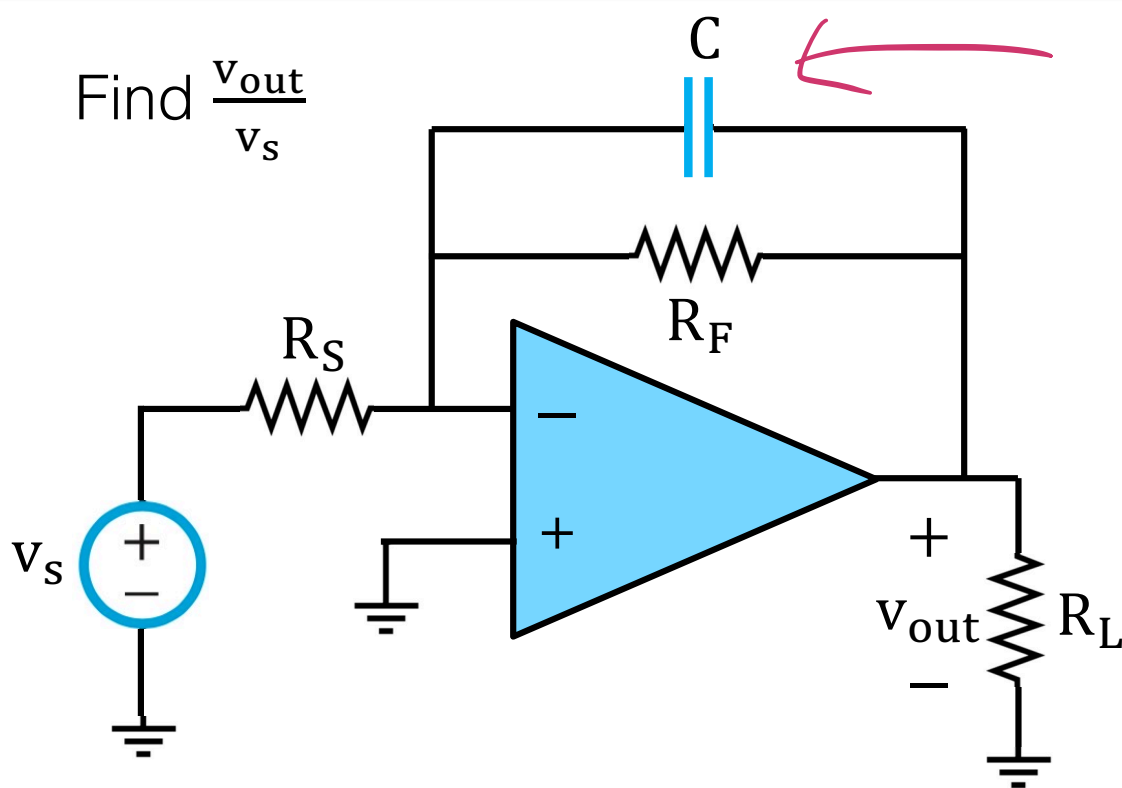

phasor domain

$$z_C = \frac{1}{j\omega C}$$

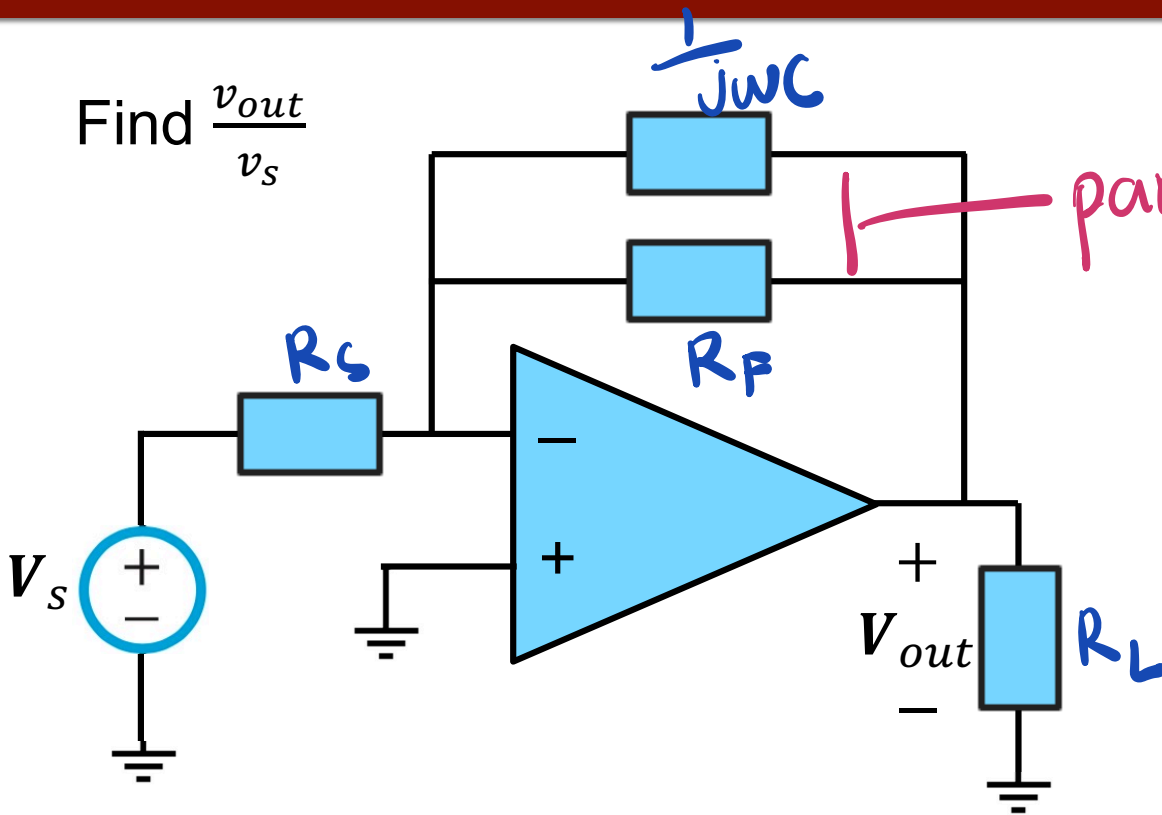

parallel


$$z_F = \frac{\frac{R_F}{j\omega C}}{R_F + \frac{1}{j\omega C}}$$

$$\times \frac{j\omega C}{j\omega C}$$

$$= \frac{R_F}{j\omega C R_F + 1}$$



Active Low-Pass Filter

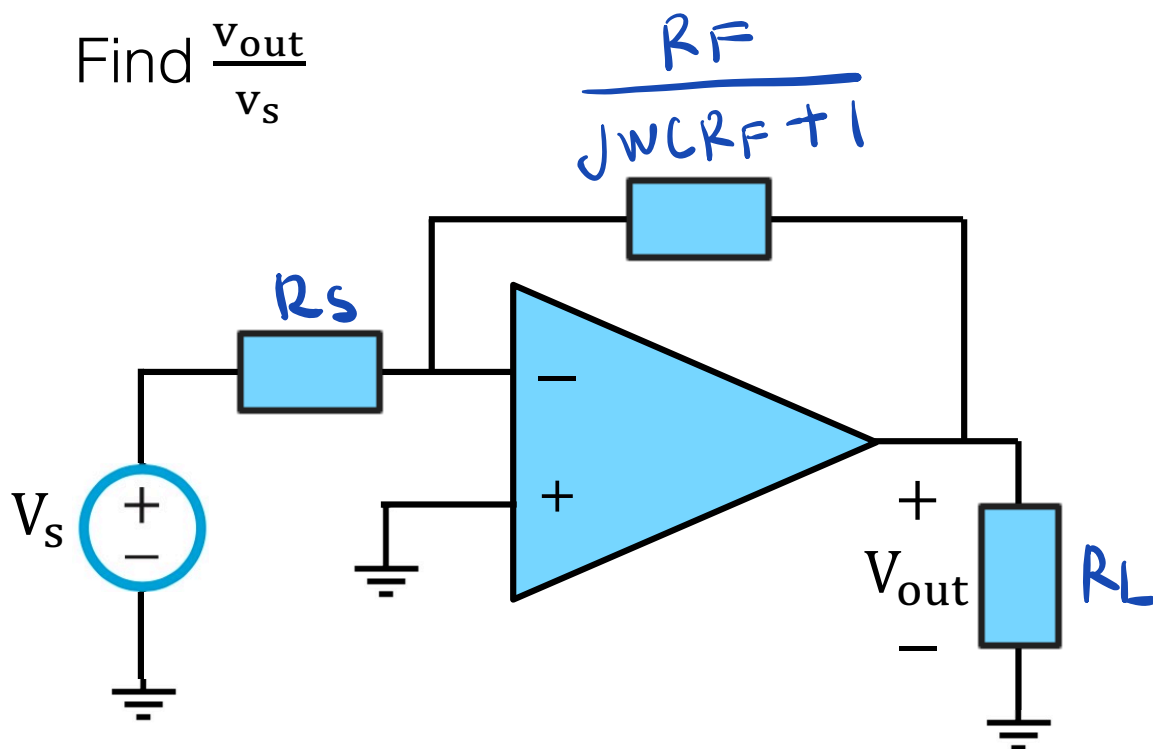
Find $\frac{V_{out}}{V_s}$ 


inverting op-amp.


$$\frac{V_{out}}{V_s} = - \frac{Z_F}{R_s}$$

$$= - \frac{\frac{R_F}{j\omega C R_F + 1}}{R_s}$$
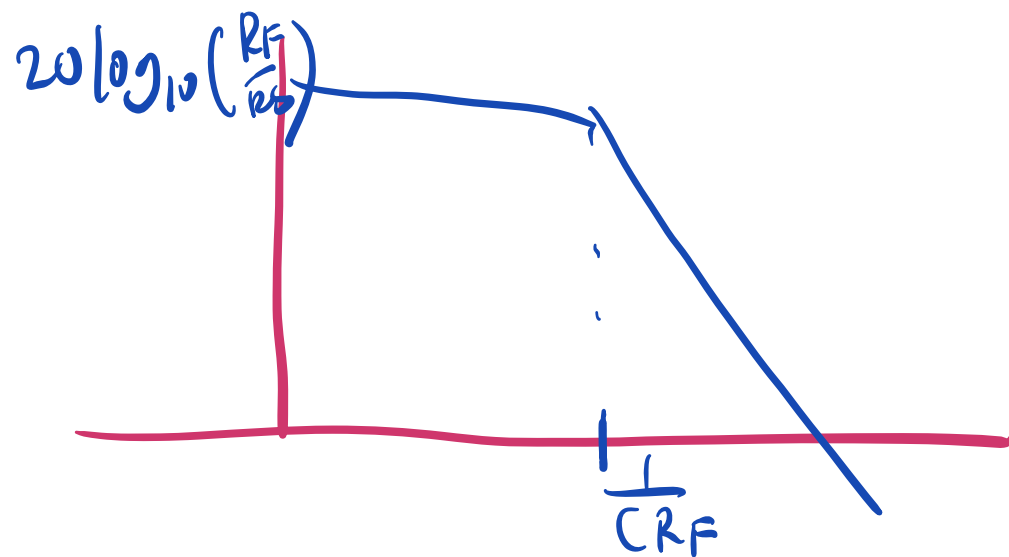
$$= \underbrace{- \frac{R_F}{R_s}}_{\text{gain}} \cdot \underbrace{\frac{1}{1 + j\omega C R_F}}_{\text{LPF}}$$



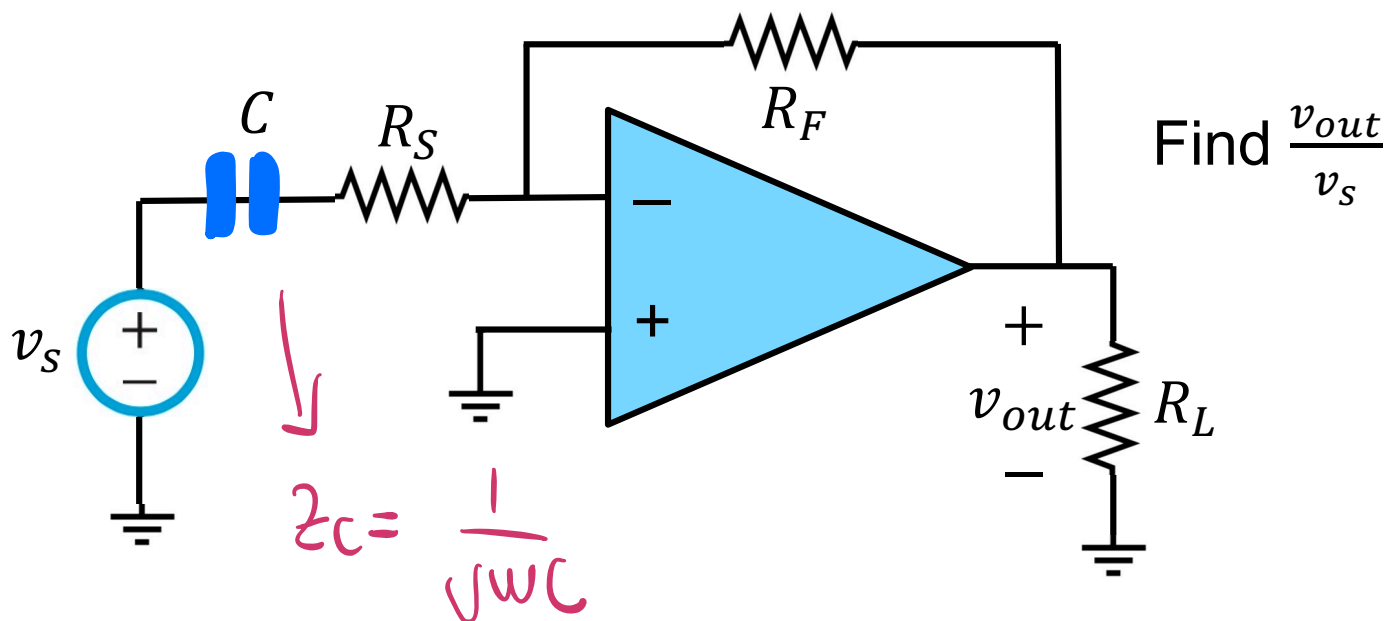


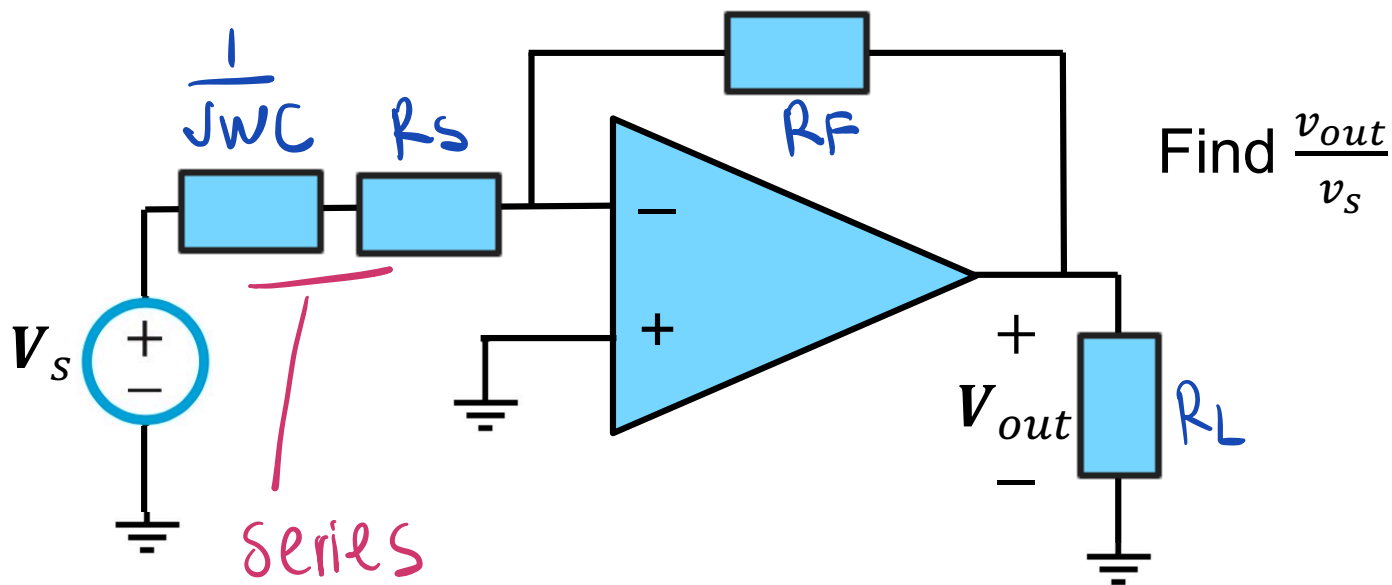

$$\frac{1}{j\omega C} + R_s = \frac{1 + j\omega C R_s}{j\omega C}$$



Active High-Pass Filter

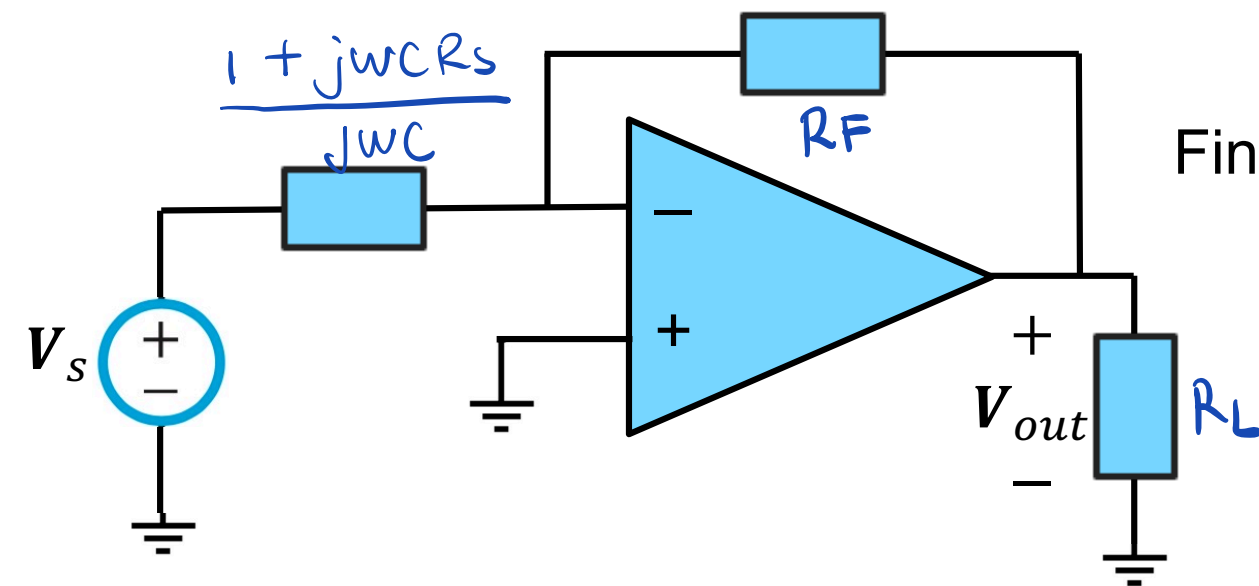

Find $\frac{v_{out}}{v_s}$ *inverting op-amp*

$$= - \frac{R_F}{Z_s}$$

$$= \frac{-R_F / 1}{1 + j\omega C R_s}$$

$$= - \frac{j\omega C R_F}{1 + j\omega C R_s}$$

$$= \underbrace{-\frac{R_F}{R_s}}_{\text{gain}} \cdot \underbrace{\frac{j\omega C R_s}{1 + j\omega C R_s}}_{\text{HPF}}$$

