



In this problem inverters have a propagation delay of 3 ns, 2-input gates have a propagation delay of 4 ns, and three input gates have a propagation delay of 5 ns.

The vertical lines in the timing diagram indicate 1 ns increments in time.

Complete the timing diagrams for the five requested signals given the input waveforms shown here.

