
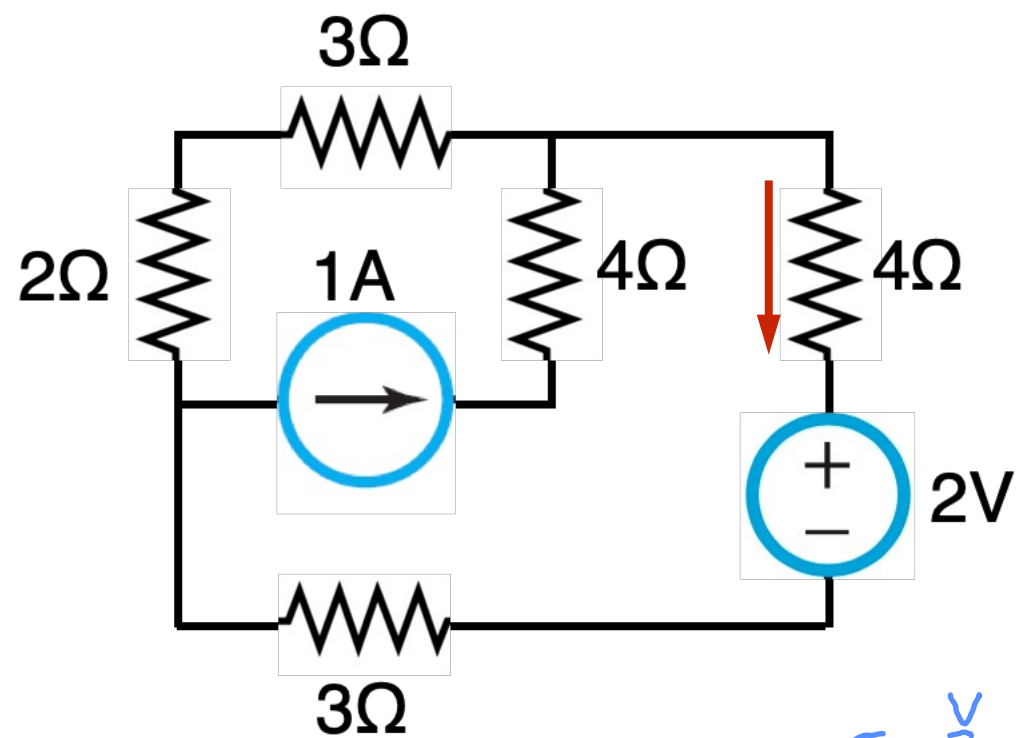


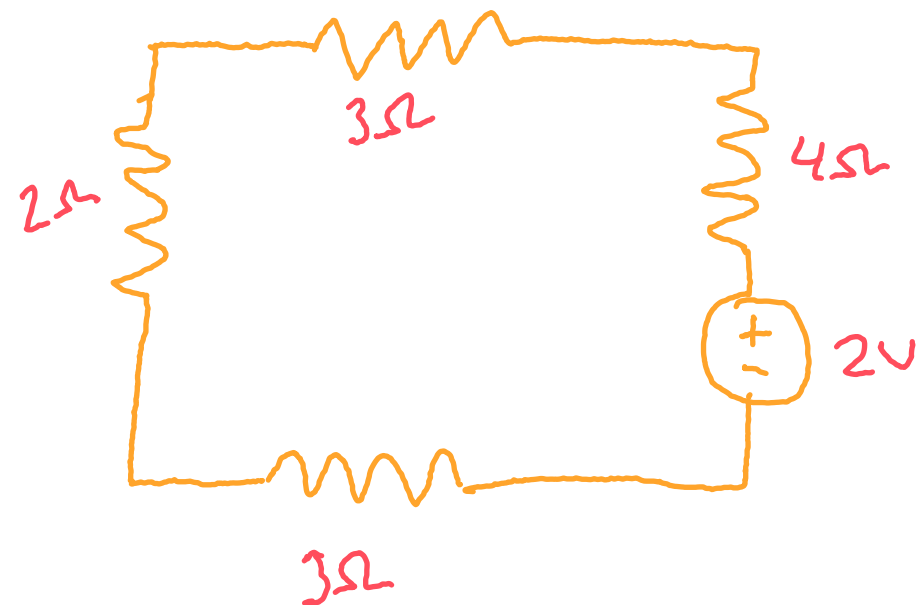

Use the principle of superposition to find the current i .



$$I = \frac{V}{R}$$



$$I = \frac{2}{12}$$

$$I = \frac{1}{6} A$$






THE OHIO STATE UNIVERSITY

COLLEGE OF ENGINEERING

Equivalent Circuits




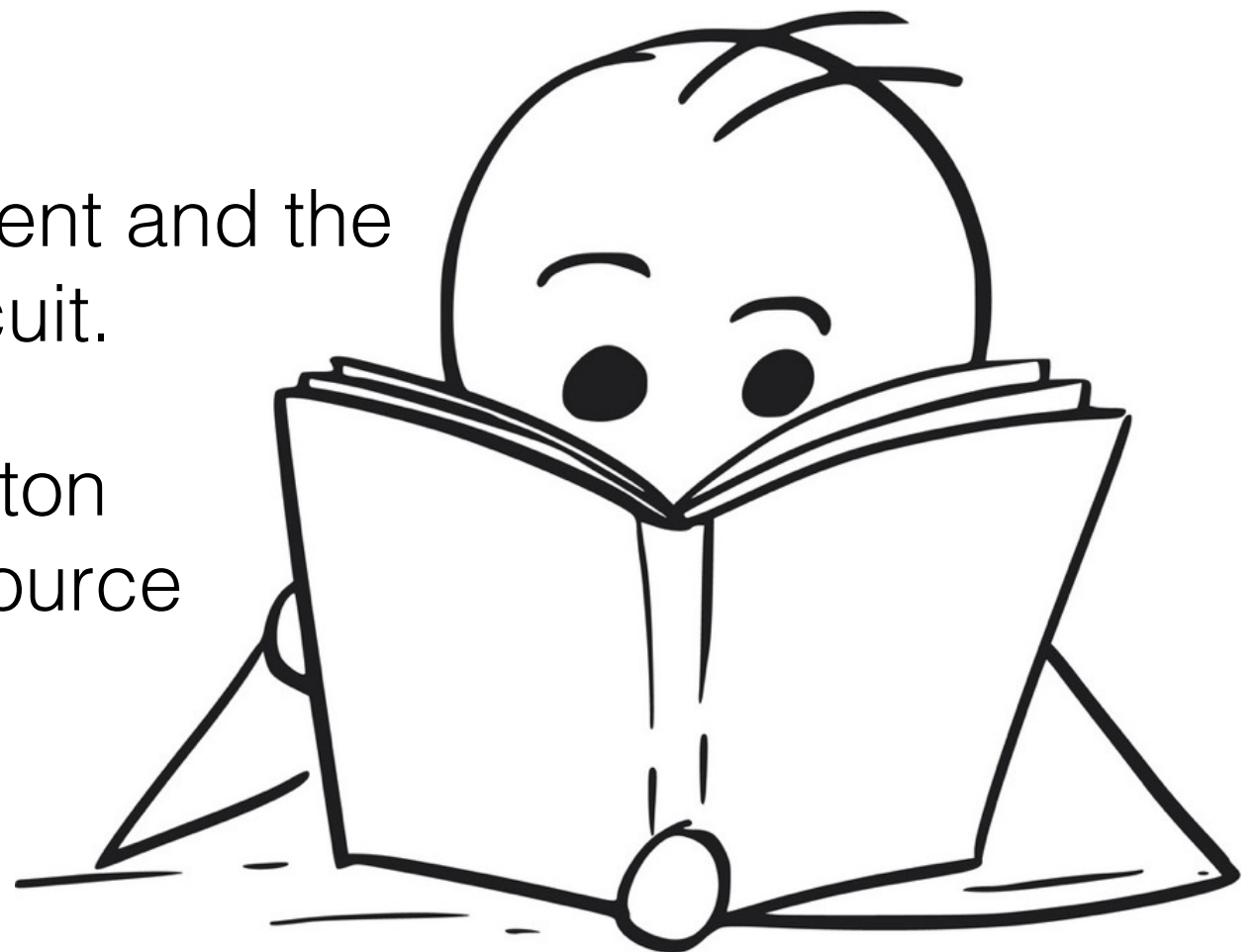- Learning Objectives:
 - Understand the importance and application of equivalent circuits.
 - Determine the Thévenin voltage and the Thevenin resistance of a circuit.
 - Determine the Norton current and the Norton resistance of a circuit.
 - Given the Thévenin or Norton equivalent circuit, apply source transformation.





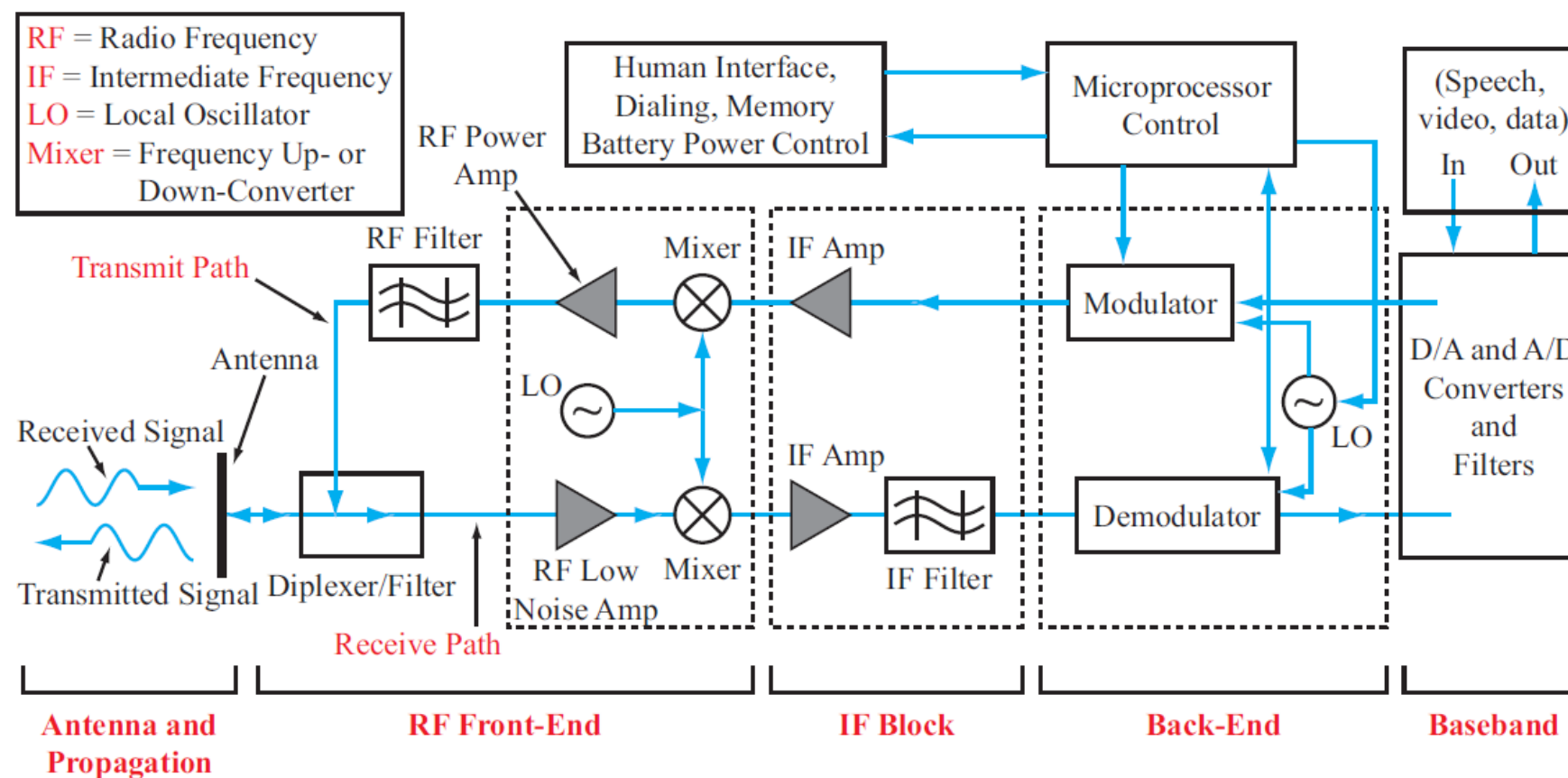
- Today's systems are complex. We use a block diagram approach to represent circuit sections.





Recall that:

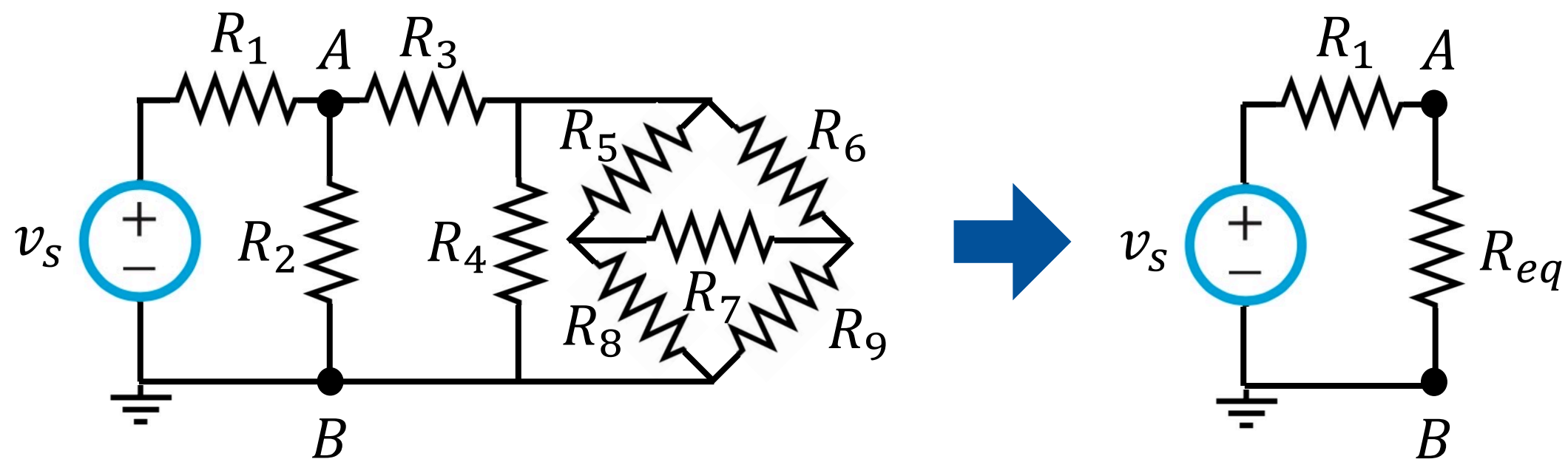
- Simplify analysis.
- Voltage and Current between A and B do not change.





Recall that:

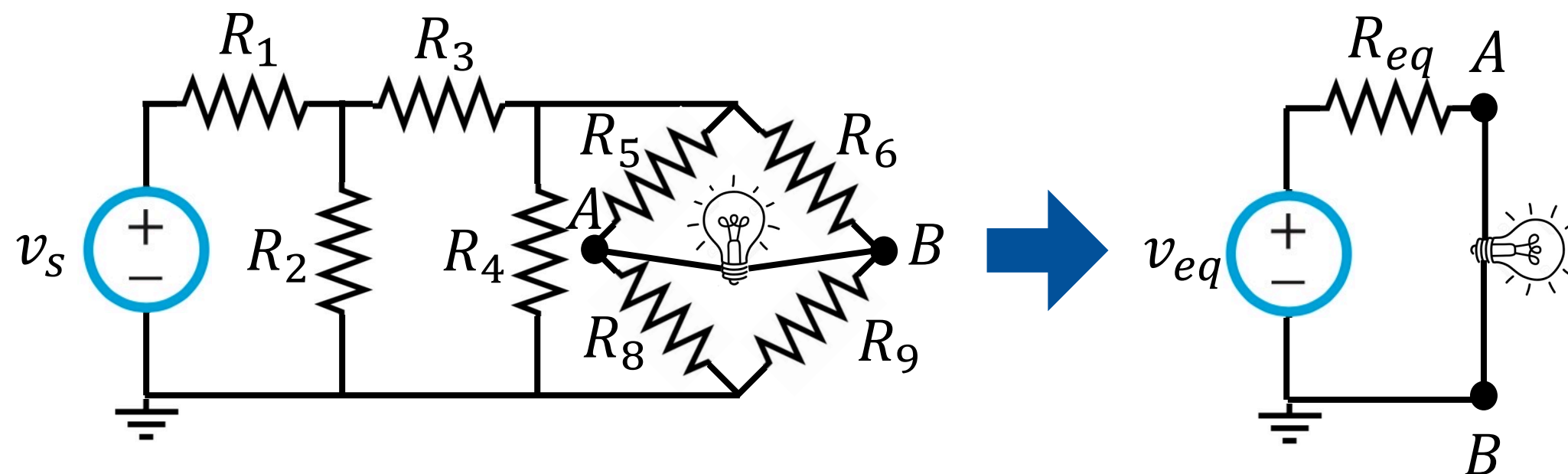
- Simplify analysis.
- Voltage and Current between A and B do not change.




Our ability to develop equivalent-circuit representations is made possible (in part) by a pair of theorems of fundamental significance known as Thévenin's and Norton's theorems.



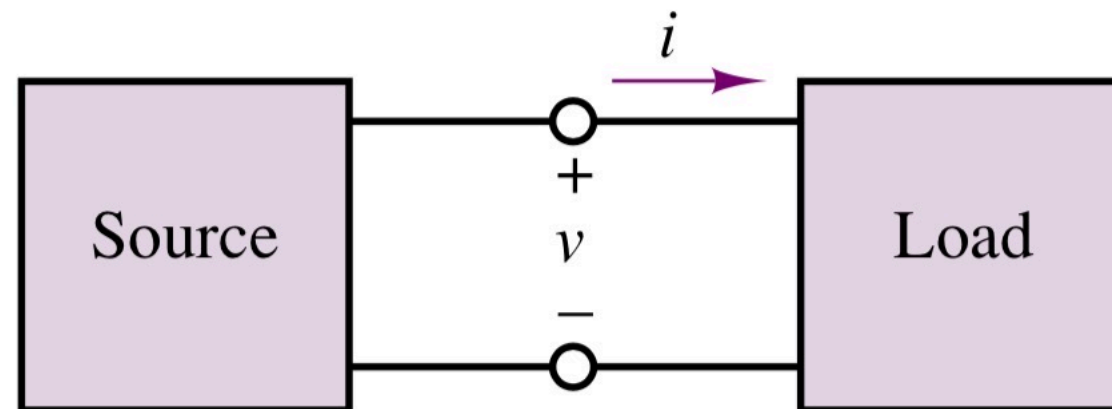- Linear two-terminal circuit can be replaced by an equivalent circuit:




Thévenin equivalent

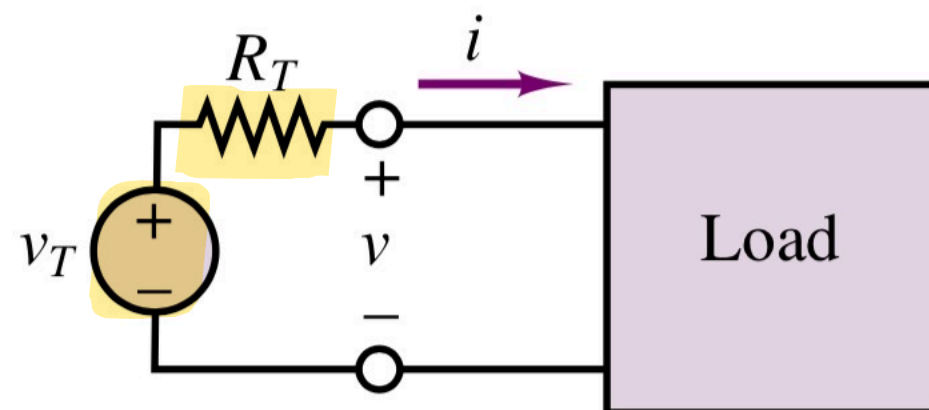

Composed of a voltage source and a series resistor.

Norton equivalent

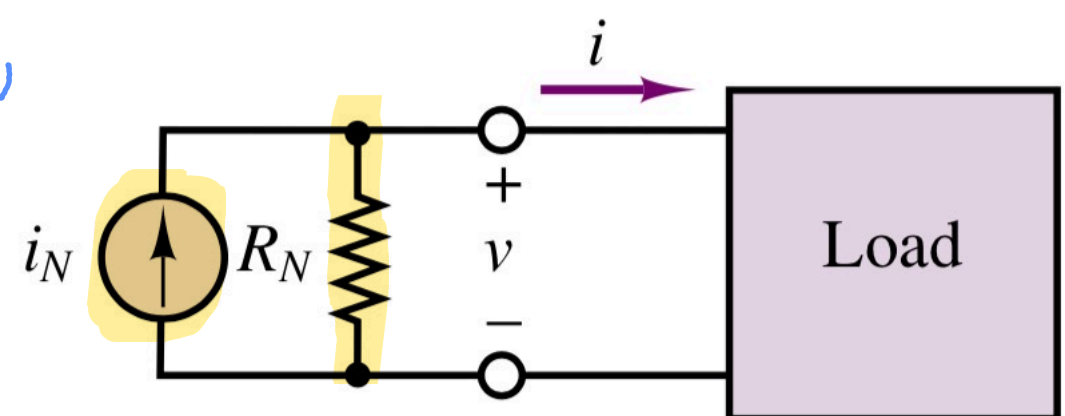


Composed of a current source and parallel resistor.

$$R_T = R_N$$




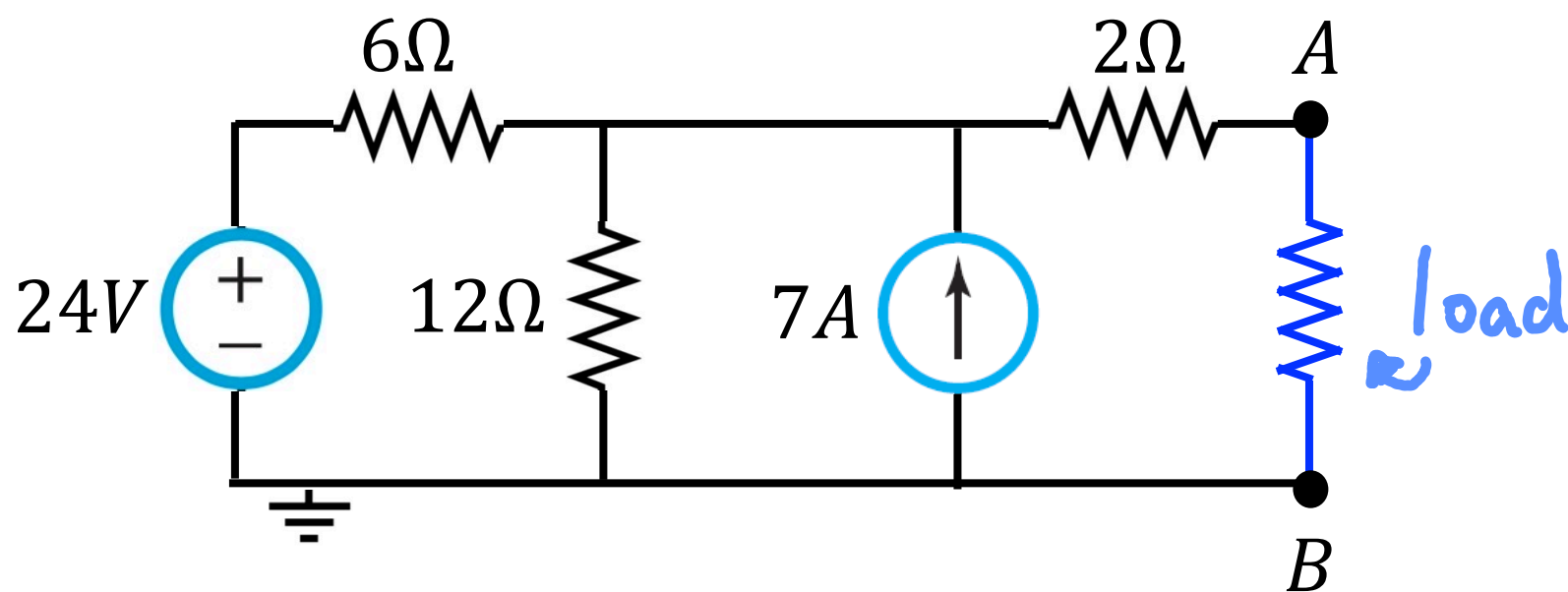1. Remove the load and set all independent sources to zero.
*turn off current
and voltage sources*







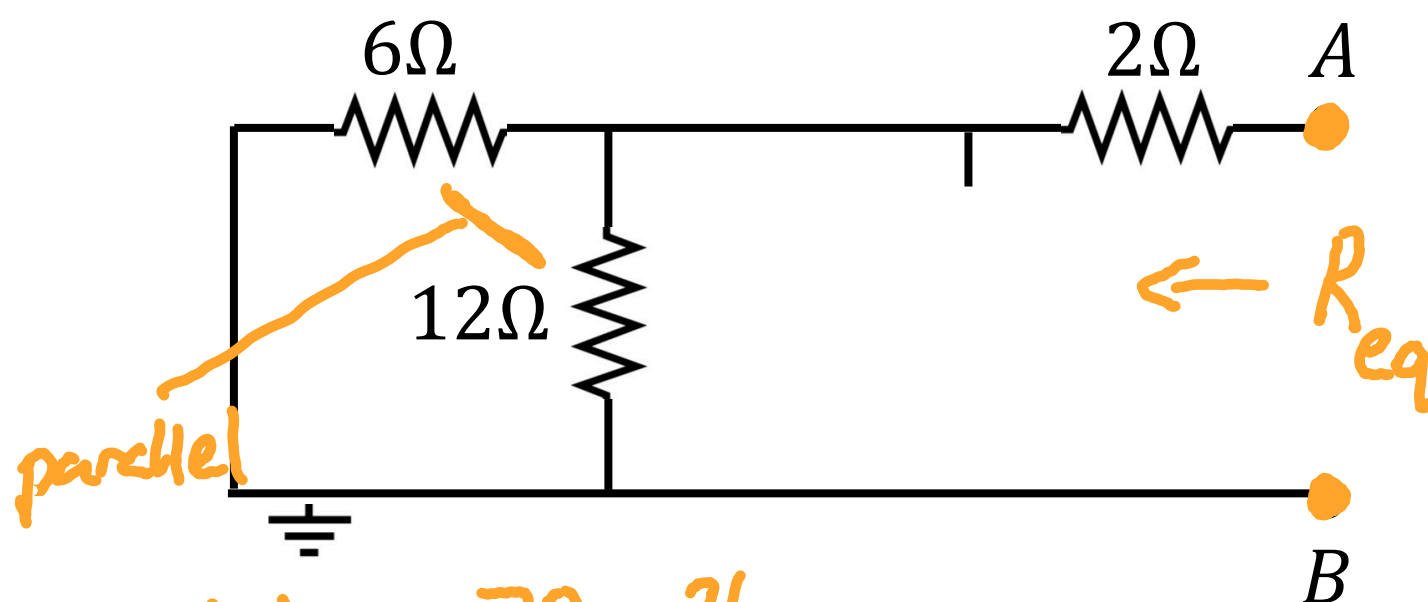1. Remove the load and set all independent sources to zero.
2. Apply series and parallel equivalent resistance substitutions to find effective equivalent resistance.
 - Sometimes may need to attach independent voltage source to the terminals (e.g., when there is a dependent source).



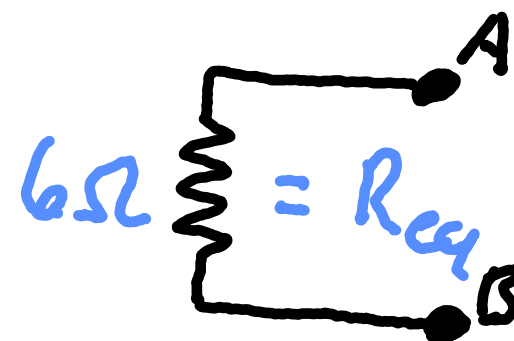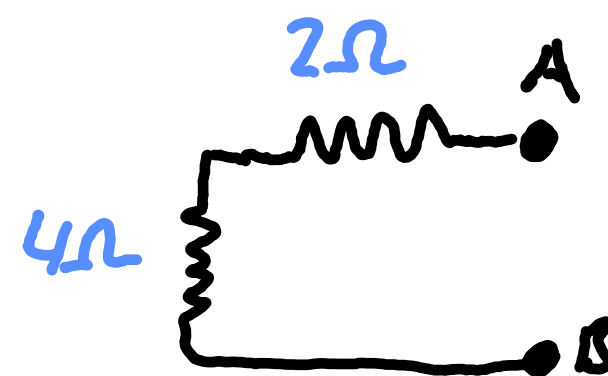
$$\frac{6(12)}{6+12} = \frac{72}{18} = \frac{36}{9} = 4\Omega$$





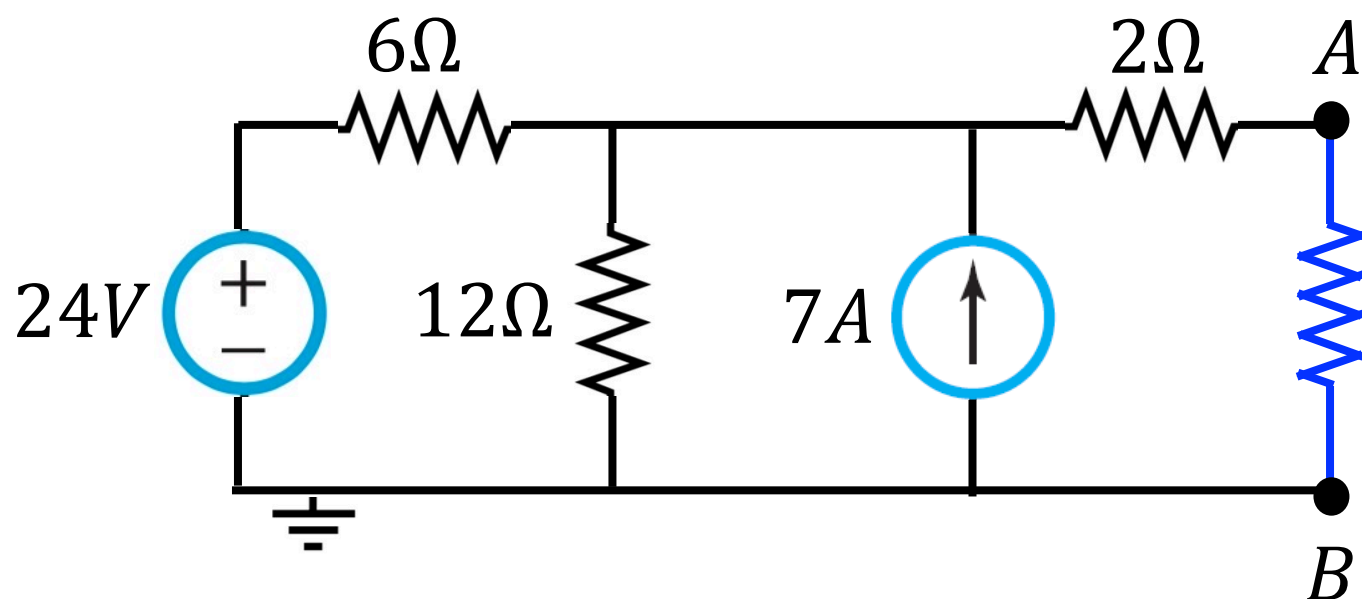
1. Remove the load, leaving the load terminals open-circuited.





1. Remove the load, leaving the load terminals open-circuited.
2. Define the open-circuit voltage v_{TH} across the open load terminals.
3. Apply any preferred method (e.g., nodal analysis, mesh analysis) to solve for v_{TH} .

$$V_B = 0V$$
$$V_C = 24V$$

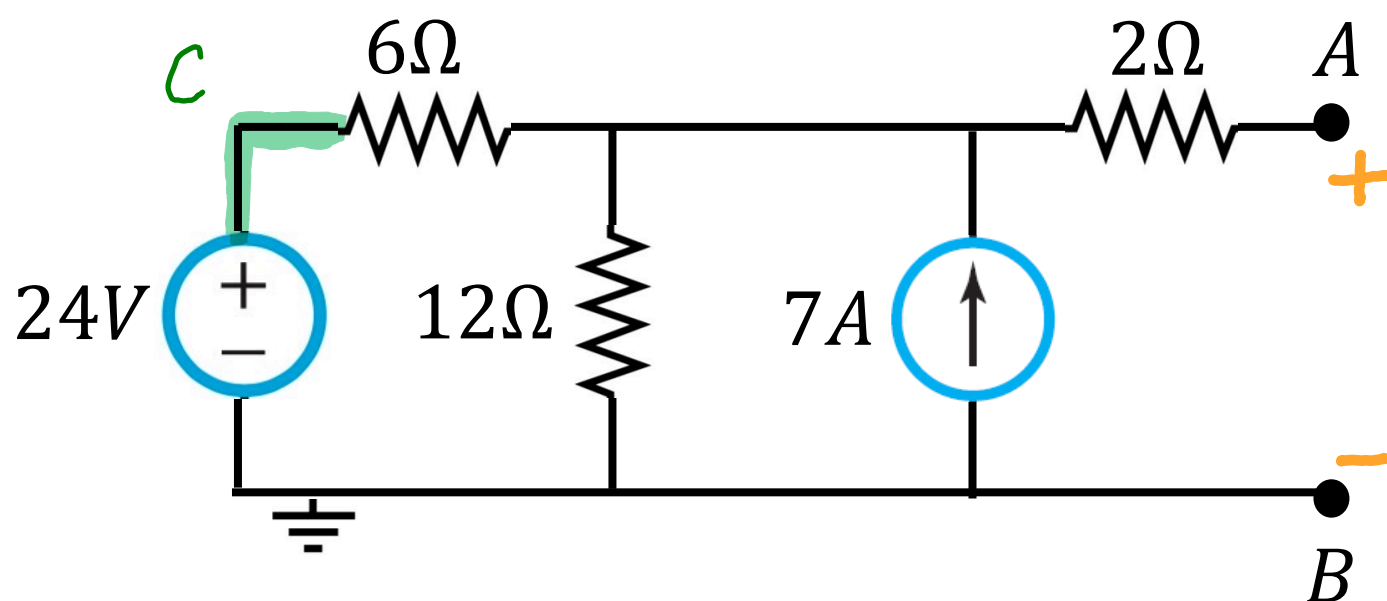

$$\text{KCL @ A: } 7 + i_6 = i_{12}$$

$$7 + \frac{V_6}{6} = \frac{V_{12}}{12}$$

$$84 + 2V_6 = V_{12}$$

$$84 + 2(24 - V_A) = V_A$$

$$84 + 48 = 3V_A$$

$$V_A = \frac{132}{3} = 44V$$


$$V_{TH} = V_A - V_B$$

$$i = 0$$

$$V_{TH} = 44V$$



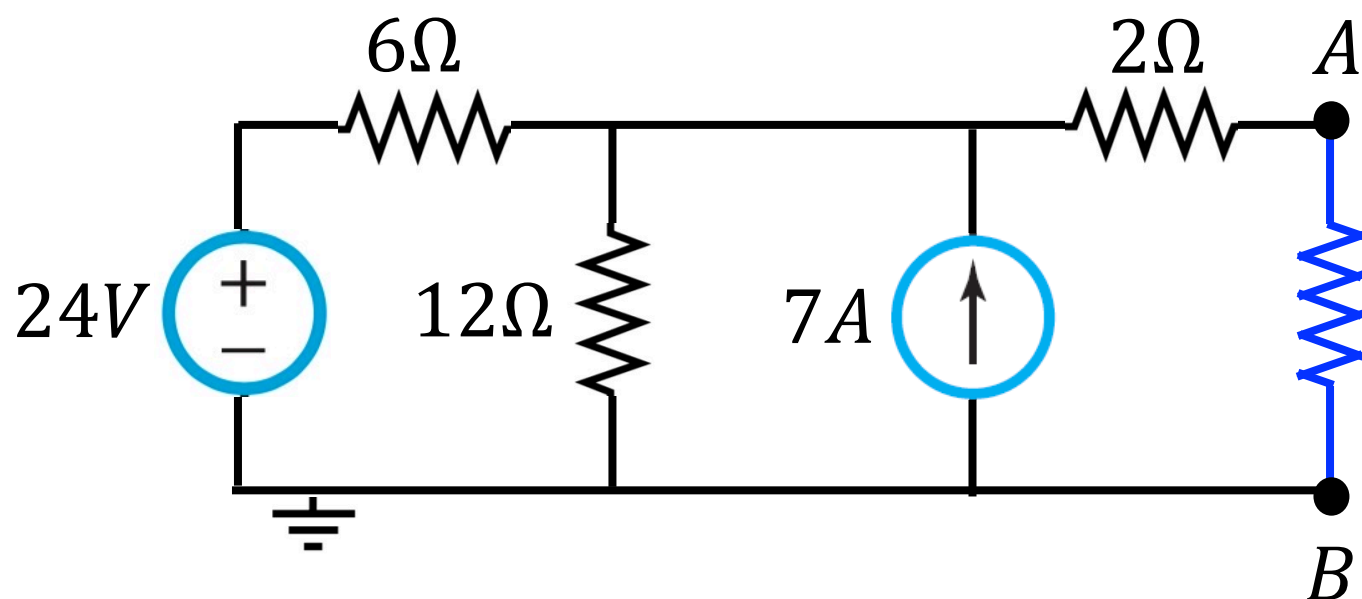1. Replace the load with a short circuit.





1. Replace the load with a short circuit.
2. Define the short circuit current, i_N , to be the Norton equivalent current.
3. Apply any preferred method (e.g., nodal analysis) to solve for i_N .

$V_B = 0V$
 $V_C = 24V$

$i_N = i_2 = \frac{V_2}{2} = \frac{V_D}{2}$

$i_N = \frac{44}{3} = \frac{22}{3} A$

KCL @ D = $7 + i_6 = i_{12} + i_2$


$7 + \frac{V_C}{6} = \frac{V_{12}}{12} + \frac{V_2}{2}$

$84 + 2V_C = V_{12} + 6V_2$

$84 + 2(24 - V_D) = V_D + 6V_D$


$84 + 48 = 9V_D$

$V_D = \frac{132}{9} = \frac{44}{3} V$

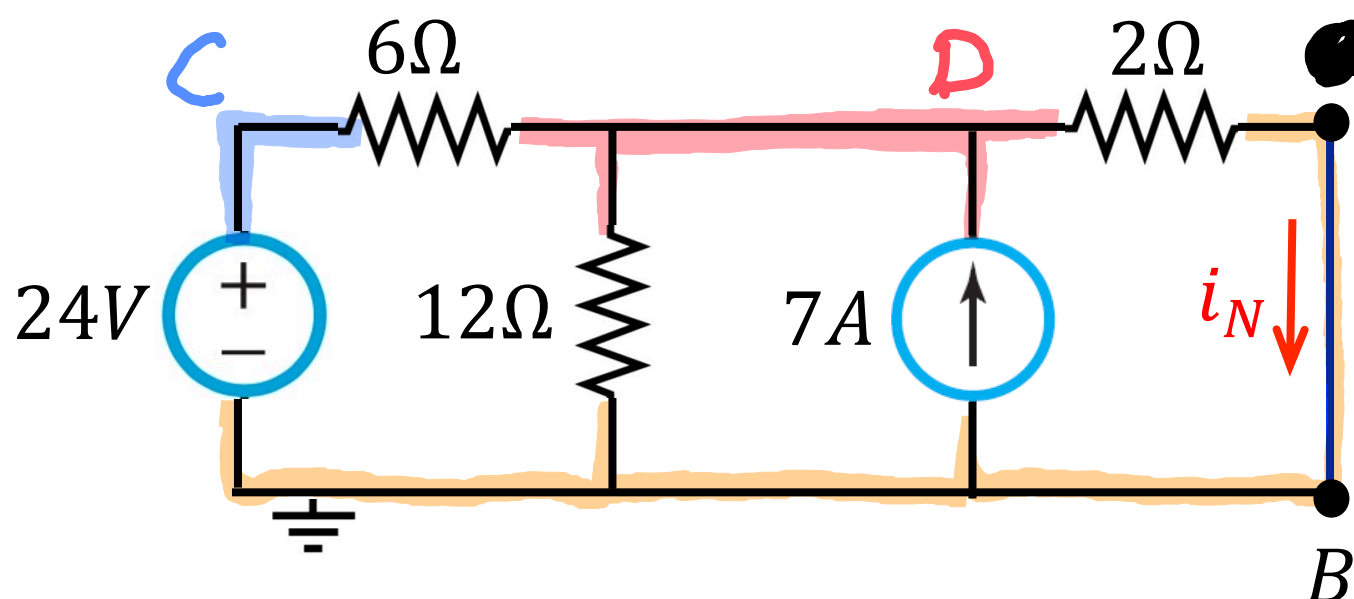



Thevenin Circuit

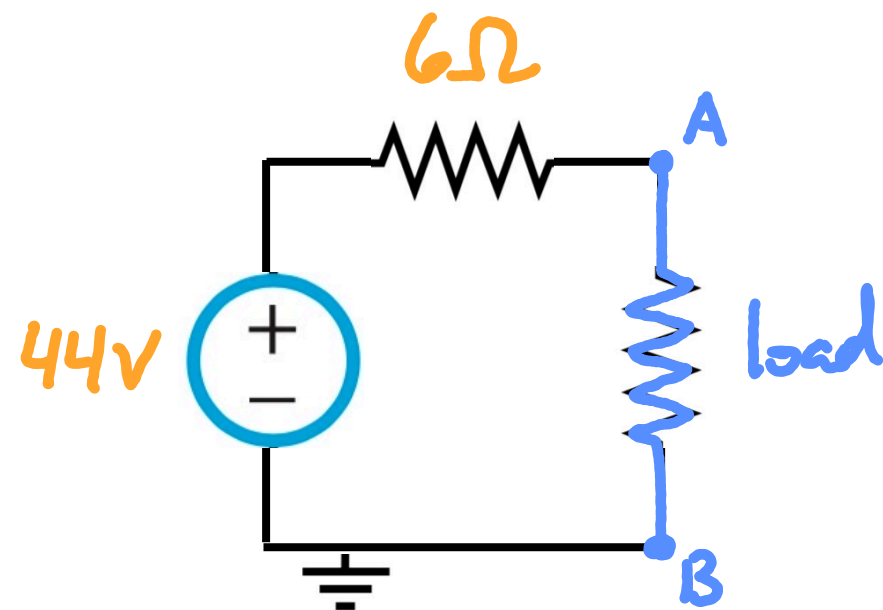

Norton Circuit

