


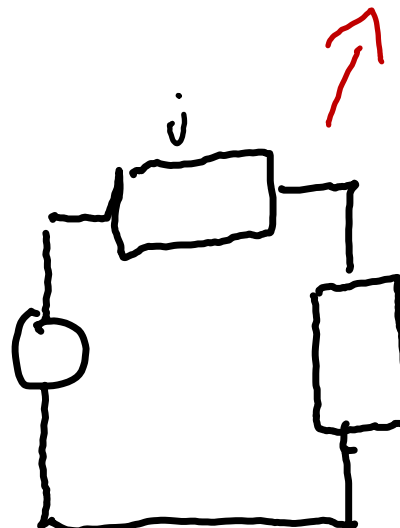
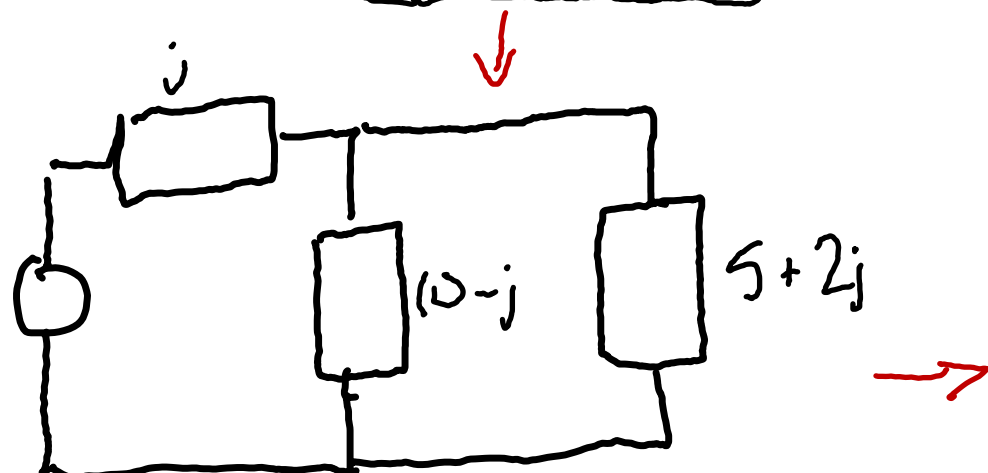


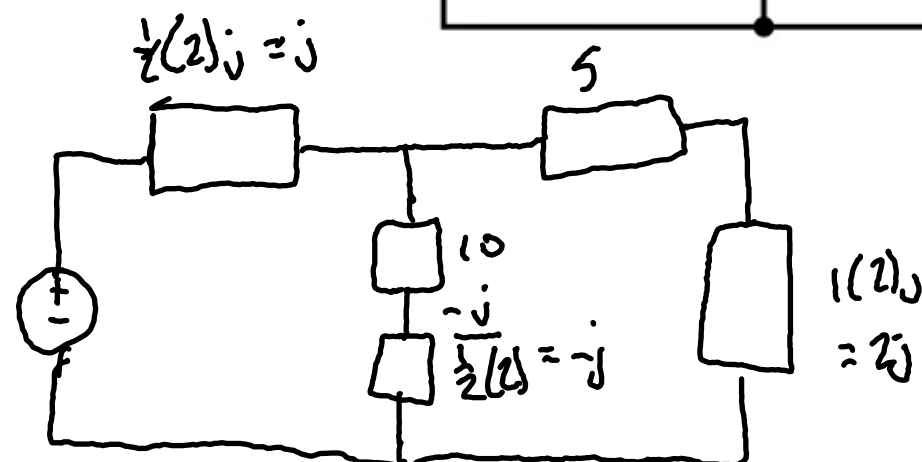

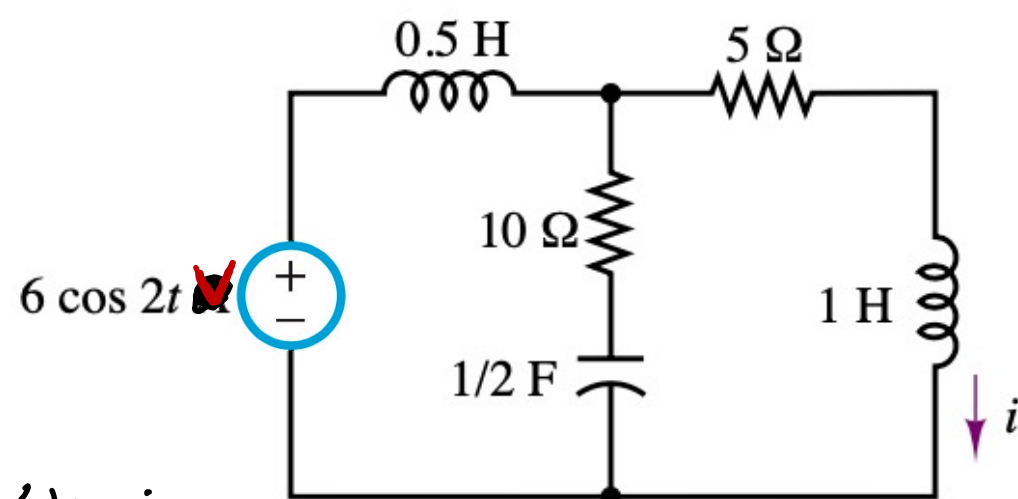Use mesh current analysis to solve for  $i(t)$  in the circuit below.


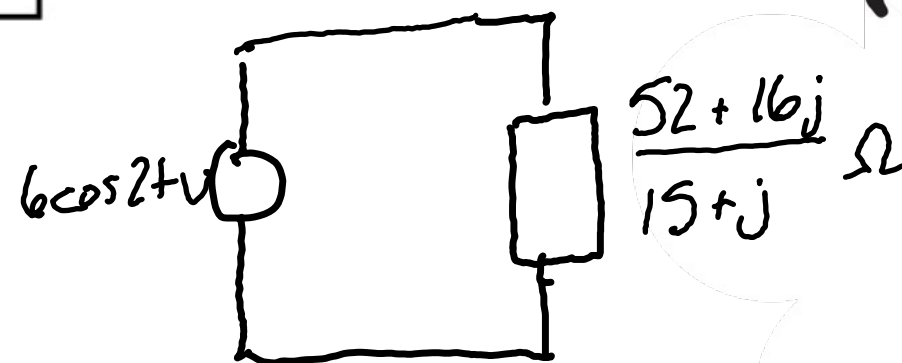
$$i(t) = \frac{6 \cos 2t}{\frac{52 + 16j}{15 + j}} = (6 \cos 2t) \left( \frac{15 + j}{52 + 16j} \right)$$



$$\frac{(10 - j)(5 + 2j)}{10 - j + 5 + 2j} = \frac{50 + 20j - 5j + 2}{15 + j} = \frac{52 + 15j}{15 + j}$$

I don't know how to do this stuff on my calculator





**THE OHIO STATE UNIVERSITY**

---

COLLEGE OF ENGINEERING

# AC Power




- Determine the complex power, average real power, and reactive power for any complex load with known input voltage or current.





- AC Circuit:

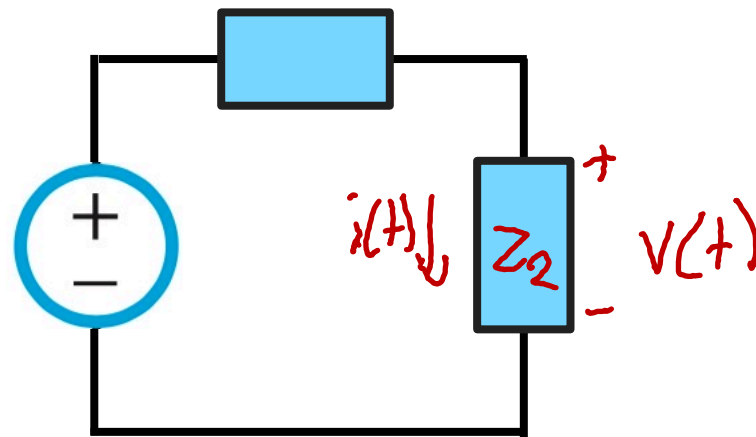

- On DC:  $p = vi$
- Instantaneous power:  $p(t) = v(t)i(t)$
- Average Power:
  - Power delivery (utilities).
  - Electronics (laptops, mobile phones, etc.).
  - Logic circuits.



The average amount of work done or energy transferred per unit time.

$$P = \frac{1}{T_0} \int_0^{T_0} \overbrace{v(t)i(t)}^{p(t)} dt = \frac{V_m I_m}{2} \cos(\phi_V - \phi_I) \quad \xrightarrow{\text{in phasor domain}} \quad \frac{V_m I_m}{2} \cos(\theta_Z)$$

$$v(t) = V_m \cos(\omega t + \phi_V)$$

$\angle$  magnitude  $\angle$  phase

$$i(t) = I_m \cos(\omega t + \phi_I)$$

$$Z_R = R e^{j0}$$

$$Z_C = \frac{1}{j\omega C} e^{-j90^\circ}$$

$$Z_L = j\omega L e^{j90^\circ}$$

$$P_R = \frac{V_m I_m}{2}$$

$$P_C = 0$$

$$P_L = 0$$

Avg Power

Reactive Power makes more sense

Polar form  $\downarrow$

$$Z = \frac{V}{I}$$

$$Z_m \angle \theta_Z = \frac{V_m \angle \theta_V}{I_m \angle \theta_I}$$

$$Z_m \angle \theta_Z = \frac{V_m}{I_m} \angle \theta_V - \theta_I$$

$$Z_m = \frac{V_m}{I_m}$$

$$\theta_Z = \theta_V - \theta_I$$



Define  $S$  as complex power

$$S = \frac{VI^*}{2}$$

↓ Average ↓

$S$  = "Complex Power" = Real Power + Reactive Power

$$S = P + jQ$$

- \* indicates the complex conjugate
- Real part is the real power
- Imaginary part is the reactive power
  - The dissipated power resulting from inductive and capacitive loads measured in volt-amperes reactive (VAR).
  - A purely reactive load can store power and then release it, but the net average power it absorbs is zero

$$\begin{aligned} x &= a + bj \\ x^* &= a - bj \\ \gamma &= m \angle \theta \\ \gamma^* &= m \angle -\theta \end{aligned}$$



$$\frac{VI^*}{2}$$

$S$  = "Complex Power" = Real Power + Reactive Power

$$V = V_m \angle \theta_v$$


$$I = I_m \angle \theta_i$$

From polar to rectangular:

$$S = \frac{(V_m \angle \theta_v)(I_m \angle -\theta_i)}{2} = \frac{V_m I_m}{2} \angle \theta_v - \theta_i$$

$$S = \underbrace{\frac{V_m I_m}{2} \cos(\theta_v - \theta_i)}_{\text{Real}} + \underbrace{\frac{V_m I_m}{2} \sin(\theta_v - \theta_i)j}_{\text{Imaginary}}$$

Avg Power + Reactive Power

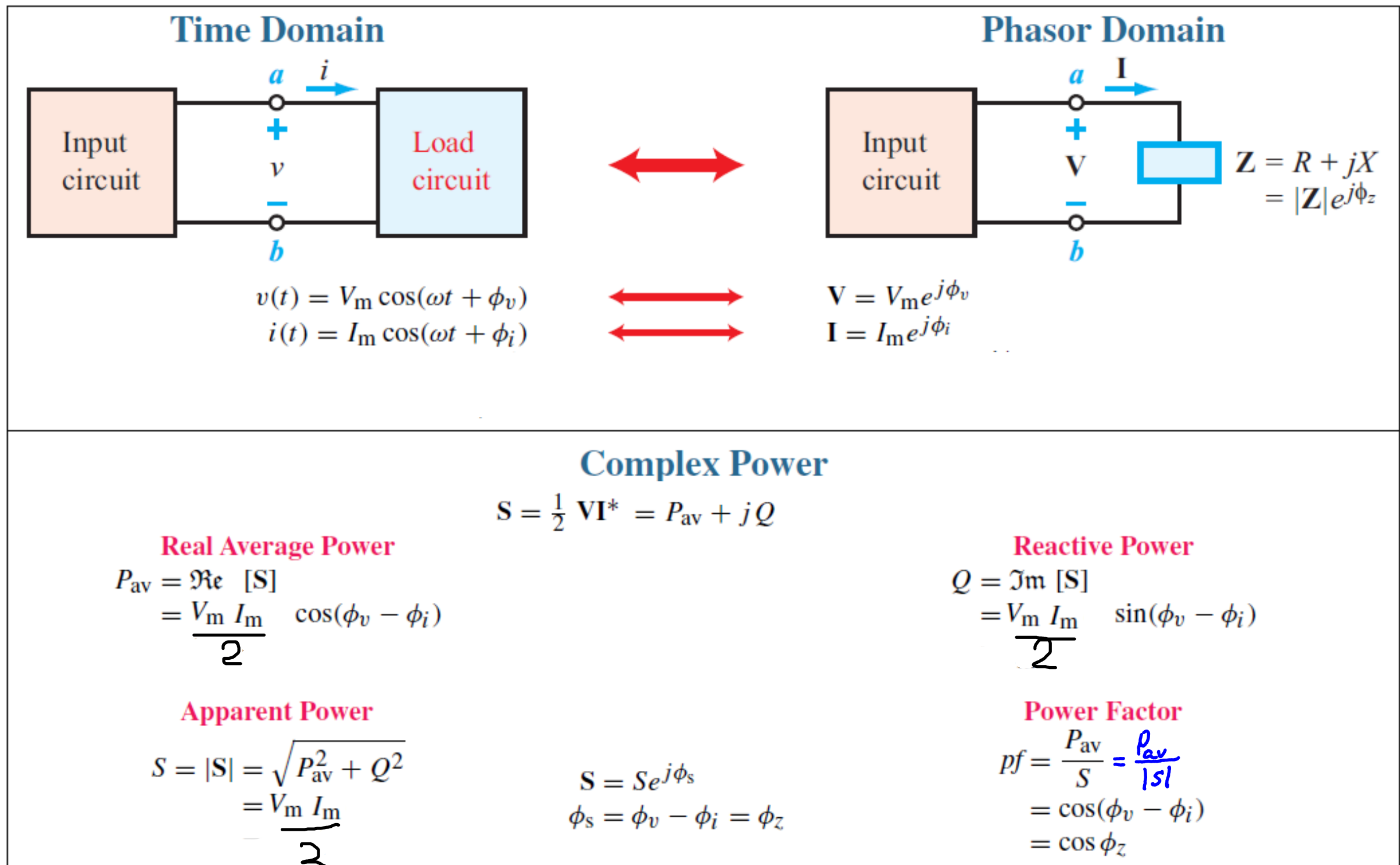





From the perspective of an energy supplier:

- The amount of power the company has to supply is  $S$ , but it can charge for only  $P_{av}$ , because  $P_{av}$  is the only real power consumed by the load.
- The company appears to supply  $S$ —hence, the name apparent power—but it gets paid for a fraction of that, and the power factor is that fraction.