## Homework 5 Due: Friday, March 2nd, 2023 by 7PM.

Note: In order to receive full credit, you must show your work and carefully justify your answers. The correct answer without any work will receive little or no credit.

- 1. Find the phasor form of the following functions:
  - A.  $v(t) = 155 \cos (377t 25^{\circ}) V$
  - B.  $v(t) = 5 \sin (1000t 40^{\circ}) V$
  - C.  $i(t) = 10 \cos(10t + 63^\circ) + 15 \cos(10t 42^\circ) A$
  - D.  $i(t) = 460 \cos (500\pi t 25^{\circ}) 220 \sin (500\pi t + 15^{\circ}) A$

- 2. Determine the instantaneous time functions corresponding to the following phasors:
  - A.  $11 = 6 \angle 60^{\circ} A$  at f = 60 Hz
  - B.  $V1 = -2 \angle -30^{\circ}V$  at f = 1kHz
  - C. I2= j3A at f = 1MHz
  - D. V2 = -(3 + j4)V at f = 10kHz

$$0 = \frac{5e^{-2.21}}{5cos(20000\pi + -126.87)}$$

$$-221 \cdot \frac{180}{\pi} - 7 - 126.87$$

$$10kHz \cdot 2\pi = 20\pi kHz$$

3. Determine the equivalent impedance Z5. Assume w = 400 rad/s.

