

Give the reduced sum of products expression for the following logic circuits.

