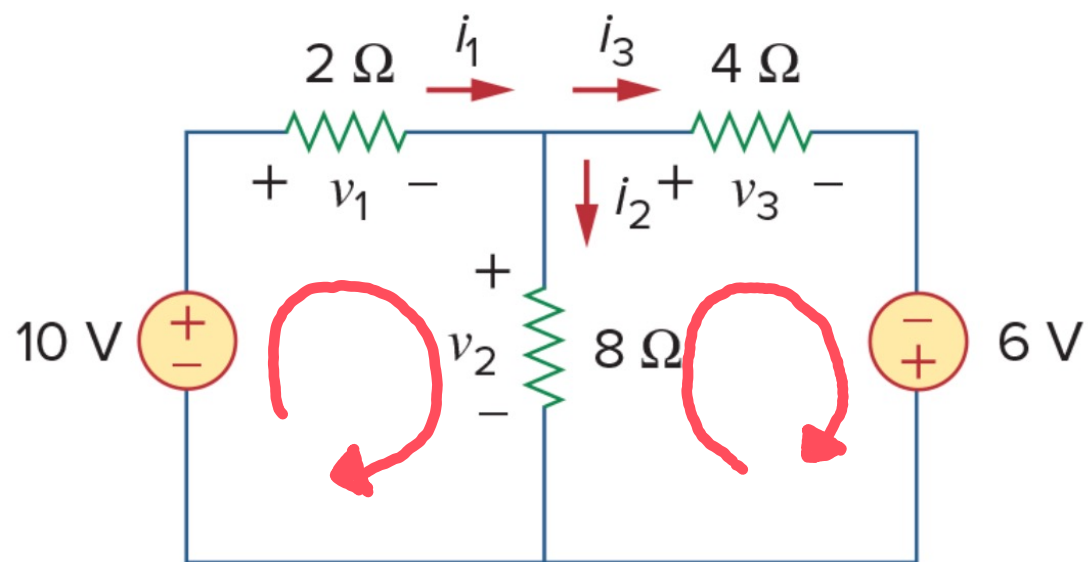




Apply KCL, KVL, and Ohm's Law to find  $i_1$ ,  $i_2$  and  $i_3$ .



$$i_1 - i_2 - i_3 = 0$$

$$i_1 = \frac{10}{2} = 5 \text{ A}$$

$$i_2 = \frac{8}{2} = 4 \text{ A}$$

$$i_3 = \frac{6}{1} = 6 \text{ A}$$

$$10 \text{ V} = v_1 + v_2$$

$$10 \text{ V} = v_3 - v_2$$

$$v_1 =$$

$$v_2 =$$

$$v_3 =$$

$$v_2 = 10 \text{ V} - v_1 = v_3 - 10 \text{ V}$$





**THE OHIO STATE UNIVERSITY**

---

COLLEGE OF ENGINEERING

# Equivalent Resistance




- Learning Objectives:
  - Combine resistors in series and in parallel.
  - Find equivalent circuits for resistive circuits.
  - Understand the difference between open, closed, and short circuit.





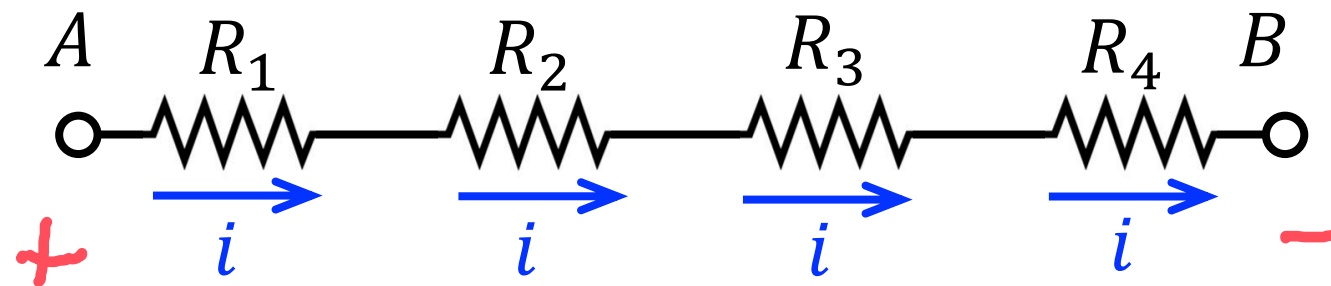
- Recall: Components on the same branch are said to be in series.



Same current flows through all of the resistances in series.

Equivalent circuits:

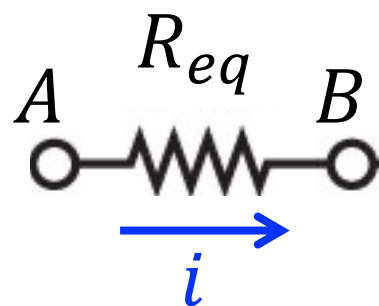- Simplify analysis.
- Voltage and Current between A and B do not change.




$R_{eq}$  = sum of all resistors

$$R_{eq} = \sum_{\text{Series}} R_i = R_1 + R_2 + \dots + R_n$$

ONLY for resistors  
in series




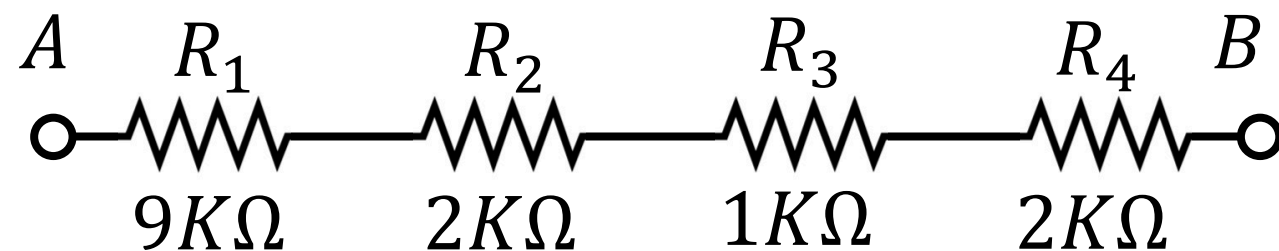- What is  $R_{eq}$  between  $A$  and  $B$ ?



$$R_{eq} = 14 K\Omega$$

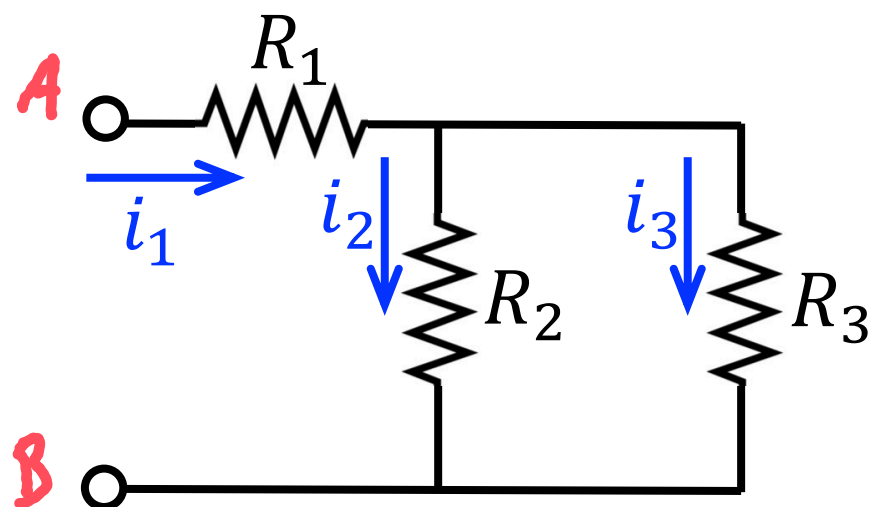
- What is  $R_{eq}$  between  $A$  and  $B$ ?





- Recall: Components sharing the same nodes on both sides are said to be in parallel.

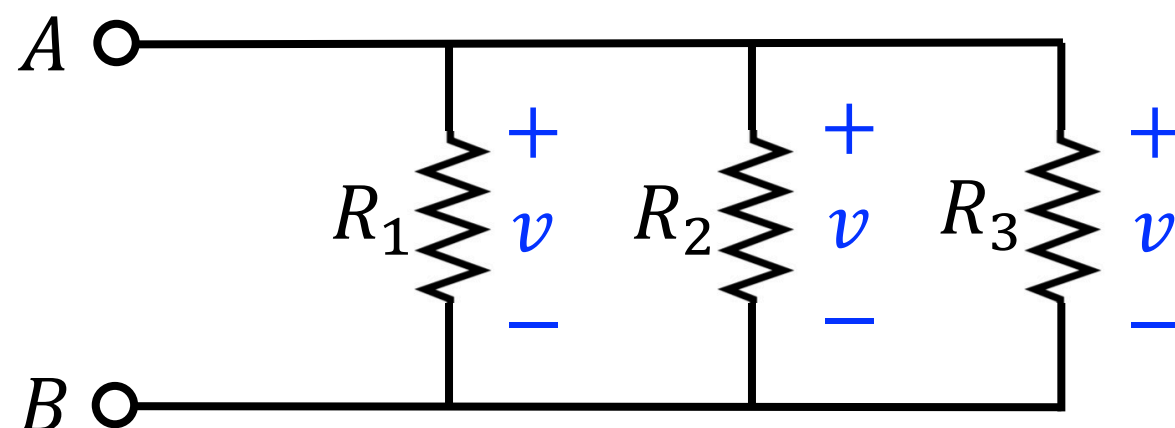
$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$



Same voltage across them.


Equivalent circuits:

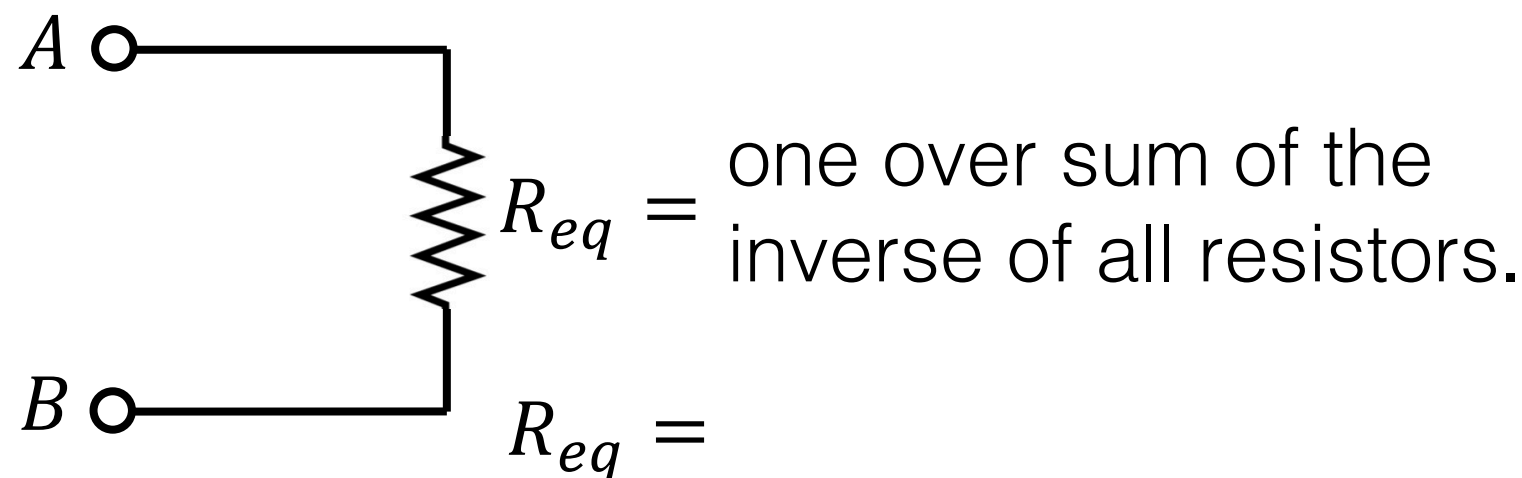- Simplify analysis.
- Voltage and Current between A and B do not change.






- What is  $R_{eq}$  between A and B?

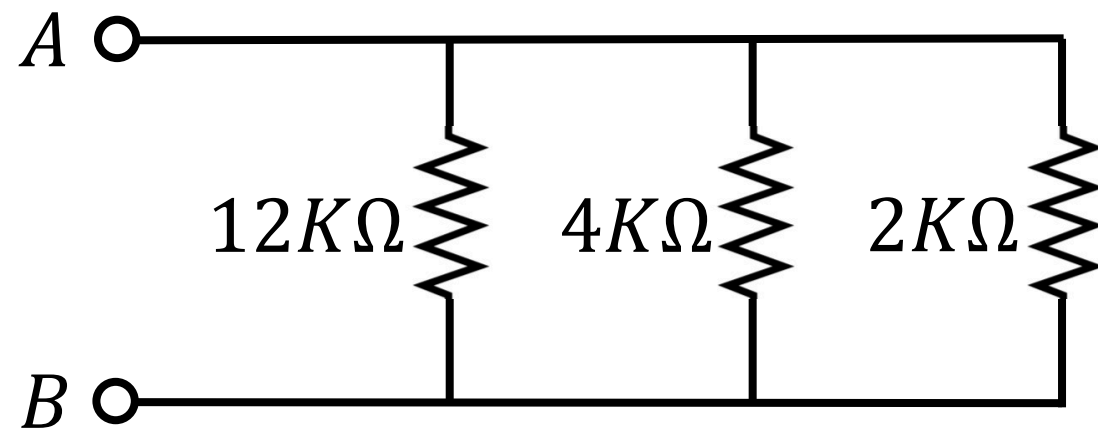

$$R_{eq} = \frac{1}{\frac{1}{12} + \frac{1}{4} + \frac{1}{2}} = \frac{1}{\frac{1+3+6}{12}} = \frac{12}{10} = 1.2k\Omega$$

- What is  $R_{eq}$  between A and B?

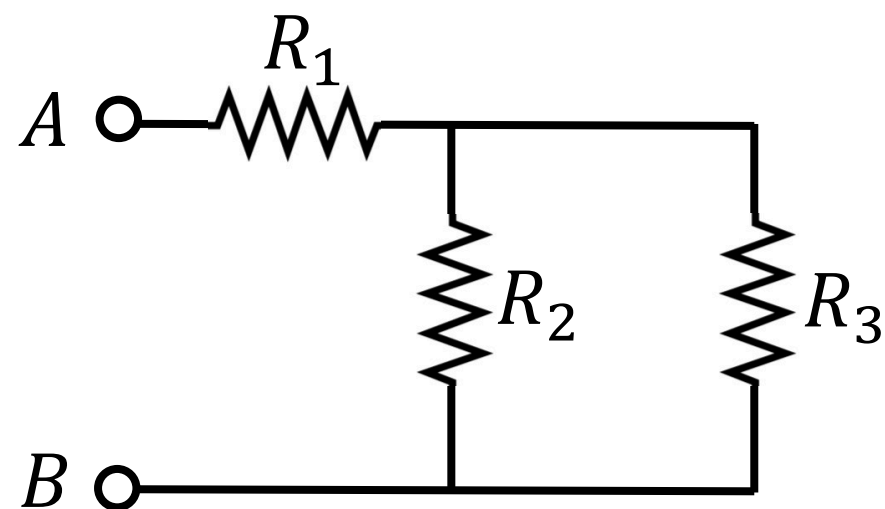

Only  $R_2$  &  $R_3$  in parallel



Recall - Equivalent circuits:


- Simplify analysis.
- Voltage and Current between 2 nodes do not change.

Series

$$R_{eq} = R_1 + R_2 + \dots + R_n$$

Parallel
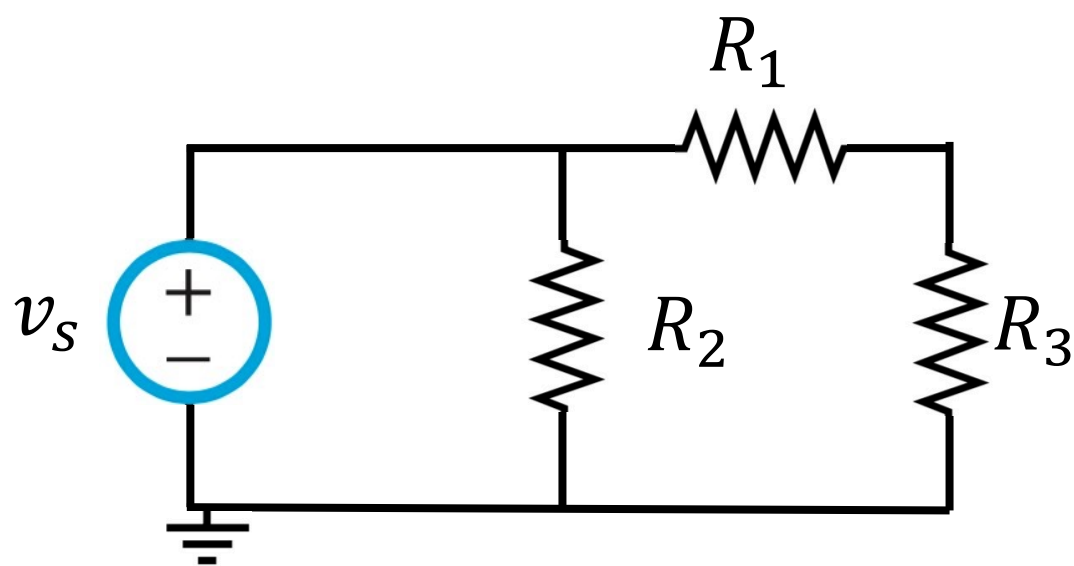
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$




NOT in Series or Parallel

1. The current through all resistors is the same (series circuit condition).
2. The voltage across all resistors is the same (parallel circuit condition).







Find  $R_{eq}$

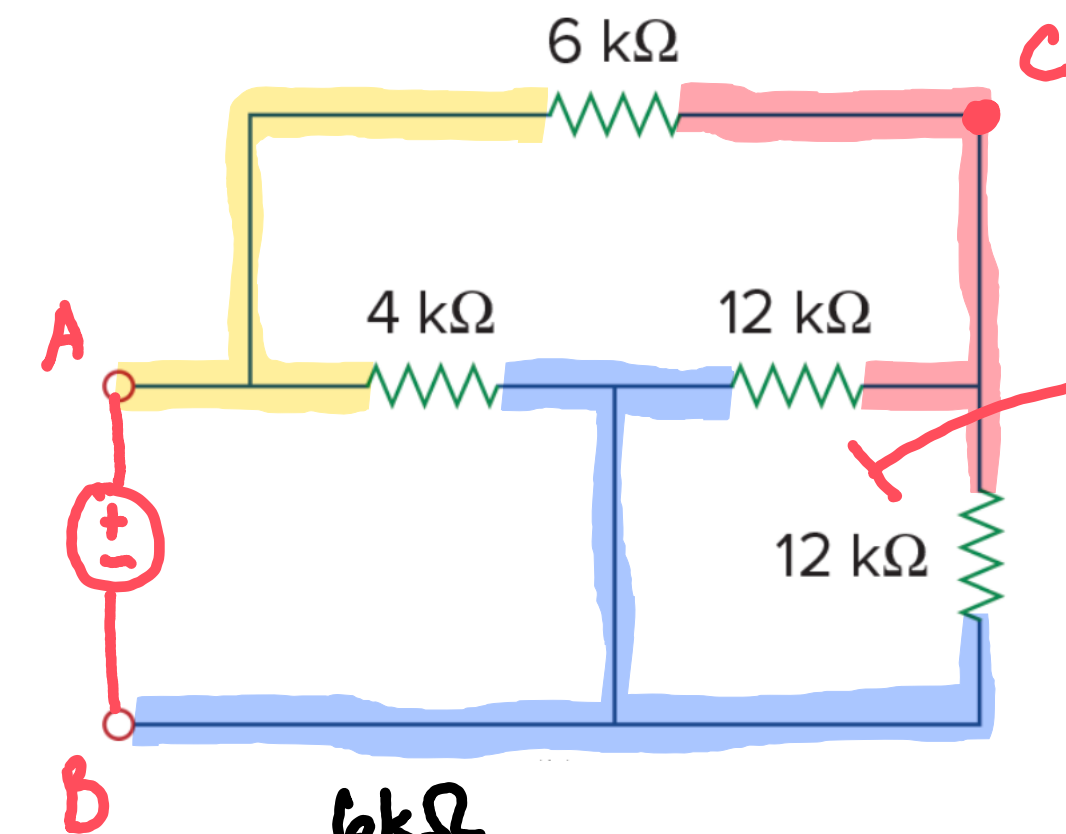

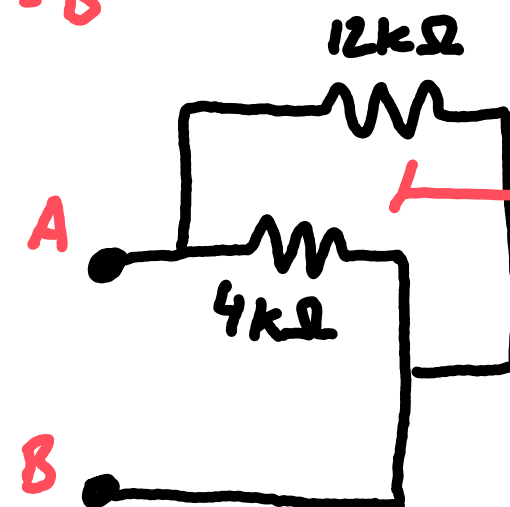Parallel  $C-B$   $\rightarrow \frac{1}{\frac{1}{12} + \frac{1}{12}} = \frac{12}{2} = 6k\Omega$




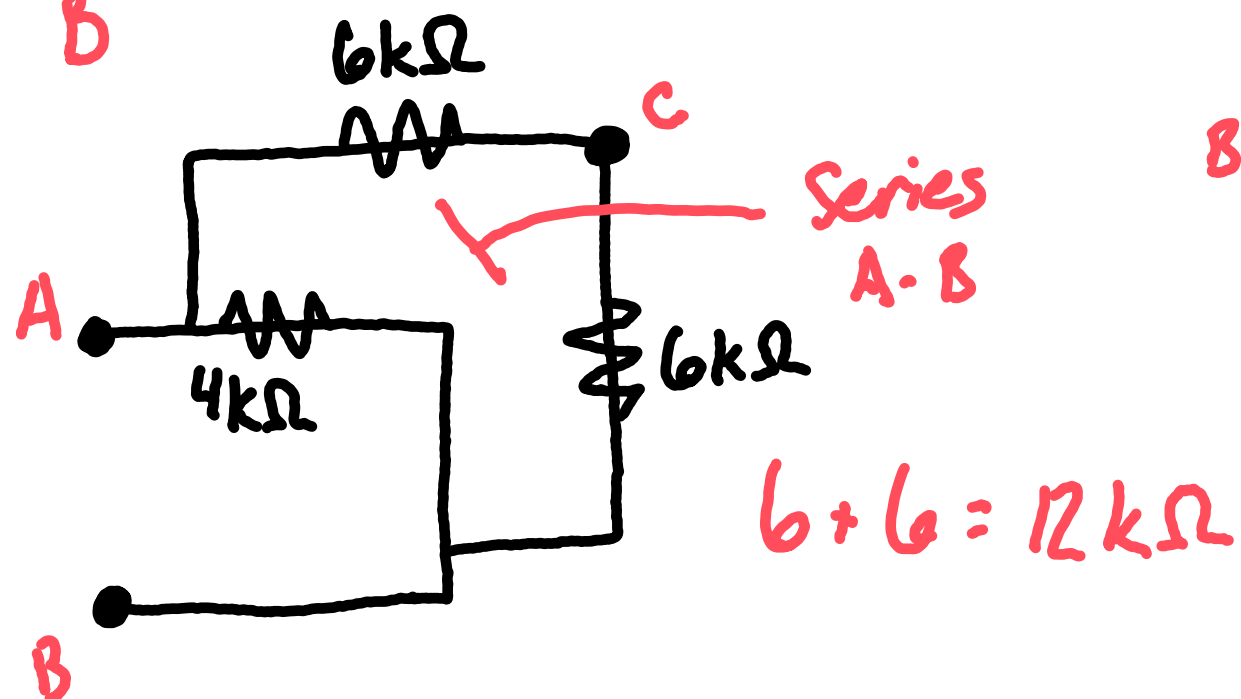
Parallel  $A-B$   $\frac{1}{\frac{1}{4} + \frac{1}{12}} = \frac{1}{\frac{3+1}{12}} = \frac{1}{\frac{4}{12}} = 3k\Omega$






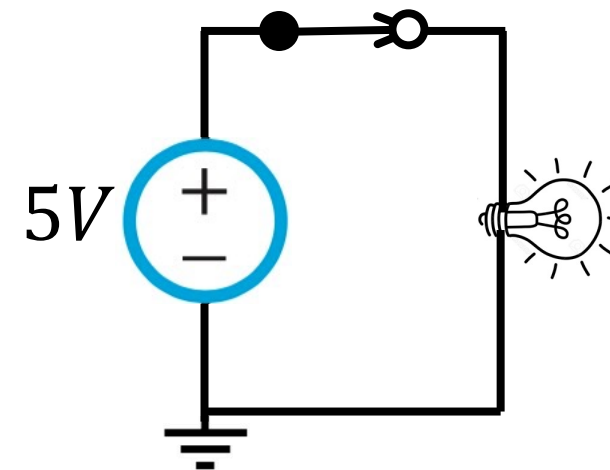
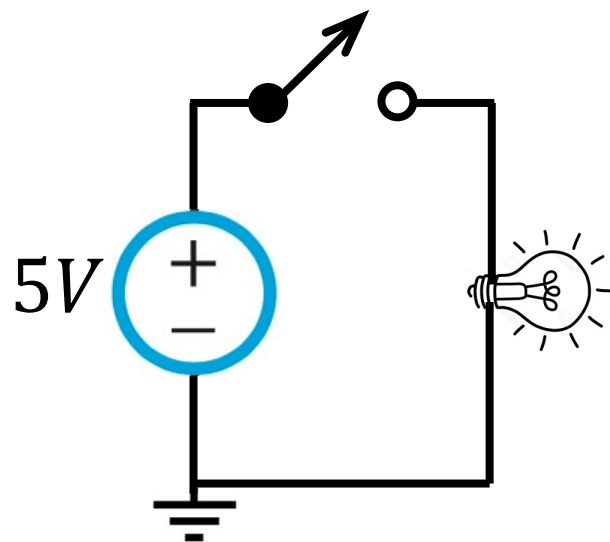
# Open and Closed Circuit

- You need a closed path, or closed circuit, to get electric current to flow.







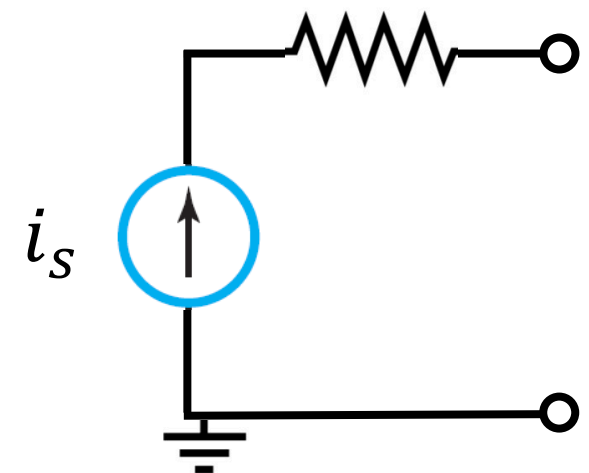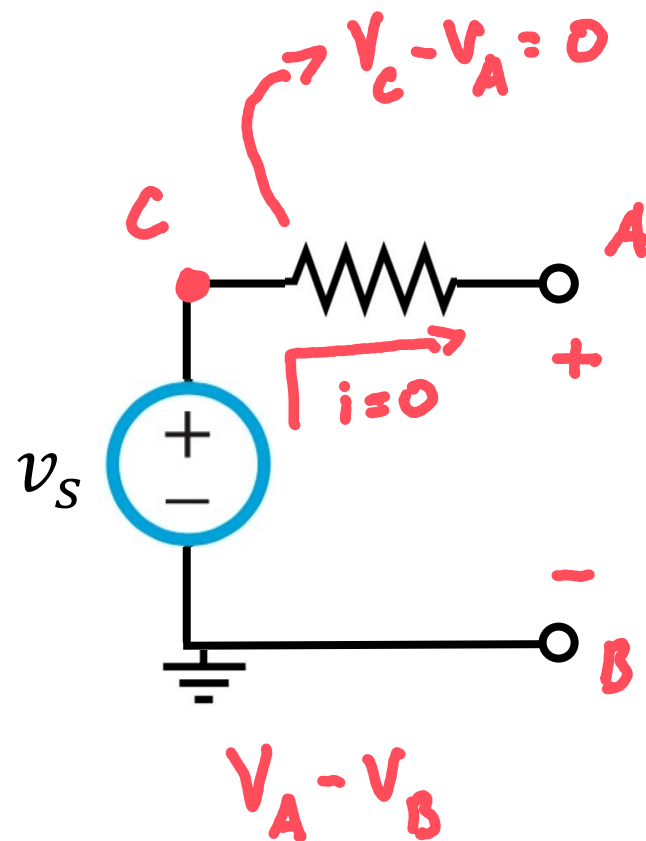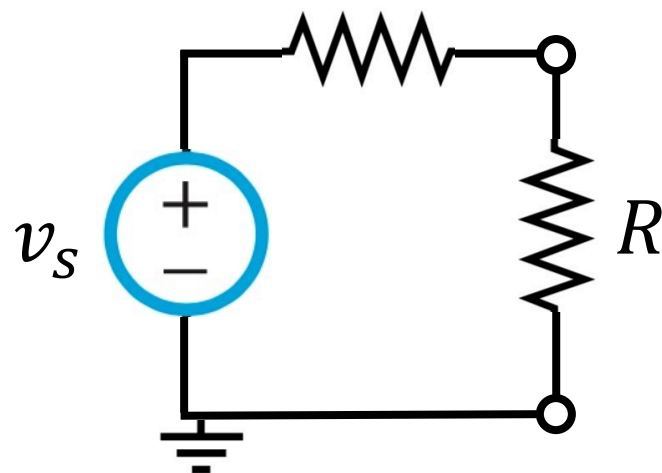- An **open circuit** refers to the condition of path discontinuity (infinite resistance) between two points.
- No current can flow through an open circuit, regardless of the voltage across it





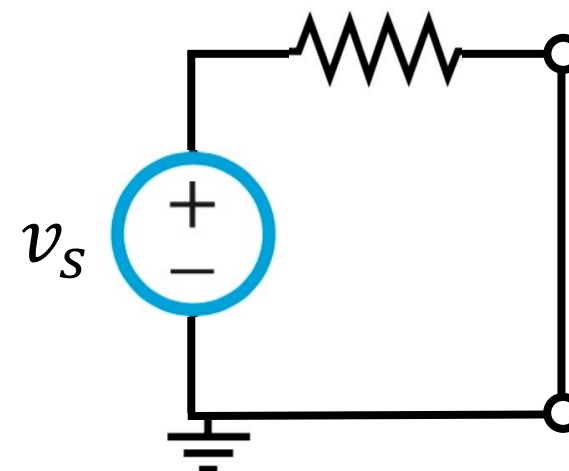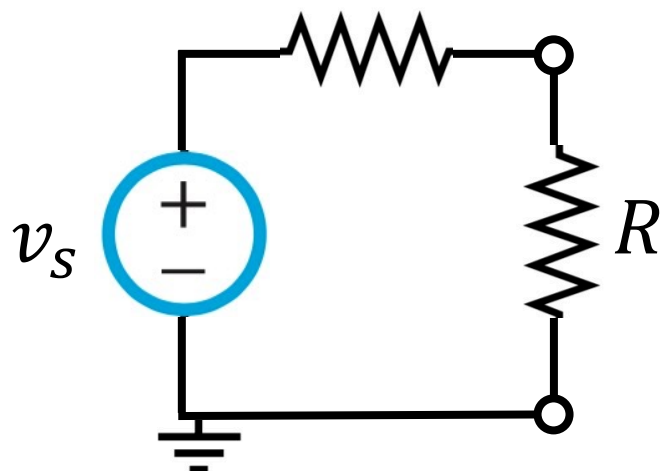- A **short circuit** constitutes the condition of complete path continuity (with zero electrical resistance) between two points.
- No voltage drop occurs across a short circuit, regardless of the magnitude of the current flowing through it.





- A **short circuit** constitutes the condition of complete path continuity (with zero electrical resistance) between two points.
- No voltage drop occurs across a short circuit, regardless of the magnitude of the current flowing through it.

