
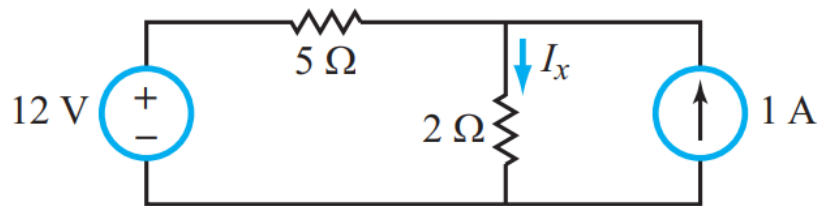


## Spring 2024 – ECE 3020



### Homework 0

Due: 01/10/2024

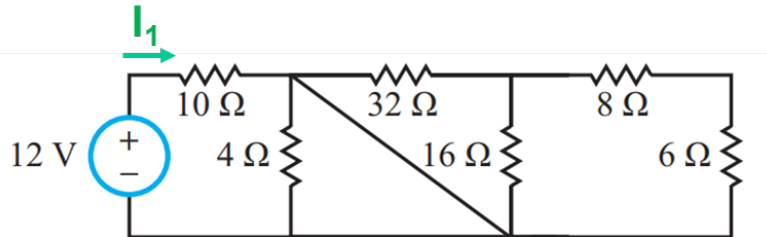
1. Find the value of  $I_1$  and  $I_x$  in the circuits below



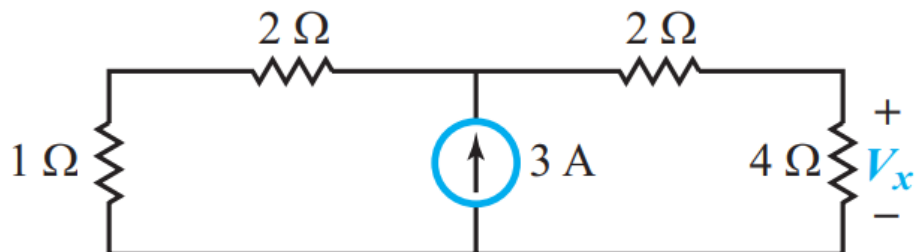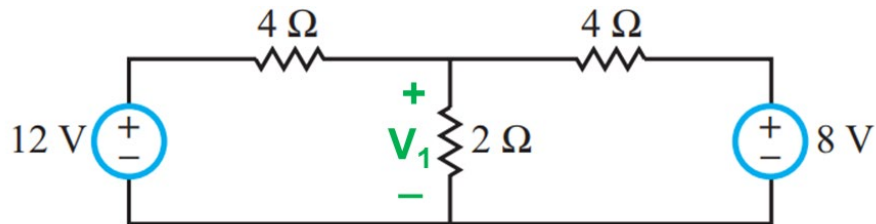
2. Find the value of  $V_1$  and  $V_x$  in the circuit below



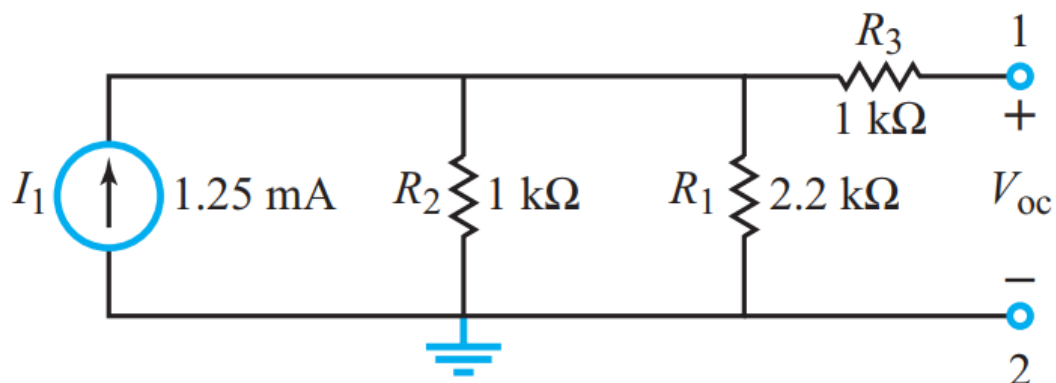
3. For the circuit shown below.
- Determine the open circuit voltage.
  - Determine the short circuit current between the output terminals.
  - Determine the Thevenin resistance for the circuit.



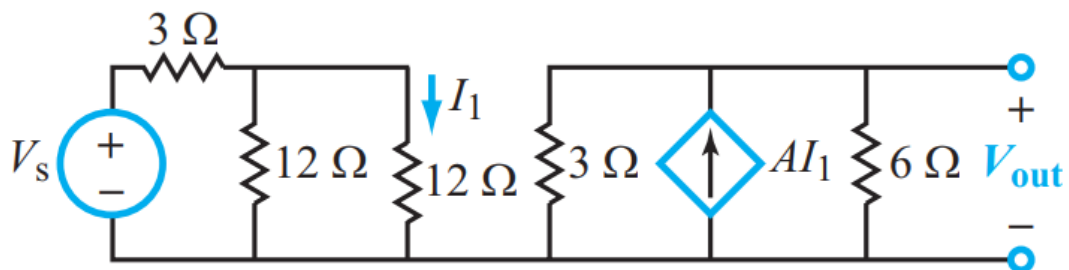
4. Determine  $V_{out}/V_s$  for  $A = 36A/A$ .



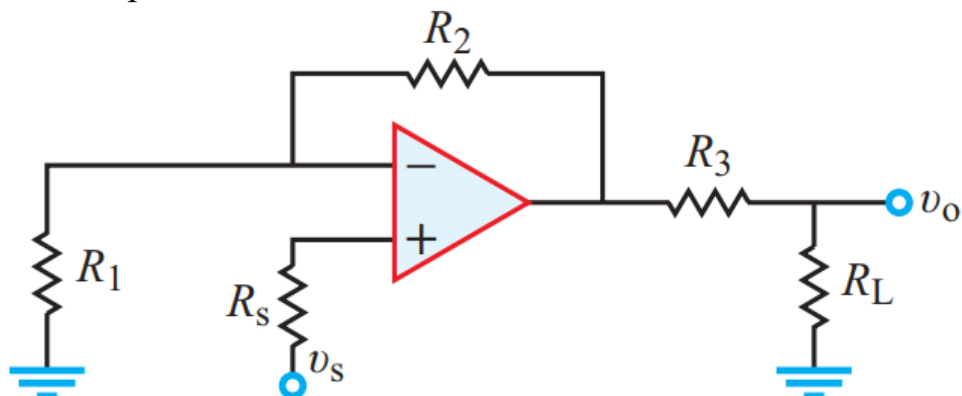5. Write an expression for  $v_o$  in terms of  $v_s$ .



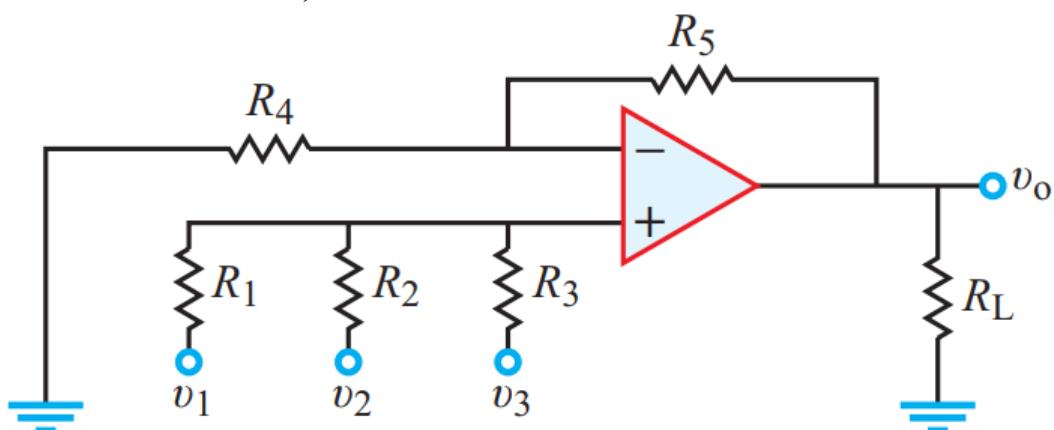6. Find  $v_o$  in terms of  $v_1$ ,  $v_2$  and  $v_3$ .



7. For the circuits below, assuming the opamp is ideal

- Write the transfer functions ( $T(s) = v_o/v_i$ ) of each circuits below.
- Write the expression for the magnitude ( $|T(j\omega)|$ ) and phase ( $\angle T(j\omega)$ ) for each
- Sketch their Bode plots marking all relevant magnitudes and frequencies for  $R = 10k\Omega$  and  $C = 15.91pF$ .

