




A current source in a linear circuit has  $i = 15 \cos(25\pi t + 25)$

A. What is the amplitude of the current?  $A = 15$

B. What is the angular frequency?  $\omega = 25\pi$

C. Find the frequency of the current.  $f = \frac{\omega}{2\pi} = 12.5 \text{ Hz}$

D. What is the phase?  $\phi = 25^\circ$

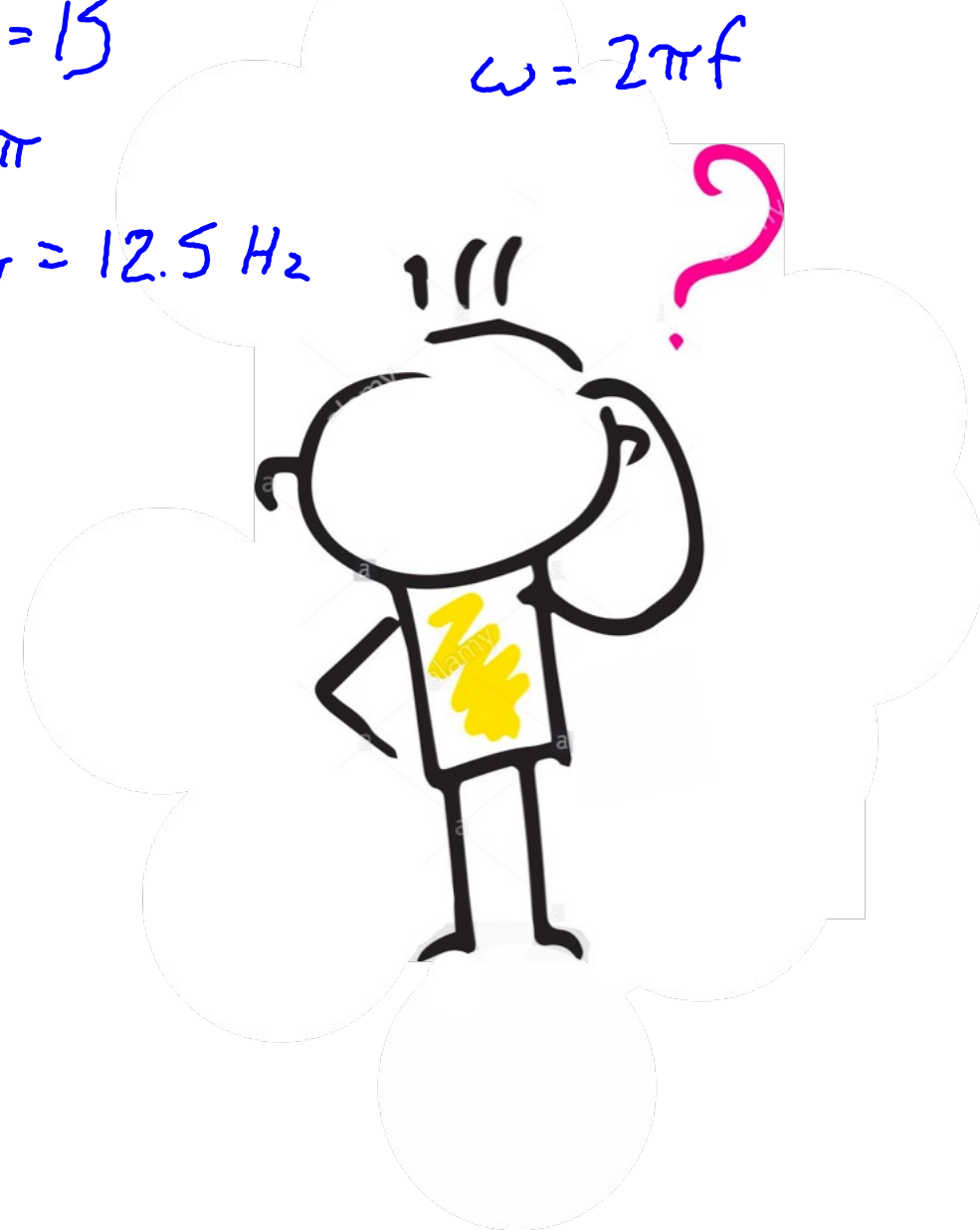



**THE OHIO STATE UNIVERSITY**

---

COLLEGE OF ENGINEERING

# Phasor Domain




- Learning Objectives:
  - Transform time-varying sinusoidal functions to the phasor domain and vice versa.





On time domain:

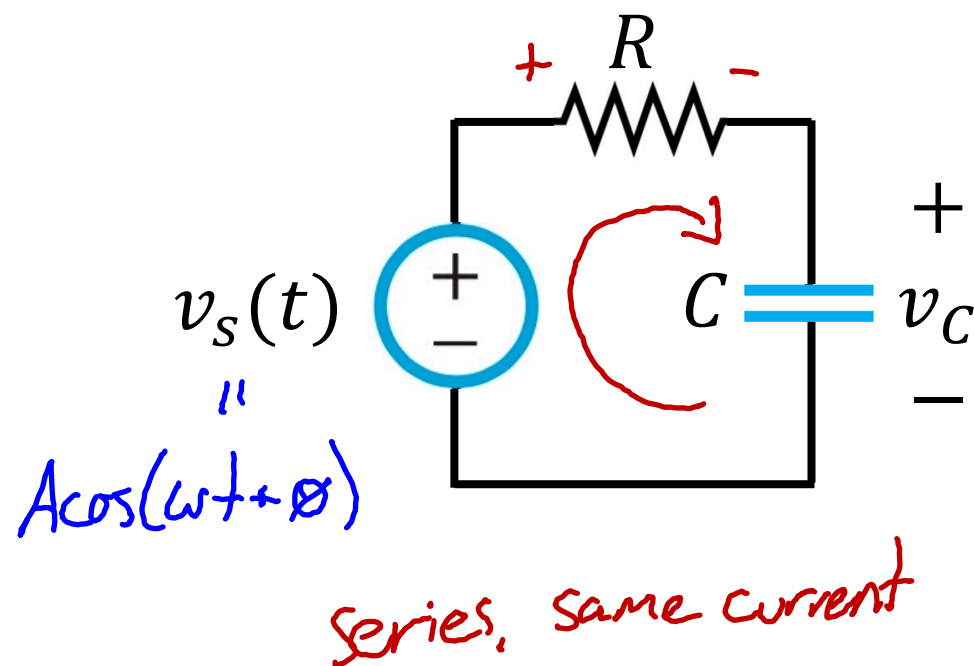- AC circuit with capacitors or inductors challenging
  - i-v relationships are time dependent



$$i_C(t) = C \cdot \frac{dv_C(t)}{dt} = i_R$$

KVL


$$A\cos(\omega t + \phi) = V_R + V_C(t)$$

$$A\cos(\omega t + \phi) = R \cdot i_R + V_C(t)$$

$$A\cos(\omega t + \phi) = RC \frac{dV_C(t)}{dt} + V_C(t)$$



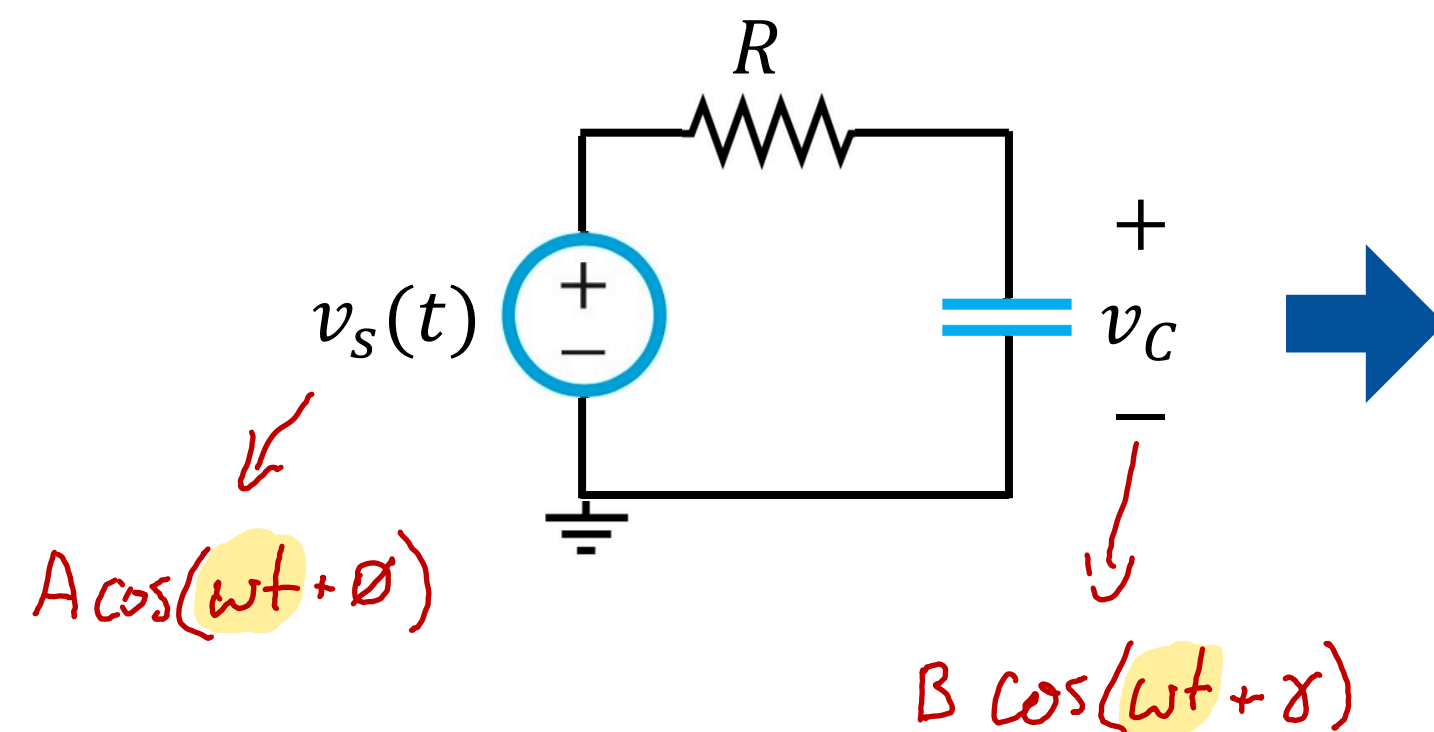- AC circuit: Circuit with a sinusoidal source.
- AC circuit with capacitors or inductors is described by a differential equation.
  - May be challenging to solve because i-v relationships are time dependent.



### Phasor domain

- Sinusoidal signals can be represented as complex numbers.
- Differential equations get converted into linear equations with no sinusoidal functions.



- The phasor-analysis technique transforms equations from the time domain to the phasor domain.

Time domain:

*time is increase*

$$v(t) = A \cos(\omega t + \varphi)$$

$$= \text{Real} \{ A e^{(\omega t + \varphi)j} \}$$

*same  $\omega$*

$$= \text{Real} \{ \underbrace{A e^{\varphi j}}_{\text{Real}} + \underbrace{e^{\omega t j}}_{\text{Same for everything}} \}$$

Phasor domain:

*phasor is bold*

$$\mathbf{V}(j\omega) = A e^{\varphi j}$$


Frequency is common to all voltages and currents, so it is avoided in the phasor form.

Euler's identity:

$$Z = m e^{\theta j}$$

$$\downarrow$$
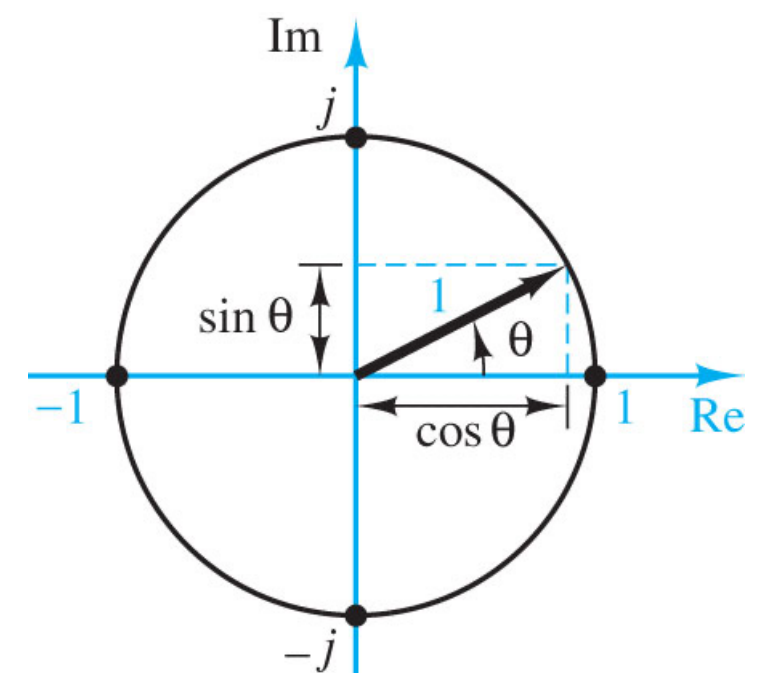
$$Z = \underbrace{m \cos(\theta)}_{\text{real}} + \underbrace{m \sin(\theta)j}_{\text{imaginary}}$$





Time domain:

$$v_1(t) = A \cos(\omega t + \varphi) = 10 \cos(5t + 45)$$

$$v_2(t) = A \cos(\omega t) = \cos(100t)$$

$$v_3(t) = A \cos(\omega t - 90^\circ) = 5 \cos(t - 90)$$

$$v_4(t) = A \sin(\omega t) = 20 \sin(2t) \\ \hookrightarrow 20 \cos(2t - 90)$$

$$\frac{dv(t)}{dt}$$

$$\int v(t) dt$$

$$v_c(t) = 10 \cos(10t + 15) \leftarrow V_5(10j) = 10e^{15j}$$

Phasor domain:

$$V_1(5j) = 10e^{45j}$$

$$V_2(100j) = 1e^{0j} = 1$$


$$V_3(1j) = 5e^{-90j} = -5j$$

$$V_4(2j) = 20e^{-90j} = -20j$$



- $i$ - $v$  relationships of resistors, inductors, and capacitors can be expressed in phasor notation.
- Phasors and impedance simplify AC circuit analysis.
  - Allow use of same solution methods as DC circuits.


time domain

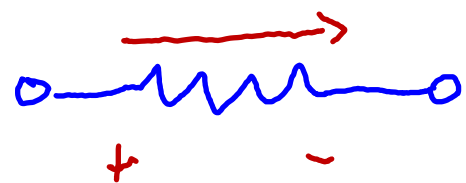

$$V_R = R \cdot i_R$$




$$i_C(t) = C \cdot \frac{dV_C(t)}{dt}$$

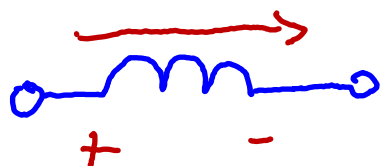

$$V_L(t) = L \cdot \frac{di_L(t)}{dt}$$

phasor domain

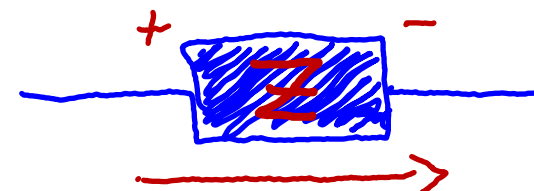

$$\mathbf{V} = \mathbf{Z} \mathbf{I}$$


$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}}$$





i-v relationships of resistors, inductors, and capacitors can be expressed in phasor notation.

Time domain:

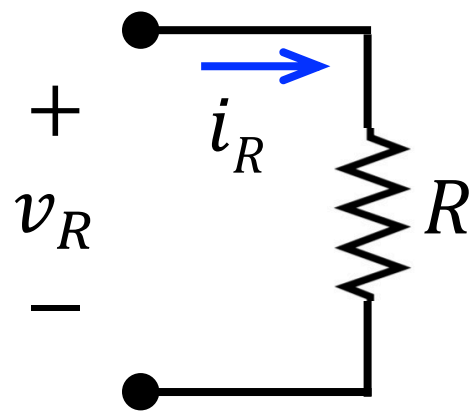


$$i_R = I_m \cos(\omega t + \theta_I)$$

$$V_R = R \cdot i_R$$

$$= R I_m \cos(\omega t + \theta_I)$$

**Impedance:** Ratio of phasor voltage to phasor current.

Phasor domain:

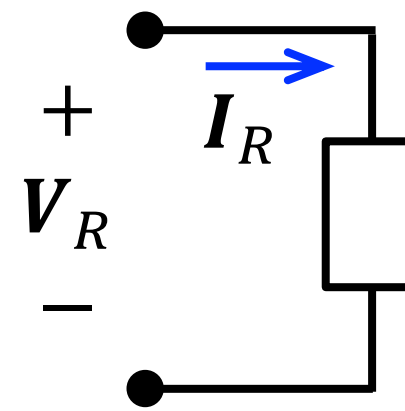

$$I_R(j\omega) = I_m e^{j\theta_I}$$

$$V_R(j\omega) = R I_m e^{j\theta_I} \\ = R I_R(j\omega)$$


$$\frac{V_R(j\omega)}{I_R(j\omega)} = R = Z_R$$



Impedance: Ratio of phasor voltage to phasor current.

$$Z = \frac{V}{I}$$

Time domain:

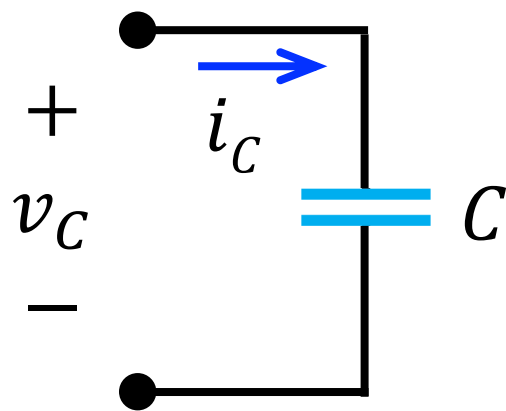


$$V_C(t) = V_m \cos(\omega t + \theta_v)$$

$$i_C(t) = C \cdot \frac{dV_C(t)}{dt}$$

$$= -C V_m \sin(\omega t + \theta_v) \cdot \omega$$

$$= -\omega C V_m \cos(\omega t + \underbrace{\theta_v - 90}_{\text{phase}})$$

Phasor domain:

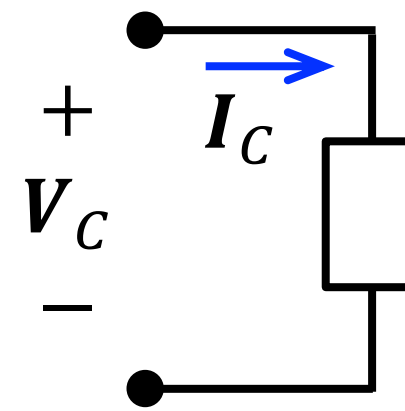

$$V_C(j\omega) = V_m e^{j\theta_v}$$

$$I_C(j\omega) = -\omega C V_m e^{j(\theta_v - 90)}$$

$$= -\omega C V_m e^{j\theta_v} e^{-j90}$$

$$= j\omega C V_m e^{j\theta_v}$$

$$= j\omega C V_C(j\omega)$$

$$\frac{V_C(j\omega)}{I_C(j\omega)} = \frac{1}{j\omega C} = Z_C$$


- Same



Impedance: Ratio of phasor voltage to phasor current.

$$Z = \frac{V}{I}$$

Time domain:

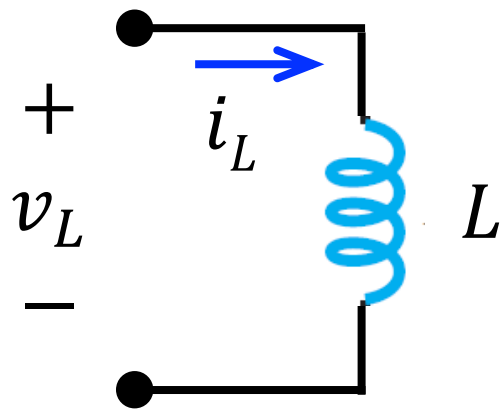


$$i_L(t) = I_m \cos(\omega t + \theta_I)$$

$$V_L(t) = L \cdot \frac{di_L(t)}{dt}$$

→

→

Phasor domain:

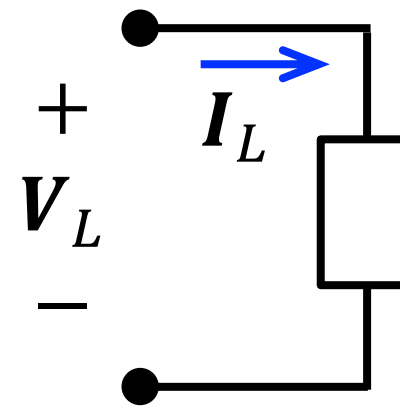

$$I_L(j\omega) = I_m e^{j\theta_I}$$

$$V_L(j\omega) = L \cdot j\omega \cdot I_L(j\omega)$$



Rectangular form    Polar form

$$V = IZ$$

Resistor:  $Z_R = R = R + 0j$

Capacitor:  $Z_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$

Inductor:  $Z_L = j\omega L = 0 + j\omega L$

