
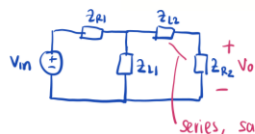


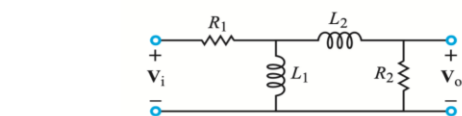
Determine the transfer function $H = V_o/V_i$




series, same current

$$V_o = I_o z_{R2}$$
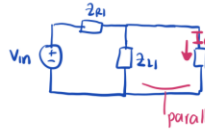
$$z_{eq1} = z_{L1} \parallel (z_{L2} + z_{R2}) = \frac{z_{L1}(z_{L2} + z_{R2})}{z_{L1} + z_{L2} + z_{R2}}$$



parallel, same voltage

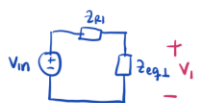

$$V_i = V_{series} \quad I_o = \frac{V_{series}}{z_{L1} + z_{R2}}$$

$$V_i = V_{in} \cdot \frac{z_{eq1}}{z_{R1} + z_{eq1}}$$

$$= V_{in} \frac{z_{L1}(z_{L2} + z_{R2})}{z_{L1} + z_{L2} + z_{R2} + \frac{z_{L1}(z_{L2} + z_{R2})}{z_{L1} + z_{L2} + z_{R2}}}$$

$$= V_{in} \frac{z_{L1}(z_{L2} + z_{R2})}{z_{R1}(z_{L1} + z_{L2} + z_{R2}) + z_{L1}(z_{L2} + z_{R2})}$$

$$I_o = \frac{V_{series}}{z_{L1} + z_{R2}}$$

$$V_o = V_{in} \frac{z_{L1}(z_{L2} + z_{R2})}{z_{R1}(z_{L1} + z_{L2} + z_{R2}) + z_{L1}(z_{L2} + z_{R2})}$$

$$= V_{in} \frac{z_{L1}}{z_{R1}(z_{L1} + z_{L2} + z_{R2}) + z_{L1}(z_{L2} + z_{R2})}$$

$$V_o = I_o z_{R2}$$

$$V_o = V_{in} \frac{z_{L1} z_{R2}}{z_{R1}(z_{L1} + z_{L2} + z_{R2}) + z_{L1}(z_{L2} + z_{R2})}$$

$$\frac{V_o}{V_{in}} = \frac{z_{L1} z_{R2}}{z_{R1}(z_{L1} + z_{L2} + z_{R2}) + z_{L1}(z_{L2} + z_{R2})}$$

$$= \frac{j\omega L_1 R_2}{R_1(j\omega L_1 + j\omega L_2 + R_2) + j\omega L_1(j\omega L_2 + R_2)}$$

$$= \frac{j\omega L_1 R_2}{R_1 R_2 + R_1 j\omega(L_1 + L_2) + j\omega L_1 R_2 - \omega^2 L_1 L_2}$$

$$z_{R2} = R_2$$

$$z_{R1} = R_1$$

$$z_{L1} = j\omega L_1$$

$$z_{L2} = j\omega L_2$$

Extra Problem 2

Convert the following voltage ratios to dB:

$$1. 3 \times 10^2 \rightarrow 20 \log_{10}(300) = 49.54 \text{ dB}$$

$$2. 0.510^{-2} \rightarrow 20 \log_{10}(0.005) = -46.02 \text{ dB}$$

$$3. \sqrt{2000} \rightarrow 20 \log_{10}(\sqrt{2000})$$

$$= 20 \log_{10}(2000)^{1/2}$$

$$4. (360)^{1/4} \rightarrow 10 \log_{10}(2000) = 33.01 \text{ dB}$$

$$\downarrow$$

$$20 \log_{10}(360^{1/4}) = 5 \log_{10}(360) = 12.78 \text{ dB}$$

Extra Problem 3

Convert the following dB values to voltage ratios:

$$1. 36 \text{ dB} \rightarrow 10^{36/20} = 63.09 \text{ V/V}$$

$$20 \log_{10}\left(\frac{V_{out}}{V_{in}}\right) = \text{dB}$$

$$2. 0.6 \text{ dB} \rightarrow 10^{0.6/20} = 1.07 \text{ V/V}$$

$$\log_{10}\left(\frac{V_{out}}{V_{in}}\right) = \frac{\text{dB}}{20}$$

$$3. -2 \text{ dB} \rightarrow 10^{-2/20} = 0.79 \text{ V/V}$$

$$\frac{V_{out}}{V_{in}} = 10^{\text{dB}/20}$$

$$4. -60 \text{ dB} \rightarrow 10^{-60/20} = 10^{-3} = 0.001$$

Generate Bode magnitude and phase plots (straight-line approximations) for the following voltage transfer function.

$$H(j\omega) = \frac{j\omega}{10 + j\omega} \times \frac{V_o}{V_i}$$

$$1 + j\omega/10 \quad \omega_c = \frac{1}{10}$$

$$= \frac{j\omega/10}{1 + j\omega/10} \quad \frac{1}{10} = \frac{1}{\omega_c}$$



$$\omega_c = 10$$

$$M(\omega) = \frac{\omega/10}{\sqrt{1 + \omega^2/100}}$$

$$\phi(\omega) = 90 - \tan^{-1}\left(\frac{\omega/10}{1}\right)$$

$$\lim_{\omega \rightarrow 0} H(\omega) = \frac{0}{1 + 0} = 0$$
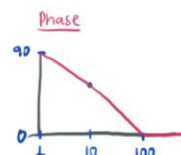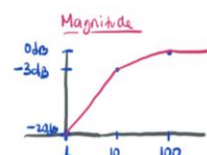
$$\lim_{\omega \rightarrow \infty} H(\omega) = \frac{\infty}{1 + \infty} = 0$$



Extra Practice 5

Generate Bode magnitude and phase plots (straight-line approximations) for the following voltage transfer function



$$H(s) = \frac{30(j\omega + 10)}{(2j\omega + 200)(2j\omega + 1000)}$$

$$= 30 \cdot (j\omega + 10) \cdot \frac{1}{2j\omega + 200} \cdot \frac{1}{2j\omega + 1000}$$

$$= 30 (j\omega/10 + 1) \cdot \frac{1}{(2j\omega/200) 200} \cdot \frac{1}{(2j\omega/1000) 1000}$$

$$j\omega/\omega_c + 1$$

Magnitude

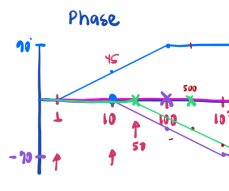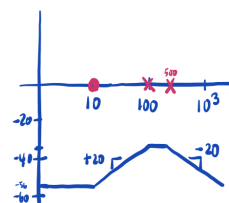

$$= \frac{3}{2 \times 10^3} (j\omega/10 + 1) \cdot \frac{1}{(2j\omega/200) 200} \cdot \frac{1}{(2j\omega/1000) 1000}$$

$$\text{zeros} \rightarrow 10$$

$$\text{poles} \rightarrow 100, 500$$

$$K = \frac{3}{2 \times 10^3} \rightarrow 20 \log_{10}(1.5 \text{ m}) = -56.48$$

Extra Problem 2

Convert the following voltage ratios to dB:

$$1. 3 \times 10^2 \rightarrow 20 \log_{10}(300) = 49.54 \text{ dB}$$

$$2. 0.510^{-2} \rightarrow 20 \log_{10}(0.005) = -46.02 \text{ dB}$$

$$3. \sqrt{2000} \rightarrow 20 \log_{10}(\sqrt{2000})$$

$$= 20 \log_{10}(2000)^{1/2}$$

$$4. (360)^{1/4} \rightarrow 10 \log_{10}(2000) = 33.01 \text{ dB}$$

$$\downarrow$$

$$20 \log_{10}(360^{1/4}) = 5 \log_{10}(360) = 12.78 \text{ dB}$$

Extra Problem 3

Convert the following dB values to voltage ratios:

$$1. 36 \text{ dB} \rightarrow 10^{36/20} = 63.09 \text{ V/V}$$

$$20 \log_{10}\left(\frac{V_{out}}{V_{in}}\right) = \text{dB}$$

$$2. 0.6 \text{ dB} \rightarrow 10^{0.6/20} = 1.07 \text{ V/V}$$

$$\log_{10}\left(\frac{V_{out}}{V_{in}}\right) = \frac{\text{dB}}{20}$$


$$3. -2 \text{ dB} \rightarrow 10^{-2/20} = 0.79 \text{ V/V}$$

$$\frac{V_{out}}{V_{in}} = 10^{\text{dB}/20}$$

$$4. -60 \text{ dB} \rightarrow 10^{-60/20} = 10^{-3} = 0.001$$

Extra Practice 6

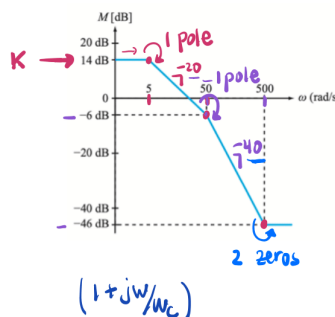Determine the voltage transfer function $H(j\omega)$ corresponding to the Bode magnitude plot shown



$$H(j\omega) = \frac{5.012 (1 + j\omega/500)^2}{(1 + j\omega/5)(1 + j\omega/50)}$$

$$20 \log_{10}(K) = 14$$

$$10^{14/20} = K$$

$$K = 5.012$$


For the op-amp circuit below, use the behavioral model to find an expression for the current gain $G_i = i_L/i_S$.

Ideal values

$$R_{out} = 0\Omega$$

$$R_{in} = \infty$$

$$A \rightarrow \infty$$

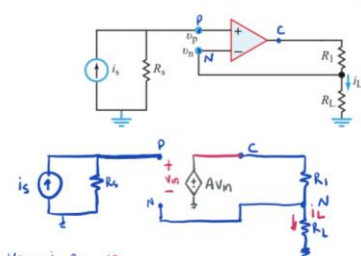

$$V_P = i_S R_S \quad (1)$$

$$V_N = V_P - V_N \quad (2)$$

voltage division:

$$(3) V_N = V_{RL} = A V_{in} \cdot \frac{R_L}{R_L + R_1}$$

(2) in (3)

$$V_N = A(V_P - V_N) \cdot \frac{R_L}{R_L + R_1}$$

$$(1) \rightarrow V_N = A(i_S R_S - V_N) \cdot \frac{R_L}{R_L + R_1}$$

$$V_N \left[1 + \frac{A R_L}{R_L + R_1} \right] = \frac{A i_S R_S R_L}{R_L + R_1}$$

$$V_N = \frac{A i_S R_S R_L}{R_L + R_1 + A R_L}$$

$$V_N = \frac{A i_S R_S R_L}{R_L + R_1 + A R_L}$$

$$V_N = V_{RL} = R_L \cdot i_L$$


$$\frac{A i_S R_S R_L}{R_L + R_1 + A R_L} = R_L i_L$$

$$\frac{i_L}{i_S} = \frac{A R_S R_L}{R_L + R_1 + A R_L}$$

$$\lim_{A \rightarrow \infty} \frac{i_L}{i_S} = \frac{R_S R_L}{R_L^2} = \frac{R_S}{R_L}$$

$$\boxed{\frac{i_L}{i_S} = \frac{R_S}{R_L}}$$

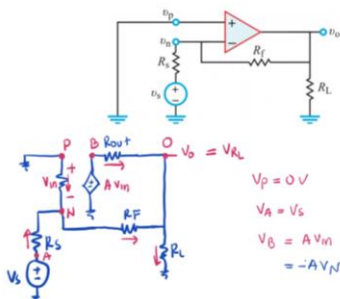- Use the behavioral circuit model to obtain an expression for the closed-loop gain $G = v_o/v_i$, in terms of R_S, R_i, R_o, R_L, R_F , and A .
- Determine the value of G for $R_S = 10\Omega, R_i = 10M\Omega, R_o = 50\Omega, R_L = 1k\Omega, R_F = 1k\Omega$, and $A = 10^6$.
- Determine the value of G by letting $A \rightarrow \infty, R_i \rightarrow \infty, R_o \rightarrow 0$ (ideal op-amp model).



KCL @ N:

$$i_{S1} + i_{N1} = i_{R_F}$$

$$\frac{V_{S1}}{R_L} + \frac{V_{N1}}{R_{in}} = \frac{V_{R_F}}{R_F}$$

KCL @ O:

$$i_{R_F} + i_{out} = i_L$$

$$\frac{V_{R_F}}{R_F} + \frac{V_{out}}{R_{out}} = \frac{V_L}{R_L}$$

$$\left[\frac{V_N - V_O}{R_F} + \frac{-A V_N - V_O}{R_{out}} \right] R_F R_L = \frac{V_O - V_N}{R_L} R_F R_L$$

$$R_{out} R_L V_N - R_{out} R_L V_O - A R_L R_F V_N - R_F R_L V_O = R_F R_{out} V_O$$

$$(R_{out} R_L - A R_F R_L) V_N = (R_F R_{out} + R_F R_L + R_{out} R_L) V_O$$

$$V_N = \frac{(R_F R_{out} + R_F R_L + R_{out} R_L) V_O}{(R_{out} R_L - A R_F R_L)} \quad (1)$$

$$\frac{R_{in} R_F V_S + R_S R_{in} V_O}{R_S R_{in} + R_{in} R_F + R_S R_F} = \frac{(R_F R_{out} + R_F R_L + R_{out} R_L) V_O}{(R_{out} R_L - A R_F R_L)}$$

$$R_{in} R_F V_S (R_{out} R_L - A R_F R_L) + V_O R_S R_{in} (R_{out} R_L - A R_F R_L) =$$

$$(R_S R_{in} + R_{in} R_F + R_S R_F) (R_F R_{out} + R_F R_L + R_{out} R_L) V_O$$

$$R_{in} R_F V_S (R_{out} R_L - A R_F R_L) = V_O [R_S R_{in} (A R_F R_L - R_{out} R_L) +$$

$$(R_S R_{in} + R_{in} R_F + R_S R_F) (R_F R_{out} + R_F R_L + R_{out} R_L)]$$

$$\frac{V_O}{V_S} = \frac{R_{in} R_F (R_{out} R_L - A R_F R_L)}{R_S R_{in} (A R_F R_L - R_{out} R_L) + (R_S R_{in} + R_{in} R_F + R_S R_F) (R_F R_{out} + R_F R_L + R_{out} R_L)}$$

$$B) \frac{V_O}{V_S} = -99.98$$


$$C) \lim_{A \rightarrow \infty} \frac{V_O}{V_S} = \frac{R_{in} R_F (R_{out} R_L - A R_F R_L)}{R_S R_{in} (A R_F R_L - R_{out} R_L) + (R_S R_{in} + R_{in} R_F + R_S R_F) (R_F R_{out} + R_F R_L + R_{out} R_L)}$$

$$\lim_{A \rightarrow \infty} \frac{-A R_F R_L R_{in} R_F}{R_S R_{in} (A R_F R_L - R_{out} R_L) + (R_S R_{in} + R_{in} R_F + R_S R_F) (R_F R_{out} + R_F R_L + R_{out} R_L)}$$

$$\lim_{A \rightarrow \infty} \frac{-A R_F R_L R_{in} R_F}{A R_F R_L R_S R_{in}} = -\frac{R_F}{R_S}$$

$$\frac{-R_F}{R_S} = \text{Inverting amplifier.}$$

- Solve for v_o in terms of v_s .

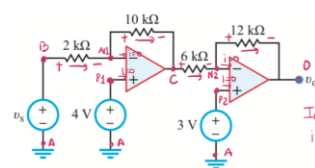

$$\text{Node voltage analysis } V_A = 0V, V_B = V_S, V_{P1} = 4V, V_{P2} = 3V, V_{N1} = V_{P1} = 4V, V_{N2} = V_{P2} = 3V$$

Do not do KCL @ C and O

KCL @ N1:

$$i_{2K} = i_{10K}$$

$$\frac{V_{2K}}{2K} = \frac{V_{10K}}{10K}$$

$$\frac{V_S - V_{N1}}{2K} = \frac{V_{N1} - V_C}{10K}$$

$$10K(V_S - 4) = 2K(4 - V_C)$$

$$10K V_S - 40K = 8K - 2K V_C$$

$$5V_S - 20 = 4 - V_C$$

$$5V_S - 24 = -V_C \quad (1)$$

$$5V_S - 24 = -V_C \quad (1)$$

$$(1) - (2) \rightarrow -5V_S + 24 = \frac{9 - V_O}{2}$$

$$-10V_S + 48 = 9 - V_O$$

$$V_O = 10V_S - 39$$

KCL @ N2:

$$i_{6K} = i_{12K}$$

$$\frac{V_{6K}}{6K} = \frac{V_{12K}}{12K}$$

$$\frac{V_C - V_{N2}}{6K} = \frac{V_{N2} - V_O}{12K}$$

$$2V_C - 2(3) = 3 - V_O$$

$$2V_C - 6 = 3 - V_O$$


$$2V_C - 9 = -V_O$$

$$2V_C - 9 = -V_O$$

$$(2) V_C = \frac{9 - V_O}{2}$$

For the op-amp circuit below:

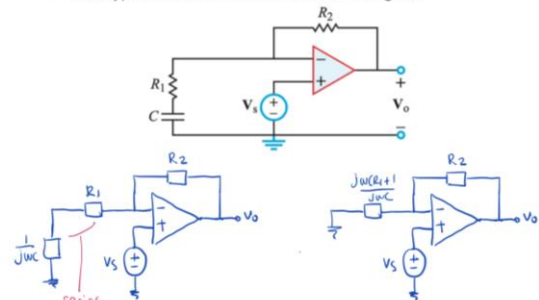- Obtain an expression for $H(\omega) = V_o/V_s$ in standard form.
- Generate spectral plots for the magnitude and phase of $H(\omega)$, given that $R_1 = 1k\Omega, R_2 = 4k\Omega$, and $C = 1\mu F$.
- What type of filter is it? What is its maximum gain?



$$R_1 + \frac{1}{j\omega C} = \frac{j\omega C R_1 + 1}{j\omega C}$$

Non-inverting amplifier.

$$\frac{V_O}{V_S} = \frac{R_2 + 2 \text{ series}}{2 \text{ series}}$$

$$= \frac{R_2 + \frac{j\omega C R_1 + 1}{j\omega C}}{\frac{j\omega C R_1 + 1}{j\omega C}}$$

$$= \frac{j\omega C R_2 + j\omega C R_1 + 1}{1 + j\omega C R_1}$$

$$= \frac{j\omega C (R_1 + R_2) + 1}{1 + j\omega C R_1}$$

$$1 + j\omega C R_1 \rightarrow \frac{j\omega C (R_1 + R_2) + 1}{1 + j\omega C R_1}$$

$$\frac{V_O}{V_S} = \frac{j\omega (1 \times 10^{-3}) 5k + 1}{1 + j\omega (1 \times 10^{-3}) 1k} = \frac{1 + j\omega 5 \times 10^{-3}}{1 + j\omega 1 \times 10^{-3}}$$

$$H(j\omega) = \frac{\sqrt{1 + (5 \times 10^{-3})^2 \omega^2}}{\sqrt{1 + (1 \times 10^{-3})^2 \omega^2}}$$


$$\omega \rightarrow 0 \quad M = 1$$

$$\omega \rightarrow \infty \quad M = 5$$

HPF

$$M = 1 \quad 20 \log(1) = 0 \text{ dB}$$



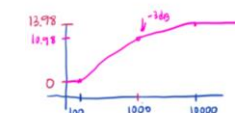
$$M = 5 \quad 20 \log(5) = 13.98 \text{ dB}$$



$$1 + j\omega (1 \times 10^{-3}) = 1 + \frac{j\omega}{1000}$$

$$\omega_c = \frac{1}{1 \times 10^{-3}} = 1000$$

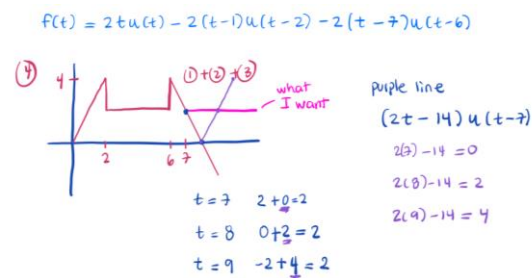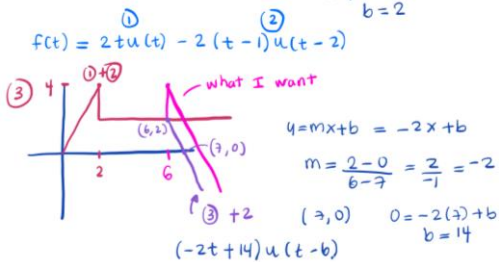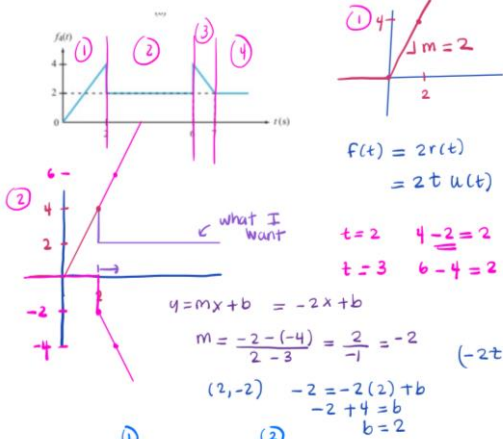- Express the waveforms in terms of step functions and then determine its Laplace transform. [Recall that the ramp function is given by $r(t-T) = (t-T)u(t-T)$. Assume that all waveforms are zero for $t < 0$.]



$$f(t) = 2t u(t) - 2(t-1)u(t-2) - 2(t-7)u(t-6) + 2(t-7)u(t-7)$$

$$F(s) = \frac{2}{s^2} - \frac{2}{s^2} e^{-2s} - \frac{2}{s^2} e^{-6s} + \frac{2}{s^2} e^{-7s} + \frac{2}{s^2} e^{-7s}$$

Find the Laplace transform of the following signals:

- $h_1(t) = 4te^{-2t}u(t)$
- $h_2(t) = 10\cos(12t + 60^\circ)u(t)$
- $h_3(t) = 12e^{-3(t-4)}u(t-4)$


$$H_1(s) = \frac{4}{(s+2)^2}$$

$$H_2(s) = 10 \cdot \frac{s \cos(60^\circ) - 12 \sin(60^\circ)}{s^2 + 12^2} = \frac{5s - 10.392}{s^2 + 144}$$

$$H_3(s) = 12 \cdot \frac{e^{-4s}}{s+3}$$

| $f(t)$ | $F(s) = \mathcal{L}\{f(t)\}$ |
|---------------------|--|
| $\delta(t)$ | 1 |
| $\delta(t-T)$ | e^{-sT} |
| 1 | $\frac{1}{s}$ |
| t | $\frac{1}{s^2}$ |
| t^n | $\frac{n!}{s^{n+1}}$ |
| e^{-at} | $\frac{1}{s+a}$ |
| $e^{-at} \cos(bt)$ | $\frac{s+a}{(s+a)^2 + b^2}$ |
| $e^{-at} \sin(bt)$ | $\frac{b}{(s+a)^2 + b^2}$ |
| $\cos(bt)$ | $\frac{s}{s^2 + b^2}$ |
| $\sin(bt)$ | $\frac{b}{s^2 + b^2}$ |
| $\cos(bt-T)$ | $\frac{s \cos(bT) - b \sin(bT)}{s^2 + b^2} e^{-sT}$ |
| $\sin(bt-T)$ | $\frac{b \cos(bT) + s \sin(bT)}{s^2 + b^2} e^{-sT}$ |
| $t^n \cos(bt)$ | $\frac{(-1)^n (s^n - b^2 s^{n-2} + \dots)}{(s^2 + b^2)^{n+1}}$ |
| $t^n \sin(bt)$ | $\frac{(-1)^n (b^n - s b^{n-2} + \dots)}{(s^2 + b^2)^{n+1}}$ |
| $\cos(bt) \cos(ct)$ | $\frac{1}{2} \left(\frac{s}{s^2 + b^2} + \frac{s}{s^2 + c^2} \right)$ |
| $\sin(bt) \sin(ct)$ | $\frac{1}{2} \left(\frac{b}{s^2 + b^2} - \frac{b}{s^2 + c^2} \right)$ |
| $\cos(bt) \sin(ct)$ | $\frac{1}{2} \left(\frac{b}{s^2 + b^2} + \frac{s}{s^2 + c^2} \right)$ |
| $\sin(bt) \cos(ct)$ | $\frac{1}{2} \left(\frac{s}{s^2 + b^2} - \frac{b}{s^2 + c^2} \right)$ |

Determine $v_C(t)$ for $t \geq 0$.

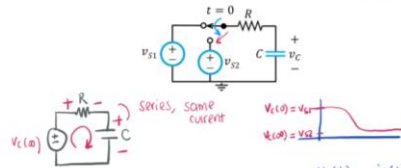

KVL: $v_C(\omega) = v_R(\omega) + v_C(\omega)$
 $v_C(\omega) = R \cdot i_C(\omega) + v_C(\omega)$
 differential eqn $\rightarrow v_C(\omega) = RC \cdot \frac{di_C(\omega)}{dt} + v_C(\omega)$
 Laplace Transform
 $\frac{v_C(\omega)}{s} = RC \cdot (s v_C(\omega) - v_C(0)) + \frac{v_C(0)}{s}$
 $\frac{v_C(\omega)}{s} + RC v_C(\omega) = \frac{v_C(0)}{s} + RC v_C(0)$
 $v_C(s) = \frac{v_C(0)}{s} + \frac{RC v_C(0)}{s+1/RC}$
 $= \frac{v_C(0)}{s} + \frac{RC v_C(0)}{s+1/RC}$
 $= \frac{v_C(0)}{s} + \frac{1/RC}{s+1/RC}$

Partial Fraction Expansion

$$v_C(s) = \frac{A}{s} + \frac{B}{s+1/RC}$$

$$A = v_C(s) \cdot s \Big|_{s=0} = \frac{v_C(0)}{1/RC} + 0 \cdot v_C(0) = v_C(0)$$

$$B = v_C(s) \cdot (s+1/RC) \Big|_{s=-1/RC} = \frac{v_C(0)}{-1/RC} + \frac{1/RC}{-1/RC} = -v_C(0) + \frac{1}{RC}$$

$$v_C(s) = \frac{v_C(0)}{s} + \frac{v_C(0) - 1/RC}{s+1/RC}$$

$$v_C(t) = \left[v_C(0) + (v_C(0) - 1/RC) e^{-t/RC} \right] u(t)$$

Use partial fraction expansion to find $f(t)$:

$$F(s) = \frac{3s^3 + 36s^2 + 131s + 144}{s(s+4)(s^2+6s+9)}$$

$$= \frac{A}{s} + \frac{B}{s+4} + \frac{C}{s+3} + \frac{D}{(s+3)^2}$$

$$A = F(s) \cdot s \Big|_{s=0} = \frac{3s^3 + 36s^2 + 131s + 144}{(s+4)(s+3)^2} \Big|_{s=0} = \frac{144}{(4)(3^2)} = \frac{144}{36}$$

$$\boxed{A = 4}$$

$$B = F(s) \cdot (s+4) \Big|_{s=-4} = \frac{3s^3 + 36s^2 + 131s + 144}{(s)(s+3)^2} \Big|_{s=-4} = \frac{3(-4)^3 + 36(-4)^2 + 131(-4) + 144}{-4(-4+3)^2}$$

$$= \frac{-3(64) + 36(16) - 131(4) + 144}{-4} = -1$$

$$\boxed{B = -1}$$

$$D = F(s) \cdot (s+3)^2 \Big|_{s=-3} = \frac{3s^3 + 36s^2 + 131s + 144}{(s)(s+4)} \Big|_{s=-3} = \frac{3(-3)^3 + 36(-3)^2 + 131(-3) + 144}{-3(-3+4)}$$

$$= \frac{-81 + 36(9) + 131(-3) + 144}{-3} = 2$$

$$\boxed{D = 2}$$

$$F(s) = \frac{4}{s} + \frac{-1}{s+4} + \frac{C}{s+3} + \frac{2}{(s+3)^2}$$

$$N(s) = 4(s+3)^2(s+4) - s(s+3)^2 + C(s+4)(s+3)s + 2(s+4)s$$

$$= 4(s^2+6s+9)(s+4) - s^3 - 6s^2 - 9s + C(s^3+7s^2+12s) + 2s^2 + 8s$$

$$= 4s^3 + 40s^2 + 132s + 144 - s^3 - 6s^2 - 9s + C(s^3 + 7s^2 + 12s) + 2s^2 + 8s$$

$$= s^3(4-1+C) + s^2(40-6+7C+2) + s(132-9+12C+8) + 144$$

$$\begin{matrix} 3 & 36 & 131 & 144 \end{matrix}$$

$$3+C = 3$$


$$C = 0$$

$$F(s) = \frac{4}{s} - \frac{1}{s+4} + \frac{2}{(s+3)^2}$$

$$f(t) = 4u(t) - e^{-4t}u(t) + 2t e^{-3t}u(t)$$

$$= [4 - e^{-4t} + 2t e^{-3t}] u(t)$$

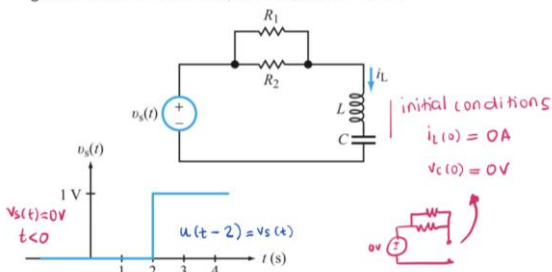- $v_s(t)$ is given by the waveform displayed. Determine $i_L(t)$, given that $R_1 = R_2 = 4\Omega$, $L = 2H$, and $C = 0.5F$.



$$v_s(t) = \frac{e^{-2s}}{s}$$

$$Z_L = sL = 2s$$

$$Z_C = \frac{1}{sC} = \frac{2}{s}$$

$$Z_{eq} = \frac{2(s^2+1)}{s} + 2$$

$$I_L = \frac{V_s}{Z_{eq}} = \frac{e^{-2s}/s}{\frac{2(s^2+1)}{s} + 2} = \frac{e^{-2s}}{2(s^2+s+1)}$$

$$s_{1,2} = \frac{-1 \pm \sqrt{1-4}}{2} = -0.5 \pm 0.87j$$

$$F(s) = \frac{A}{s+0.5+0.87j} + \frac{B}{s+0.5-0.87j}$$


$$A = F(s) \cdot (s+0.5+0.87j) \Big|_{s=-0.5-0.87j} = \frac{0.5}{-0.5-0.87j+0.5-0.87j} = 0.29j = 0.29e^{90^\circ}$$

$$B = F(s) \cdot (s+0.5-0.87j) \Big|_{s=-0.5+0.87j} = \frac{0.5}{-0.5+0.87j+0.5+0.87j} = -0.29j = 0.29e^{-90^\circ}$$

$$I_L(s) = \left[\frac{0.29e^{90^\circ}}{s+0.5+0.87j} + \frac{0.29e^{-90^\circ}}{s+0.5-0.87j} \right] e^{-2s}$$

$$i_L(t) = [2(0.29)e^{-0.5t-2} \cos(0.87t-90^\circ)] u(t-2) \text{ line 15}$$

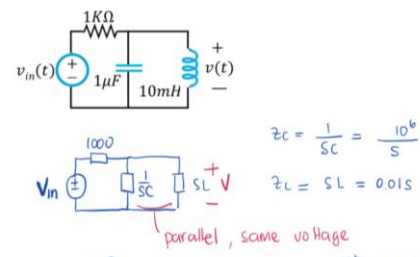- For the circuit below, assume all initial conditions are 0.
- a. Find the s-domain transfer function $V(s)/V_{in}(s)$.



$$Z_C = \frac{1}{sC} = \frac{10^6}{s}$$


$$Z_L = sL = 0.01s$$

$$Z_{eq} = \frac{(10^6)(0.01s)}{10^6 + 0.01s}$$

$$V(s) = V_{in}(s) \cdot \frac{Z_{eq}}{Z_{eq} + 1000}$$

$$\frac{V(s)}{V_{in}(s)} = \frac{10^4 s}{1000 + \frac{10^4 s}{10^6 + 0.01s}} = \frac{10^4 s}{10^6 s^2 + 10^9 + 10^4 s} = \frac{10^3 s}{s^2 + 10^3 s + 10^6}$$

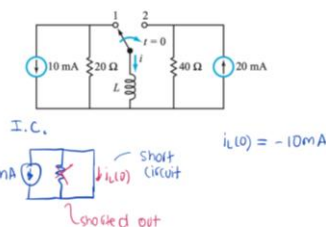- The switch in the below was moved from position 1 to position 2 at $t = 0$, after it had been in position 1 for a long time. Determine $i(t)$ for $t \geq 0$, if $L = 80mH$.



$$I_s(s) = \frac{20m}{s}$$

$$Z_R = 40$$

$$Z_L = sL = 80ms$$

$$Z_L \cdot i_L(0) = 80m(-10m) = -800\mu = -0.8m$$

$$KVL @ A: V_s + V_R = V_{L1}$$

$$-0.8m + 40(I_B - I_A) = 80ms I_A$$

$$-0.8m + \frac{0.8}{s} = (80ms + 40) I_A$$

$$I_A = \frac{0.8 - 0.8ms}{s(80ms + 40)} \cdot \frac{1}{1000} = \frac{10 - 0.01s}{s(s + 500)}$$

$$I_A = I_L = \frac{A}{s} + \frac{B}{s+500}$$

$$A = F(s) \cdot s \Big|_{s=0} = \frac{10 - 0.01(0)}{0 + 500} = 0.02$$

$$B = F(s) \cdot (s+500) \Big|_{s=-500} = \frac{10 - 0.01(-500)}{-500} = -0.01$$

$$I_L = \frac{0.02}{s} - \frac{0.01}{s+500}$$

$$i_L(t) = [0.02 - 0.01e^{-500t}] u(t) \text{ A}$$

$$= [20 - 10e^{-500t}] u(t) \text{ mA}$$