



Lecture Outline

Reminders to self:

- ☐ Turn on lecture recording to Cloud
- ☐ Turn on Zoom microphone

- Last Lecture

- Finished ROM
- Programmable Logic Arrays
- Started Latches & Flip-Flops (groundwork for S-R Latch)

- Today's Lecture

- Latches
- Gated Latches
- Flip-Flops




- Announcements
 - Homework Problem 9-4
 - Posted on Carmen yesterday (2/21)
 - Due: 11:25am Monday 2/27
 - Homework Reminder:
 - HW 9-1 past due
 - HW 9-2 & 9-3 due: 11:59pm Thursday 2/23
 - Read for Friday: pages 352-358, 370, 375-380



Set-Reset Latch

Set-Reset Latch (SR Latch)

- Can be made from two NOR gates with feedback in cross-coupled form
- Term *present state* $[Q(t)]$ used to denote state of Q output of the latch or flip-flop at time any input signal changes
- Term *next state* $[Q(t + \varepsilon)]$ denotes state of Q output after latch or flip-flop has reacted to input change and stabilized
- Normally we will write next state with + superscript, without explicitly showing $t + \varepsilon$

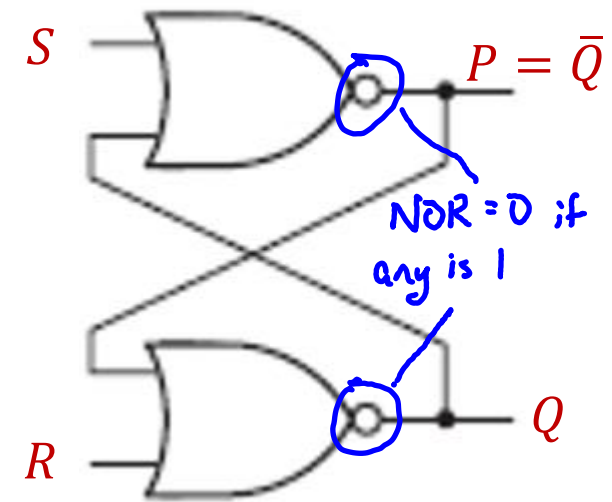

Present State				Next State	
S	R	Q	P	Q^+	P^+
0	0	0	1	0	1
0	0	1	0	1	0
0	1	0	1	0	1
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	0	1	0

} Hold state

} Reset state

} Set State



Set-Reset Latch


Set-Reset Latch (**SR Latch**)

$$\left. \begin{array}{l} S = 1 \\ R = 1 \end{array} \right\} \text{BAD!}$$

- Makes both $P = Q = 0$, but then $P \neq \bar{Q}$
- If S and R are simultaneously changed to 0, both P and Q may both change to 1
- The 1s propagate through the NOR gates changing P and Q to 0
- Latch may continue to oscillate if the gate delays are equal
- *Unstable* : $S = R = 1$ must be avoided

The designer of the circuit using the SR Latch is responsible for avoiding it!

ME!

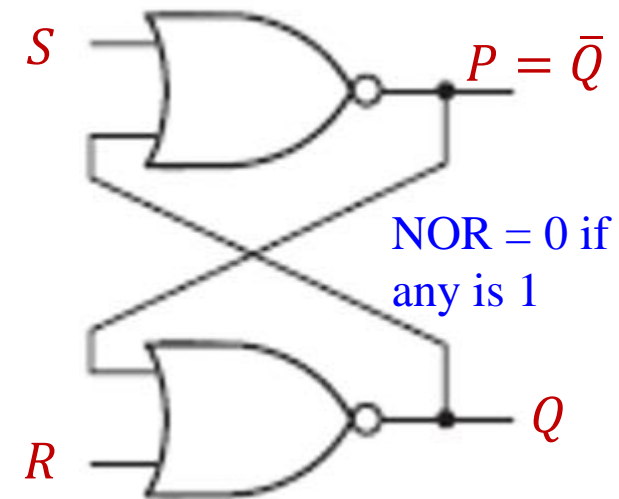





Set-Reset Latch

Set-Reset Latch (**SR Latch**)

SR Latch Component

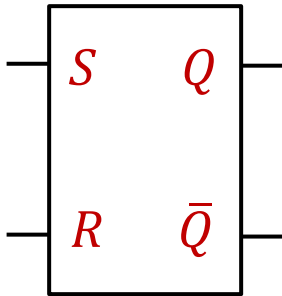

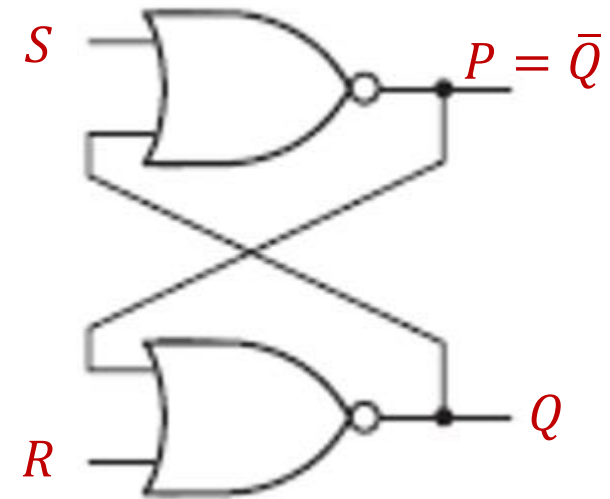- $S = 0, R = 0$ "Hold" $Q^+ = Q$
- $S = 0, R = 1$ "Reset" $Q^+ = 0$
- $S = 1, R = 0$ "Set" $Q^+ = 1$
- $S = 1, R = 1$ **Do Not Allow**
Very Bad



- Note: No clock input in component figure
- We will later use SR flip-flops, which will have a clock input
- That is how you can tell them apart





Set-Reset Latch

Set-Reset Latch (SR Latch)

- A useful application of the SR Latch is switch debouncing
- Switch contacts tend to vibrate open and closed several times before settling to their final position
- Produces an electronically noisy transition
- This noise can interfere with proper operation of a logic circuit

FIGURE 11-9
Switch Debouncing
with an S-R Latch


© Cengage Learning 2014

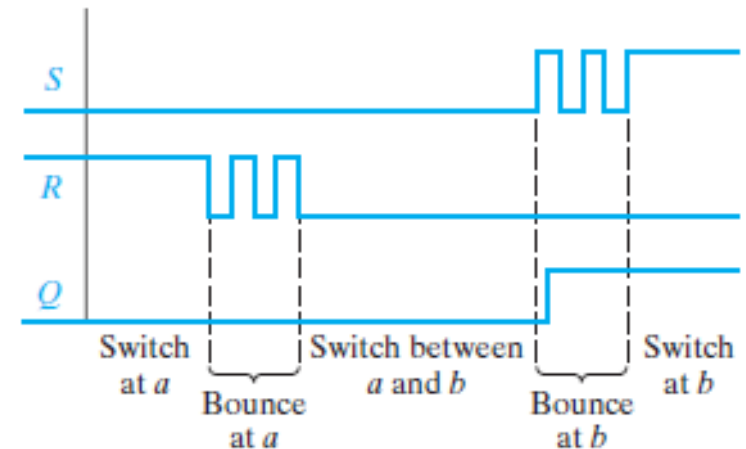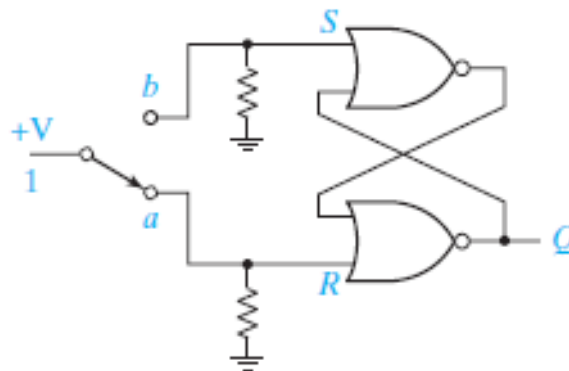

- This debouncing circuit works for double-throw switches (position *a* or position *b*)
- Debouncing a single-throw switch requires a different circuit

 \bar{S} - \bar{R} Latch

A NAND version is also possible

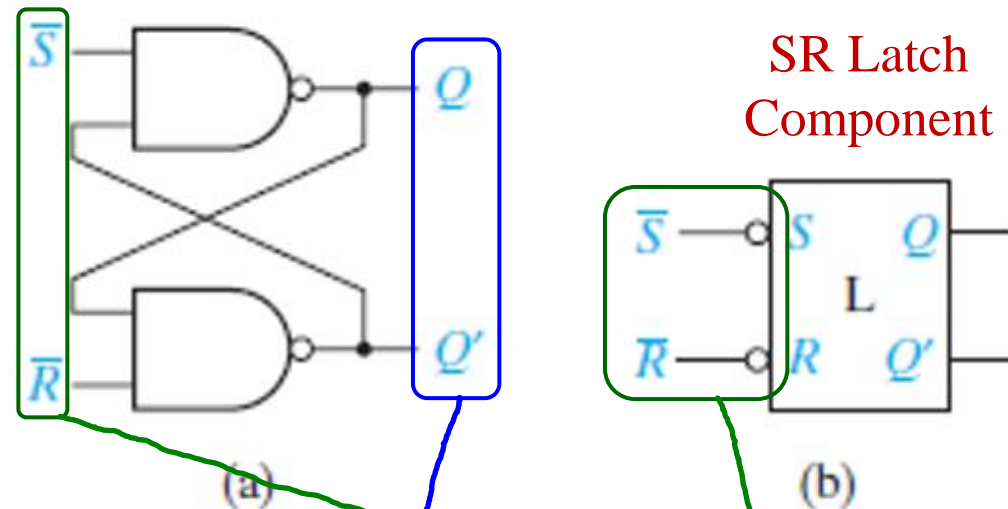 \bar{S} - \bar{R} Latch Circuit

Note swapped outputs and complemented inputs

- $\bar{S} = 1, \bar{R} = 1$ Hold
- $\bar{S} = 0, \bar{R} = 1$ Set
- $\bar{S} = 1, \bar{R} = 0$ Reset
- $\bar{S} = 0, \bar{R} = 0$ Unstable: Do Not Allow

Present
State

Next
State

\bar{S}	\bar{R}	Q	Q^+
1	1	0	0
1	1	1	1
1	0	0	0
1	0	1	0
0	1	0	1
0	1	1	1
0	0	0	-
0	0	1	-

Inputs not allowed




Gated Latches

- Gated latches have an additional input called the *gate* or *enable* input
- When the gate input is inactive
 - Which may be the high or low value
 - State of the latch cannot change
- When the gate input is active
 - Active-high or active-low
 - Latch is controlled by the other inputs
 - Operates as previously described

Gated \bar{S} - \bar{R} Latch

FIGURE 11-11
NAND-Gate Gated
S-R Latch

© Cengage Learning 2014

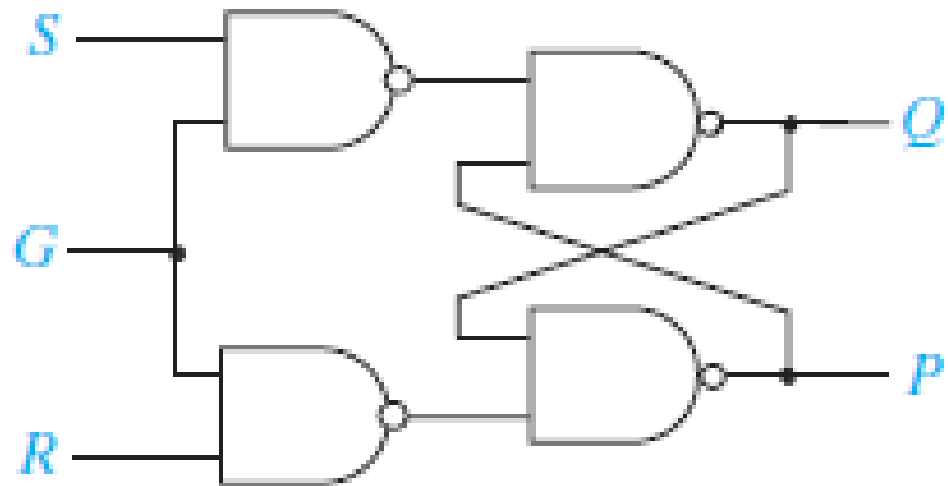


$G = 0 \Rightarrow X = Y = 1$ Hold

$G = 1 \Rightarrow \begin{cases} X = \bar{S} \\ Y = \bar{R} \end{cases}$ Regular operation

Avoid $X = Y = 0$: $G = 1, S = 1, R = 1$

Avoid changing S or R when $G = 1$

 



- Let S and R stabilize before changing G from 0 to 1
- Else glitches from static or dynamic hazards in circuits that generate S or R can change latch to undesired state if they arrive after $G = 1$



Gated S-R Latch

Timing diagram with G serving as a “clock”


→|← Gate
delay

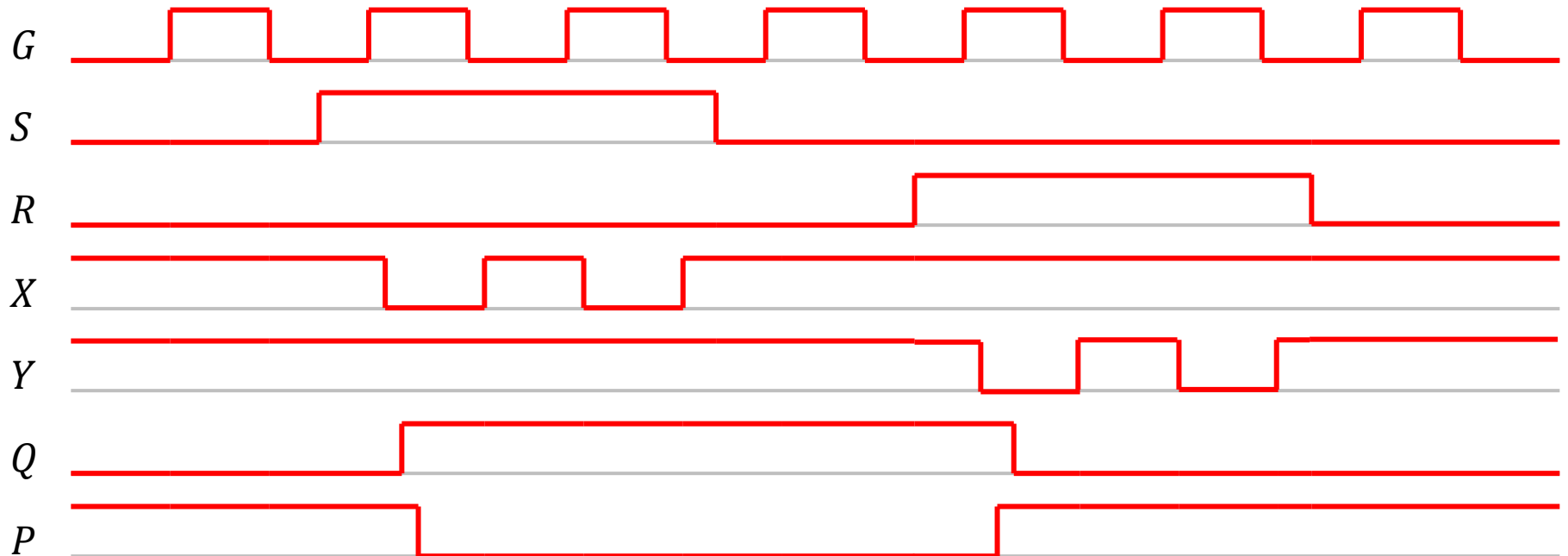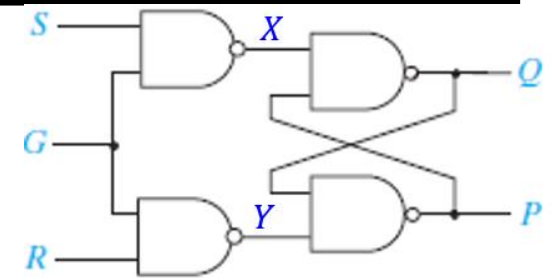



D Latch

D-Latch: *Data Latch*

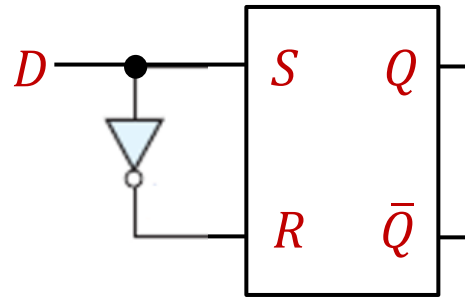

$D = 1 \Rightarrow S = 1, R = 0, Q^+ = 1$ *Set*


$D = 0 \Rightarrow S = 0, R = 1, Q^+ = 0$ *Reset*

Inverter results in: No Hold State (00); No Bad State (11)

But without Hold state it does not really have memory \Rightarrow *Make it gated*




Gated D Latch

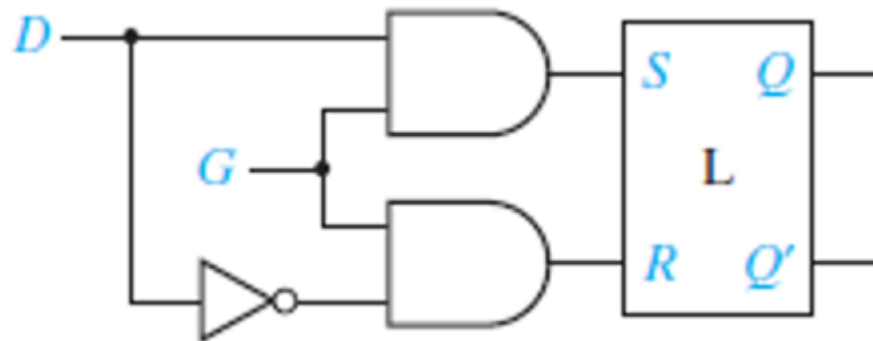

$G = 1 \Rightarrow S = D, R = \bar{D}$ Set or Reset based on value of D

$G = 0 \Rightarrow \begin{cases} S = 0 \\ R = 0 \end{cases}$ Hold

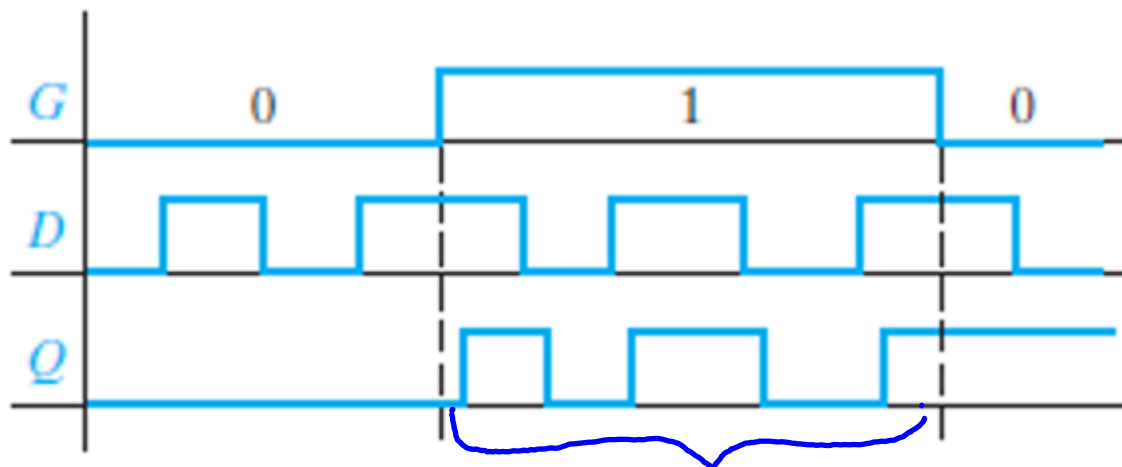Change due to $G = 1$ while D is already stable



Changes due to D changing while $G = 1$

A.k.a. "transparent latch" since $Q = D$ when G is active



Gated Latches vs Edge-Triggered Flip-Flops

- With Gated Latches (*Gated Memory*)
 - Wait until input (*S and R, or D*) is stable before setting $G = 1$ (or 0 if active-low) to write to Q
 - This is “ *Level-Sensitive* ” memory
 - Q updated based on G level of 0 or 1
 - Must avoid changing input(s) while G active
 - Using G as a clock for synchronizing writing to memory might be doable for one or a few latches
 - But ensuring all that timing for stable inputs is problematic for large numbers of latches
- Edge-Triggered Flip-Flops
 - Better if we could set up latches that would update at a *specific moment in time*
 - Use “Edge-triggered” Flip-Flops, designed to change states based on either
 - Rising edge of clock only, or
 - Falling edge of clock only.
 - Rather than whenever clock is at 1 (or at 0)



Edge-Triggered and Leader-Follower Flip-Flops

- **Edge-Triggered**

- If inputs to flip-flop only need to be stable for a short period of time around the clock edge,
- Then we refer to the flip-flop as edge-triggered

- **Leader-Follower Edge-Triggered**


- Refers to a particular implementation
- Uses two gated latches in such a way that the flip-flop outputs only change on a clock edge

- **Alert!**

- Not all leader-follower flip-flops are edge-triggered
- Leader-follower *can* be used to make an edge-triggered flip-flop
- But is not sufficient to guarantee it is edge-triggered (details matter)




Edge-Triggered D Flip-Flop

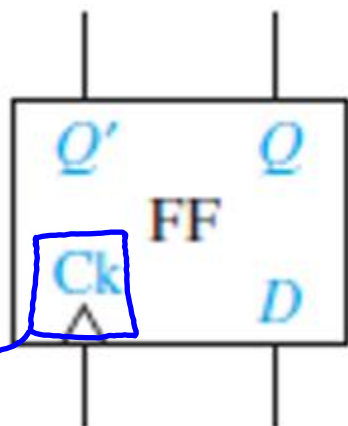

 (a) Rising-edge trigger

Arrowhead identifies clock input (even if not labeled "Ck")

Output can change in response to a 0→1 transition on the clock (*positive sloped edge*)



(b) Falling-edge trigger

Bubble on clock input flips action of clock

Output can change in response to a 1→0 transition on the clock (*negative sloped edge*)

D	Q	Q^+
0	0	0
0	1	0
1	0	1
1	1	1

(c) Truth table

Since flip-flop is edge-triggered:

- Refers to output state **after** active edge of clock hits
- Output **does not** change on change of D by itself



Edge-Triggered D Flip-Flop


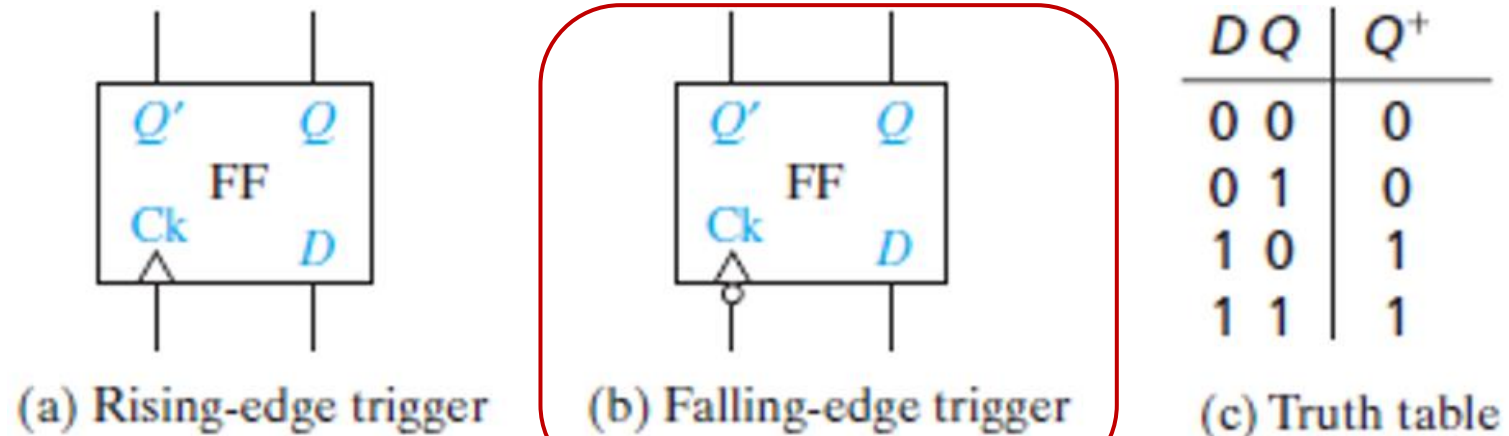


FIGURE 11-18

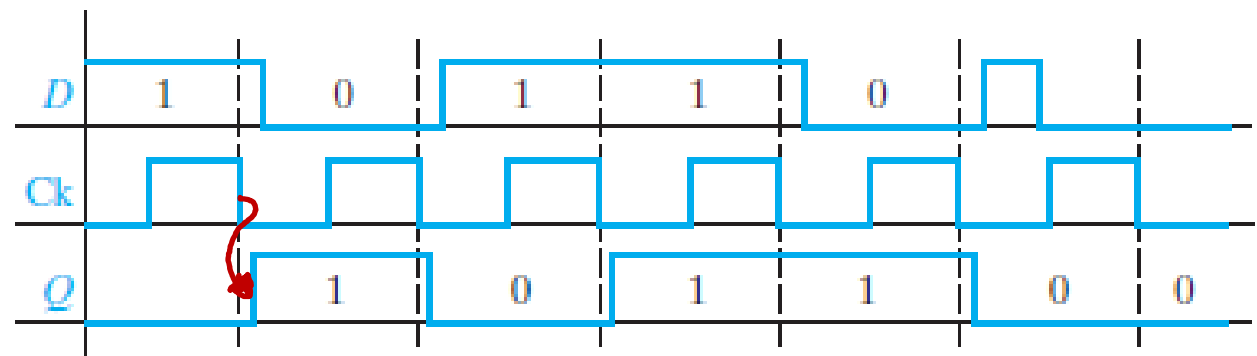Timing for
D Flip-Flop
(Falling-Edge
Trigger)






Edge-Triggered D Flip-Flop


FIGURE 11-19

D Flip-Flop (Rising-Edge Trigger)

© Cengage Learning 2014

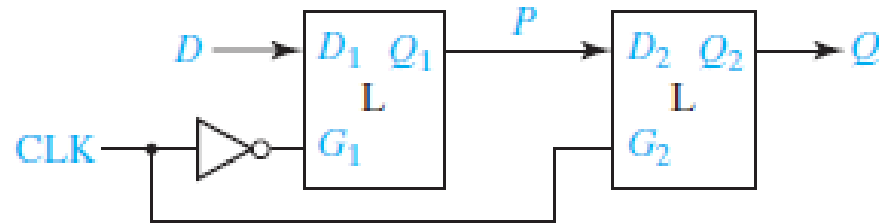

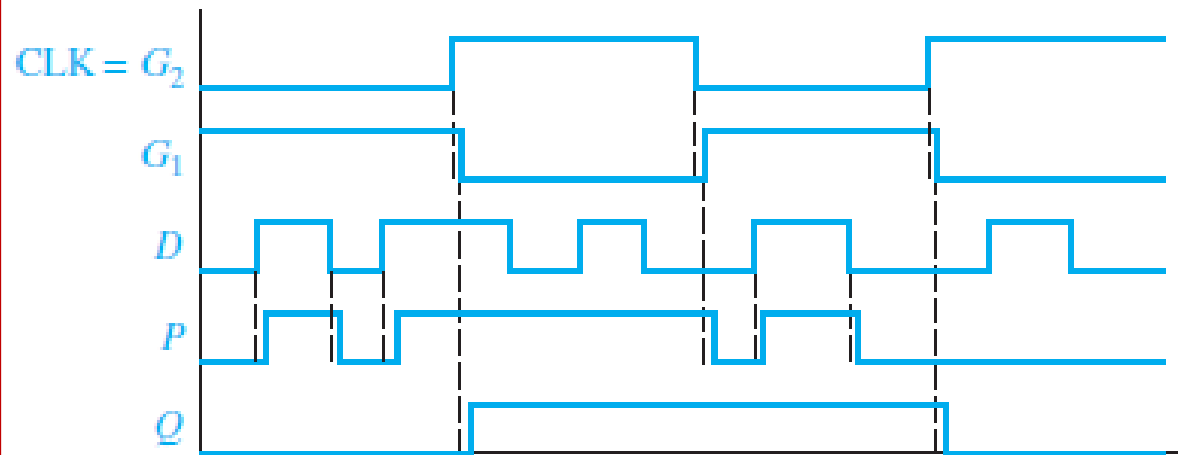(a) Construction from two gated D latches



(b) Timing analysis


The two D latches will not be transparent at the same time

- There is a small interval due to inverter gate delay when it looks like both might be transparent
- But there is also a delay through the latches during that interval
- Careful attention to internal timing needed




Edge-Triggered D Flip-Flop

- To function properly, D input must be stable for a period of time before and after the active edge of clock
 - Set up time $\equiv t_{su}$ is time D must be stable before active edge of clock
 - Allows D to propagate through first gated latch
 - Hold time $\equiv t_h$ is time D must be stable after active edge of clock
 - Needed so that current D is stored in first latch, before any change
- Shown here for rising-edge triggered case
- Usually found on data sheets

 



S-R Flip-Flop

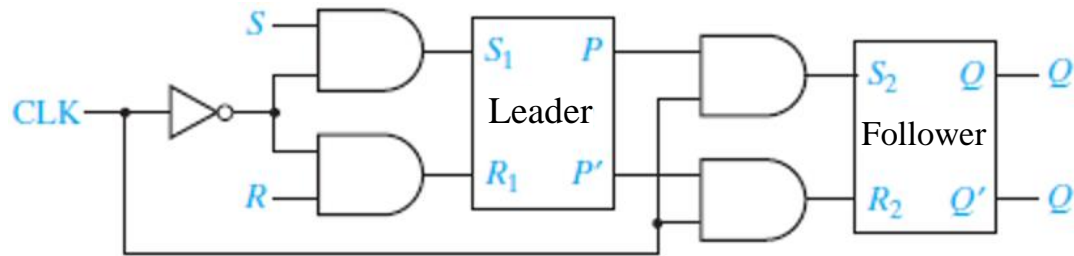


Operation Details

- Leader-Follower configuration
- $CLK = 0$ S and R set or reset outputs P and P' of Leader gated latch
- CLK changes to 1 Leader gated latch holds values of P and P' and
- $CLK = 1$ Leader gated latch continues to hold values of P and P'
- CLK changes to 0 Values of Q and Q' latched into the Follower gated latch




S-R Flip-Flop

 

Operation Details

- $CLK = 0$ S and $R \rightarrow P$, Follower holds previous Q
- $CLK \rightarrow 1$ Leader holds P , transfers it to Follower
- $CLK = 1$ Leader continues to hold P ,
 Q does not change even if S or R change
- $CLK \rightarrow 0$ Q latched into Follower, Leader processes new inputs

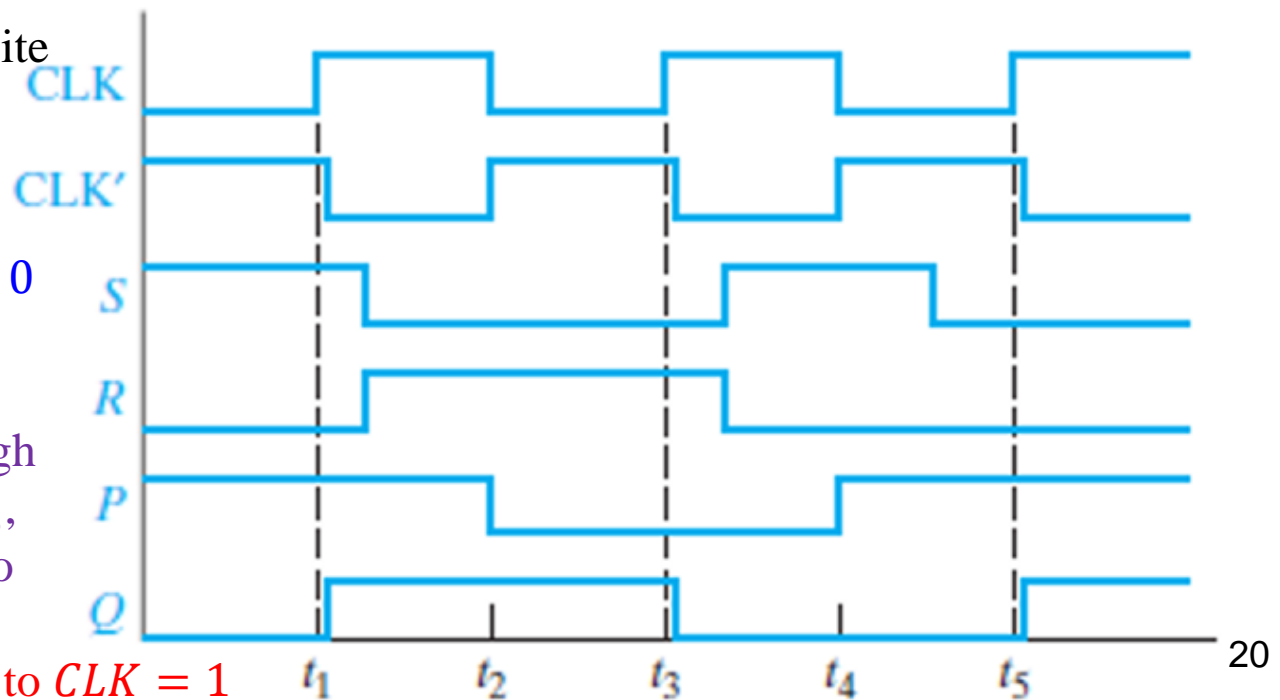
- S-R leader-follower not quite identical to edge-triggered
- Look at t_4
- P changes as leader processes new $S = 1, R = 0$
- R and S both at 0 before rising clock edge at t_5
- Since P already latched high in leader, Q goes high at t_5 , even though should be zero for $R = S = 0$
- Fix: Restrict R, S changes to $CLK = 1$





J-K Flip-Flop

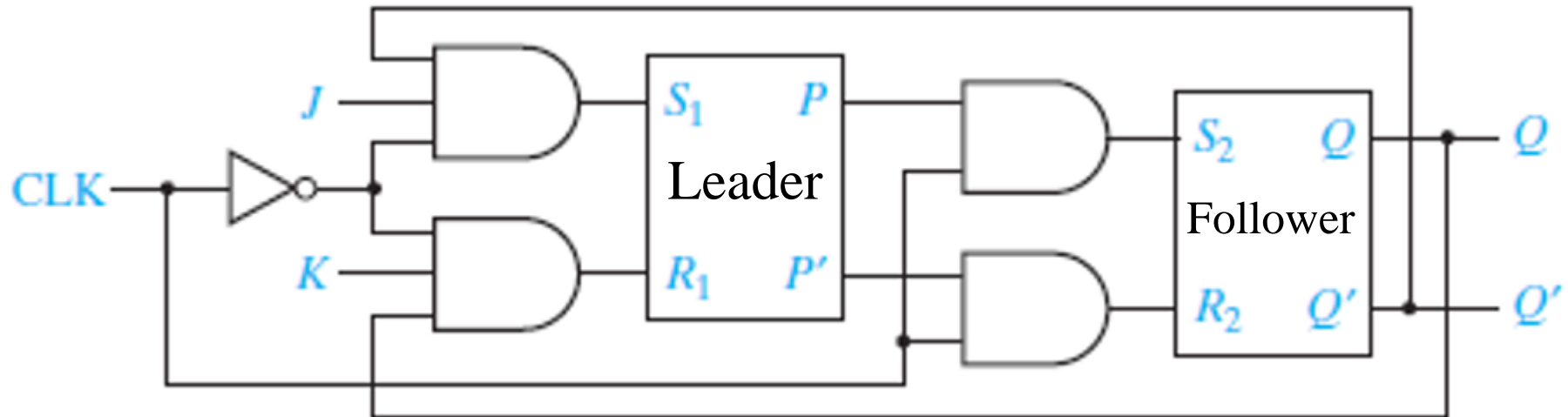- Uses present values of Q and Q' to make $[S = 1, R = 1]$ into a “Toggle” condition
- One way to implement with rising-edge CLK : Gate for follower enabled by CLK




Gate for leader, enabled by \overline{CLK} , with
of Q and Q' also fed back in cross-connected manner

Note: While $J = K = 1$ is OK, feeding present Q and Q' through ANDs ensures S_1 and R_1 not = 1 at same time

- $CLK = 0, J = 1, K = 1$ $S_1 = Q'$ and $R_1 = Q$
If $Q = 1 \rightarrow S_1 = 0, R_1 = 1 \Rightarrow$
If $Q = 0 \rightarrow S_1 = 1, R_1 = 0 \Rightarrow$
- Toggle mode:



J-K Flip-Flop

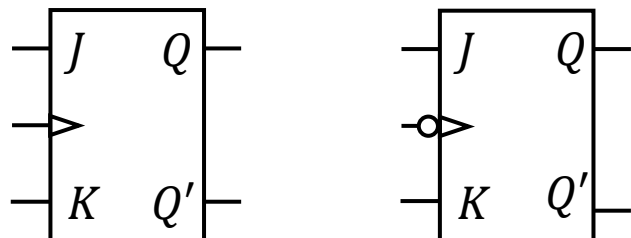

J-K Flip-Flop \Rightarrow General purpose do everything flip-flop

- $J = K = 0$ Hold
- $J = 0, K = 1$ Reset
- $J = 1, K = 0$ Set
- $J = K = 1$ Toggle


Present state			After active-edge of clock
J	K	Q	Q ⁺
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0



J-K Flip-Flop

J-K Flip-Flop \Rightarrow General purpose, do everything flip-flop

- For example, D Flip-Flop from J-K

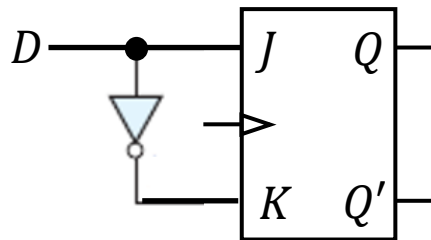



D	Q	Q^+
0	X	0
1	X	1



T Flip-Flop

J-K Flip-Flop \Rightarrow General purpose, do everything flip-flop

- For example, T Flip-Flop from J-K

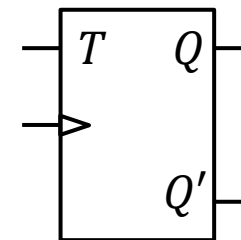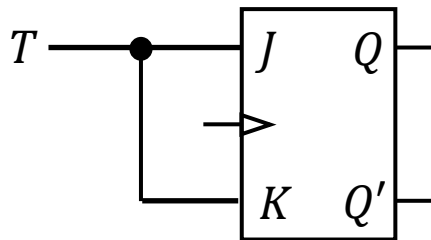

T	Q	Q^+
0	X	Q
1	X	\bar{Q}