



Lecture 1 Outline

Reminders to self:

- ☐ Turn on lecture recording to Cloud
- ☐ Turn on Zoom microphone

- Last Lecture
 - Addition with 1's complement binary encoding
 - Binary codes
 - Started Boolean algebra – through AND operation
- Today's Lecture
 - Continue Boolean algebra – resume with OR operation



Handouts and Announcements

- Announcements
 - Homework Problems 2-2
 - Posted on Carmen yesterday (1/22)
 - Due in Carmen 11:25am, Monday 1/30
 - Homework Problem 1-7, 1-8, and 2-1 reminder
 - HW 1-7, 1-8 due: 11:25am Wednesday 1/25
 - HW 2-1 due: 11:59pm Thursday 1/26
 - Read for Wednesday: Pages 97-107



Handouts and Announcements

- Announcements

- **Mini-Exam 1 – Final Reminder**

- Available 5pm Monday 1/23 through 5:00pm Tuesday 1/24
 - Due in Carmen PROMPTLY at 5:00pm on 1/24
 - Designed to be completed in ~36 min, but you may use more
 - When planning your schedule:
 - I recommend building in 10-15 min extra
 - To allow for downloading exam, signing and dating honor pledge, saving solution as pdf, and uploading to Carmen
 - I also recommend not procrastinating





Boolean Algebra – Basic Operations

Parallel Switching Circuits / Operation:

A	B	$C = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

  - Operation defined by this truth table is called
- Written algebraically as $C = A + B$
- OR operation also referred to as logical (or Boolean) addition



Note: the plus sign is often (actually usually) not shown. Shape identifies function.
(IEEE Std 91/91a-1991 does not include the plus)




Boolean Operations and Truth Tables


Examples: Boolean Expressions & Corresponding Diagrams

- Expressions

- $AB' + C$

 

- $[A(C + D)]' + BE$

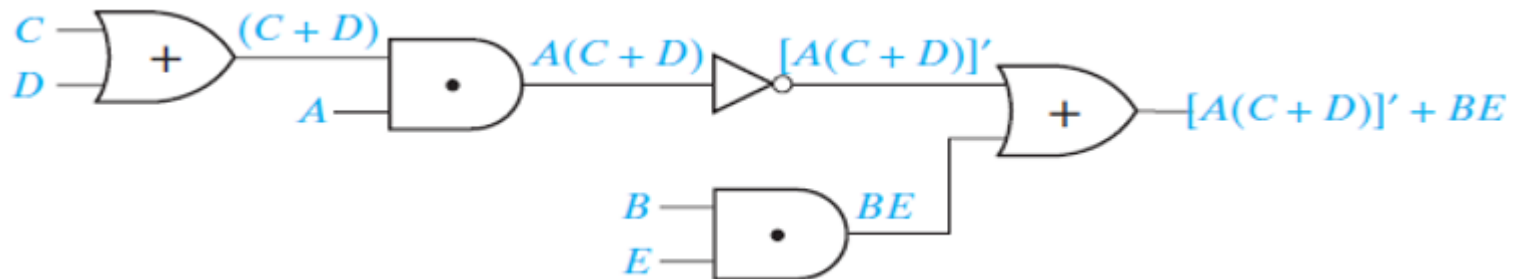

- Order of operations:

- 1.
- 2.
- 3.
- 4.

For the second expression,
if $A = B = D = 1$ and $C = E = 0$ then
 $[A(C + D)]' + BE =$



Boolean Operations and Truth Tables

- Expression** $AB' + C$



TABLE 2-1

A B C	B'	AB'	AB' + C	A + C	B' + C	(A + C)(B' + C)
0 0 0	1	0	0	0	1	0
0 0 1	1	0	1	1	1	1
0 1 0	0	0	0	0	0	0
0 1 1	0	0	1	1	1	1
1 0 0	1	1	1	1	1	1
1 0 1	1	1	1	1	1	1
1 1 0	0	0	0	1	0	0
1 1 1	0	0	1	1	1	1

© Cengage Learning 2014

Discuss
order of
filling input
columns

Equal Boolean Expressions:

Two Boolean expressions are said to be equal if they have the same value for every possible combination of the variables



Boolean Algebra – Basic Operations

A bit more about Complementation / Inversion:

- Also known as the **operation**
- Our textbook uses the prime mark to indicate inversion
 - $X' = 1$ if $X = 0$, and
 - $X' = 0$ if $X = 1$
- It is very common to see an overbar mark used for inversion
 - $\bar{X} = 1$ if $X = 0$, and
 - $\bar{X} = 0$ if $X = 1$
- Looking at the same two expressions from a few slides ago:
 - $AB' + C \Leftrightarrow A\bar{B} + C$
 - $[A(C + D)]' + BE \Leftrightarrow \overline{A(C + D)} + BE$



Crossovers vs. Connections

Wires in circuit schematics: 1) Sometime branch. 2) Sometimes they cross without connecting

	Connected	Not Connected
Preferred		
Accepted		
But see sometimes		
Archaic		



Basic Theorems

Single Variable Basic Theorems:

$$X + 0 = X$$

$$X \cdot 1 = X$$

$$X + 1 = 1$$

$$X \cdot 0 = 0$$

denoting an element of a set which is unchanged in value when multiplied or otherwise operated on by itself

$$X + X = X$$

$$X \cdot X = X$$

$$(X')' = X$$

$$X + X' = 1$$


$$X \cdot X' = 0$$



Boolean Algebra – Literals

Each appearance of a *variable* or its *complement* is called a “*Literal*”

 - $C\bar{D} + ABD$
- Four variables
- Five literals





Boolean Algebra – Other Logic Gates

NAND: “NOT AND” ($\text{AND} \rightarrow \text{NOT}$)


- $Z = \overline{AB}$ (A NAND B)

A	B	$Z = \overline{AB}$
0	0	1
0	1	1
1	0	1
1	1	0

$$F = \overline{ABC}$$


- At transistor level

- Require fewer components
- Faster

 

(a) Three-input NAND gate

(b) NAND gate equivalent

 

(c) n -input NAND gate




Boolean Algebra – Other Logic Gates

NOR: “NOT OR” (OR \rightarrow NOT)

- $Z = \overline{A + B}$ (A NOR B)


- $F = \overline{A + B + C}$

A	B	$Z = \overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

 

(a) Three-input NOR gate

(b) NOR gate equivalent

 


(c) n -input NOR gate



Boolean Algebra – Other Logic Gates

XOR: “eXclusive OR”

 - Operator symbol is \oplus
- Logic gate symbol for XOR $\Rightarrow X \oplus Y$



- $Z = A \oplus B \Rightarrow Z = 1$ if $A = 1$ or $B = 1$, but not if both = 1
- Truth table

A	B	$Z = X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0


- $Z = A \oplus B = A\bar{B} + \bar{A}B$



Boolean Algebra – Other Logic Gates

XNOR: “eXclusive NOR”

 - Complement of XOR $\Rightarrow \overline{X \oplus Y}$
- Logic gate symbol for XNOR $\Rightarrow \overline{X \oplus Y}$



- $Z = \overline{A \oplus B} \Rightarrow Z = 1 \text{ iff } A = B \therefore \text{also known as } \textit{Equivalence}$
- Truth table

A	B	$Z = \overline{A \oplus B}$
0	0	1
0	1	0
1	0	0
1	1	1

- $Z = \overline{A \oplus B} = AB + \bar{A}\bar{B}$



Boolean Algebra – Basic Laws

Commutative & Associative Laws:

- Many basic laws of ordinary algebra also apply to Boolean algebra
- Commutative:
 - Order variables written does not affect result of AND & OR operations
 - $XY = YX$
 - $X + Y = Y + X$
- Associative:
 - Result of AND & OR operations independent of which variables we associate together first
 - $(XY)Z = X(YZ) = XYZ$
 - $(X + Y) + Z = X + (Y + Z) = X + Y + Z$
 - XOR:
 - $A \oplus B \oplus C = (A \oplus B) \oplus C = A \oplus (B \oplus C)$
 - Output = 1 for odd # of 1s



Boolean Algebra – Basic Laws

Develop $A \oplus B \oplus C = (A \oplus B) \oplus C = A \oplus (B \oplus C)$ truth table

A	B	C	$A \oplus B$	$(A \oplus B) \oplus C$	$B \oplus C$	$A \oplus (B \oplus C)$
0	0	0	0	0	0	0
0	0	1	0	1	1	1
0	1	0	1	1	1	1
0	1	1	1	0	0	0
1	0	0	1	1	0	1
1	0	1	1	0	1	0
1	1	0	0	0	1	0
1	1	1	0	1	0	1



Boolean Algebra – Basic Laws

Distributive Law of Boolean Algebra:

- Ordinary Distributive Law:
 - $X(Y + Z) = XY + XZ$
- Second Distributive Law (not valid for ordinary algebra)
 - $X + YZ = (X + Y)(X + Z)$
 - This is the “ ” of the first distributive law
- “ ” concept satisfied in Boolean algebra
 - Given a Boolean algebra expression
 - Interchange all constants 1 and 0
 - Interchange AND and OR operations
 - Variables and complements unchanged
- A more direct algebraic proof of the second distributive law is shown on page 45 of the textbook



Boolean Algebra – DeMorgan's Laws

Duality Examples:

- Interchange all constants 1 and 0
- Interchange AND and OR operations
- Variables and complements unchanged
- Examples:
 - $F = X + X' = 1 \Rightarrow \text{DUAL}(F) \rightarrow XX' = 0$
 - $G = X + X = X \Rightarrow \text{DUAL}(G) \rightarrow XX = X$
 - $H = X + 0 = X \Rightarrow \text{DUAL}(H) \rightarrow X \cdot 1 = X$
 - $K = X + 1 = 1 \Rightarrow \text{DUAL}(K) \rightarrow X \cdot 0 = 0$
 - $L = X + Y = Y + X \Rightarrow \text{DUAL}(L) \rightarrow XY = YX$
 - OR & AND forms of Associative Law also related by duality
 - Distributive Laws by duality shown on previous slide



Boolean Algebra – DeMorgan's Law

DeMorgan's Law:

- The NOT operation isn't distributable by normal means
- Special rule \Rightarrow DeMorgan's Law to find the complement
 1. Take the DUAL
 2. Complement each literal
- First form of DeMorgan's Law: $\overline{X + Y} = \bar{X}\bar{Y}$
- Second form of DeMorgan's Law: $\overline{XY} = \bar{X} + \bar{Y}$
- Note: Two forms are duals of each other
- Truth table proof of DeMorgan's Laws:

X	Y	X'	Y'	$X + Y$	$(X + Y)'$	$X'Y'$	XY	$(XY)'$	$X' + Y'$
0	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	0	0	1	1
1	0	0	1	1	0	0	0	1	1
1	1	0	0	1	0	0	1	0	0



Boolean Algebra – DeMorgan's Law

DeMorgan's Examples:

$$F = (A + \bar{B})(C + D)$$

Find \bar{F}

$$\bar{G} = A\bar{C}D + \bar{B}C$$

Find G



Functional Completeness:

- A set of logic operations is said to be functionally complete if any Boolean function can be expressed in terms of this set of operations
- The set {NOT, AND, OR} is functionally complete
- Similarly, the set {NOT, NAND, NOR} is functionally complete
- But OR can be realized using NOT & AND, etc.
- Can implement any Boolean expression with just
 - {NOT, AND}, or
 - {NOT, OR}, or
 - {NOT, NAND}, or
 - {NOT, NOR}
- But a NAND gate (or NOR gate) with inputs tied together is a NOT
- Any Boolean expression can be implemented with just NAND gates (or just NOR gates)



Boolean Algebra – Simplification

- Boolean algebra laws and theorems can be used to algebraically simplify expressions into forms that are more readily implemented with logic gates
- Theorems and algebraic techniques useful for simplification and proving validity are covered in greater depth in some sections of Chapters 2 and 3
- But we are going to learn a graphical technique for reducing Boolean Expressions
 - Karnaugh Maps
 - Often abbreviated K-Maps