



# Lecture Outline

---

## Reminders to self:

- ☐ Turn on lecture recording to Cloud
- ☐ Turn on Zoom microphone

## • Last Lecture

### – Registers

- Basic register, data transfer, accumulator register w/adder
- Started shift registers

## • Today's Lecture

### – Finish Shift Registers

### – Start Counters

- Three-bit synchronous binary counter
- Brief look at binary ripple counter (not synchronous)
- Formal design procedures



# Handouts and Announcements

---

- Announcements

- Homework Problem 12-1

- Posted on Carmen this morning
- Due: 11:25am Wednesday 3/8
- Data Sheet for CD40194B in Data Sheet Module on Carmen

- Homework Reminder

- HW 11-3 posted on Carmen 2/25
- Due: 11:59pm Thursday 3/2

- Read for Friday: pages 395-402

- Mini-Exam 3 regrade in progress

- Problem 2 & 3 rubric interpretation by GTA
- Inconsistencies and errors I observed during requested regrades



# Handouts and Announcements

---

- Announcements

- Mini-Exam 4 Reminder

- Available 5pm Monday 3/6 through 5:00pm Tuesday 3/7
- Due in Carmen PROMPTLY at 5:00pm on 3/7
- Designed to be completed in ~36 min, but you may use more
- When planning your schedule:
  - I recommend building in 10-15 min extra
  - To allow for downloading exam, signing and dating honor pledge, saving solution as pdf, and uploading to Carmen
- I also recommend not procrastinating

- Exam review topics available on Carmen



- Sample Mini-Exams 5 and 6 from Au20 also available


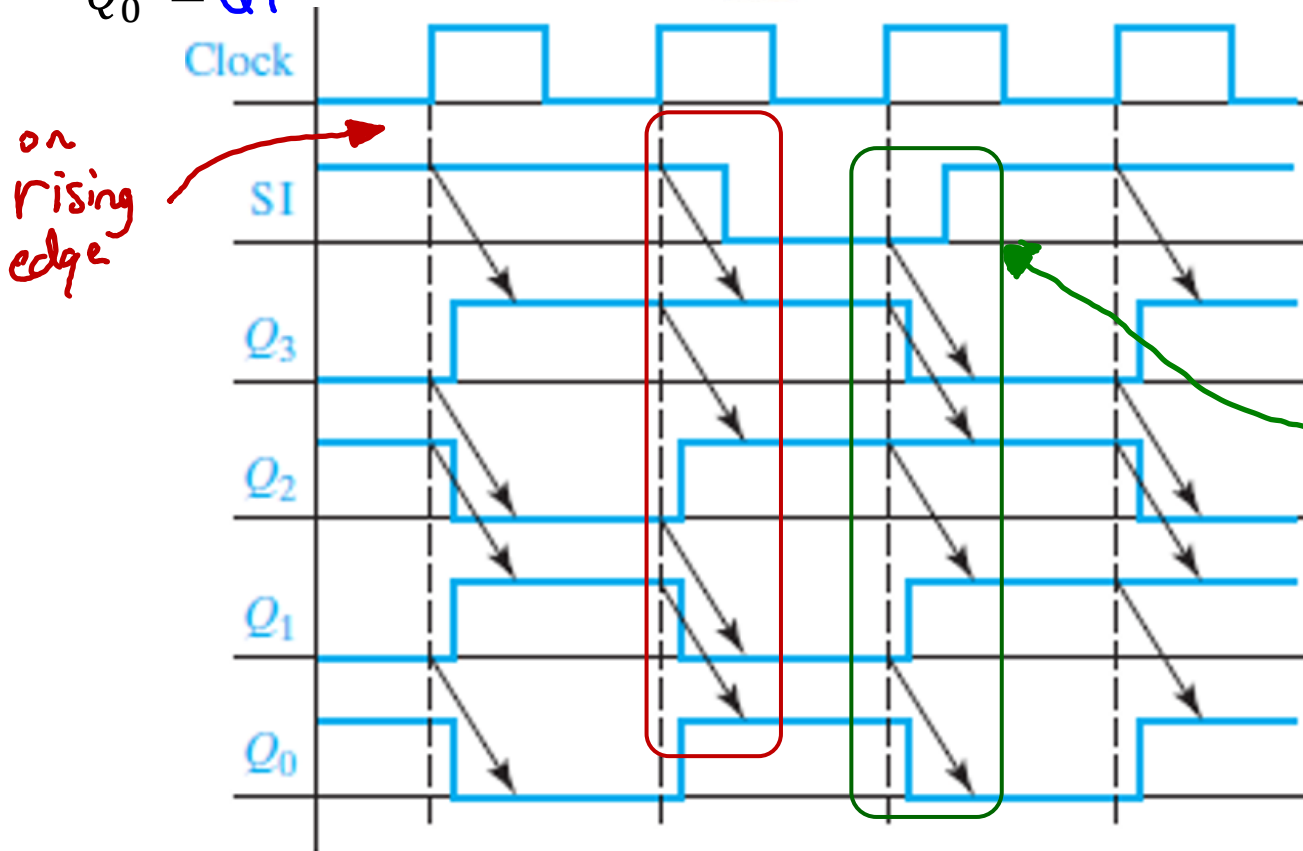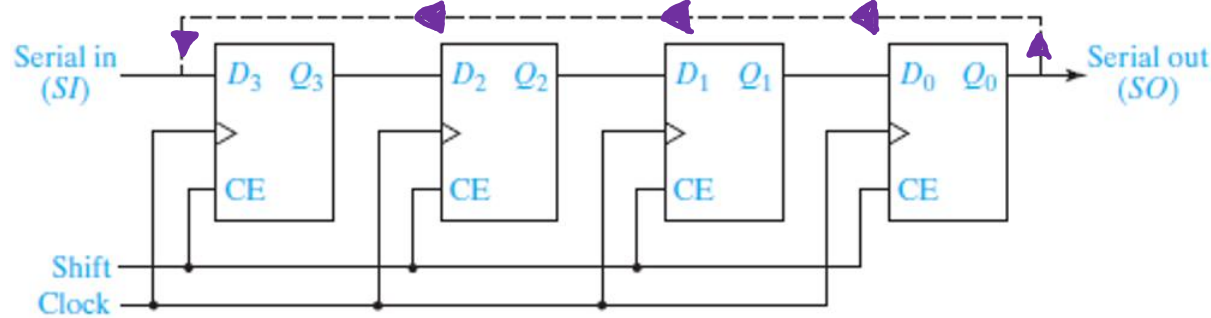
## Shift Registers

*Shift = 1 @ 1st Clock ↑*


- $Q_3^+ = SI$
  - $Q_2^+ = Q_3$
  - $Q_1^+ = Q_2$
  - $Q_0^+ = Q_1$
- 0101 → 1010*



- Pattern repeats at 2<sup>nd</sup> Clock ↑  
*1010 → 1101*
- Note that  $SI = 0$  before 3<sup>rd</sup> Clock ↑  
*1101 → 0110*
- Back to  $SI = 1$  before 4<sup>th</sup> Clock ↑  
*0110 → 1011*
- If  $Shift = 0$   
*(Hold) no change*



# Shift Registers

 

## Serial In / Serial Out Registers:

- **Serial in means data is**

- Shifted into *1st flip flop* one bit at a time, and
- Flip-flops cannot be loaded *in parallel*

- **Serial out means data**

- Can only be read out of the *last flip flop*, and
- Outputs from other flip-flops not connected outside register



# Shift Registers

## Shift Registers with Parallel In / Parallel Out exist

### Block diagram

- Used for serial input on  $CLK \downarrow$  when  $Sh = 1$  ( $L = 1$  or  $0$ )
- All bits shifted right

$SI$  (Serial In)


$Sh$  (Shift Enable)

$L$  (Load Enable)

$CLK$

Control inputs

 Parallel Output  
 $Q_3$   $Q_2$   $Q_1$   $Q_0$



$D_3$   $D_2$   $D_1$   $D_0$   
Parallel Input

- All four bits available for parallel output
- For serial output, simply use  $Q_0$

$SO$  (Serial Out)

HOLD for  $Sh=0$  and  $L=0$


- All four bits can be loaded at one time
- On  $CLK \downarrow$  when  $Sh = 0, L = 1$



# Shift Registers
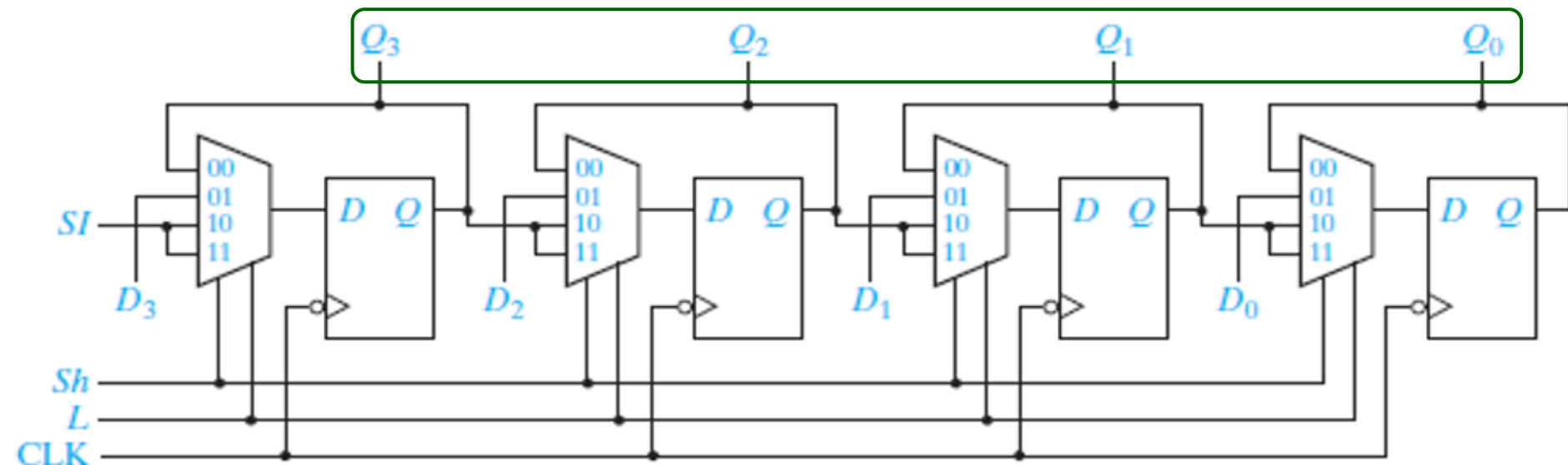
## Implementation with D Flip-Flops and MUXs

- HOLD for  $Sh = 0, L = 0$
- All four  $Q_i$  fed back to  $D_i$  inputs through MUX
- All four bits available for parallel output
- For serial output, simply use  $Q_0$




- Used for serial input on  $CLK \downarrow$  when  $Sh = 1$  ( $L = 1$  or  $0$ )
- All bits shifted right

- All four bits can be loaded at one time
- On  $CLK \downarrow$  when  $Sh = 0, L = 1$


 
# Shift Registers



- Typical application is conversion of parallel data to a serial bit stream
- Timing diagram for this assumes “cleared” 0000 initial state,  $SI = 0$
- Parallel load of 1011 at 1<sup>st</sup>  $CLK \downarrow$





Shift Registers  $\Rightarrow$  Counters

 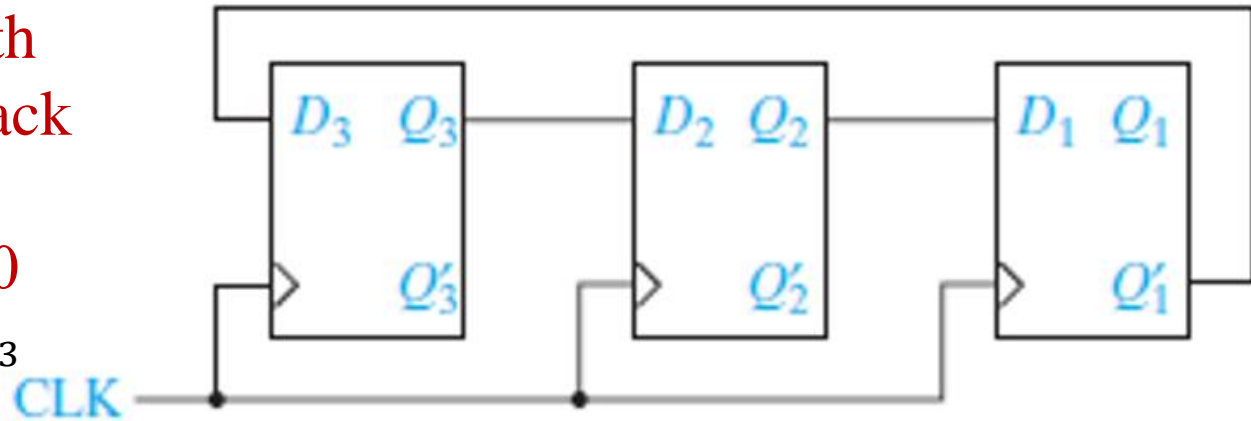- 3-bit shift register with inverted output fed back to input
- Starting “cleared” 000
  - 1 fed back from  $Q'_1$  to  $D_3$
  - Progress around “transition graph” with each  $CLK \uparrow$




- Note that only six of the eight 3-bit combinations appear on this transition graph
- *010 and 101 are missing*
- If register were loaded with *010* to start
  - Next state would be *101*
  - And then back to *010*
- This is a “secondary loop” transition graph for this *counter*
- Counter. A circuit that cycles through a fixed sequence of states







# Shift Registers $\Rightarrow$ Counters


 


- The combination of values of  $Q_3Q_2Q_1$  in each of the circles represent a “state” of the counter
- Later this semester you will learn about “state machines”
  - At that time we will introduce two types of “state graphs”
  - State graphs contain more information

  
- When asked for a “state graph”, do NOT draw a “transition graph”
- When asked for the “transition graph” of a counter, do not draw a “state graph”



State graphs

  Shift Registers  $\Rightarrow$  Counters

 - A shift register with inverted feedback is called a “Johnson counter” or “*twisted ring counter*”
- If feedback is not inverted it is simply a “*ring counter*”





## Counters

## 3-Bit Binary Counter:

Transition table

Counting  $0_{10}$  through  $7_{10}$  in binary

Present State			Next State		
C	B	A	$C^+$	$B^+$	$A^+$
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Fill in Next State from transition graph

To implement as a Synchronous counter, look for patterns of toggles by bit:

- A *always* toggles on  $Clk \uparrow$  (or  $Clk \downarrow$  if low-true clock)
- B toggles on  $Clk \uparrow$  when  $A=1$
- C toggles when *both*  $B=1$  and  $A=1$  on  $Clk \uparrow$



## 3-Bit Binary Counter: Transition Table


- $A$  always toggles on  $Clk \uparrow$
- $B$  toggles on  $Clk \uparrow$  when  $A = 1$
- $C$  toggles when both  $B = 1$  and  $A = 1$

Present State			Next State			Flip-Flop Inputs		
$C$	$B$	$A$	$C^+$	$B^+$	$A^+$	$T_C$	$T_B$	$T_A$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1


 
## 3-Bit Binary Counter: Circuit

- $A$  always toggles on  $Clk \uparrow$
- $B$  toggles on  $Clk \uparrow$  when  $A = 1$
- $C$  toggles when both  $B = 1$  and  $A = 1$






# Counters

## Synchronous and Ripple Counters:

- For *synchronous* counters, operation of flip-flops synchronized by common clock pulse: when several flip-flops must change state, state changes occur simultaneously
- Ripple* counters are those in which the state change of one flip-flop triggers another flip-flop
- Reviewing table two slides ago:
  - A always toggles
  - B toggles when A  $1 \rightarrow 0$  or  $Q'_A$   $0 \rightarrow 1$ . Use later for  $\uparrow$  clock of B
  - C toggles when B  $1 \rightarrow 0$  or  $Q'_B$   $0 \rightarrow 1$ . Use later for  $\uparrow$  clock of C

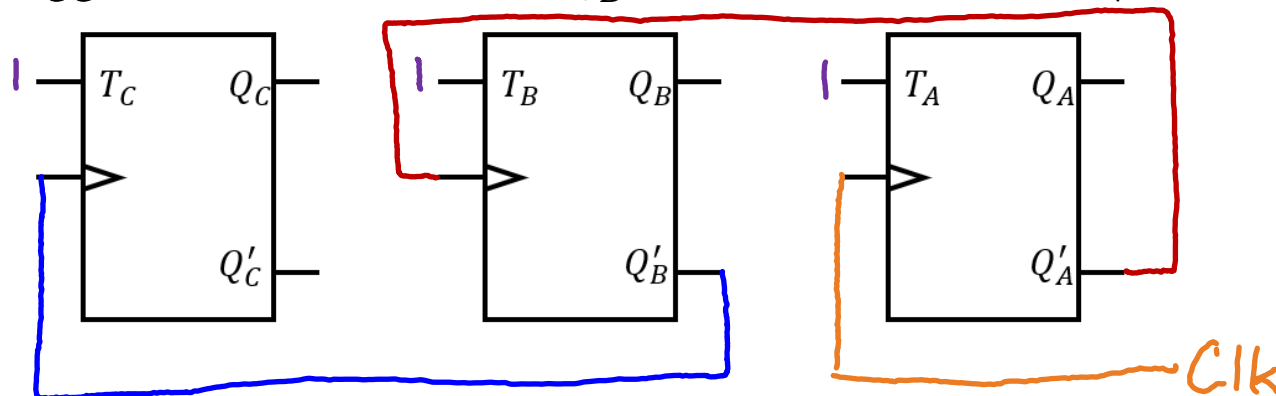



ECE2060

# Counters

- Patterns in state table for T-implementation of the 3-bit binary counter were simple enough to recognize that we did not need K-maps
- For completeness, here are the K-maps

K-map for  $T_A$ . The map shows a 2x2 grid of 1s for all combinations of BA (00, 01, 11, 10) and C (0, 1). A blue circle highlights the entire grid, with a label  $T_A = 1$  pointing to it.

$BA \backslash C$	0	1
00	1	1
01	1	1
11	1	1
10	1	1

K-map for  $T_B$ . The map shows 1s for BA = 01 and 11, regardless of C. A blue circle highlights these two rows, with a label  $T_B = A = Q_A$  pointing to it.

$BA \backslash C$	0	1
00	0	0
01	1	1
11	1	1
10	0	0

K-map for  $T_C$ . The map shows 1s for BA = 11, regardless of C. A blue circle highlights this row, with a label  $T_C = BA = Q_B Q_A$  pointing to it.

$BA \backslash C$	0	1
00	0	0
01	0	0
11	1	1
10	0	0

Present State			Next State			Flip-Flop Inputs		
C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>	T <sub>C</sub>	T <sub>B</sub>	T <sub>A</sub>
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1





## Counters

- Implementation of the 3-bit binary counter using D flip-flops:  $Q^+ = D$
- $D_A = A^+$ ;  $D_B = B^+$ ;  $D_C = C^+$
- Inspecting the transition table to fill the K-maps

$BA$	$C$	
	0	1
00	1	1
01	0	0
11	0	0
10	1	1

$BA$	$C$	
	0	1
00	0	0
01	1	1
11	0	0
10	1	1

$$D_B = AB' + A'B \\ = A \oplus B$$

Present State			Next State		
$C$	$B$	$A$	$C^+$	$B^+$	$A^+$
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

$$D_C = A'C + B'C + ABC' \\ = C(A' + B') + ABC' \\ = C(AB)' + C'(AB) \\ = C \oplus AB$$


$BA$	$C$	
	0	1
00	0	1
01	0	1
11	1	0
10	0	1


 
# Counters

- Implementation of the 3-bit binary counter using D flip-flops

- $D_C = C \oplus AB;$        $D_B = A \oplus B;$        $D_A = A' =$



- This figure from textbook uses same XOR input structure to  $D_A$  as for  $D_B$  and  $D_C$  to invert A

- 
- 
- See last paragraph of Section 11.7 for conversion of D flip-flop to T flip-flop using XOR



## 4-bit BCD counter using T flip-flops

Remember the requirement for counters with T flip-flops from last lecture:

$$T_A(D, C, B, A) =$$

$$T_B(D, C, B, A) =$$

$$T_C(D, C, B, A) =$$

$$T_D(D, C, B, A) =$$

$D$	$C$	$B$	$A$	$D^+$	$C^+$	$B^+$	$A^+$	$T_D$	$T_C$	$T_B$	$T_A$
0	0	0	0	0	0	0	1	0	0	0	
0	0	0	1	0	0	1	0	0	0		
0	0	1	0	0	0	1	1	0	0	0	
0	0	1	1	0	1	0	0	0			
0	1	0	0	0	1	0	1	0	0	0	
0	1	0	1	0	1	1	0	0	0		
0	1	1	0	0	1	1	1	0	0	0	
0	1	1	1	1	0	0	0				
1	0	0	0	1	0	0	1	0	0	0	
1	0	0	1	0	0	0	0		0	0	
1	0	1	0	-	-	-	-	X	X	X	X
1	0	1	1	-	-	-	-	X	X	X	X
1	1	0	0	-	-	-	-	X	X	X	X
1	1	0	1	-	-	-	-	X	X	X	X
1	1	1	0	-	-	-	-	X	X	X	X
1	1	1	1	-	-	-	-	X	X	X	X



---

---

4-bit BCD counter using T flip-flops

$$T_A(D, C, B, A) = 1$$

$$T_B(D, C, B, A) = \sum m(1, 3, 5, 7) + \sum d(10, 11, 12, 13, 14, 15)$$

$$T_C(D, C, B, A) = \sum m(3, 7) + \sum d(10, 11, 12, 13, 14, 15)$$

$$T_D(D, C, B, A) = \sum m(7, 9) + \sum d(10, 11, 12, 13, 14, 15)$$

$T_D$

$DC$ $BA$	00	01	11	10
00				
01				
11				
10				



# Counters

## 4-bit BCD counter using T flip-flops

$$T_A(D, C, B, A) = 1$$

$$T_B(D, C, B, A) = \sum m(1, 3, 5, 7) + \sum d(10, 11, 12, 13, 14, 15)$$

$$T_C(D, C, B, A) = \sum m(3, 7) + \sum d(10, 11, 12, 13, 14, 15)$$

$$T_D(D, C, B, A) = \sum m(7, 9) + \sum d(10, 11, 12, 13, 14, 15) = AD + ABC$$

The design of  
the rest of this  
BCD counter  
is left as  
homework

