


Spring 2024 – ECE 3020

Homework 2


Due: 01/24/2024

- For the amplifiers shown below, assume $g_m = 4\text{mA/V}$. Calculate
 - The input resistance, R_{in}
 - Thevenin equivalent source voltage
 - Overall voltage gain (v_o/v_s)
 - Overall current gain (i_o/i_s)

I.

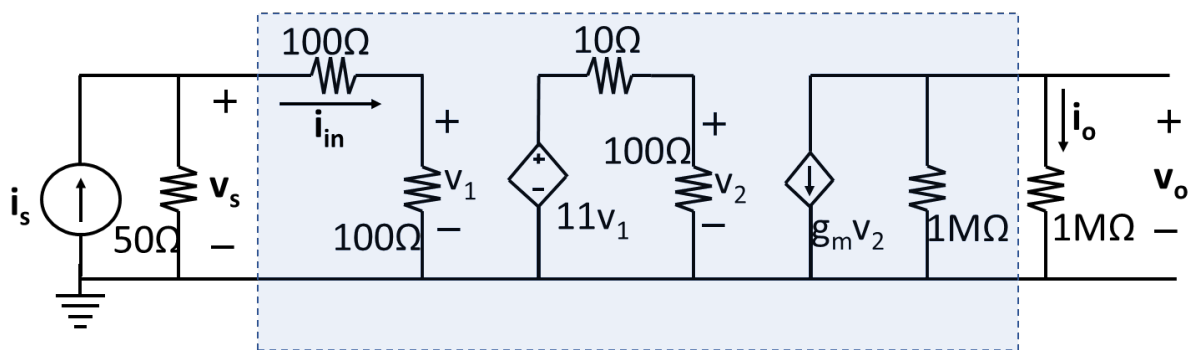

II.

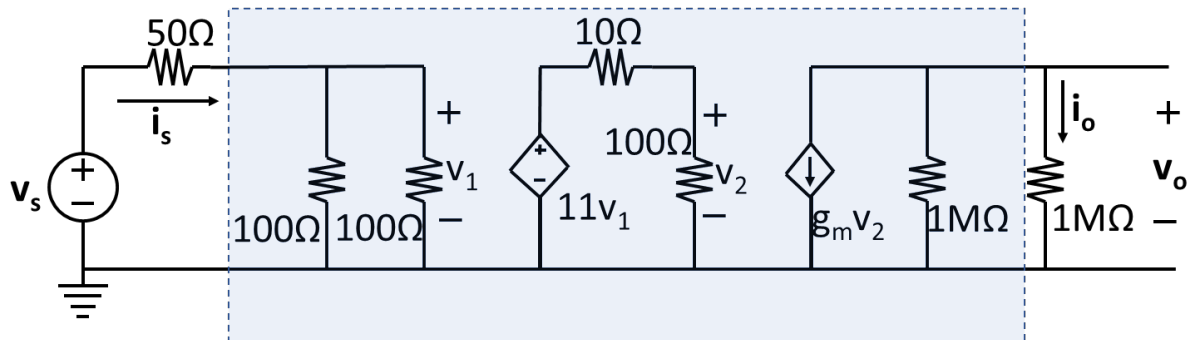

- (P1.46) A buffer amplifier with a gain of 1V/V has an input resistance of $1\text{M}\Omega$ and an output resistance of 20Ω . It is connected between a 1-V , $200\text{k}\Omega$ source and a 100Ω load. What load voltage results? What are the corresponding voltage current and power gains (in dB)?
- (P1.47) Consider the cascade amplifier in Exercise #12 (Example 1.3 from the Book). Find the overall v_L/v_s obtained when the 1st and 2nd stages are interchanged. Compare this value with the result in Exercise #12 and comment.

4. (P1.52) A voltage amplifier with an input resistance of $20\text{k}\Omega$, an output resistance of 100Ω , and a gain of 1000V/V is connected between a $100\text{-k}\Omega$ source with an open-circuit voltage of 10mV and a $100\text{-}\Omega$ load. For this situation:
- What output voltage results?
 - What is the voltage gain from source to load?
 - What is the voltage gain from the amplifier input to the load?
 - If the output voltage across the load is twice that needed and there are signs of internal amplifier overload, suggest the location and value of a single resistor that would produce the desired output. Choose an arrangement that would cause minimum disruption to an operating circuit. (*Hint: Use parallel rather than series connections.*)