



What is characteristic of an open and a closed loop circuit?

Open

+ ○ A

$i = 0$

- ○ B

$$V = V_A - V_B$$

Short

+ ○ A

- ○ B

$V = 0$

$A = B$

i is not 0





THE OHIO STATE UNIVERSITY

COLLEGE OF ENGINEERING

Capacitors and Inductors



- Learning Objectives:
 - Define the i - v relationship for capacitors and inductors.
 - Determine voltage and current across capacitors and inductors under DC and steady state conditions





- Stores energy in electric field between two conducting plates.
- For DC, capacitor looks like open circuit.


i-v characteristic


$V = IR$

$i_c(t) = C \cdot \frac{dV_c(t)}{dt}$

$V_c(t) = \frac{1}{C} \int i_c(t) dt$

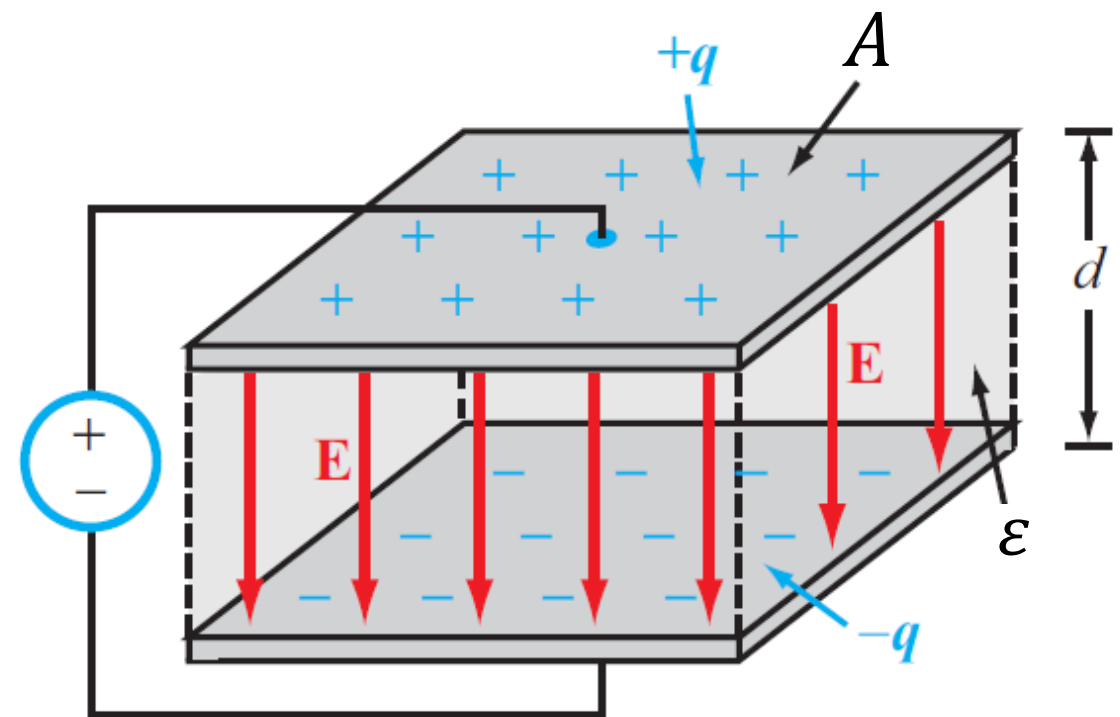$C = \text{capacitance} = \text{Farads [F]}$






$C = 10 \mu F$




Calculating equivalent capacitance:

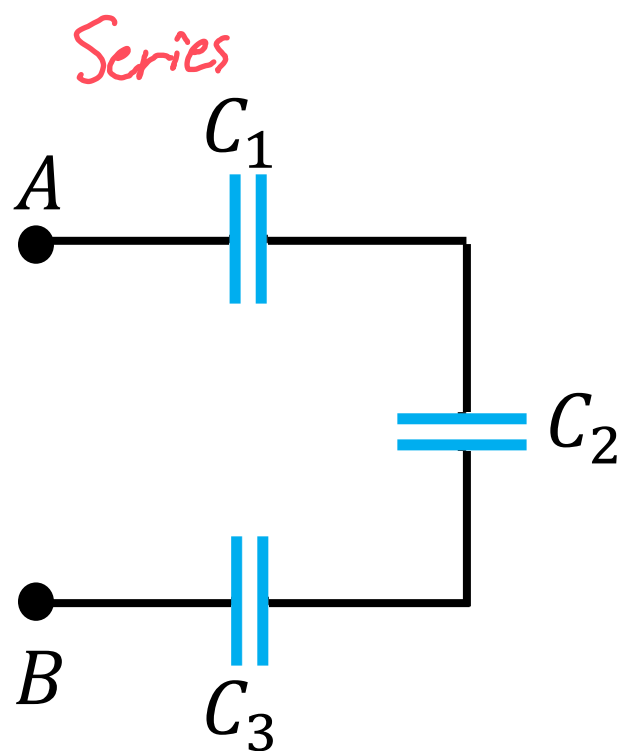- Capacitors in series combine like resistors in parallel.
- Capacitors in parallel combine like resistors in series.



Same Current
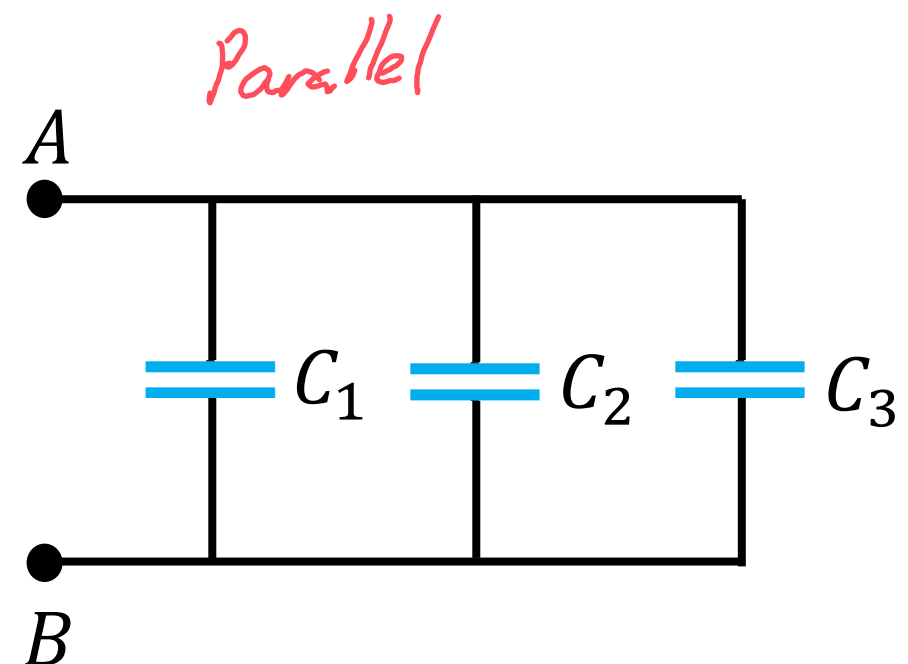
$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$



Same voltage

$$C_{eq} = C_1 + C_2 + C_3$$





Capacitor



$$i_C(t) = C \frac{dv_C(t)}{dt}$$

$$v_C(t) = \frac{1}{C} \int_0^t i_C(\tau) d\tau + v_0$$

In a DC system and steady state:

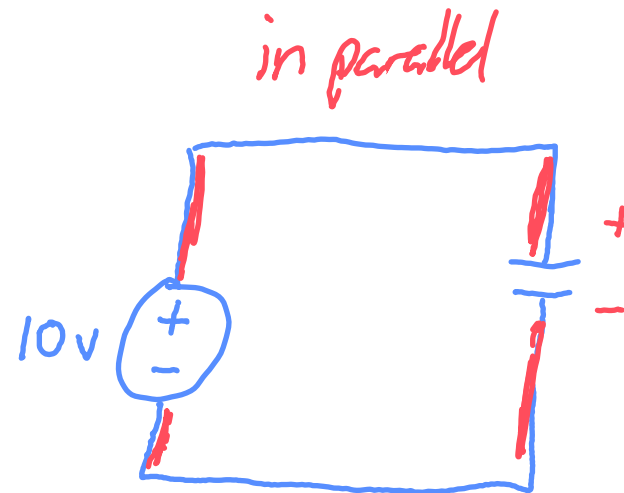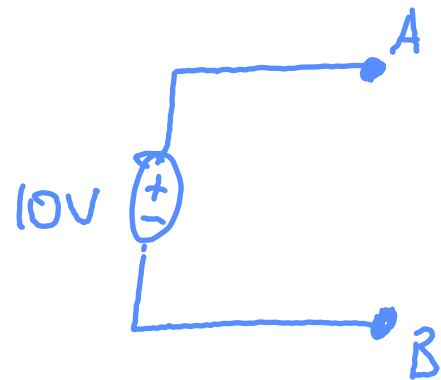

$$V_C = 10V$$

$$i_C = C \cdot \frac{d10}{dt} = 0$$

can be modeled as an open circuit (only on DC)




- Stores energy in magnetic field of a conducting coil.
- Inductor in a DC circuit equivalent to a short circuit



i-v characteristic
$$V_L(t) = L \cdot \frac{di_L(t)}{dt}$$

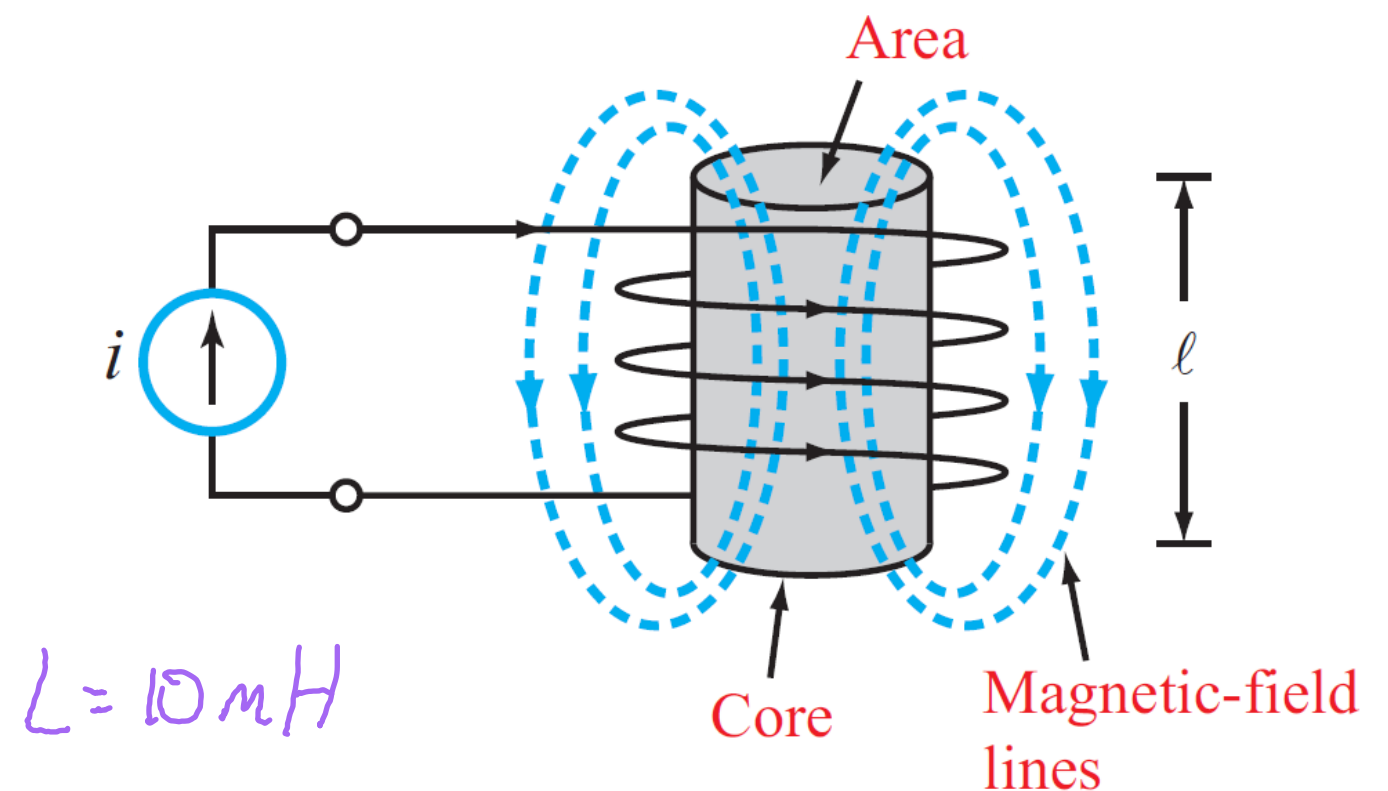
$$L = \text{inductance} = \text{Henrys [H]}$$






Calculating equivalent inductance

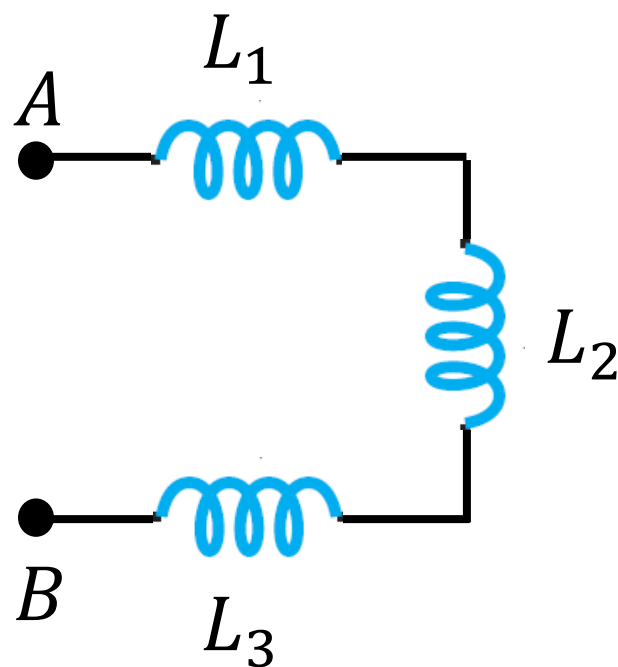- Inductors in series combine like resistors in series.
- Inductors in parallel combine like resistors in parallel.



Same current

$$L_{eq} = L_1 + L_2 + L_3$$

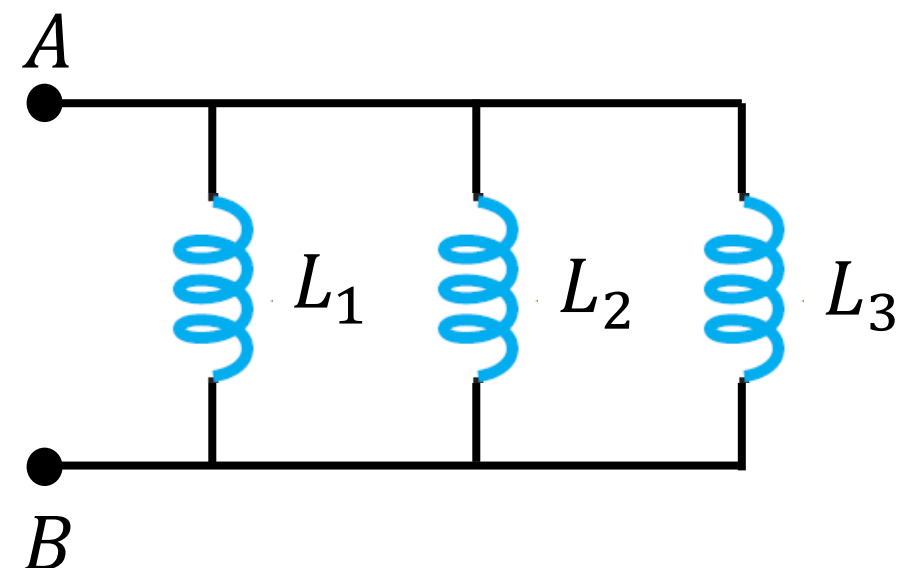

Same voltage

$$L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}}$$




Inductor

$$v_L(t) = L \frac{di_L(t)}{dt}$$

$$i_L(t) = \frac{1}{L} \int_0^t v_L(\tau) d\tau + i_0$$


In a DC system and steady state:

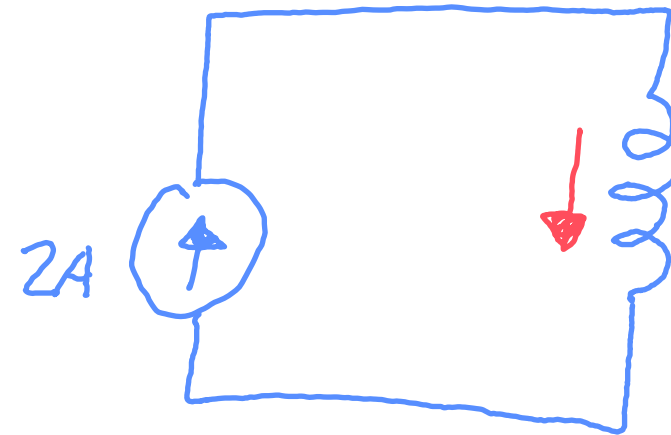

$i_L = 2A$ in series


$$V_L = L \frac{d2}{dt} = 0V$$

Can be modeled
as short circuit

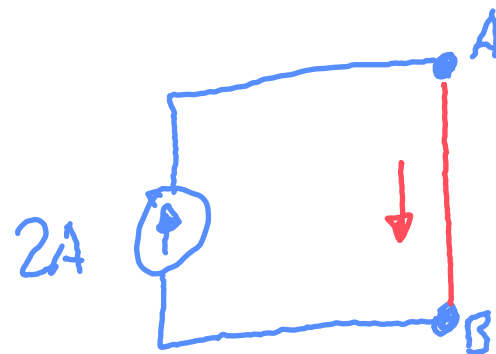




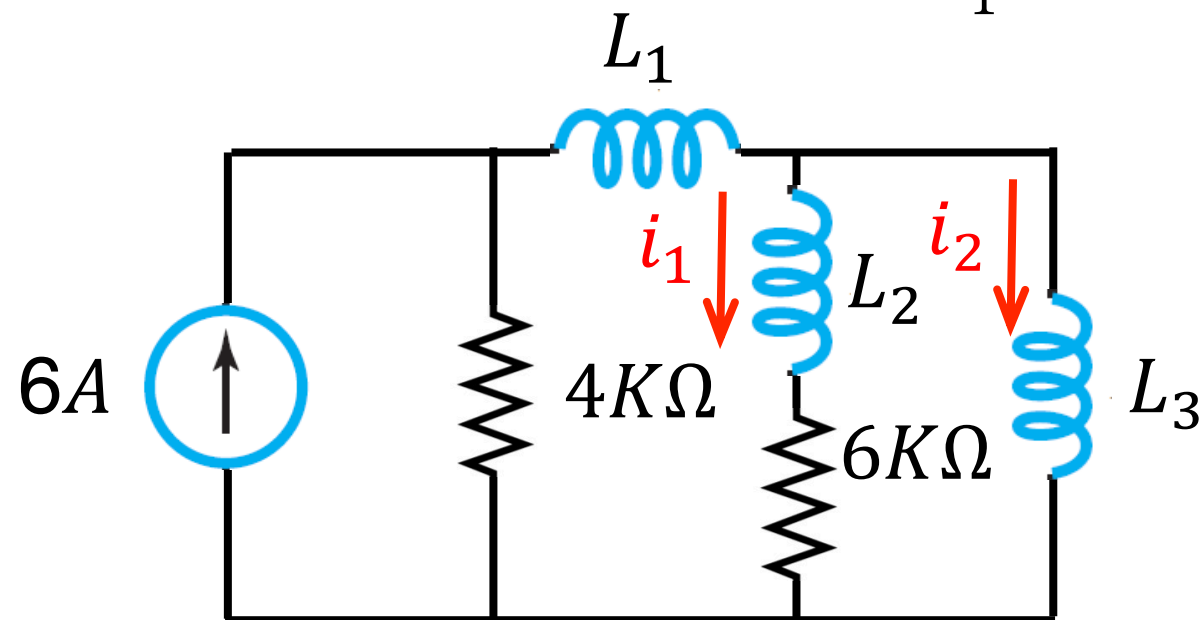Determine the current i_1 and i_2 in the circuit under DC condition.



DC \rightarrow inductors = short circuit

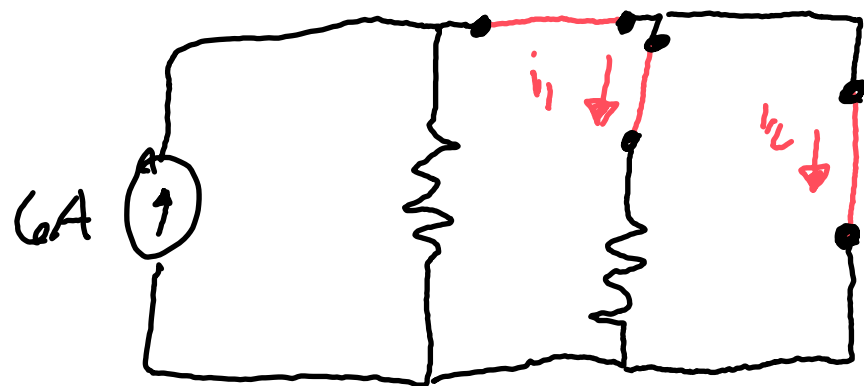

$$i_1 = 0A$$


$$i_2 = 6A$$

Shorted out

$$V=0 \rightarrow i=0$$



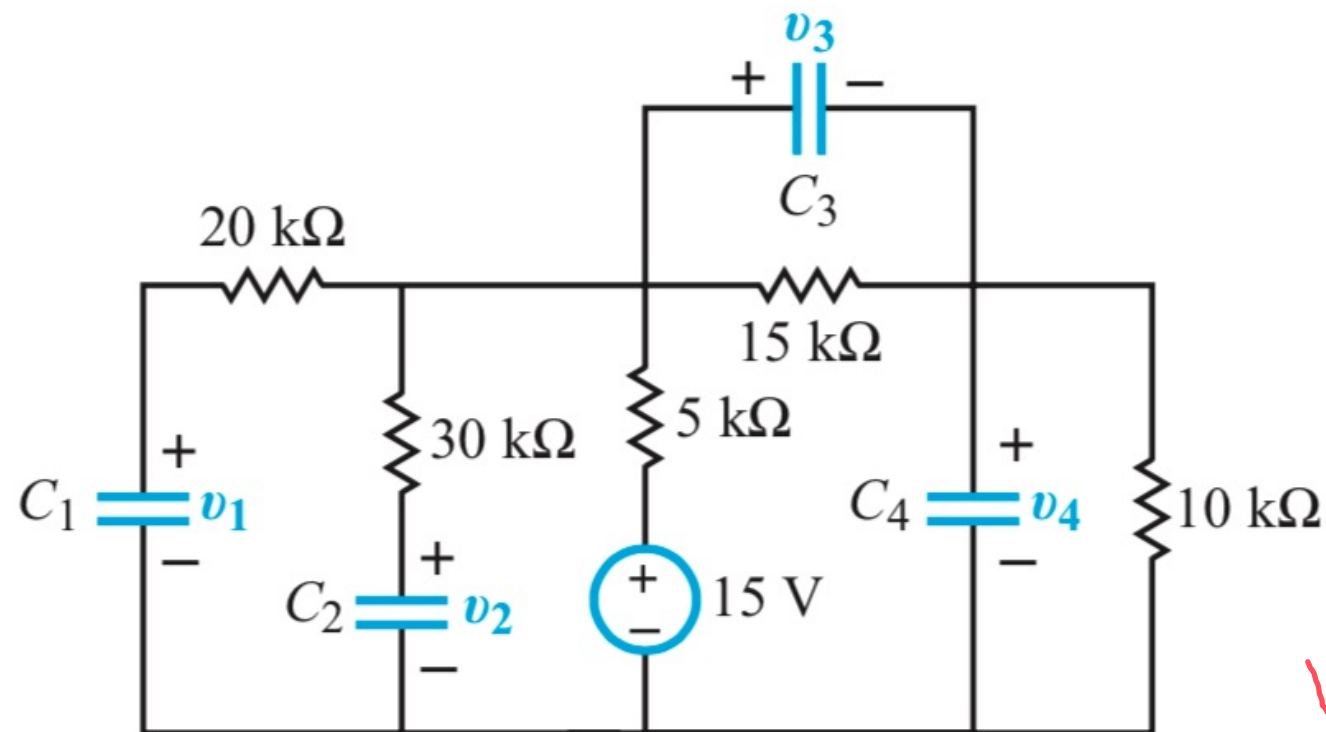Determine voltage v_1 to v_4 in the circuit under dc conditions.



$$V_1 = V_2 = V_A$$

$$V_C = 0V$$

$$V_3 = V_A - V_B$$

$$V_D = 15V$$

$$V_4 = V_B$$

Voltage Division

$$V_D = \frac{10k}{30k} \cdot 15 = 5V$$

$$V_B = 5V$$

$$V_5 = \frac{5k}{30k} \cdot 15 = 2.5V$$

$$V_5 = V_D - V_A = 15 - 2.5 = 12.5V$$

$$V_A = 12.5V$$

