

Spring 2024 – ECE 3020

Homework 8

Due: 03/06/2024

1. For the following filters, assume the op-amps are ideal.
 - i. Derive the transfer functions, $T(s)$
 - ii. If $R_1 = 10\text{k}\Omega$, $R_2 = 100\text{k}\Omega$, $C_1 = 1\mu\text{F}$, $C_2 = 0.1\mu\text{F}$, $L_1 = 1\text{nH}$, and $L_2 = 1\mu\text{H}$, plot the magnitude and phase responses of each filter.

