

For the counter circuit below find:

- a) The transition table
- b) The transition graph

The bits of the counter are  $CBA$  in that order.

