

ECE 3020

Introduction to Electronics

Section 4: Filters

Spring 2024

Tawfiq Musah, Assistant Professor

Dept. of Electrical & Computer Engineering

The Ohio State University

Acknowledgement

- ◆ The instructor would like to acknowledge and thank the following for kindly providing the lecture notes/handouts for this class. Some modifications and/or customizations to the original material is occasionally introduced by the instructor
 - Prof. Nima Ghalichechian
 - Prof. Asimina Kiourti
 - Prof. Ayman Fayed
 - Prof. George Valco



Topics Covered in this Course

- ◆ Section 1: Basic Concepts
- ◆ Section 2: Operational Amplifiers (Op-Amps)
- ◆ Section 3: Introduction to Feedback
- ◆ **Section 4: Filters**
- ◆ Section 5: Diodes and Applications
- ◆ Section 6: Field Effect Transistors (FETs) and Applications
- ◆ Section 7: Bipolar Junction Transistors (BJTs) and Applications
- ◆ Section 8: Digital and Mixed-Signal Circuits
- ◆ Section 9: Circuit Simulation Software



Reading Assignment

◆ Text → pp 35-41, 1290-1300, 1307-1322




ECE 3020: Introduction to Electronics

A SIMPLE METHOD TO DRAW THE TRANSFER FUNCTION





Effect of Constant Terms

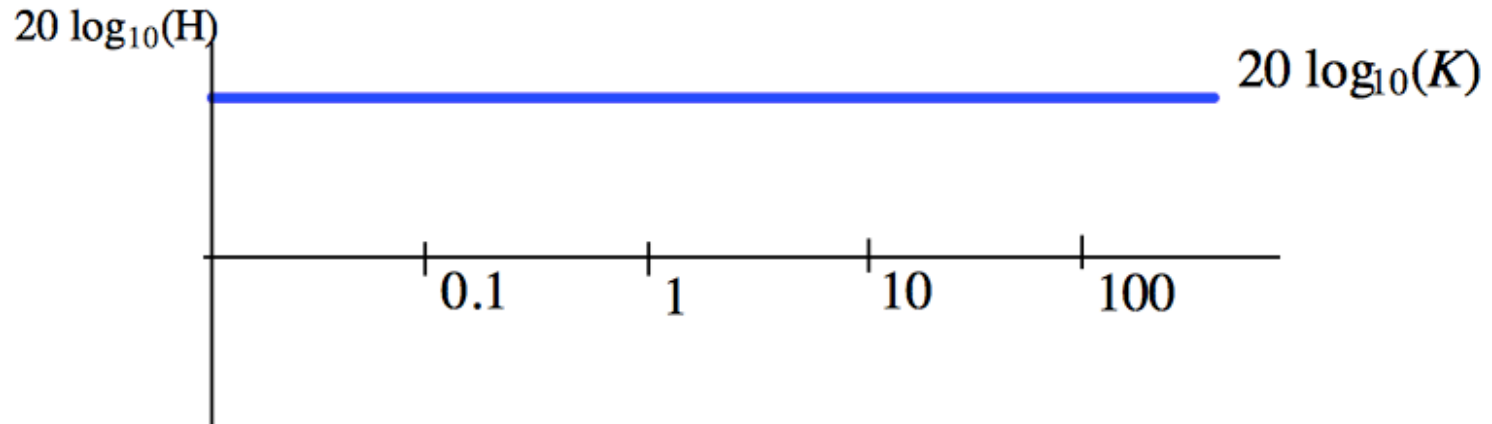


$$H = K$$



Effect of Poles and Zeros at 0

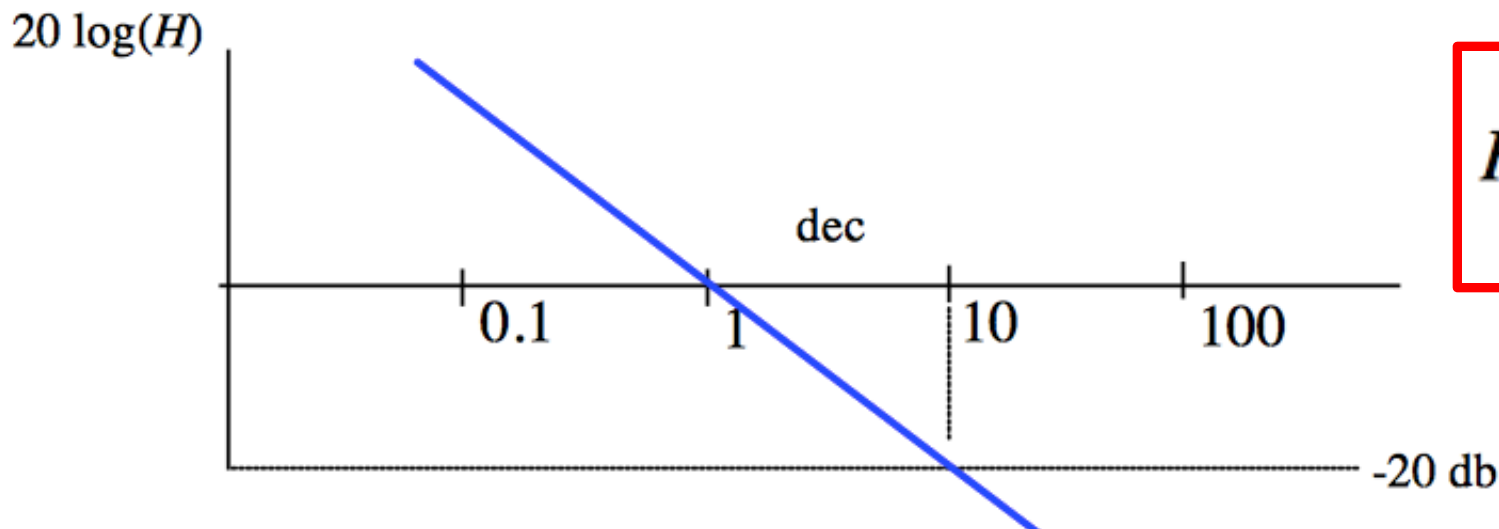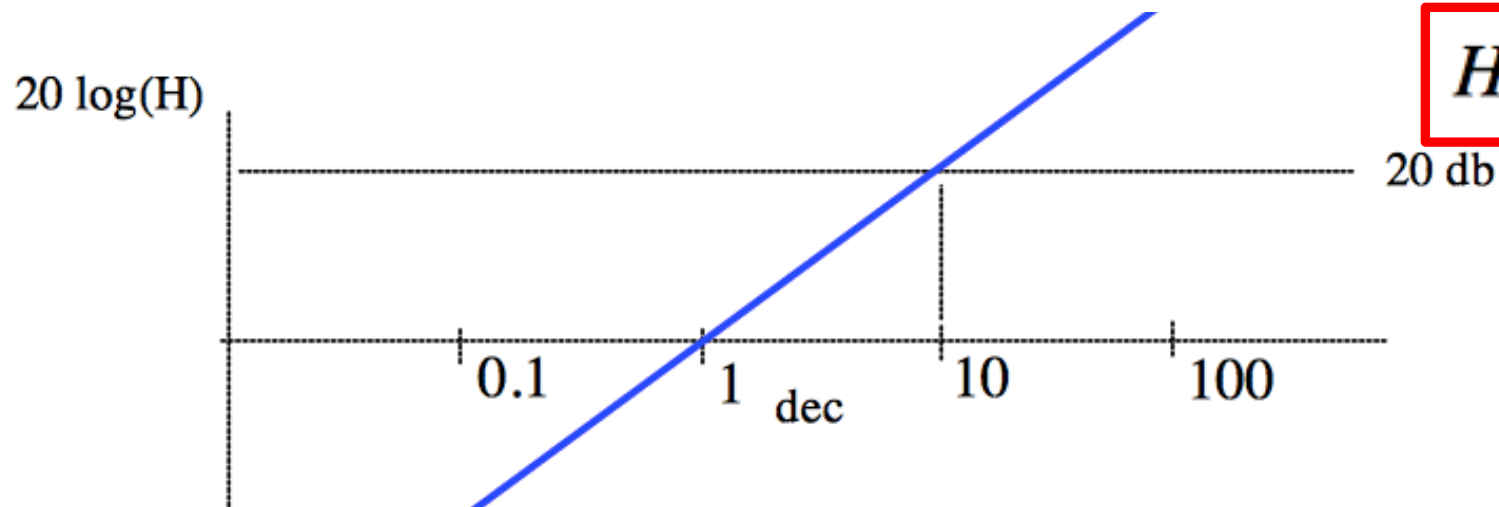

Effect of Poles and Zeros

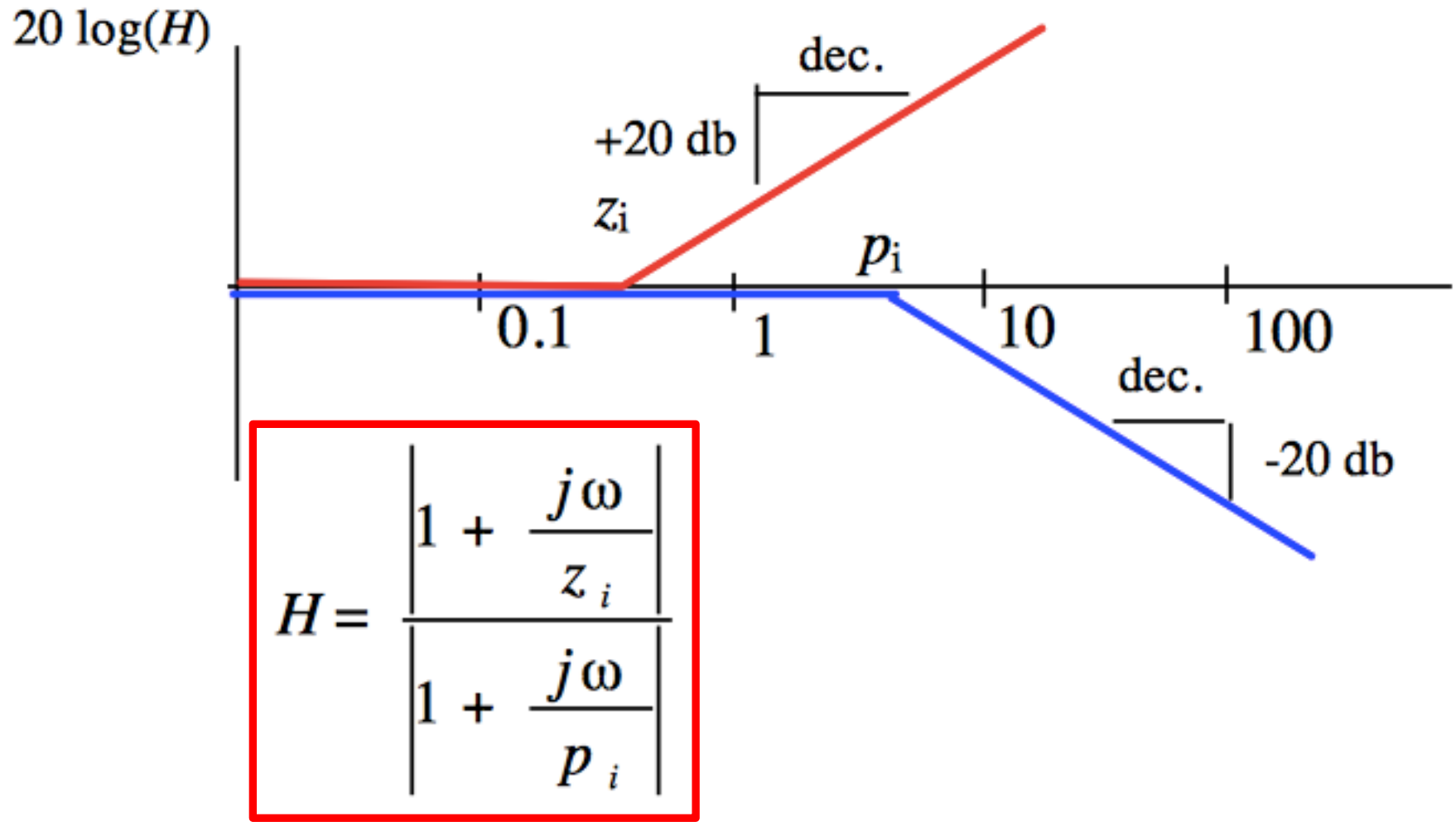

ECE 3020: Introduction to Electronics


FILTER BASICS



Analog Filters: Definitions and Types

Linear circuits
represented by general
two-port network

$$T(s) \equiv \frac{V_o(s)}{V_i(s)}$$

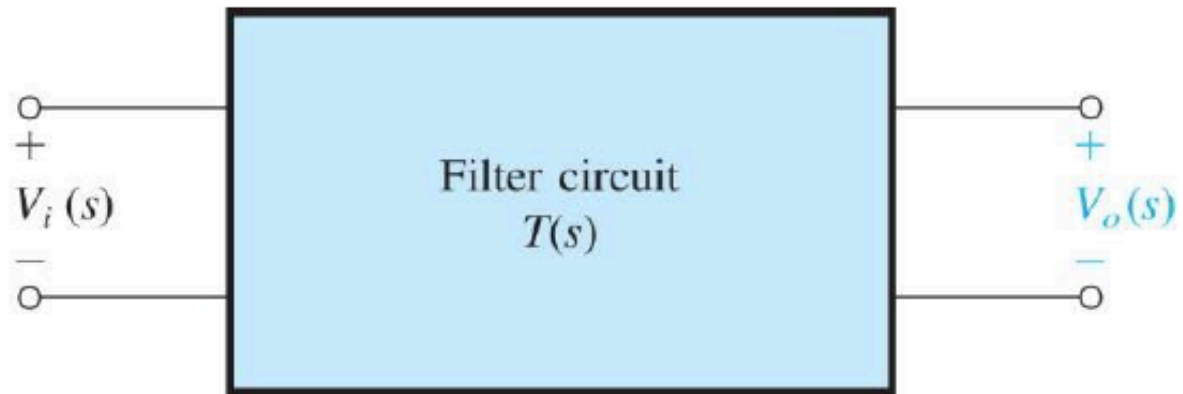

For physical frequencies $s = j\omega$ filter transmission

$$T(j\omega) = |T(j\omega)|e^{j\phi(\omega)}$$

Alternate expressions for magnitude of transmission

- Gain function $G(\omega) \equiv 20 \log|T(j\omega)|$ in dB
- Attenuation function $A(\omega) \equiv -20 \log|T(j\omega)|$ in dB







Analog Filters: Definitions and Types

Ideal filters

- Unity transmission magnitude in **passband**
- Zero transmission in **stopband**
- Vertical (brick-wall) transitions between

Assign one of the following to each of these filter types

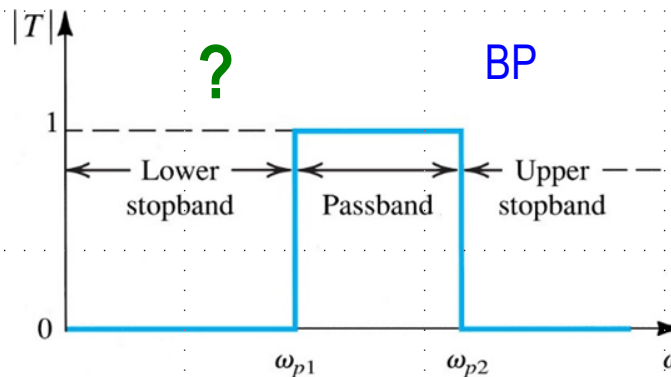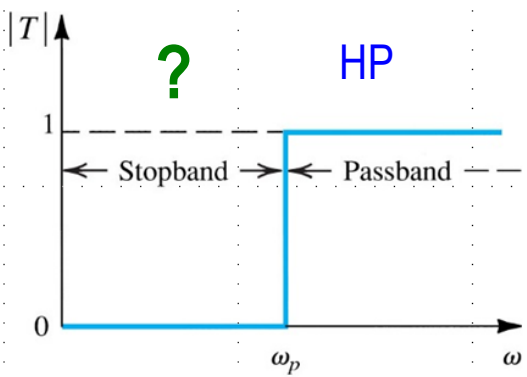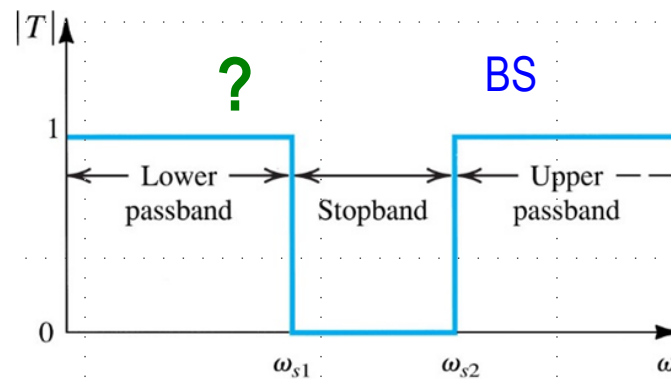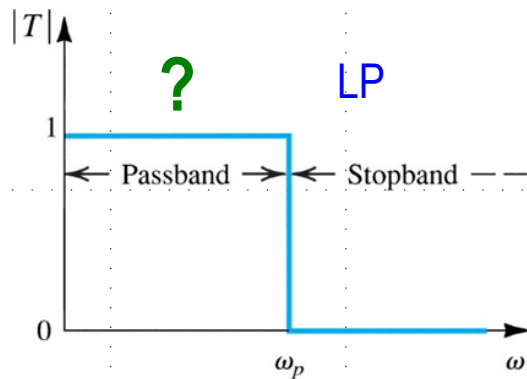- Low-pass (LP)
- High-pass (HP)
- Bandpass (BP)
- Bandstop (BS)
a.k.a. band-reject




Filter Specifications – LPF Example

- Real physical circuits cannot attain ideal characteristics
- Specifications for a filter design need to be realistic
- Use **low-pass** and bandpass as examples

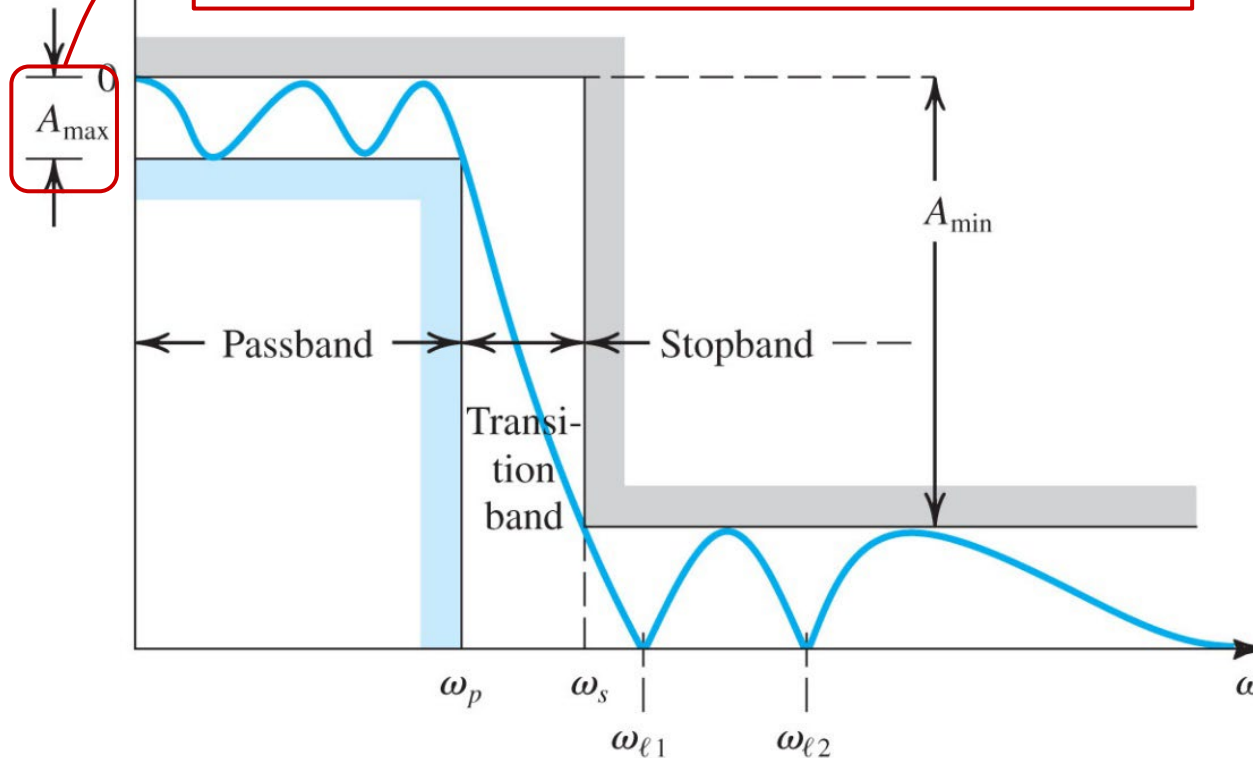- Example shows 0 dB as the reference
- If filter has gain, reference might be different dB value

Upper bound on deviation from 0 dB in passband


- Value depends on application
- 0.05 to 3 dB typical range



Filter Specifications – LPF Example

- Real physical circuits cannot attain ideal characteristics
- Specifications for a filter design need to be realistic
- Use **low-pass** and bandpass as examples

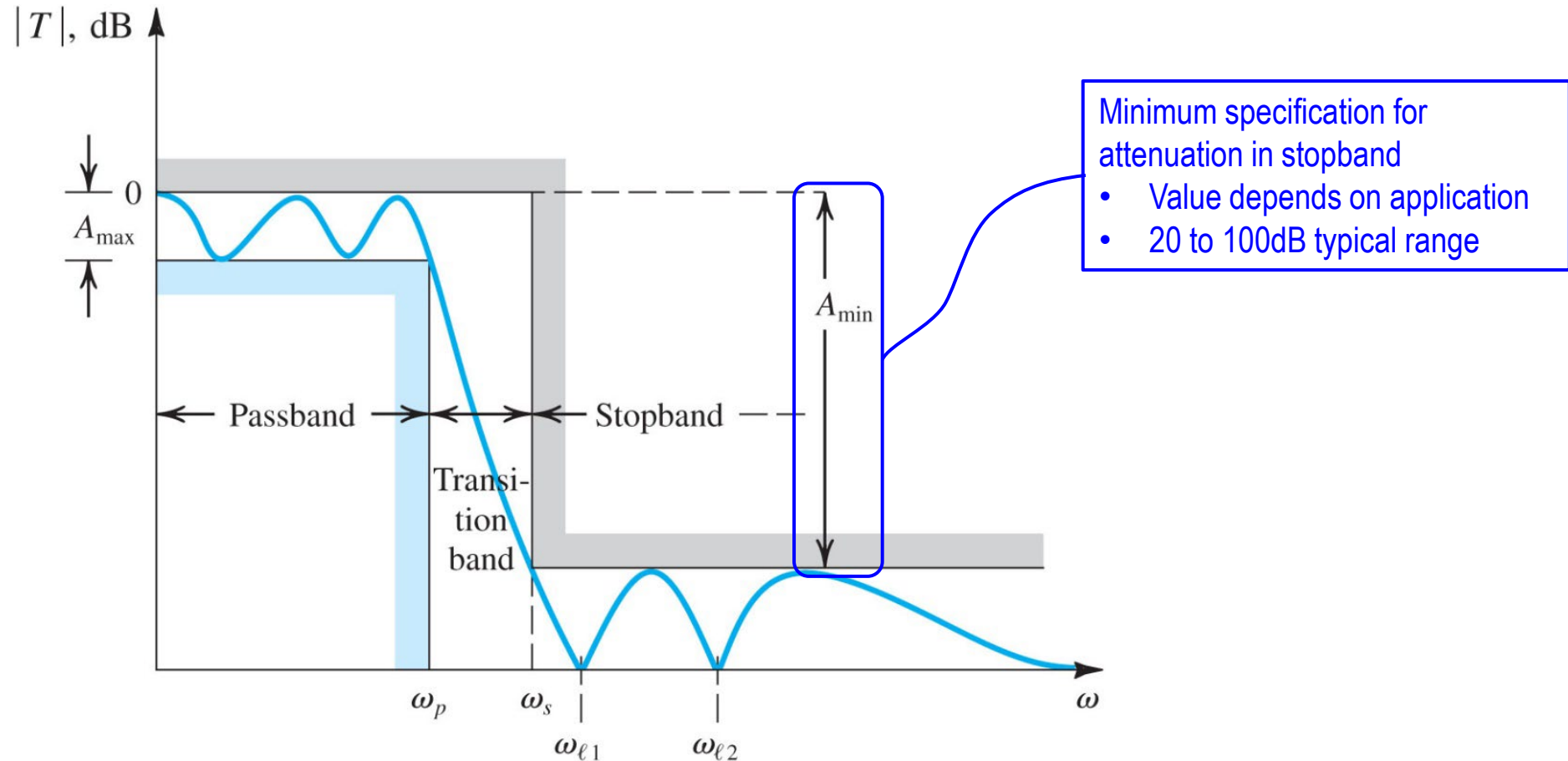
- Example shows 0 dB as the reference
- If filter has gain, reference might be different dB value



Filter Specifications – LPF Example


- Real physical circuits cannot attain ideal characteristics
- Specifications for a filter design need to be realistic
- Use **low-pass** and bandpass as examples

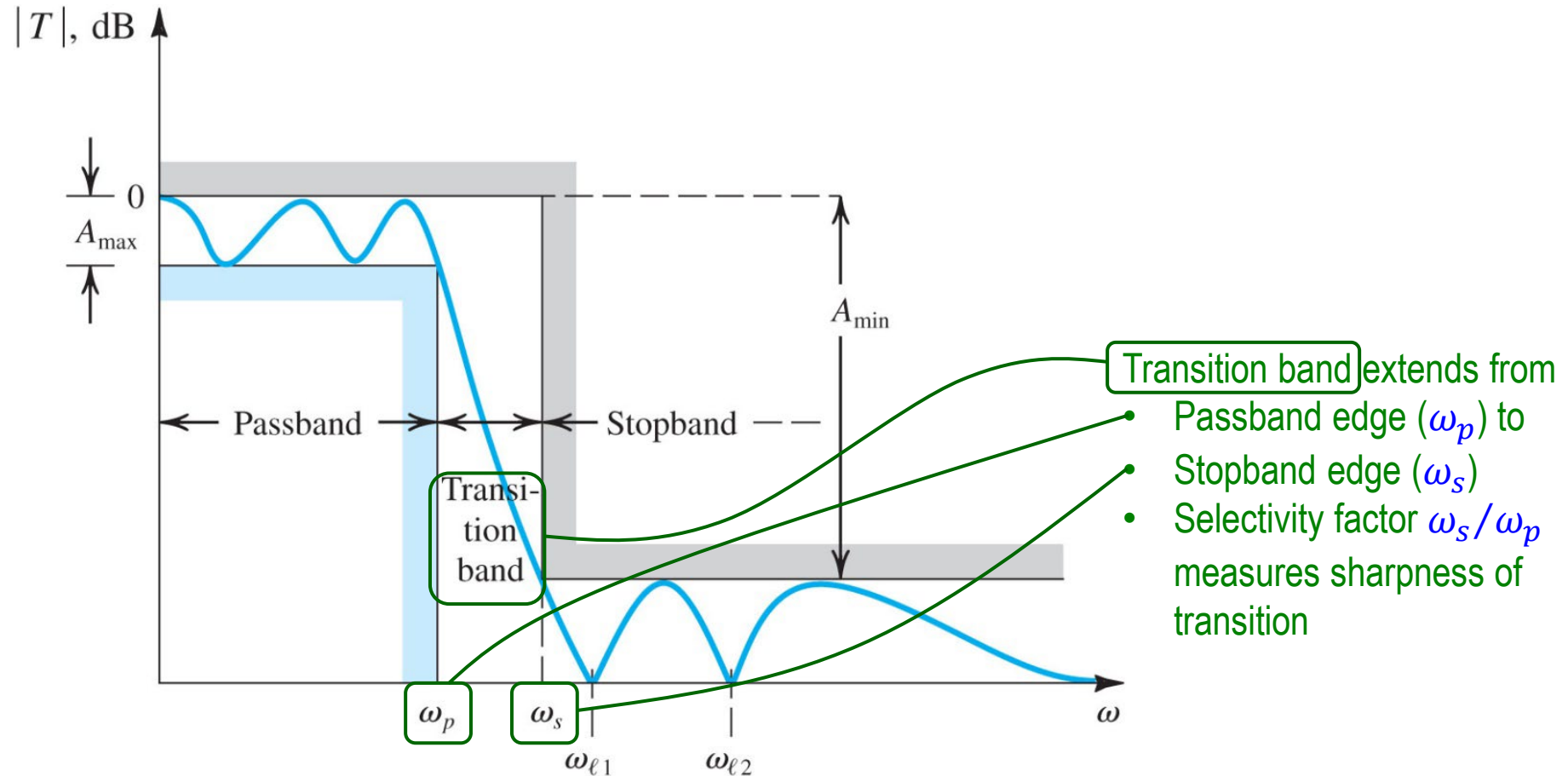- Example shows 0 dB as the reference
- If filter has gain, reference might be different dB value



Filter Specifications – BPF Example

- Real physical circuits cannot attain ideal characteristics
- Specifications for a filter design need to be realistic
- Use low-pass and **bandpass** as examples

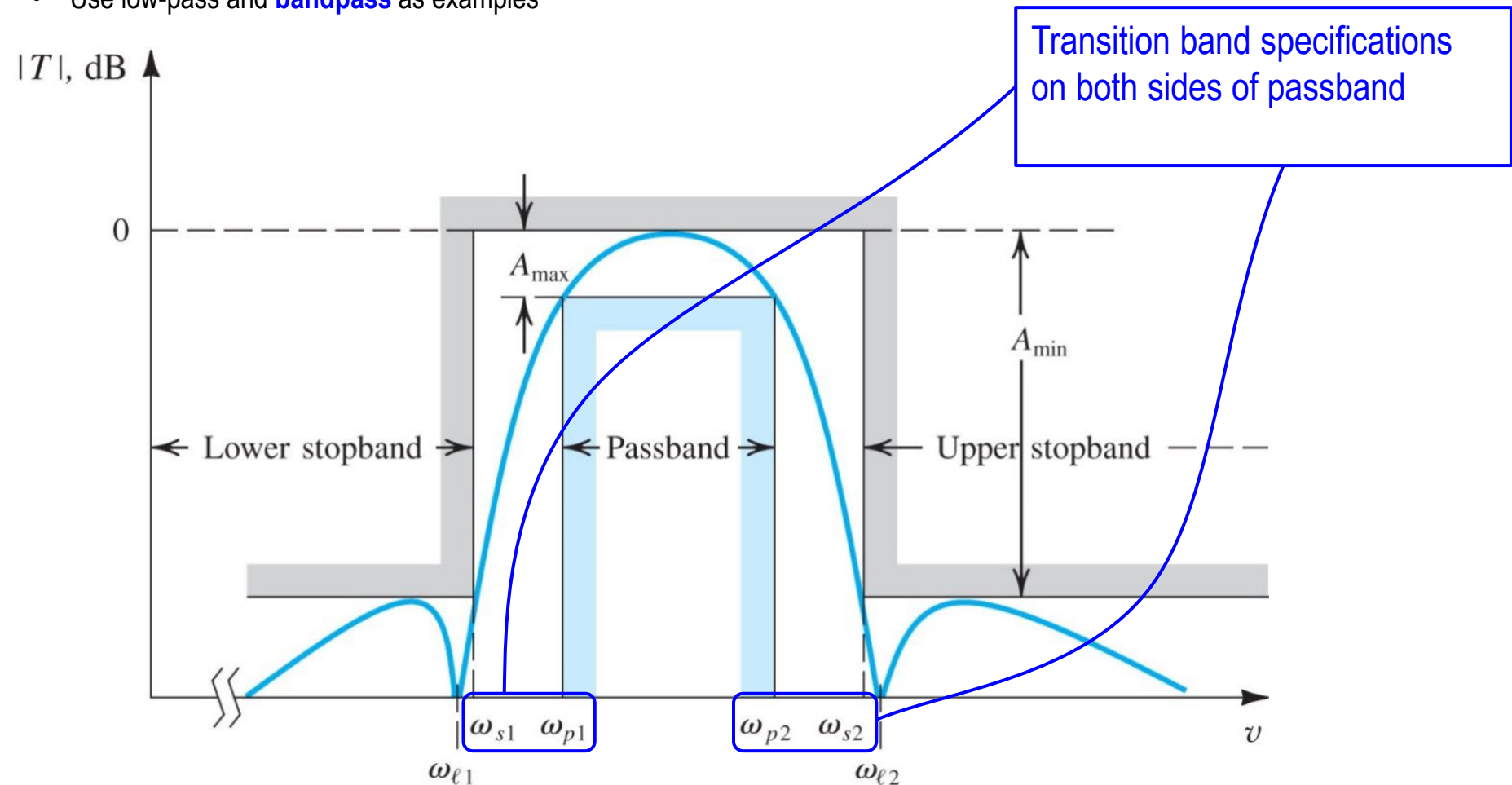


ECE 3020: Introduction to Electronics

FREQUENCY RESPONSE: FIRST-ORDER



Single Time Constant Network – LOW PASS

$$\tau = RC = \frac{1}{\omega_0}$$

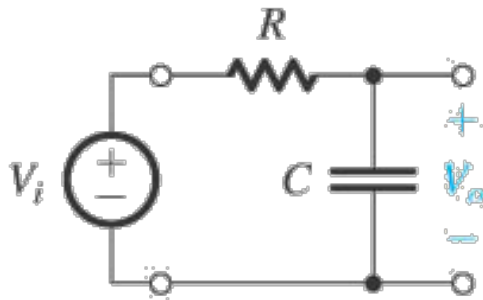

Low-pass network

$$T(s) = \frac{K}{1 + \frac{s}{\omega_0}}$$

Magnitude and Phase Response of Low-pass STC Network



Magnitude

$$|T(j\omega)|^2 = \frac{|K|^2}{1 + \left(\frac{\omega}{\omega_0}\right)^2}$$

Sinusoidal steady-state response; s replaced by $j\omega$


Phase
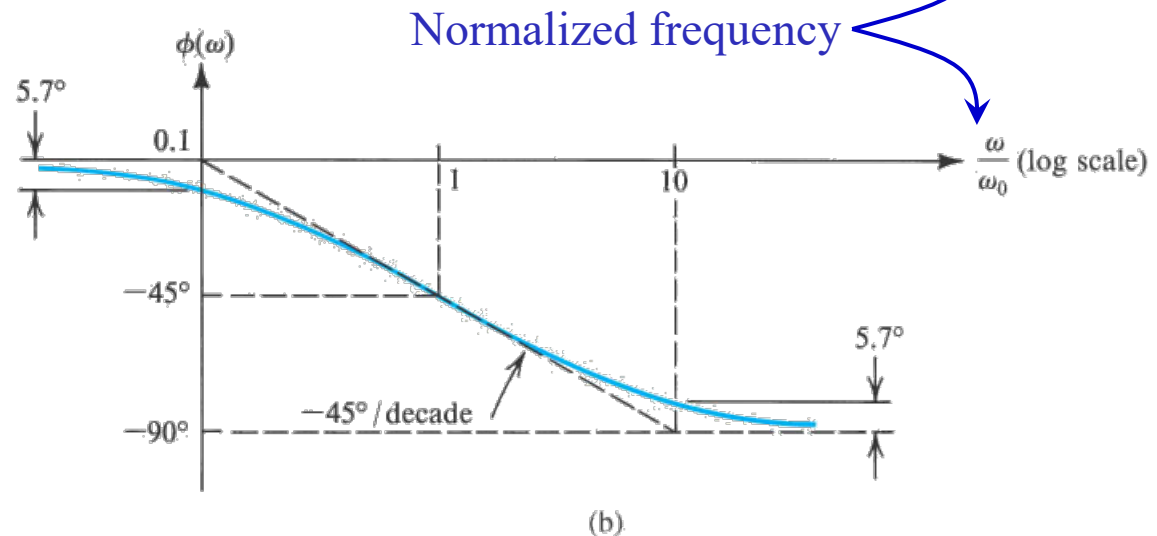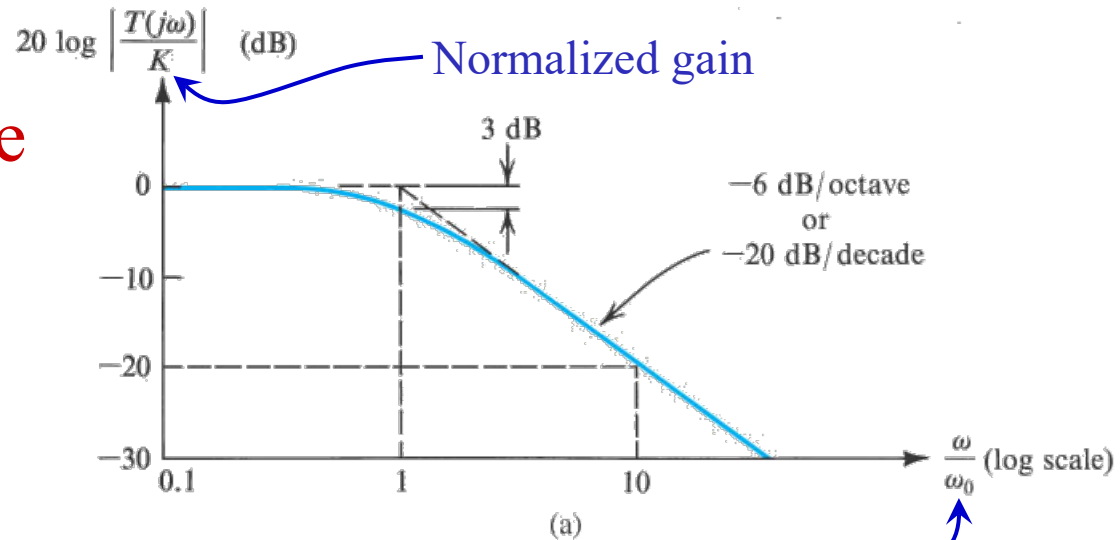
$$-\tan^{-1} \left[\frac{\omega}{\omega_0} \right]$$



Single Time Constant Network – HIGH PASS

$$\tau = RC = \frac{1}{\omega_0}$$

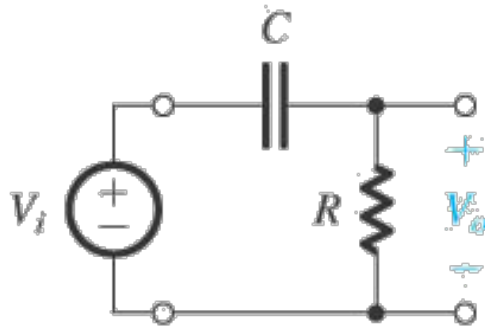

(b)

High-pass network


$$T(s) = \frac{Ks}{s + \omega_0}$$



Magnitude and Phase Response of High-pass STC Network

Magnitude


$$|T(j\omega)|^2 = \frac{|K|^2}{1 + \left(\frac{\omega_0}{\omega}\right)^2}$$

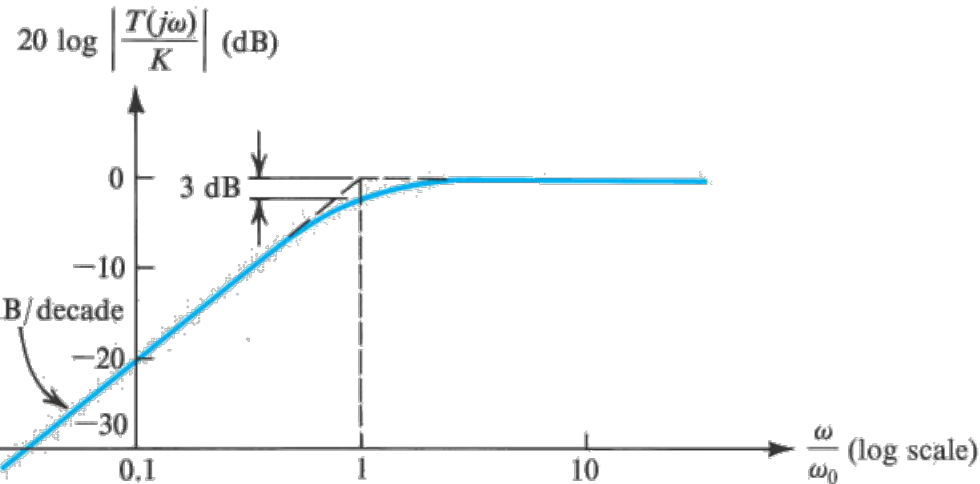

(a)

Phase
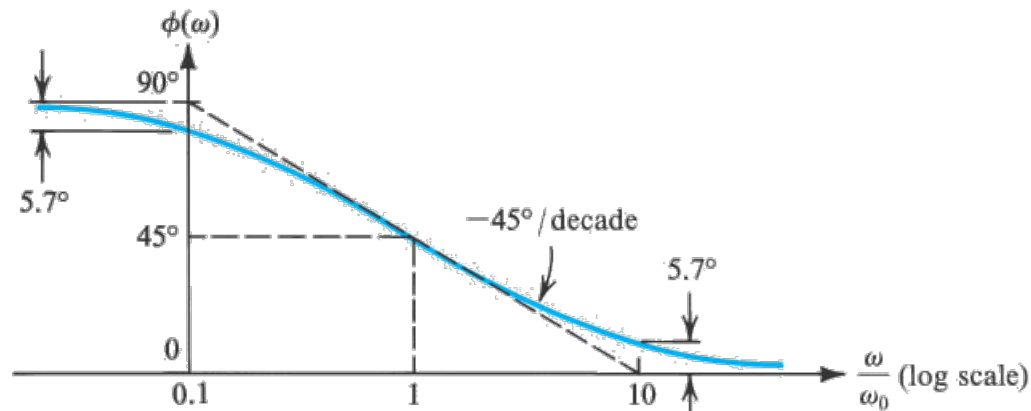
$$\tan^{-1} \left[\frac{\omega_0}{\omega} \right]$$




(b)




The Miller or Inverting Integrator

Using $Z_1 = R$ and $Z_2 = \frac{1}{Cs}$

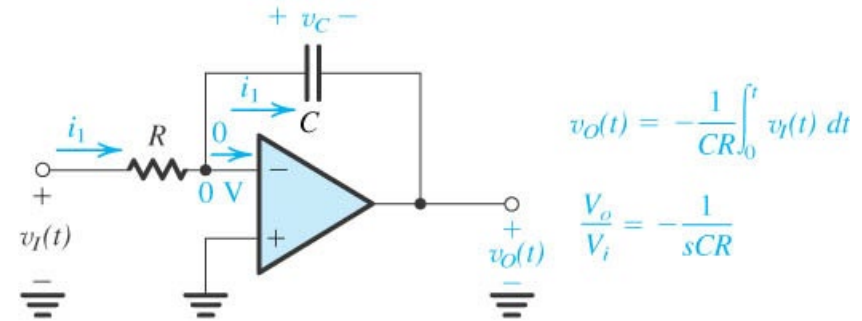

we get
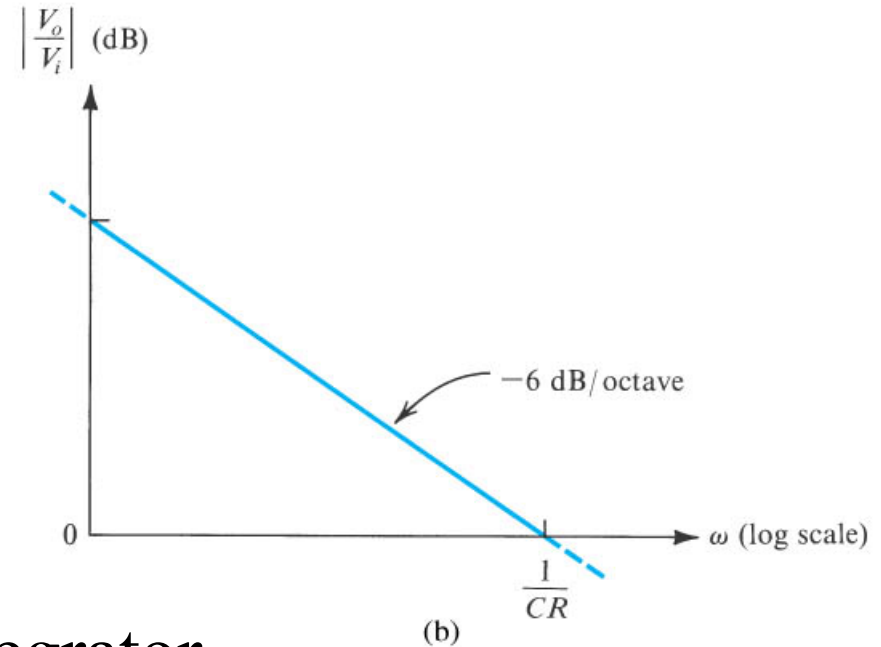
$$\frac{V_o(s)}{V_i(s)} = -\frac{Z_2(s)}{Z_1(s)} = -\frac{1}{RCs}$$



Frequency response of the integrator.




Effect of Finite Open-Loop Gain & Bandwidth on Op-Amps

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_b}}$$


with $s = j\omega$

$$\omega_b = 2\pi f_b$$

break frequency

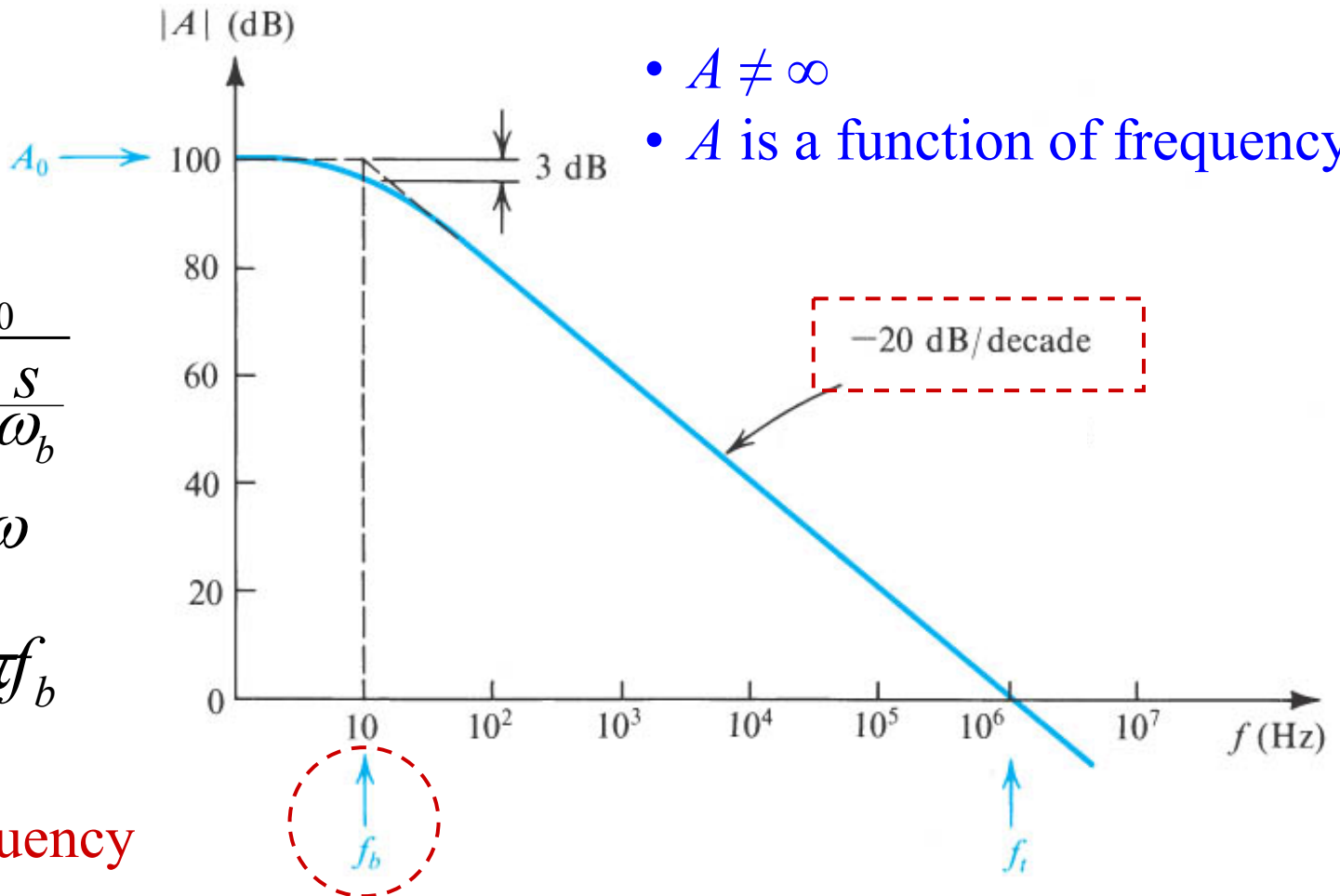

Exercise #1

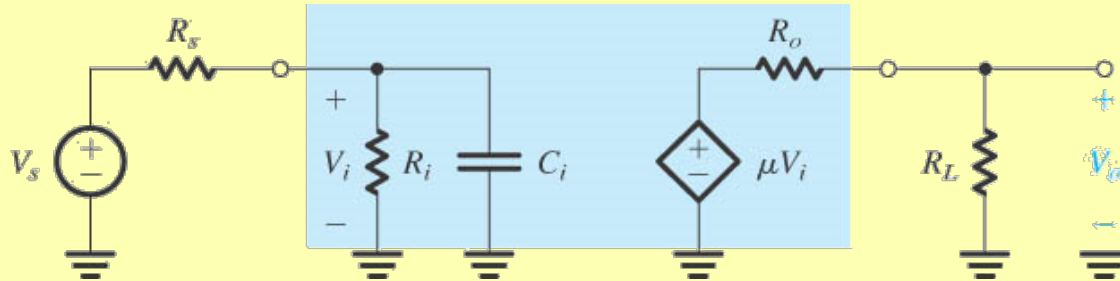


- 1) What is the voltage gain as a function of frequency?
- 2) What is the DC voltage gain?
- 3) What is the 3dB frequency?
- 4) How can I create an extra zero?

ECE 3020: Introduction to Electronics

FREQUENCY RESPONSE: SECOND-ORDER



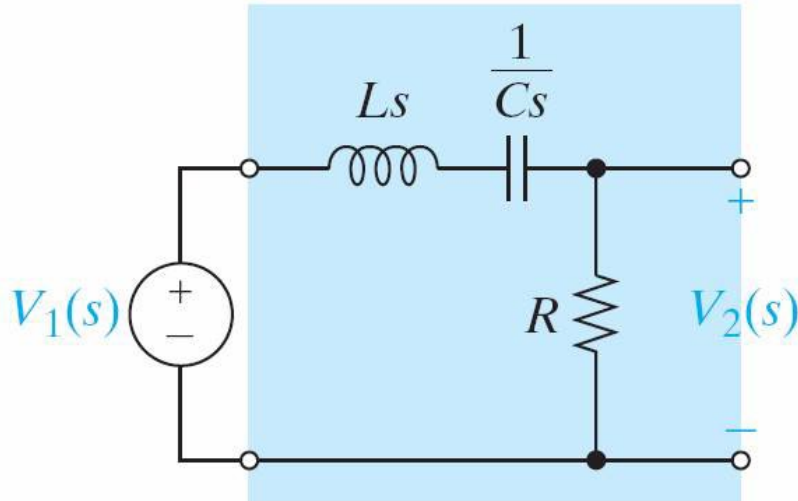Exercise #2: Second Order Frequency Response




1) What is the transfer function of this filter?


$$T(s) = \frac{R}{R + Ls + 1/Cs} = \frac{R}{R + Z_{LC}(s)}$$

2) Can I easily predict the type of this filter just by looking at its transfer function?

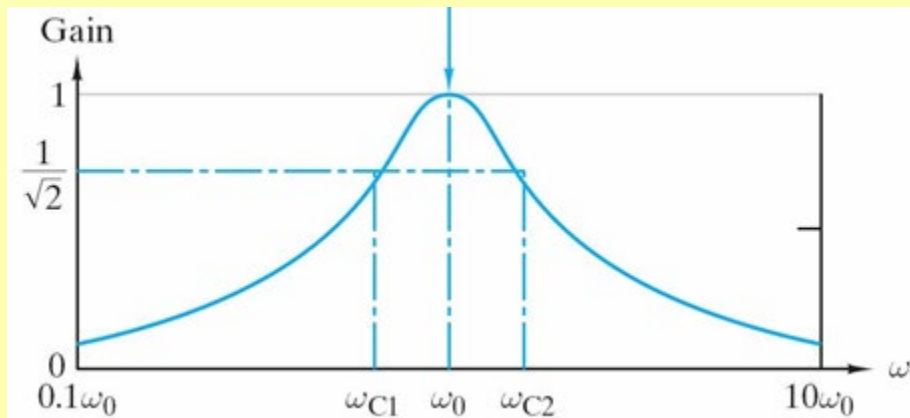3) What is the filter's resonant frequency, ω_0 ?



A) Calculation of: Resonant Frequency

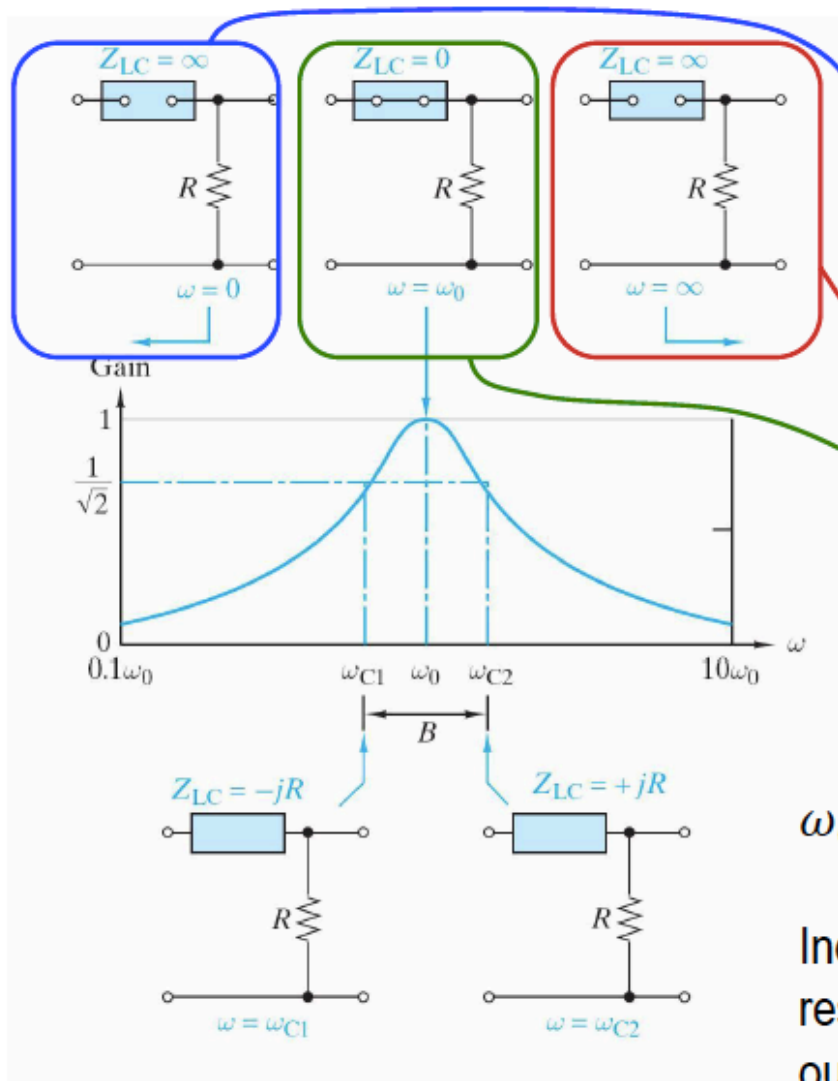

$$Z_{LC}(j\omega) = j(\omega L - 1/\omega C)$$

At DC, capacitor open, $T(0) = 0$

At high frequency, inductor open, $T(\infty) = 0$


At $\omega = \omega_0 = 1/\sqrt{LC}$,
 $Z_{LC} = j(\sqrt{L/C} - \sqrt{L/C}) = 0, T(j\omega_0) = 1$

$\omega_0 \equiv$ center frequency or resonant frequency

Inductor and capacitor interact to produce a resonant short circuit at ω_0 connecting input to output



B) Calculation of: Cut-off Frequencies

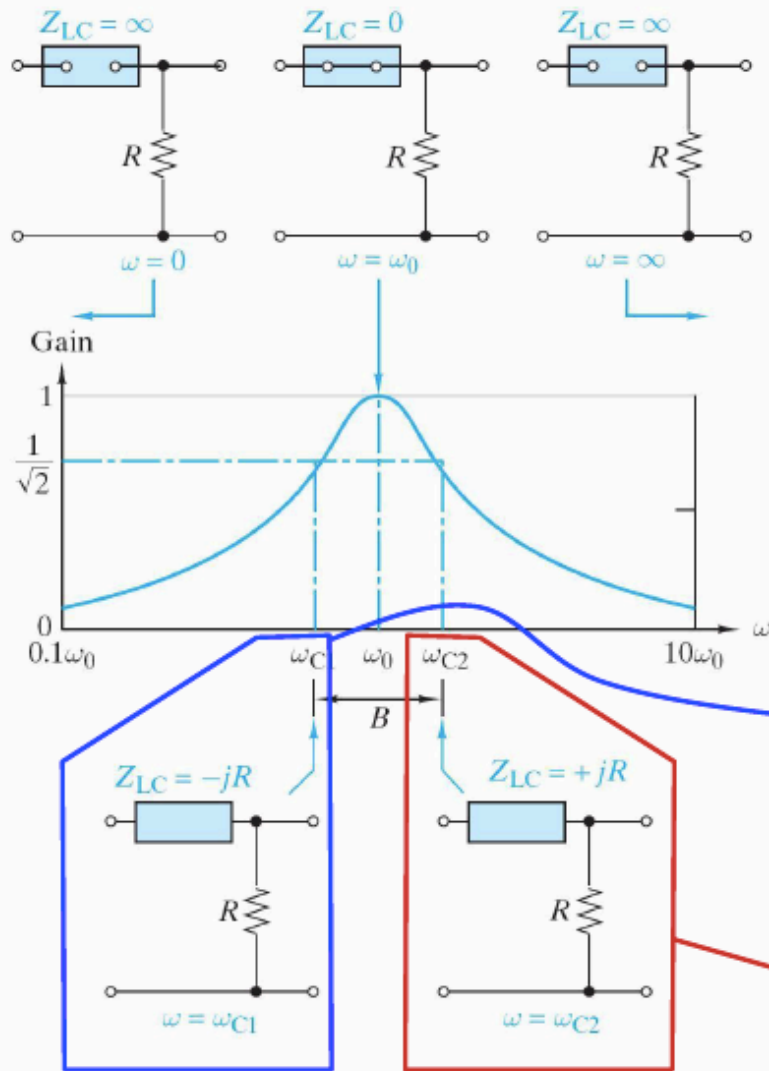

$$T(j\omega) = \frac{R}{R + Z_{LC}(j\omega)}$$

The 3dB or cutoff frequencies occur when $Z_{LC} = \pm jR$

$$|T(j\omega)| = \left| \frac{R}{R \pm jR} \right| = \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{2}} T_{max}$$

$$Z_{LC}(j\omega_c) = j(\omega_c L - 1/\omega_c C) = \pm jR$$

algebra

$$LC\omega_c^2 \pm RC\omega_c - 1 = 0$$

The physically valid roots are

$$\omega_{C1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_{C2} = +\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$






C) Calculation of: Bandwidth

$$\omega_{C1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_{C2} = +\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

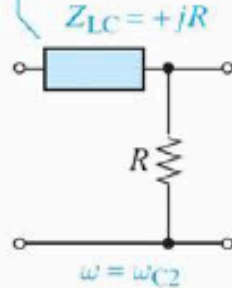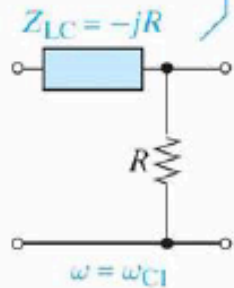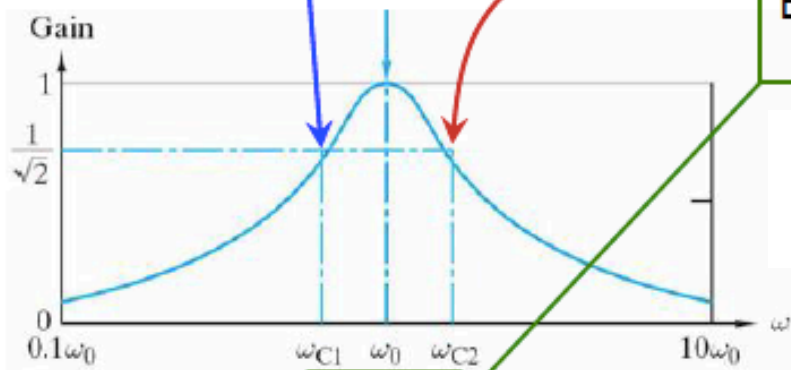
$$\text{Bandwidth} \equiv B = \omega_{C2} - \omega_{C1} = \frac{R}{L}$$



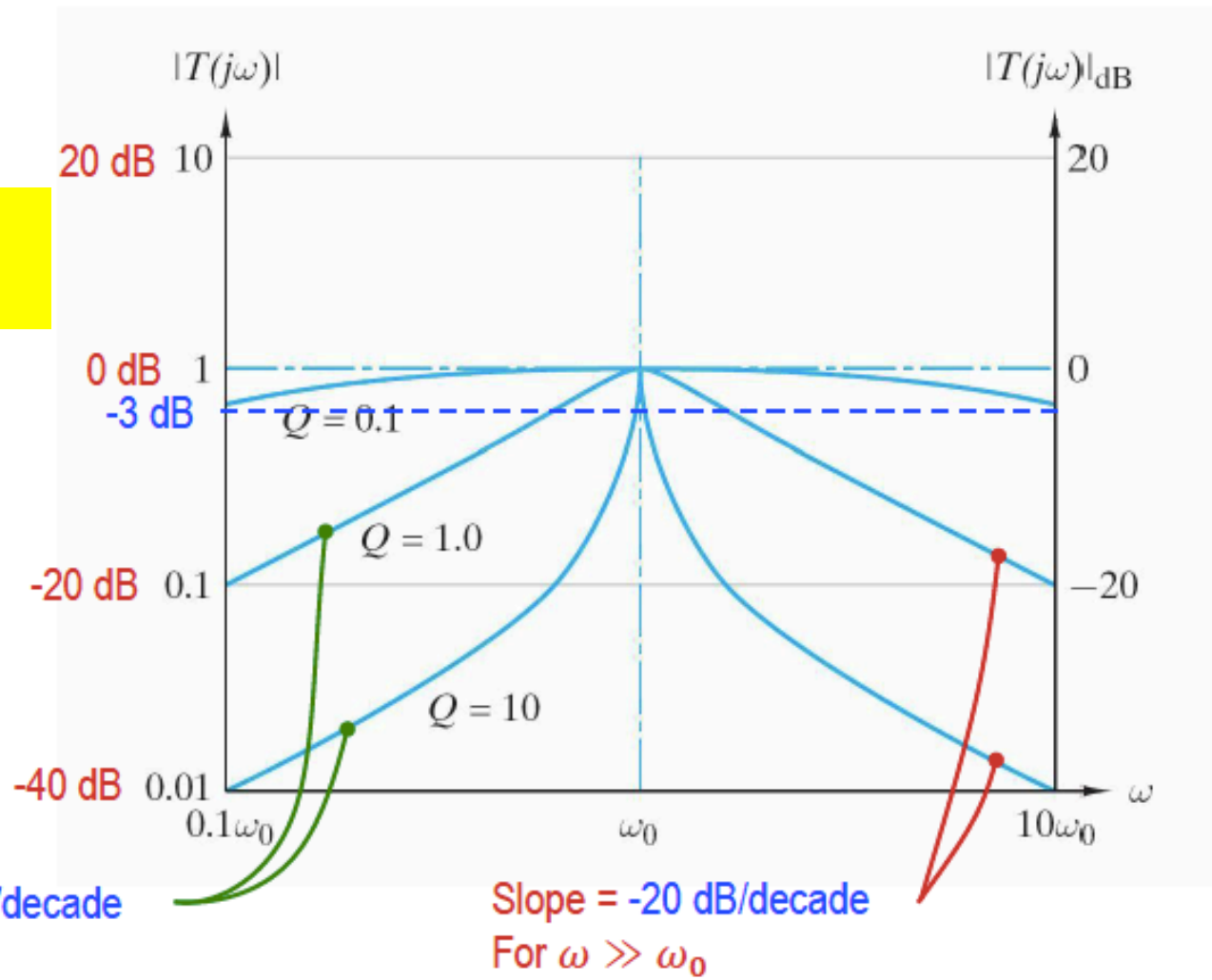D) Calculation of: Quality Factor

$$Q = \frac{\omega_0}{B} = \frac{\sqrt{L/C}}{R}$$

High Q yields narrow band, or tuned, filters.



Slope = +20 dB/decade
For $\omega \ll \omega_0$

Slope = -20 dB/decade
For $\omega \gg \omega_0$



Second Order Frequency Response Review

$$T(s) = \frac{R}{R + Ls + 1/Cs} = \frac{s \boxed{R/L}}{s^2 + s R/L + 1/LC}$$


$$T(s) = \frac{sB}{s^2 + s \left(\frac{1}{\sqrt{LC}} \right) R \sqrt{LC}/L + \boxed{1/LC}}$$

$$T(s) = \frac{sB}{s^2 + s\omega_0 \left(\frac{R}{\sqrt{L/C}} \right) + \omega_0^2}$$

$$T(s) = \frac{sB}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$



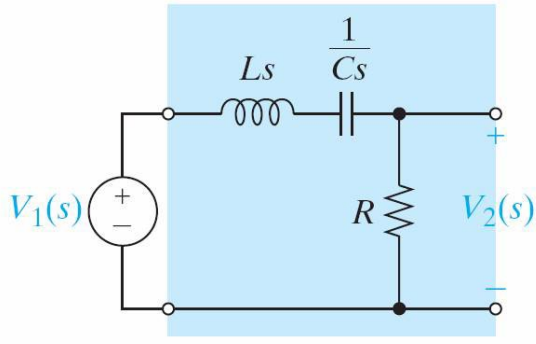
Exercise #3: Second Order Frequency Response



- 1) What is the transfer function if the output is taken across the capacitor?

$$T(s) = \frac{\omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

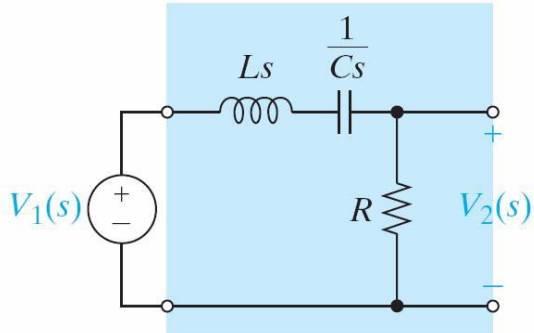Exercise #4: Second Order Frequency Response



1) What is the transfer function if the output is taken across the inductor?

$$T(s) = \frac{s^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

ECE 3020: Introduction to Electronics

FILTER POLES AND ZEROS



Analog Filters: Transfer Function

In general transfer functions of analog filters can be written as ratio of polynomials

$$T(s) = \frac{a_M s^M + a_{M-1} s^{M-1} + \dots + a_0}{s^N + b_{N-1} s^{N-1} + \dots + b_0}$$

- Degree of denominator: **filter order**
- For a stable filter $M \leq N$
- The coefficients of the polynomials are **real numbers**

The polynomials can be factored

$$T(s) = \frac{a_M (s - z_1)(s - z_2) \dots (s - z_M)}{(s - p_1)(s - p_2) \dots (s - p_N)}$$

- Numerator roots, z_1, z_2, z_M , are transfer function **zeros**, a.k.a transmission **zeros**
- Denominator roots, p_1, p_2, p_N , are transfer function **poles**, a.k.a **natural modes**
- Poles and zeros can be real numbers or complex numbers
- Any complex poles or zeros always occur in conjugate pairs



Exercise #5

A linear system is described by the transfer functions below

$$H_1(s) = 1 / (2s+100). \quad H1(s) = (2s+1) / (s^2+5s+6).$$

Find the system poles and zeros and plot the Bode plot



ECE 3020: Introduction to Electronics

REVIEW WITHIN THE FRAMEWORK OF ACTIVE FILTER REALIZATIONS



First Order Filters (Summary)

Filter Type and $T(s)$	s -Plane Singularities	Bode Plot for $ T $	Passive Realization	Op Amp-RC Realization
(a) Low pass (LP) $T(s) = \frac{a_0}{s + \omega_0}$			$CR = \frac{1}{\omega_0}$ $\text{DC gain} = 1$	$CR_2 = \frac{1}{\omega_0}$ $\text{DC gain} = -\frac{R_2}{R_1}$
(b) High pass (HP) $T(s) = \frac{a_1 s}{s + \omega_0}$			$CR = \frac{1}{\omega_0}$ $\text{High-frequency gain} = 1$	$CR_1 = \frac{1}{\omega_0}$ $\text{High-frequency gain} = -\frac{R_2}{R_1}$
(c) General $T(s) = \frac{a_1 s + a_0}{s + \omega_0}$			$(C_1 + C_2)(R_1 // R_2) = \frac{1}{\omega_0}$ $C_1 R_1 = \frac{a_1}{a_0}$ $\text{DC gain} = \frac{R_2}{R_1 + R_2}$ $\text{HF gain} = \frac{C_1}{C_1 + C_2}$	$C_2 R_2 = \frac{1}{\omega_0}$ $C_1 R_1 = \frac{a_1}{a_0}$ $\text{DC gain} = -\frac{R_2}{R_1}$ $\text{HF gain} = -\frac{C_1}{C_2}$



First order All-Pass Filter

$T(s)$	Singularities	$ T $ and ϕ	Passive Realization	Op Amp-RC Realization
<p>All pass (AP)</p> $T(s) = -a_1 \frac{s - \omega_0}{s + \omega_0}$ <p>$a_1 > 0$</p>			<p> $CR = 1/\omega_0$ Flat gain $(a_1) = 0.5$ </p>	<p> $CR = 1/\omega_0$ Flat gain $(a_1) = 1$ </p> <p> $\left \frac{V_o}{V_i} \right = 1$ $\phi(\omega) = -2 \tan^{-1}(\omega CR)$ </p>



Exercise #6

- Derive an expression of the transfer function $T(s)=V_O/V_{IN}$ in terms of R_1 , R_2 , and C .
- Determine the order of $T(s)$ and the number of poles and zeros.
- Write an expression for the location of each pole and zero in $T(s)$.
- Write an expression for the magnitude of $T(s)$ at DC and at infinite frequency in dB-scale.
- Sketch the magnitude of $T(s)$ (in dB-scale) versus ω . Indicate on the sketch the expressions for the DC gain, gain at infinity, and the location of any poles and zeros.

