
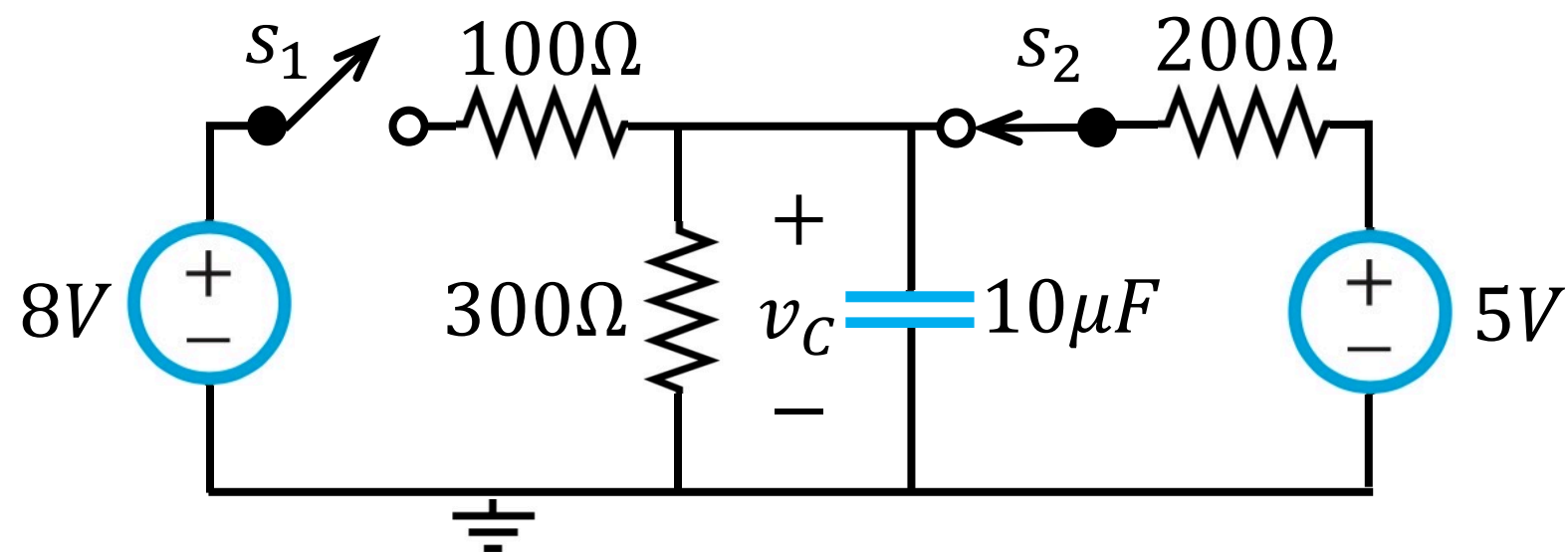


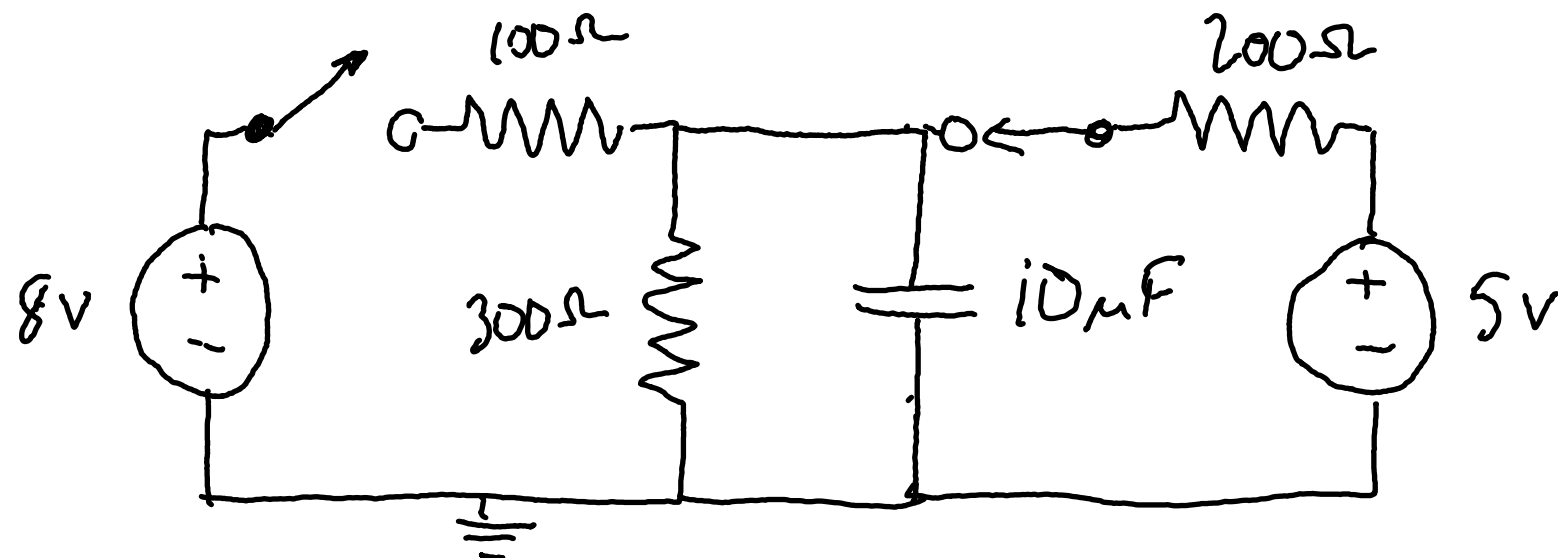


Finish example for Monday class.



*Initial Conditions*



## 2. Steady State

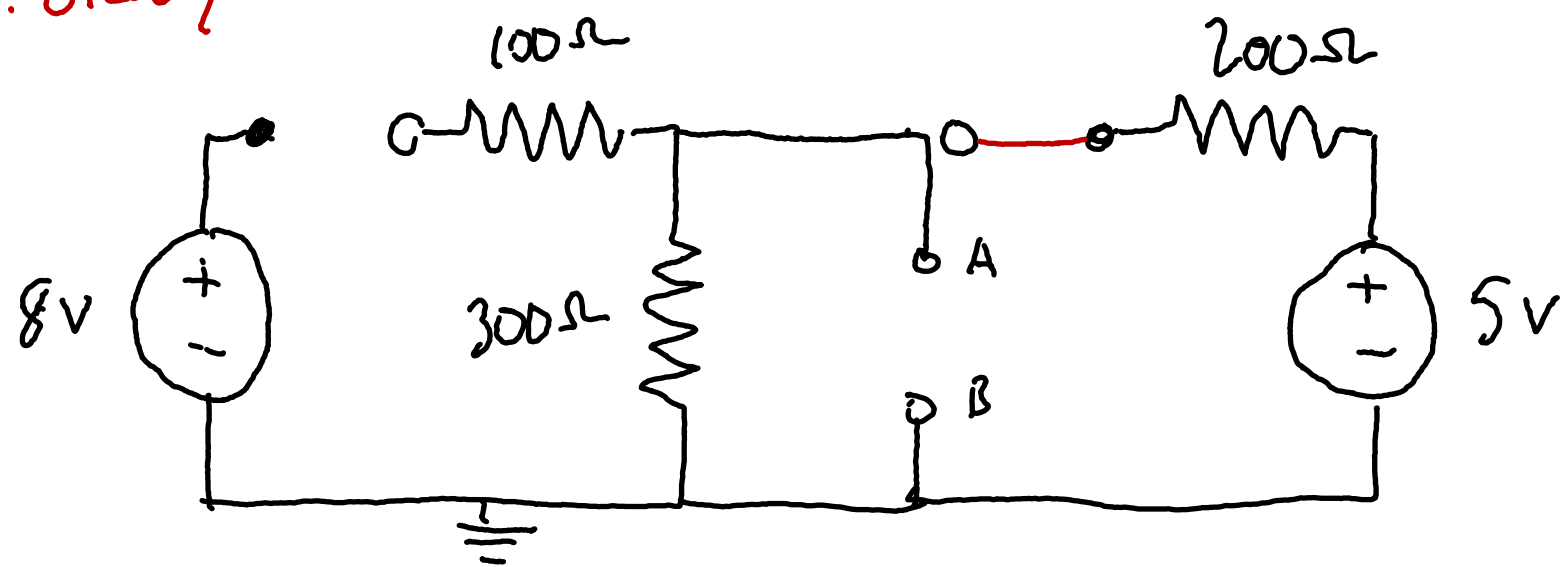

Voltage Division

$$V_c(\infty) = \frac{300}{400} \cdot 8 = 6V$$

## 3. Transient Response


$$V_c(t) = V_c(\infty) + [V_c(0) - V_c(\infty)] e^{-\frac{t}{RC}}$$

Find Thevenin Resistance

$$= 6 + [3 - 6] e^{-1333.33t}$$

$$= 6 - 3e^{-1333.33t}$$
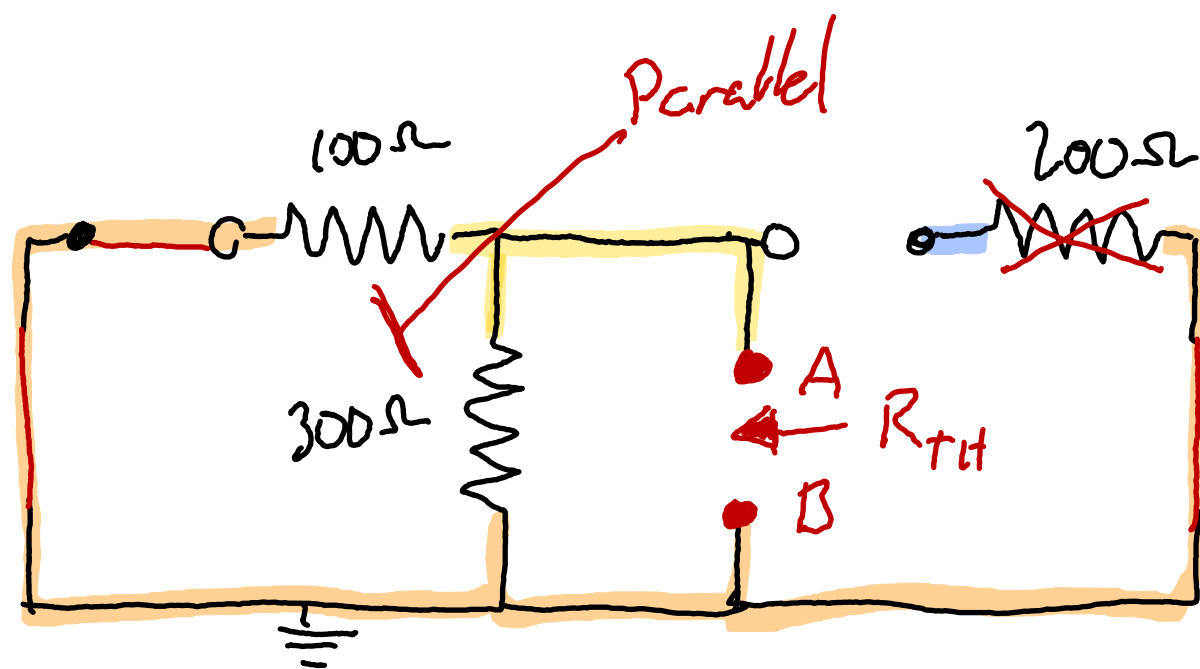
$$\frac{1}{RC} = \frac{1}{75(10^{-6})} = 1333.33$$



$$R_{TH} = 100 \parallel 300 = \frac{100(300)}{400} = \frac{300}{4} = 75\Omega$$




THE OHIO STATE UNIVERSITY

COLLEGE OF ENGINEERING
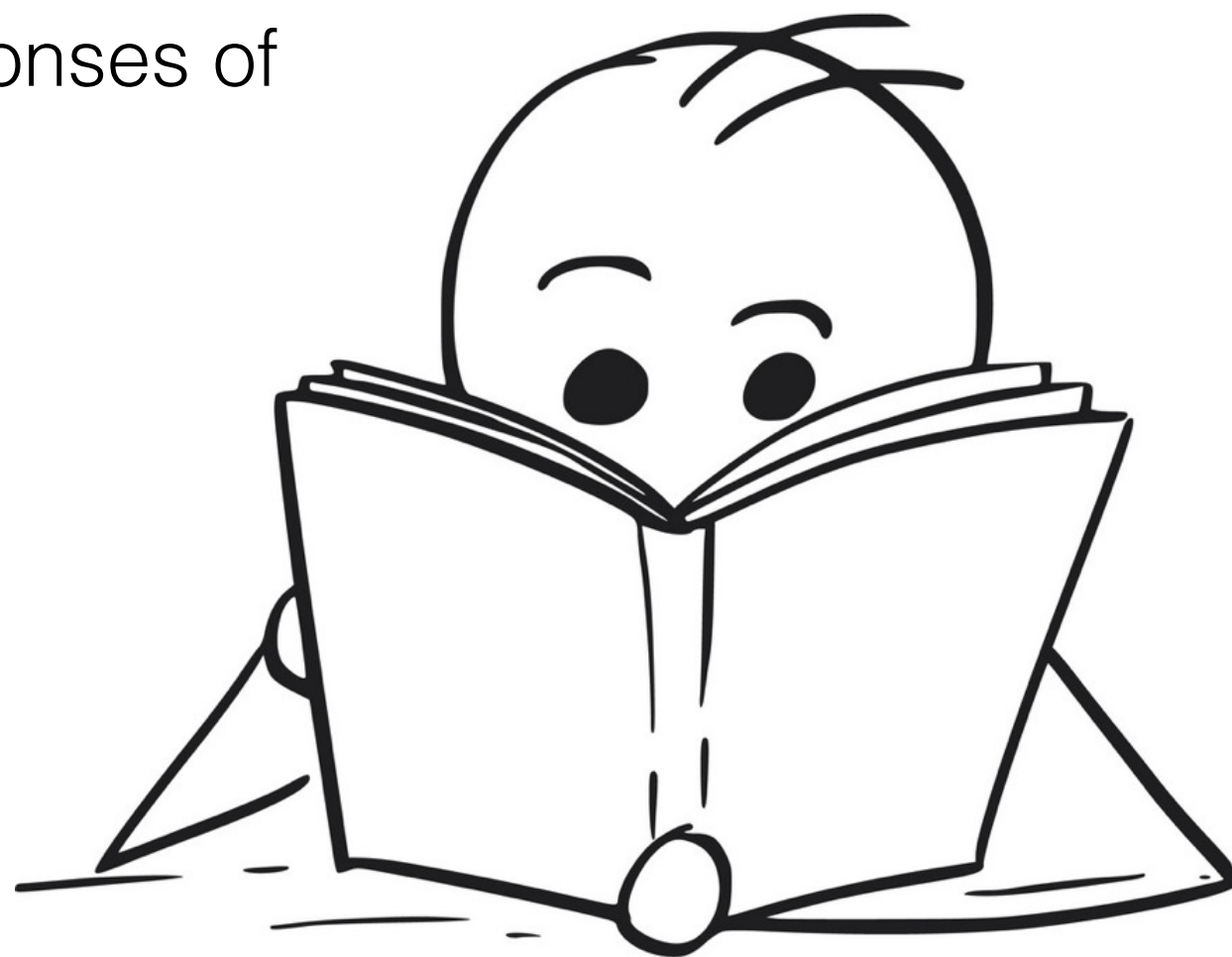
# Transient Response of $RL$ Circuits





- Learning Objectives:
  - Analyze the transient responses of first order *RL* circuits.






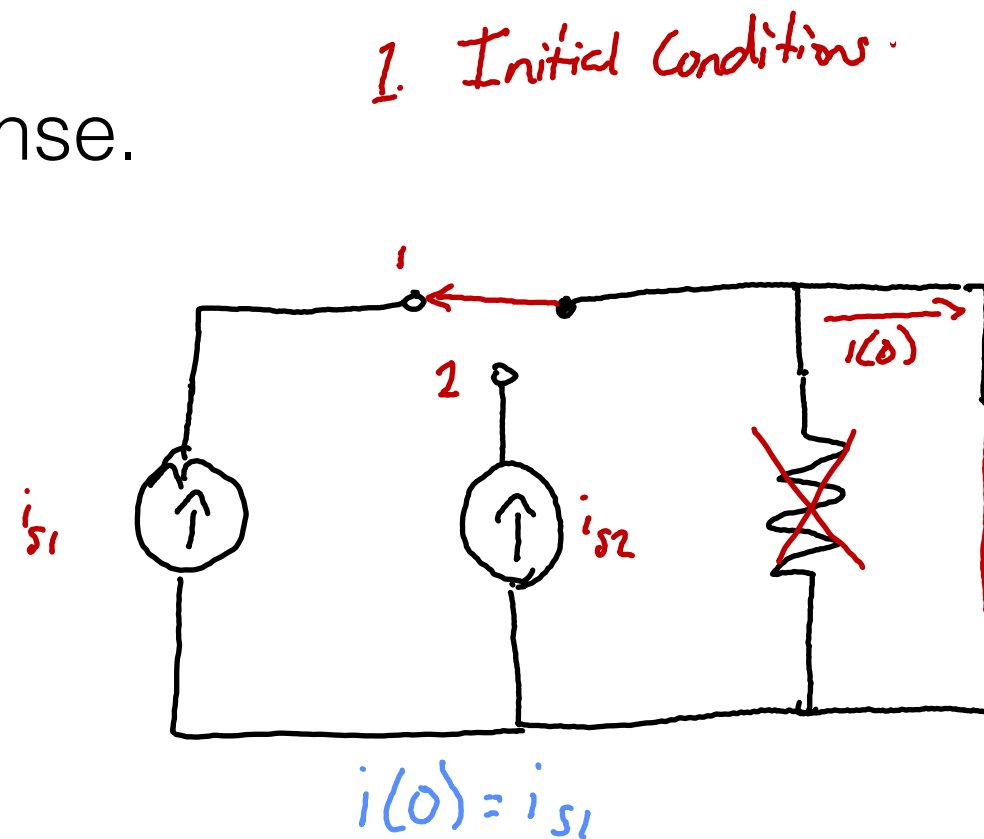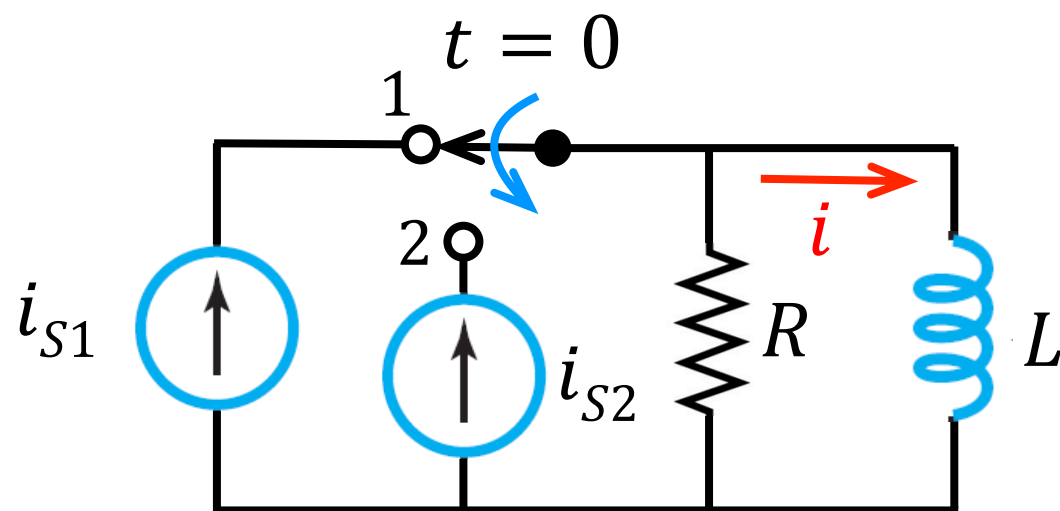1. Calculate the initial value of the inductor  $i_L(0)$  (e.g., when switch at 1).
2. Calculate the steady-state response of the inductor  $i_L(\infty)$  (e.g., when switch at 2).
3. Solve for transient response.




## 2. Steady State

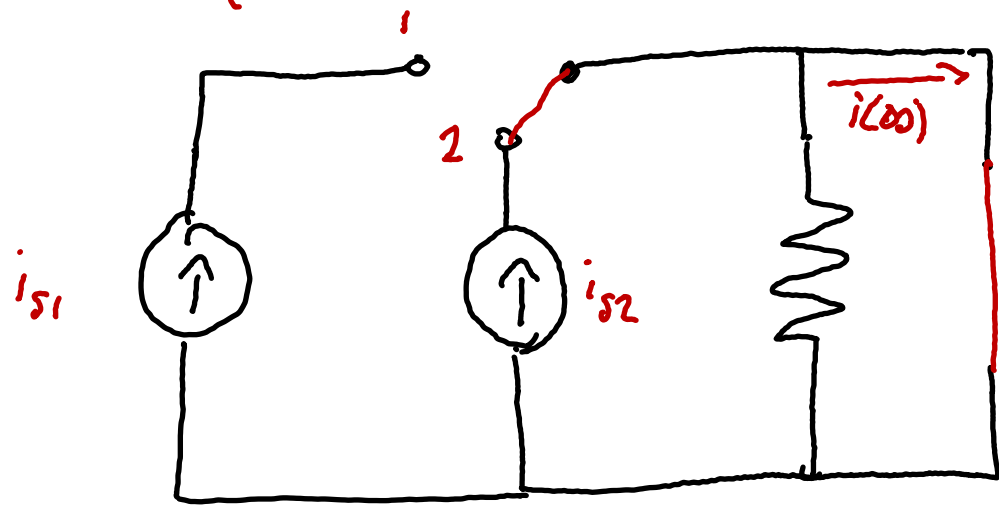

$$i(\infty) = i_{s2}$$

## 3. Transient Response

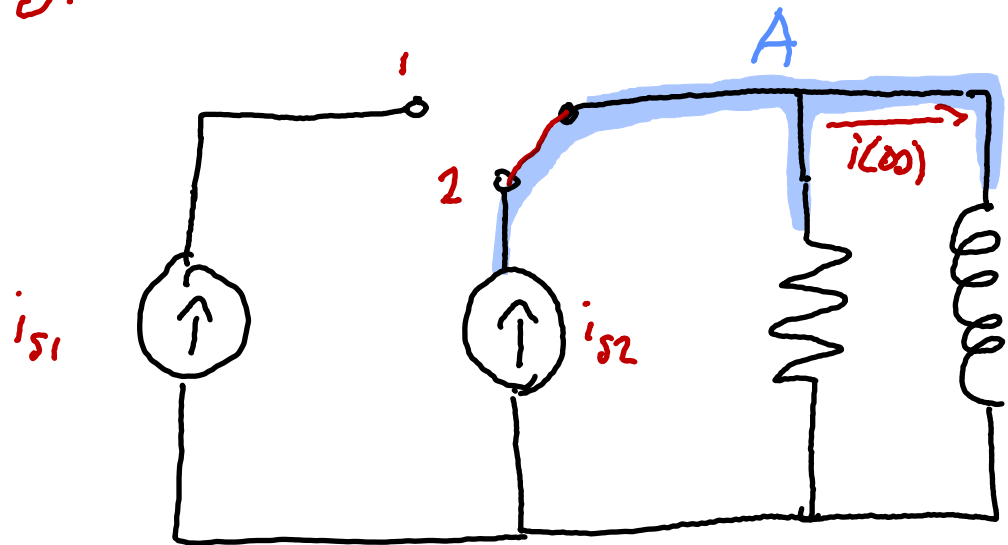

KCL @ A

$$i_{s2} = i_R + i_L$$

$$i_L(\infty) = \frac{V_R}{R} + i_L$$

$$i_L(\infty) = \frac{L}{R} \frac{di_L(t)}{dt} + i_L(t)$$



1st order diff eq.

Solution on next slide

Find Norton equivalent resistance  
if inductor is the load



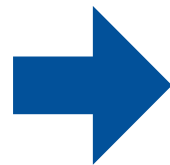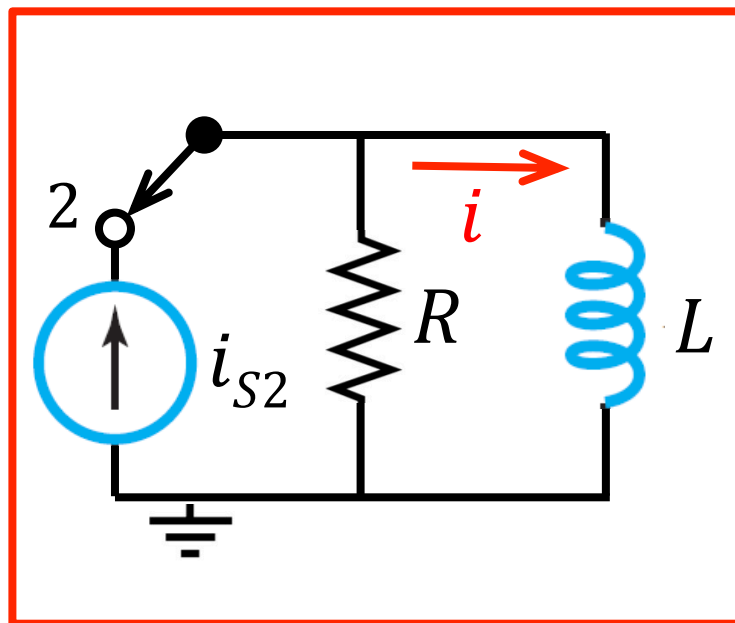
Norton equivalent circuit  
with  $L$  as the load.



Replace  $R$  with  $R_N$

$$i_L(t) = \underbrace{i_L(\infty)}_{(2)} + (\underbrace{i_L(0)}_{(1)} - \underbrace{i_L(\infty)}_{(2)}) e^{-\frac{R}{L}t}$$

$\frac{1}{RL}$  with capacitor

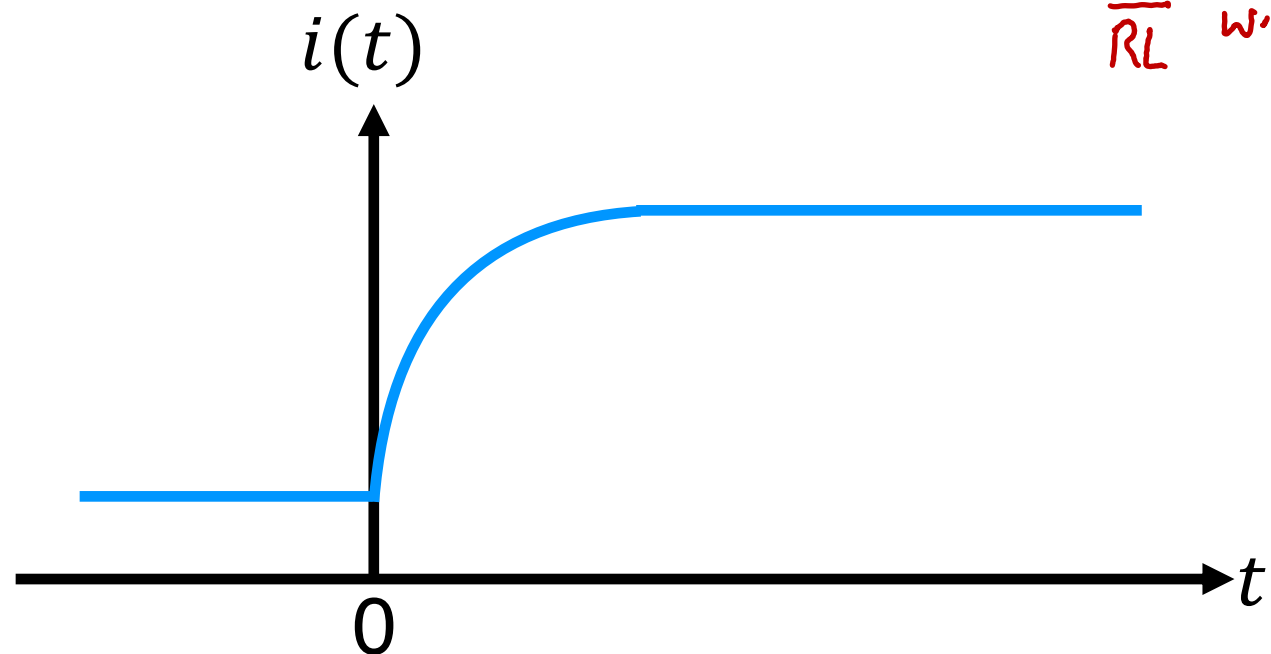


What if the circuit does  
not look like this?


How do we calculate  
the transient response?



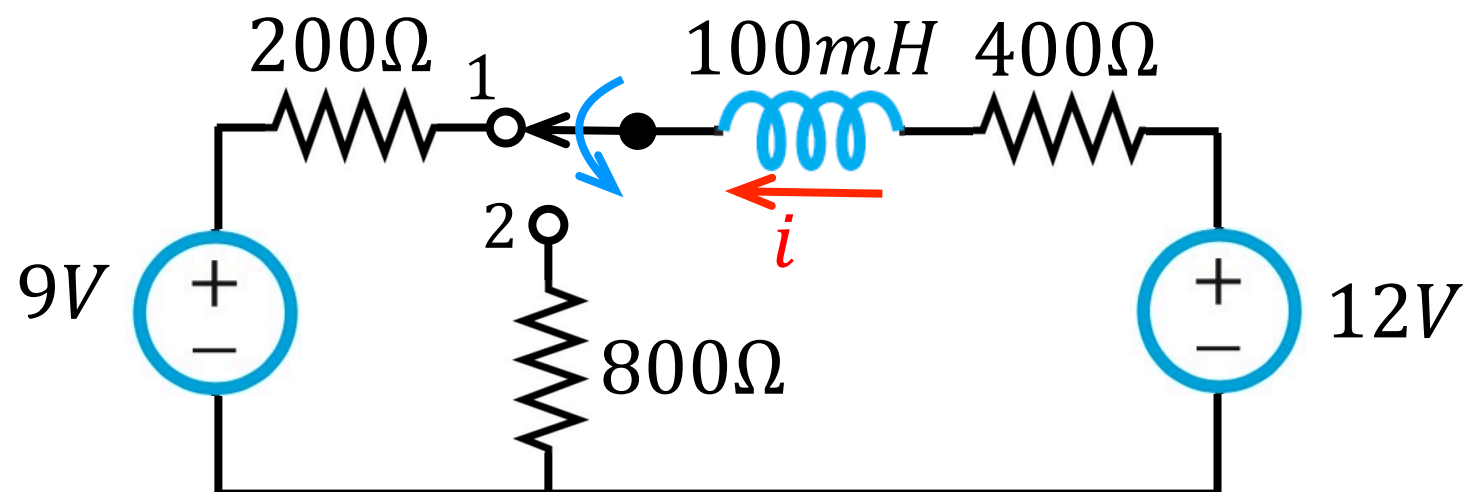“For a long time” before  $t = 0$ , switch at 1. At  $t = 0$ , switch at 2. Find  $i_L(t)$ , for  $t \geq 0$ .




1. Initial Condition

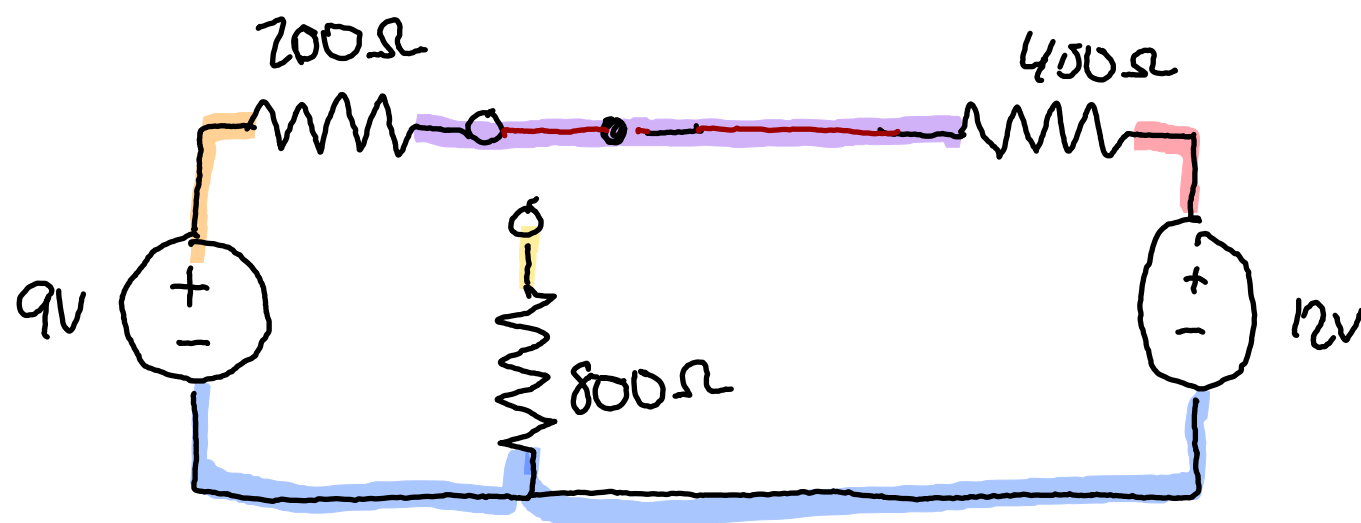

$$i_L(\infty) = \frac{600}{100} \cdot 21 = 86 \text{ A}$$



## 2. Steady State

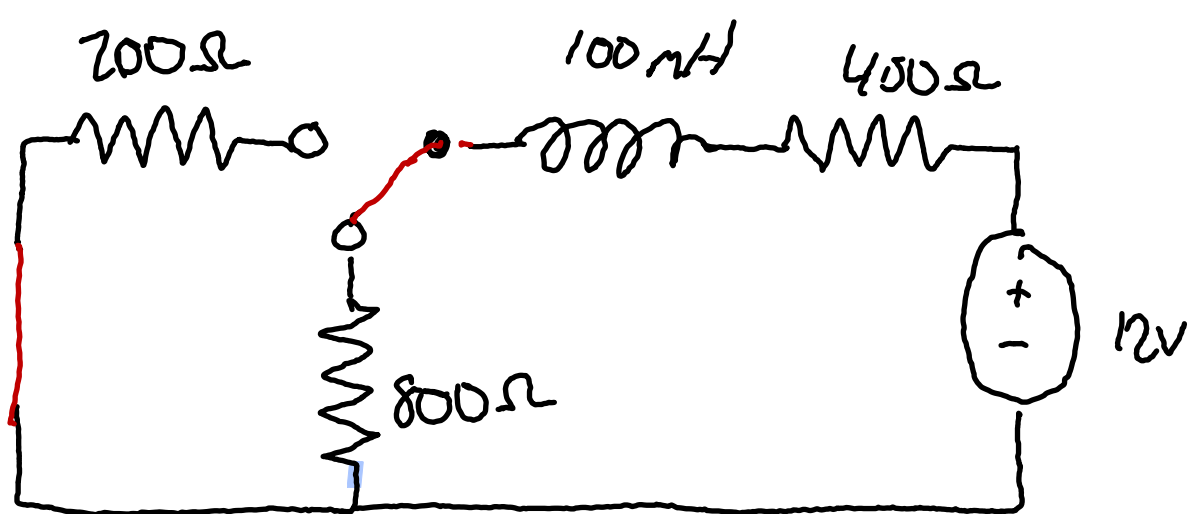



After having been in position 1 for a long time, the switch in the circuit was moved to position 2 at  $t = 0$ . Determine:

- A.  $i_L(0)$
- B.  $i_L(\infty)$
- C.  $i_L(t)$  for  $t \geq 0$
- D.  $v_L(t)$  for  $t \geq 0$

