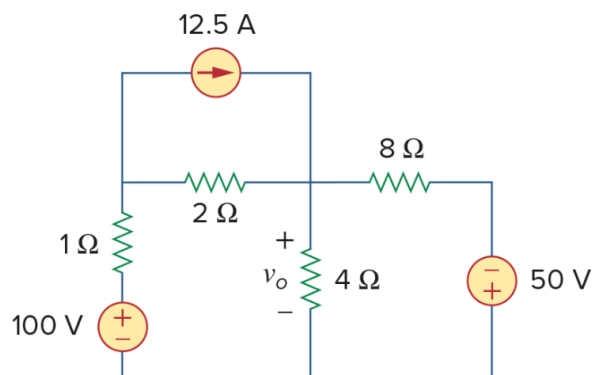



**Homework 3**  
**Due: Friday, February 10th, 2023 by 7PM.**

**Note: In order to receive full credit, you must show your work and carefully justify your answers. The correct answer without any work will receive little or no credit.**

1. Use mesh current analysis to find the voltage  $v_o$  across the  $4\Omega$  resistor.



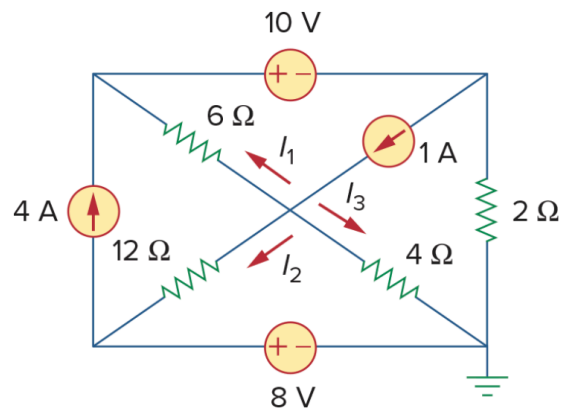2. Use either node-voltage or mesh-current analysis to find the current across the  $6\Omega$ ,  $4\Omega$ , and  $12\Omega$  resistors.



3. Using the principle of superposition:
- A. Find the contribution of the 12V voltage source to the voltage across the  $5\Omega$  resistor.
  - B. Find the contribution of the 19V voltage source to the voltage across the  $5\Omega$  resistor.
  - C. Find the contribution of the 2A current source to the voltage across the  $5\Omega$  resistor.

