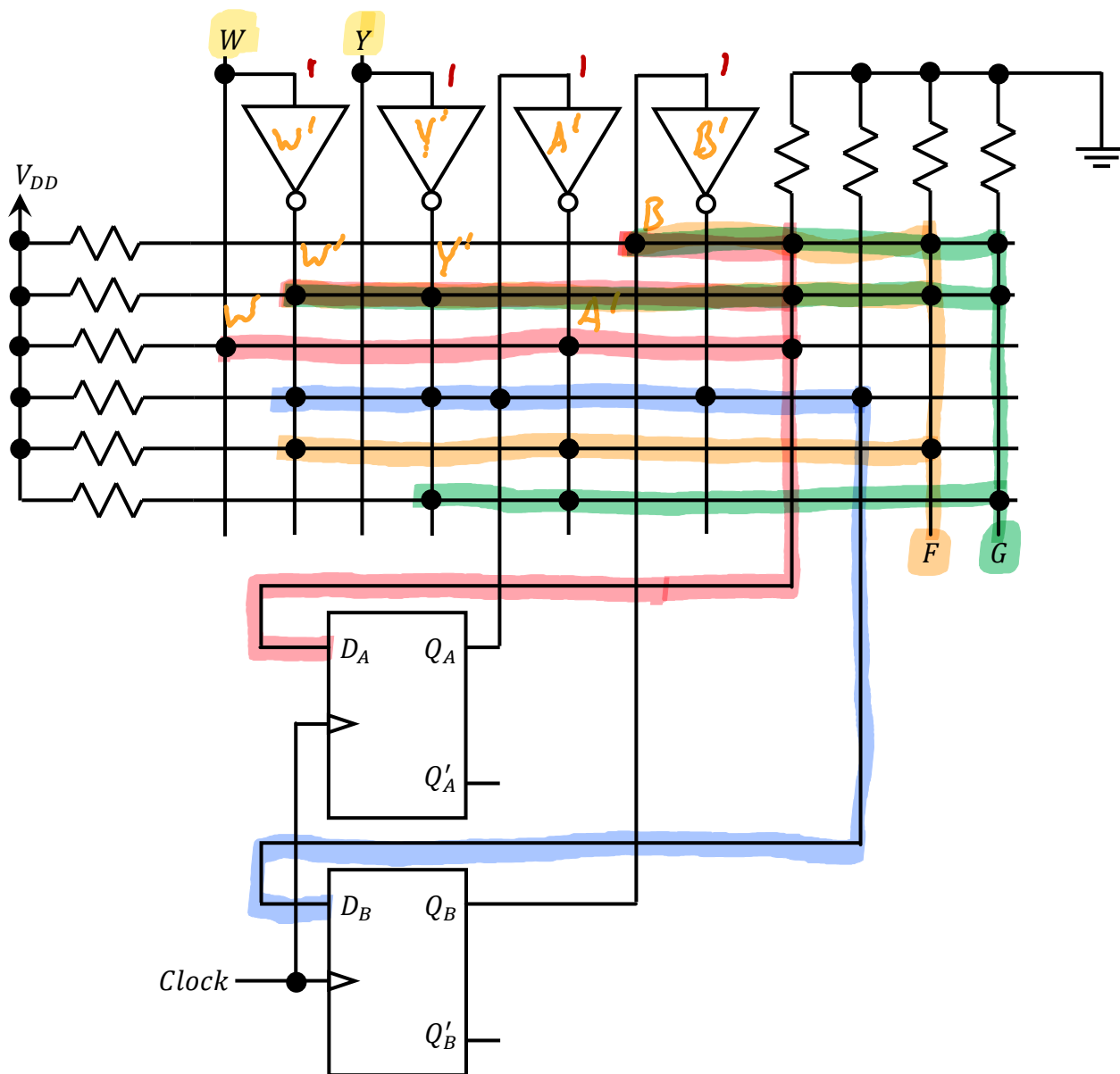


This is a 15 point problem



- What type of state machine is this? Moore Machine? Mealy Machine?
- Determine the Boolean expressions implemented by the PLA for the flip-flop inputs (D_A and D_B) and circuit outputs (F and G). All expressions should be in terms of the circuit inputs (W and Y) and flip-flop outputs ($A = Q_A$, $B = Q_B$). [For example, $D_A(W, Y, A, B) = \dots$]
- Determine the Next-State Maps for both flip-flops and the Output Maps for both outputs. [total of four maps].
- Determine the Transition Table for the state machine.
- Using the following state definitions, determine the State Table.
 S_0 ($AB = 00$), S_1 ($AB = 01$), S_2 ($AB = 10$), S_3 ($AB = 11$)
- Draw the properly formatted State Graph.
- Comment on what is unusual about state S_1 .

b)

		WY			
A	B	00	01	11	10
	00	1		1	1
	01	1	1	1	1
	11	1	1	1	1
	10	1			

$$D_A(W, Y, A, B) = 0, 1, 2, 3, 5, 7, 8, 9, 11, 12, 13, 15$$

$$D_B(W, Y, A, B) = 2$$

c)

Present State (D_A)	Inputs (WYB)	Next state (D_A^+)
0	000	1
0	001	1
0	010	0
0	011	1
0	100	1
0	101	1
0	110	1
0	111	1
1	000	1
1	001	1
1	010	0
1	011	1
1	100	0
1	101	1
1	110	0
1	111	1

Present State (D_B)	Inputs (WYA)	Next state (D_B^+)
0	000	0
0	001	1
0	010	0
0	011	0
0	100	0
0	101	0
0	110	0
0	111	0
1	000	0
1	001	0
1	010	0
1	011	0
1	100	0
1	101	0
1	110	0
1	111	0

F

WY AB	00	01	11	10
00	1	1	0	0
01	1	1	1	1
11	1	1	1	1
10	1	0	0	0

G

WY AB	00	01	11	10
00	1	0	0	1
01	1	1	1	1
11	1	1	1	1
10	1	0	0	0

d) e?)

Input	WY = 00		WY = 01		WY = 10		WY = 11	
Present State	Next State	Output (FG)	Next State	Output (FG)	Next State	Output (FG)	Next State	Output (FG)
S ₀	S ₂	11	S ₀	10	S ₂	01	S ₂	00
S ₁	S ₂	11	S ₂	11	S ₂	11	S ₂	11
S ₂	S ₃	11	S ₀	00	S ₀	00	S ₀	00
S ₃	S ₂	11	S ₂	11	S ₂	11	S ₂	11

$$S_0 = 00$$

$$S_1 = 01$$


$$S_2 = 10$$

$$S_3 = 11$$

f)

$$S = AB$$
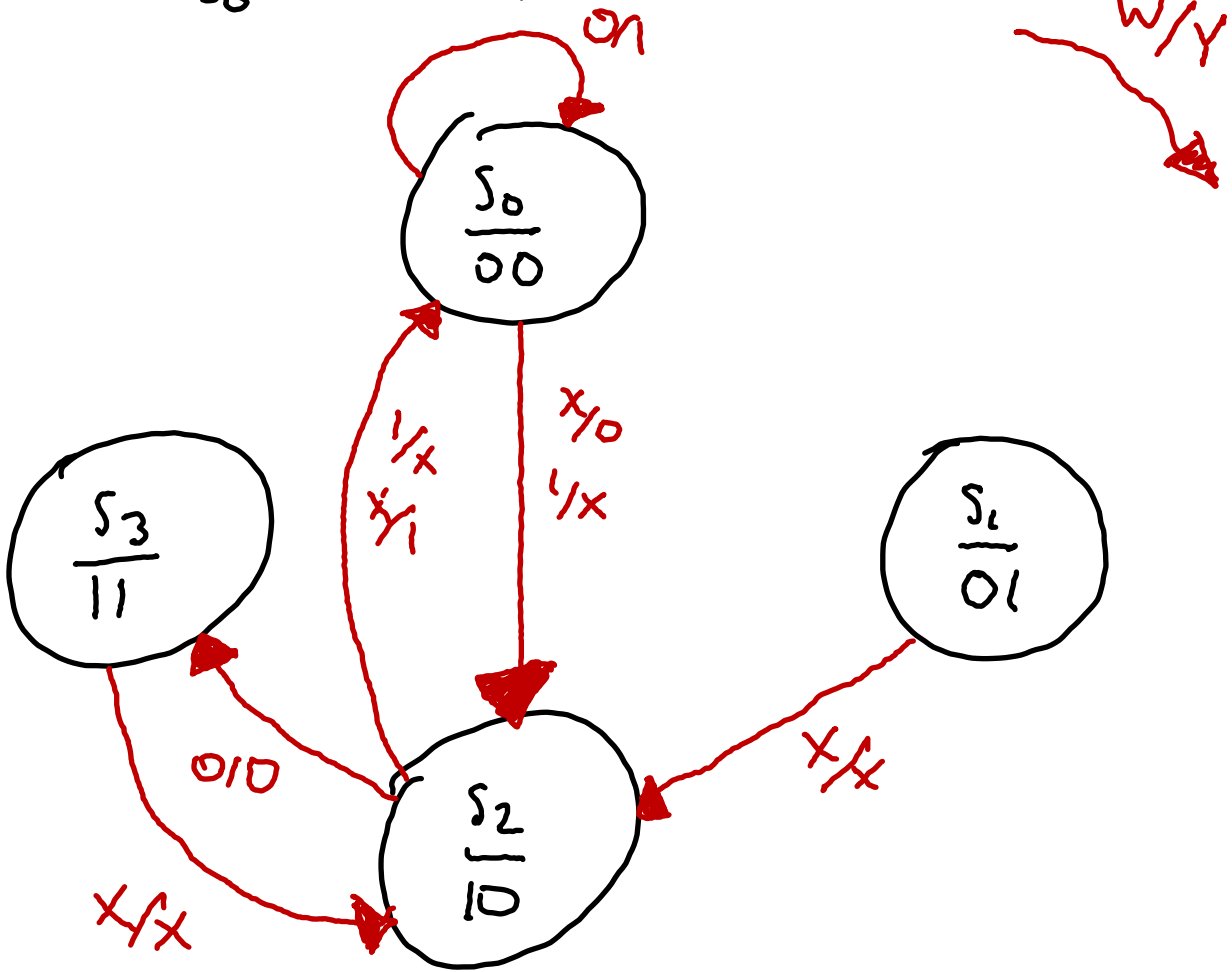
$$S_0 = 00 \quad S_1 = 01 \quad S_2 = 10 \quad S_3 = 11$$



g)

State S_1 is unusual because there is no way to intentionally reach it.