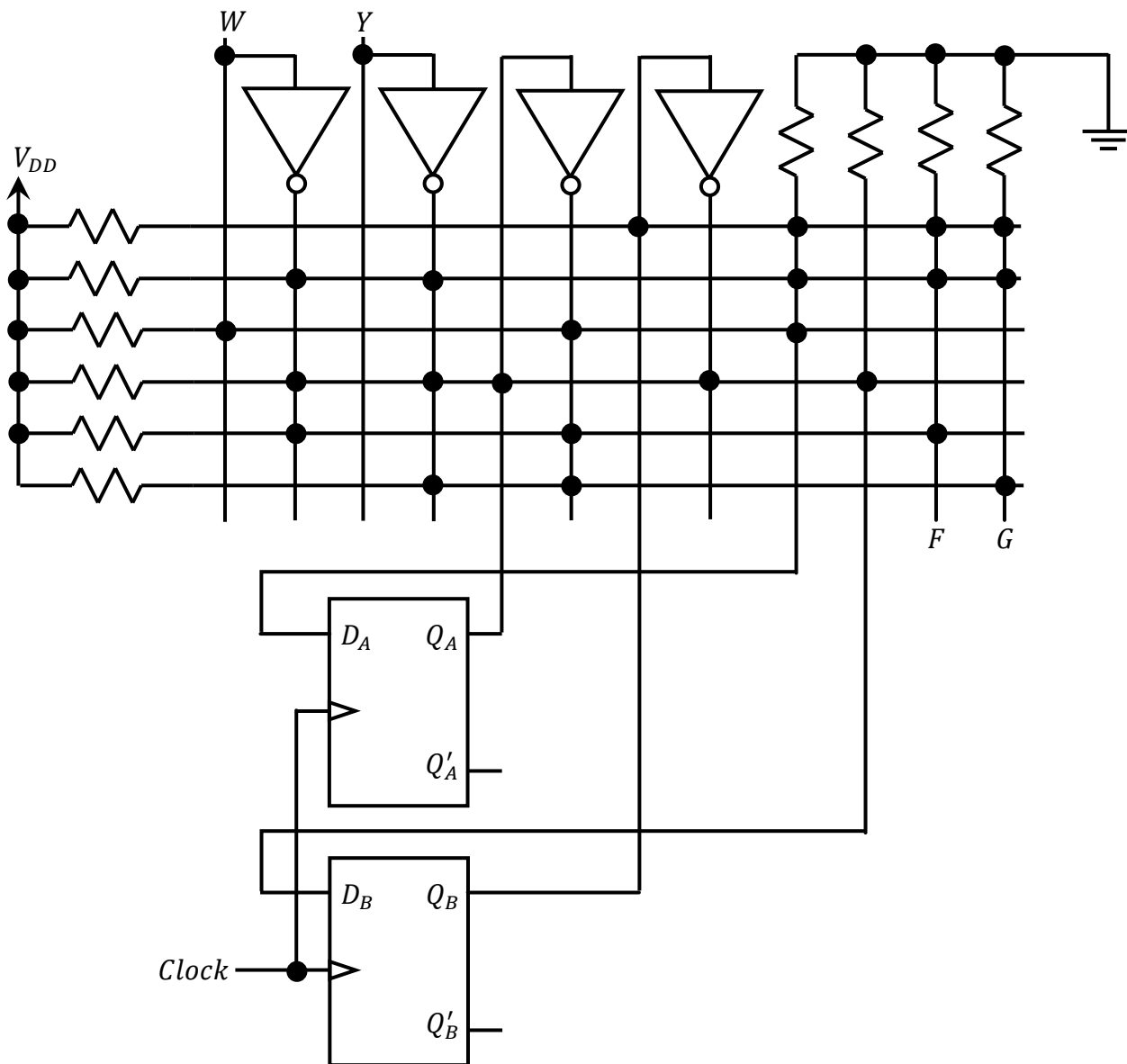


This is a 15 point problem



- What type of state machine is this? Moore Machine? Mealy Machine?
- Determine the Boolean expressions implemented by the PLA for the flip-flop inputs (D_A and D_B) and circuit outputs (F and G). All expressions should be in terms of the circuit inputs (W and Y) and flip-flop outputs ($A = Q_A$, $B = Q_B$). [For example, $D_A(W, Y, A, B) = \dots$]
- Determine the Next-State Maps for both flip-flops and the Output Maps for both outputs. [total of four maps].
- Determine the Transition Table for the state machine.
- Using the following state definitions, determine the State Table.
 S_0 ($AB = 00$), S_1 ($AB = 01$), S_2 ($AB = 10$), S_3 ($AB = 11$)
- Draw the properly formatted State Graph.
- Comment on what is unusual about state S_1 .

$$b) D_A(W, Y, A, B) =$$