



THE OHIO STATE UNIVERSITY

---

COLLEGE OF ENGINEERING

ECE 3561

Advanced Digital Design




Class 01: Review: Logic Gates and De Morgan's Laws

Drew Phillips

Spring 2024



# Review: AND, OR, and NOT Gates

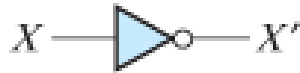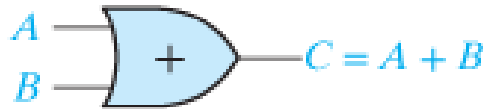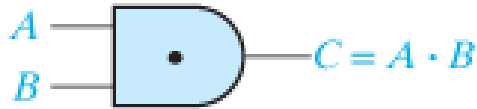

$X' = \bar{X}$  means the inverse of  $X$




# Review: NAND and NOR Gates






# Review: XOR and XNOR Gates

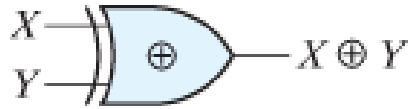

$$A \oplus B = A\bar{B} + \bar{A}B$$

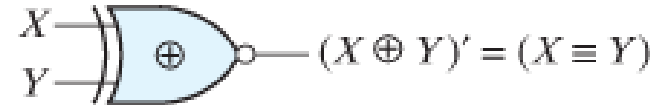


$$\overline{A \oplus B} = A \oplus \bar{B} = \bar{A} \oplus B$$



# Review: More About XOR Gate


**XOR**  
**(Exclusive OR)**

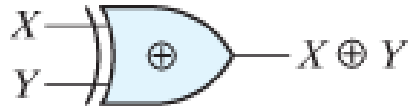

$$A \oplus B = A\bar{B} + \bar{A}B$$

Inputs		Output
A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

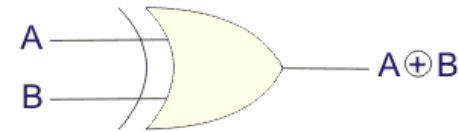Modulo-2 sum of two Boolean variables A, B



$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 0 \rightarrow \text{Carry } 1$$

**How can the logic of an inverter be implemented by using an XOR gate?**




# Review: De Morgan's Laws

$$(X + Y)' = X'Y'$$

$$(XY)' = X' + Y'$$

Move the inversion bubble around:

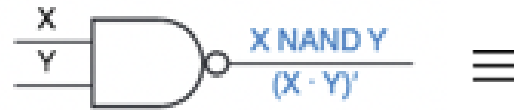

**How can Boolean functions be realized by 2-input NAND gates? (Example on next slide.)**




# Example 1

1.1 Realize the following functions, using only two-input NAND gates.

$$F = A'BC' + BD + AC + B'CD'$$

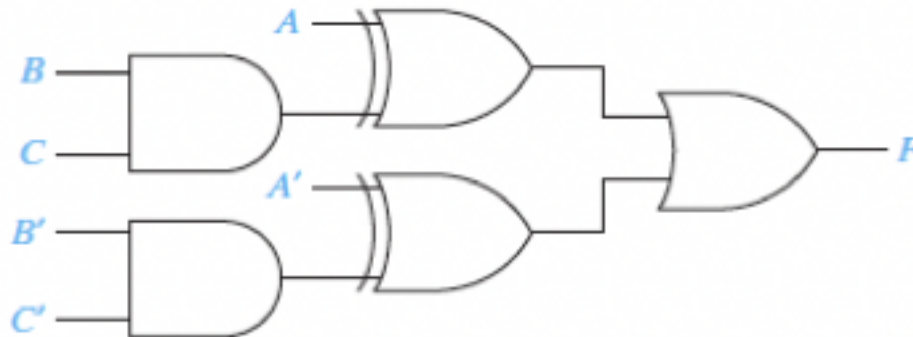1.2 Use gate conversions to convert the circuit below into one containing NAND and XOR gates.





# 1.1 Solution





**THE OHIO STATE UNIVERSITY**

COLLEGE OF ENGINEERING

Department of Electrical and Computer Engineering  
ECE 3561 Advanced Digital Design

## 1.2 Solution



**THE OHIO STATE UNIVERSITY**

COLLEGE OF ENGINEERING

Department of Electrical and Computer Engineering  
ECE 3561 Advanced Digital Design

# Questions?