
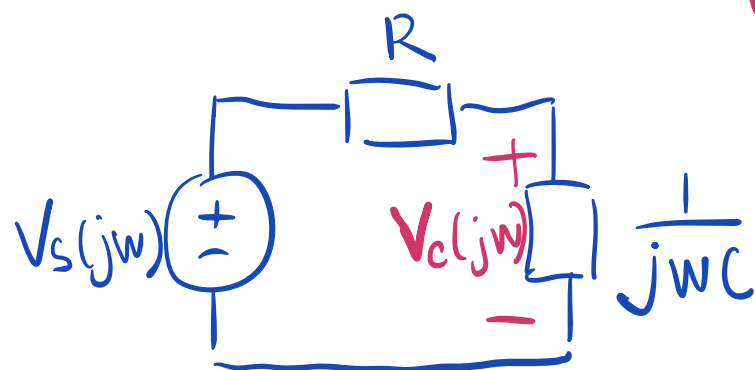


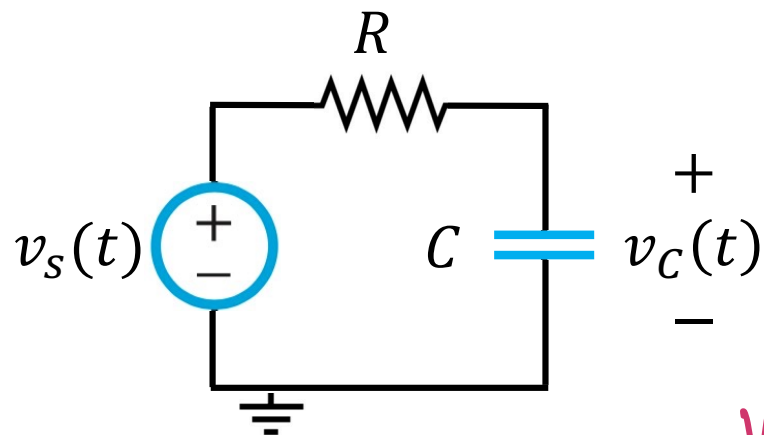

Find $V_c(j\omega)$



Voltage Division

$$V_c(j\omega) = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \cdot V_s(j\omega)$$
$$= \frac{1}{j\omega CR + 1} V_s(j\omega)$$





THE OHIO STATE UNIVERSITY

COLLEGE OF ENGINEERING


Transfer Functions

NO CLASS ON MONDAY,
MARCH 20TH





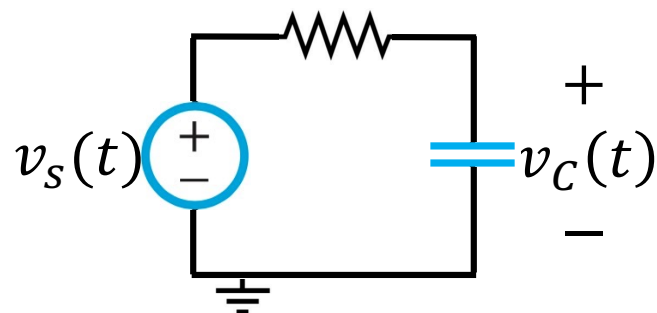- Learning Objectives:
 - Derive the transfer function of an AC Circuit.






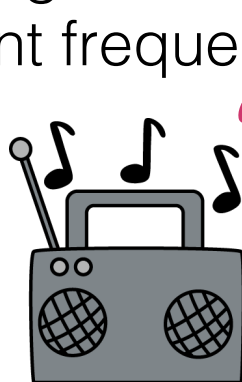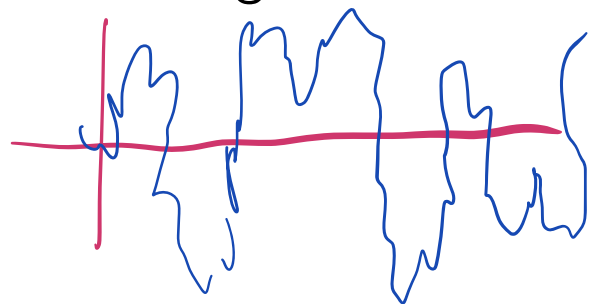
- Often, the input signal is a superposition of many sinusoidal signals at different frequencies.



97.9

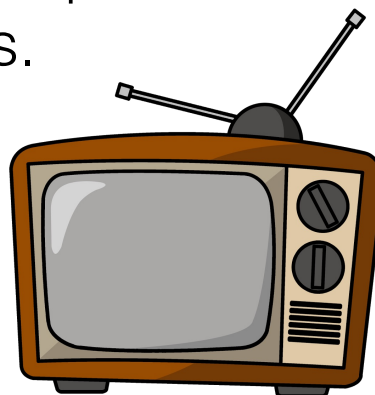

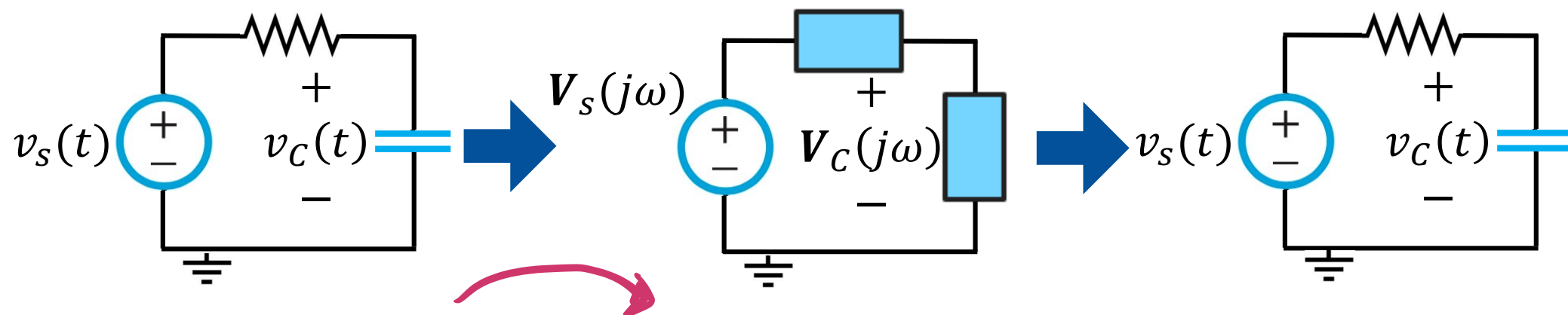- How to design RLC circuits that can **filter in** (pass through) the range of frequencies of interest and **filter out** (reject) the range of frequencies of signals that are either problematic or not of interest.



$$v_s(t) = A \cos(\omega t + \theta)$$

INPUT

$$V_s(j\omega) = A \angle \theta$$



$$V_C(j\omega) = B \angle \alpha$$

OUTPUT


$$v_C(t) = B \cos(\omega t + \alpha)$$

$$B = |p| A$$

- At a given angular frequency ω :
 - Load voltage is a sinusoid with the same frequency as the source voltage.
- $V_C(j\omega)$ is a phase-shifted and amplitude-scaled version of $V(j\omega)$.



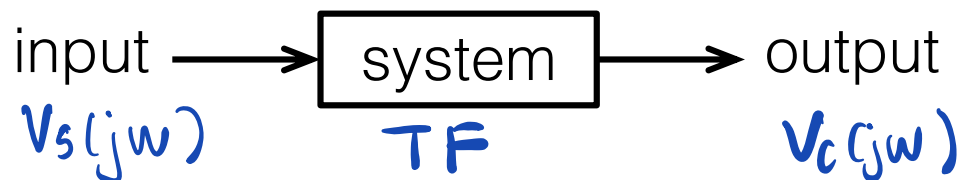- **Frequency Response:** Measures how circuit responds to sinusoidal inputs of arbitrary frequency.



- **Transfer function:** describes the output response to an input excitation as a function of the angular frequency ω .

$$TF = \frac{\text{output}}{\text{input}} = \frac{V_c(j\omega)}{V_s(j\omega)}$$

$$\text{output} = TF \cdot \text{input}$$

For example:

$$TF = 200 \angle 45^\circ$$

$$\text{input} = 10 \cos(100t - 15^\circ)$$



$$\text{output} = (200 \angle 45^\circ) \cdot (10 \angle -15^\circ)$$

$$= 2000 \angle 30^\circ$$

$$= 2000 \cos(100t + 30^\circ)$$



Voltage Gain:

$$H_V = \frac{V_{out}}{V_{in}}$$

Transfer Impedance:

$$H_Z = \frac{V_{out}}{I_{in}}$$


Current Gain:

$$H_I = \frac{I_{out}}{I_{in}}$$

Transfer Admittance:

$$H_Y = \frac{I_{out}}{V_{in}}$$

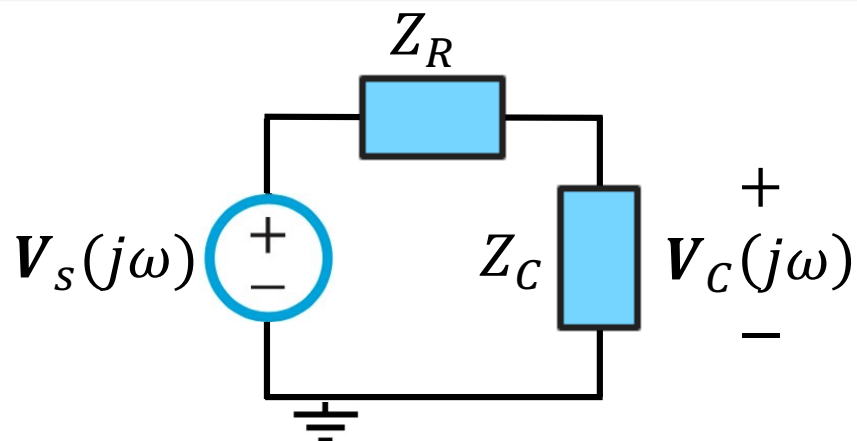- V_{in} and I_{in} are often chosen to be independent voltage and current sources.
- Outputs V_{out} and I_{out} are freely chosen and represent the load in a circuit.



Same as first slide.

$$V_C(j\omega) = \frac{1}{j\omega CR + 1} V_s(j\omega)$$

Find $\frac{V_C(j\omega)}{V_s(j\omega)} \leftarrow \text{output}$

$$\frac{V_C(j\omega)}{V_s(j\omega)} = \frac{1}{j\omega CR + 1}$$

How do I find the output?

$$V_C(j\omega) = ?$$

Denominator:


$$1 + j\omega \boxed{\text{ }} \text{ (crossed out)}$$

$$1 + j\omega \boxed{\text{ }} + (j\omega)^2 \boxed{\text{ }} \text{ (crossed out)}$$

$$\frac{V_c(j\omega)}{V_s(j\omega)} = \frac{1}{j\omega RC + 1} = M(\omega) \angle \theta(\omega)$$

$$= \frac{1 \angle 0}{\sqrt{1 + (\omega RC)^2} \angle \tan^{-1}(\omega RC)}$$
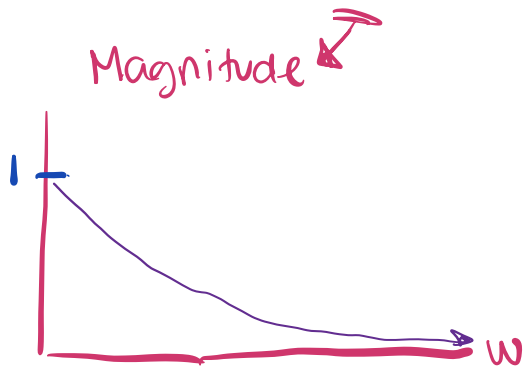
$$= \frac{1}{\sqrt{1 + (\omega RC)^2}} \angle -\tan^{-1}(\omega RC)$$




$$\lim_{\omega \rightarrow 0} M(\omega) = 1$$


$$\lim_{\omega \rightarrow \infty} M(\omega) = 0$$

$$\text{output} = \text{TF} \cdot \text{input}$$

LOW PASS FILTER

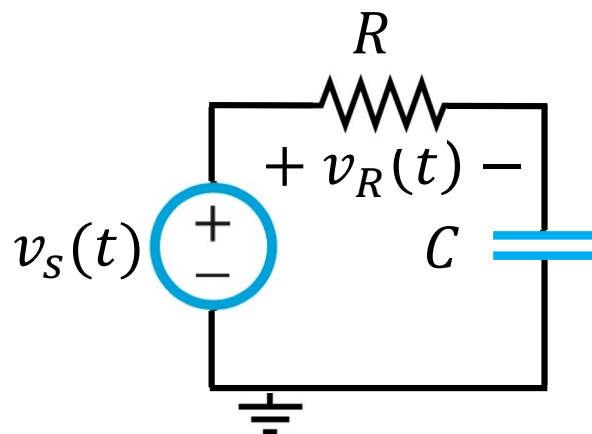

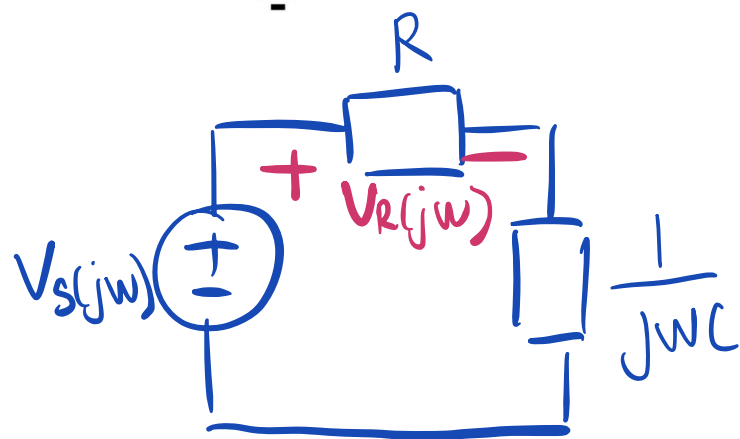Find $\frac{V_R(j\omega)}{V_S(j\omega)}$ ← output.



Voltage Division:


$$V_R(j\omega) = \frac{R}{R + \frac{1}{j\omega C}} \cdot V_S(j\omega)$$

$$\frac{V_R(j\omega)}{V_S(j\omega)} = \frac{j\omega CR}{j\omega CR + 1}$$

$$\frac{V_R(j\omega)}{V_S(j\omega)} = \frac{j\omega CR}{j\omega CR + 1}$$

$$= \frac{\omega CR \angle 90^\circ}{\sqrt{1 + (\omega CR)^2} \angle \tan^{-1}(\omega CR)}$$
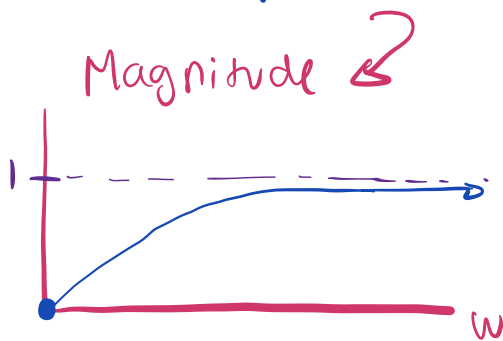
$$= \frac{\omega CR}{\sqrt{1 + (\omega CR)^2}} \angle 90 - \tan^{-1}(\omega CR)$$



$$\lim_{\omega \rightarrow 0} M(\omega) = 0$$

$$\lim_{\omega \rightarrow \infty} M(\omega) = 1$$

HIGH PASS FILTER