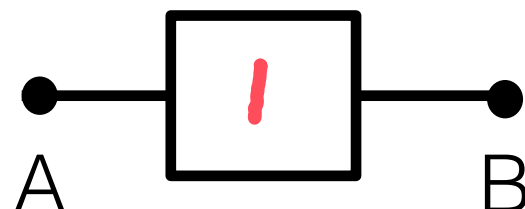





1. What is the relationship between the voltage across a component and the voltage on its nodes?

$$V_I = V_A - V_B$$



2. Will current flow across all of the element on the circuit below?

No

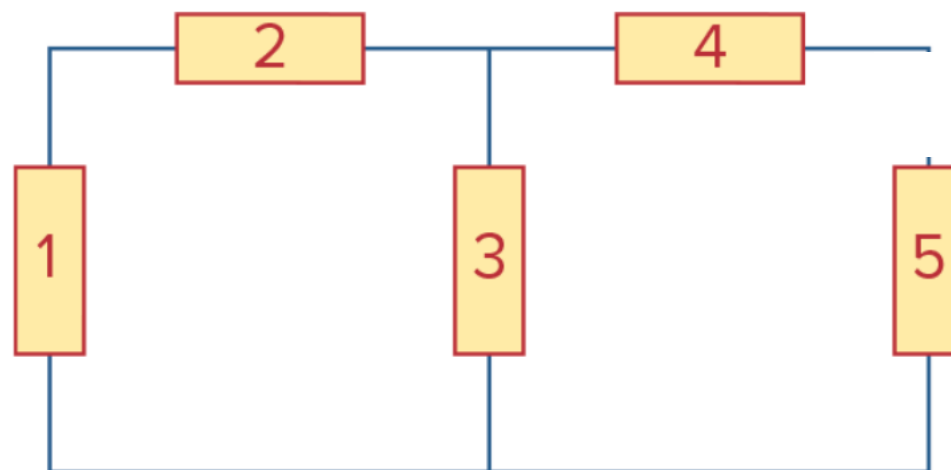



THE OHIO STATE UNIVERSITY


---

COLLEGE OF ENGINEERING

Power  
Kanye West





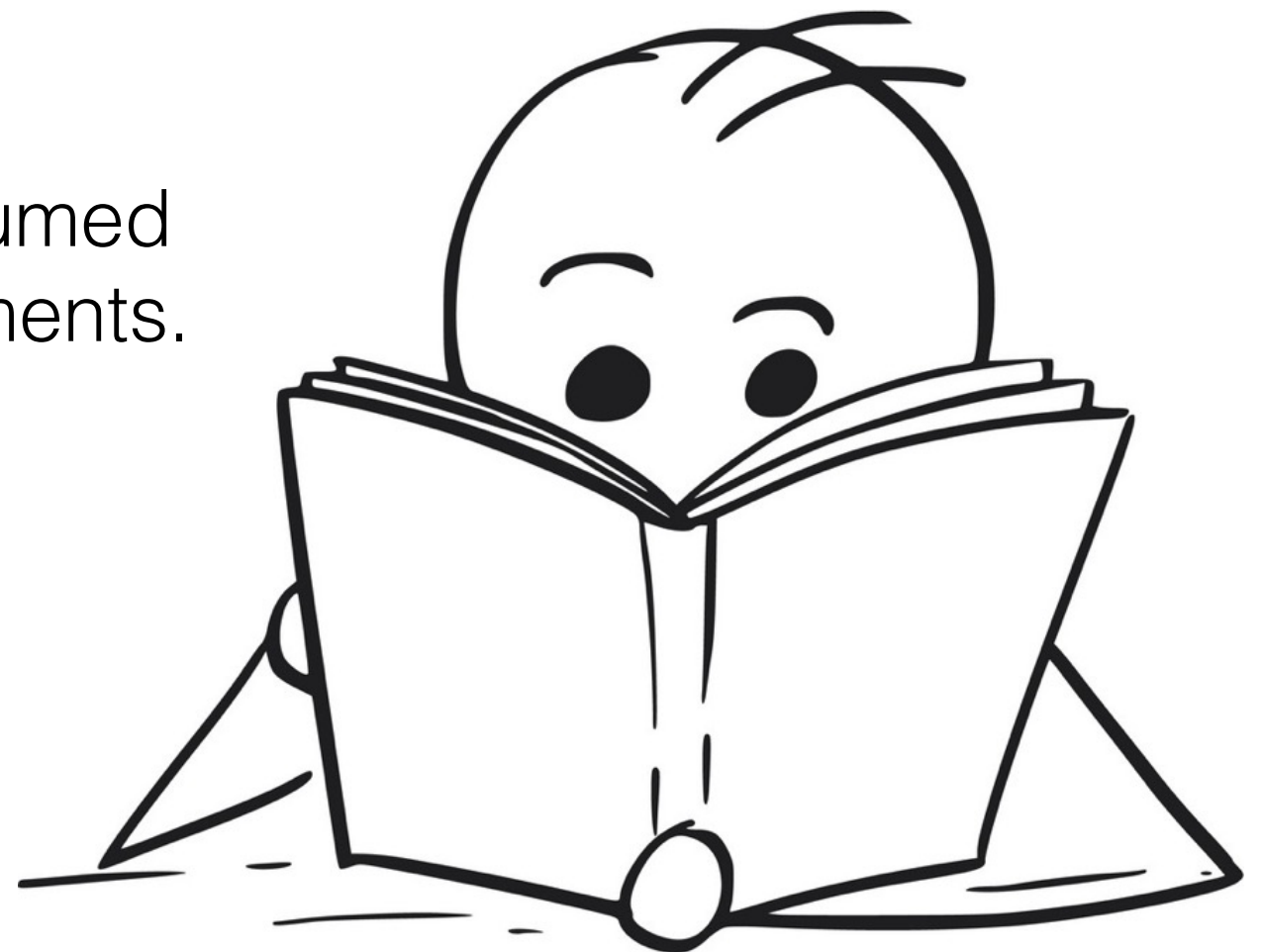
- Learning Objectives:
  - Identify voltage and current sources, ground, resistors, inductors, and capacitors in a circuit.
  - Understand what passive sign convention is.
  - Compute the power consumed or supplied by circuit elements.





# Independent Voltage Sources


- Constant Sources - DC

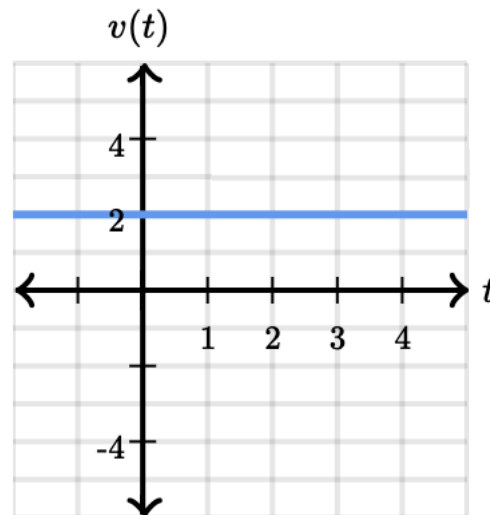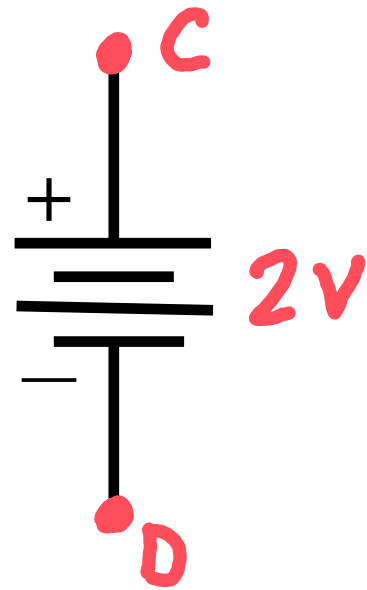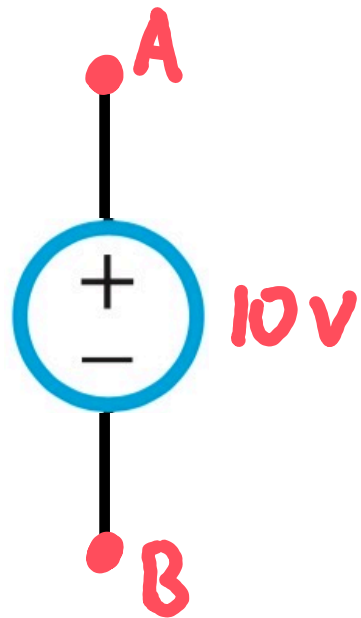

$$V_A - V_B = 10v$$

$$V_C - V_D = 2v$$


- Variable Sources - AC

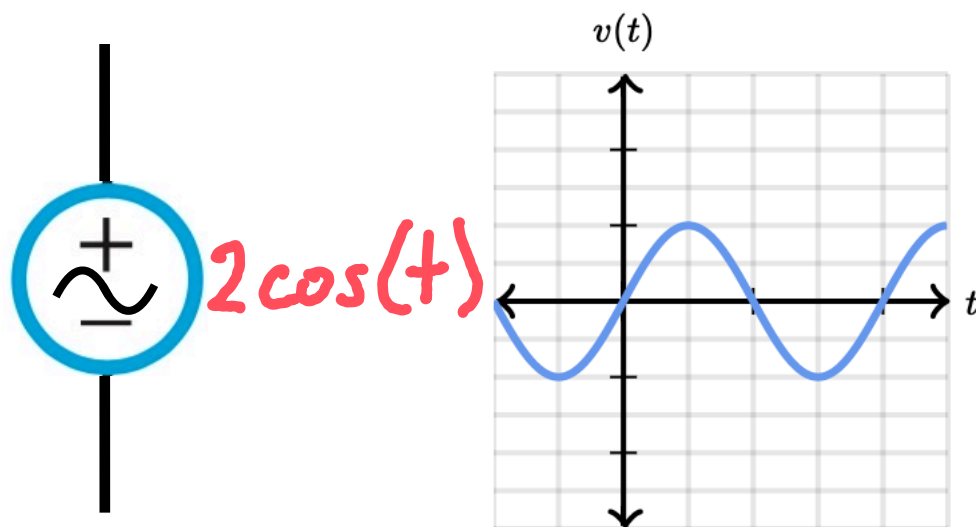

- independent of  $i$
- $i$  is determined by circuit




- Current Source

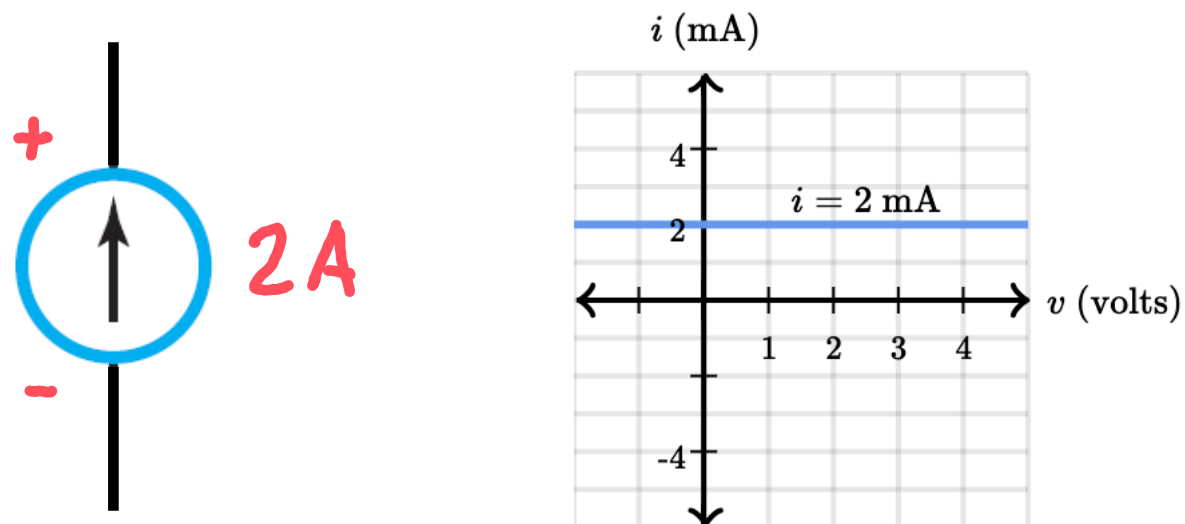

- independent of  $v$
- $v$  is determined by circuit


- Dependent Sources

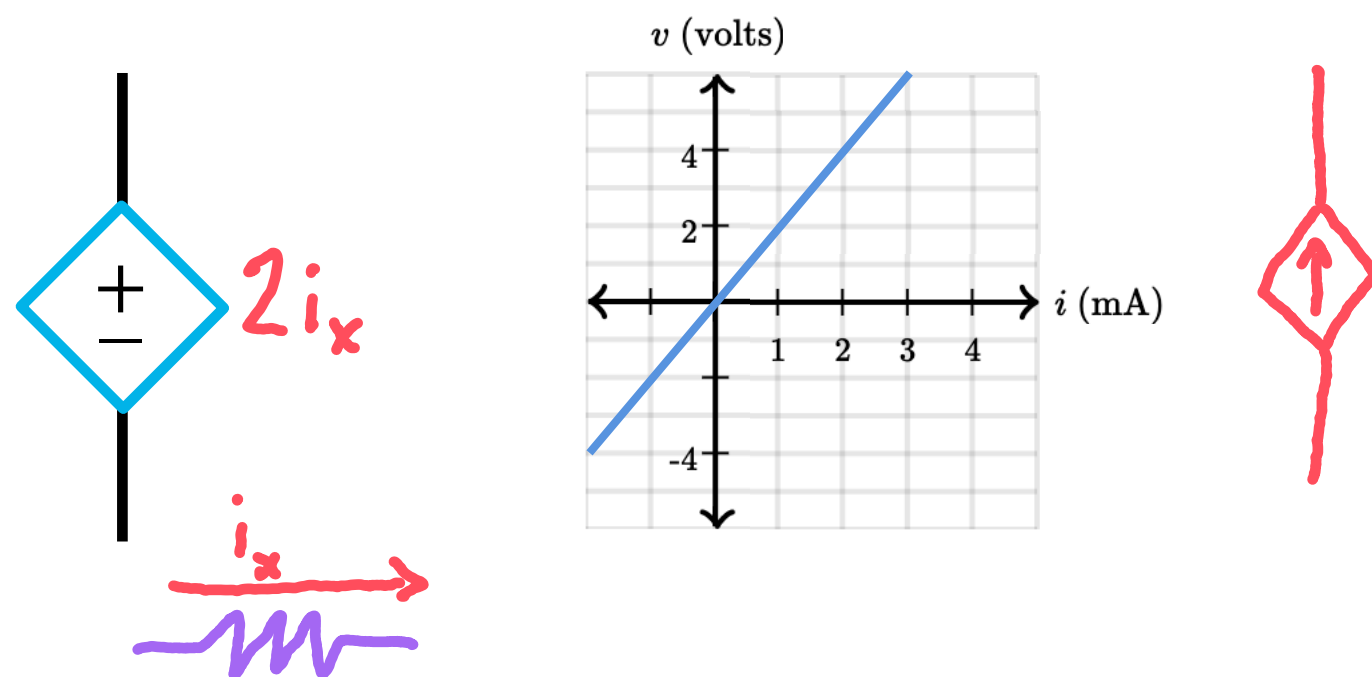


- dependent of some voltage or current
- used as a modeling tool.



- Ground  $V_G = 0_V$

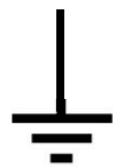

Earth

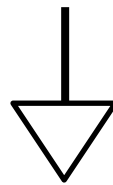


Common




Chassis

- Passive Elements

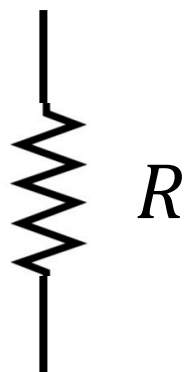

Resistor

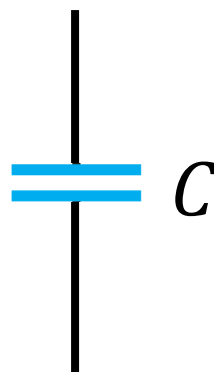

Capacitor



Inductor



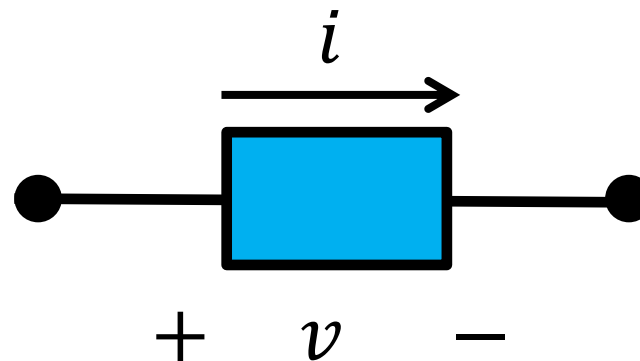
# Why do we need a Convention?




- **Passive elements** is an electrical component that does not generate power, but instead dissipates, stores, and/or releases it. E.g., resistors ( $R$ ), inductors ( $L$ ), capacitors ( $C$ ).
- **Passive components** have a defining equations that establish the relationship between voltage and current for each of them (e.g., Ohm's Law for resistor).
- Voltage polarity and current direction must be consistent with such laws for us to be able to apply them in circuit analysis.
- **Active elements** generate power so other elements can operate



- Passive Sign Convention states that current must flow from positive to negative potential (higher to lower).



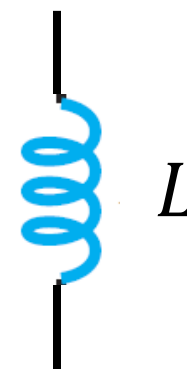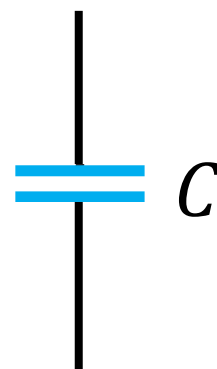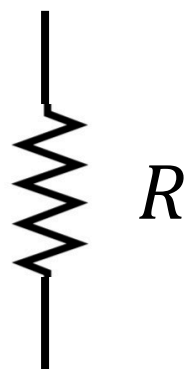
- How to apply Passive Sign Convention?
  1. Assign a current with arbitrary direction.
  2. Assign a voltage such that assigned current flows from high to low potential.








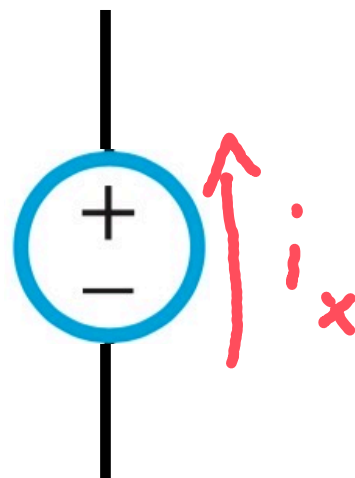- Voltage and current sources do not follow passive sign convention, they supply power to the circuit.



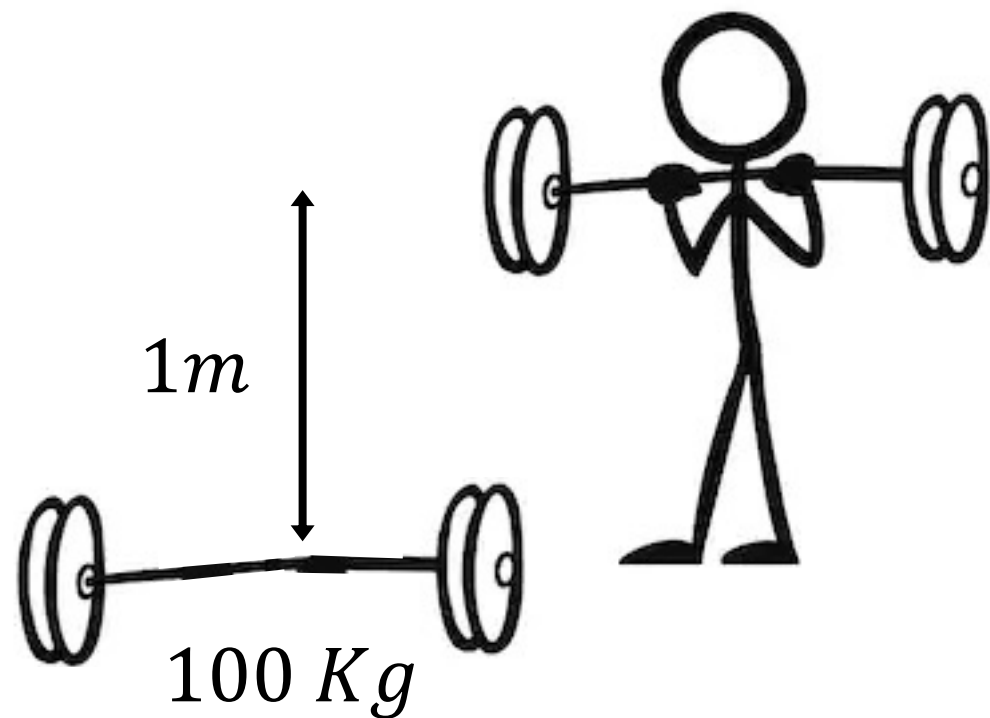

3s - requires energy.

1s - same energy, more power.

Power:

- Rate at which the energy is used.
- Work done per unit time.

$$P = \frac{dW}{dt} = [Watts] = [W]$$



$$\begin{aligned} power &= \frac{work}{time} \\ &= \frac{work}{charge} \times \frac{charge}{time} \end{aligned}$$

$$P = v \times i$$



Note: Assume passive sign convention.

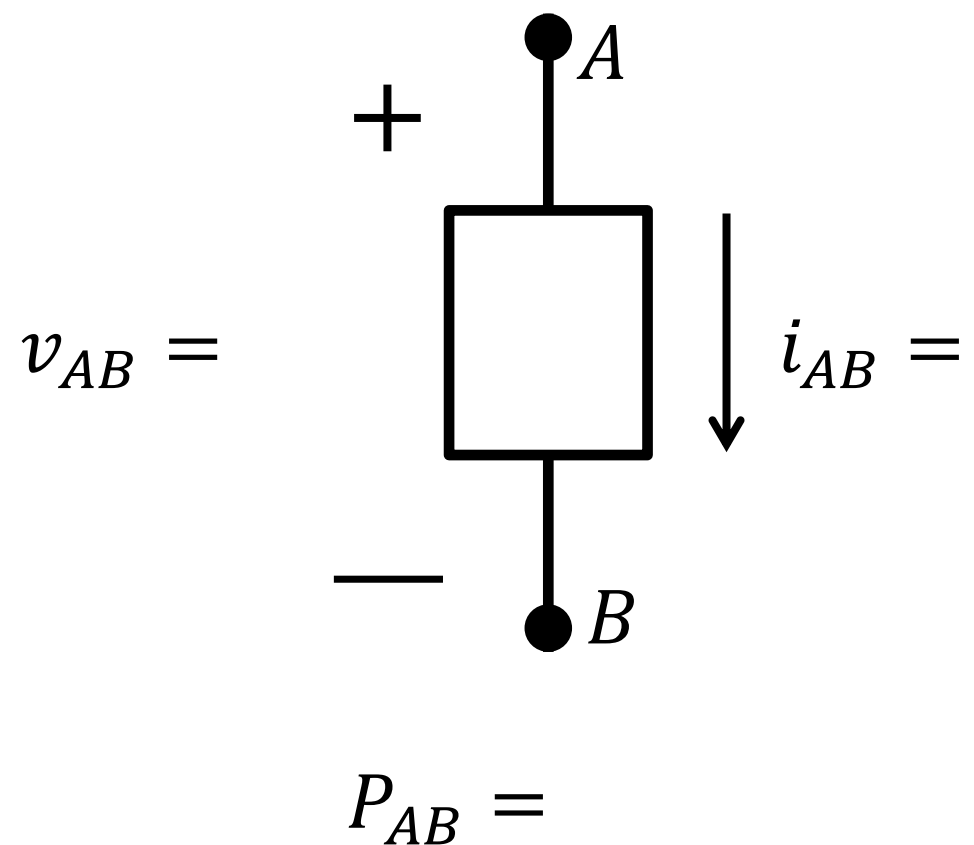
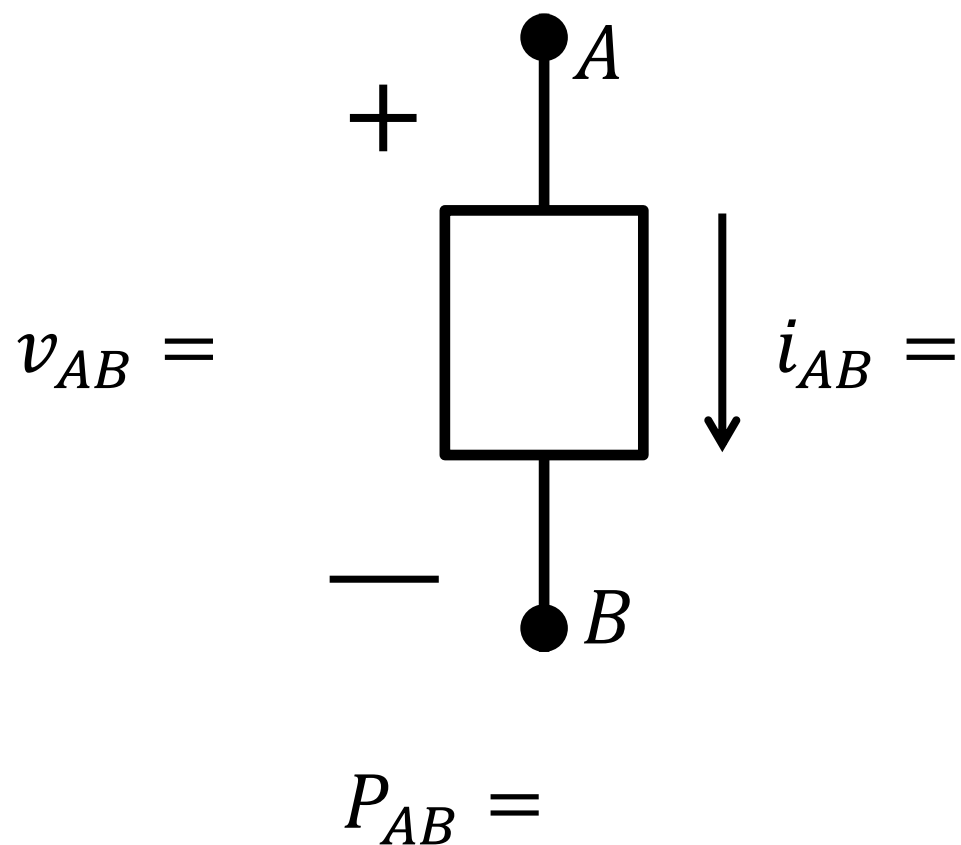
- $P > 0$  : dissipated or consumed.
- $P < 0$  : generated or supplied.





Note: Assume passive sign convention.

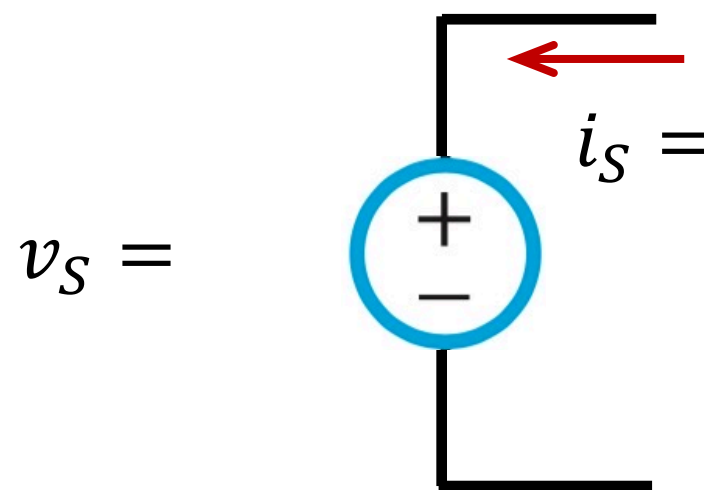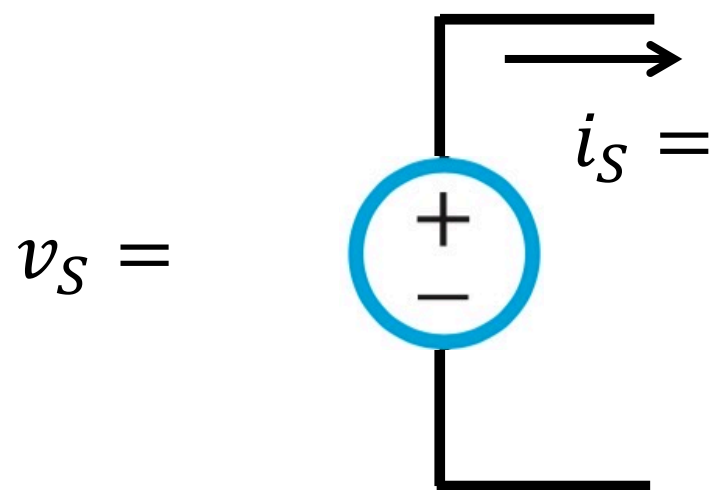- $P > 0$  : dissipated or consumed.
- $P < 0$  : generated or supplied.








# Law of Conservation of Power

$$\sum P_{system} = 0$$

Generate Power

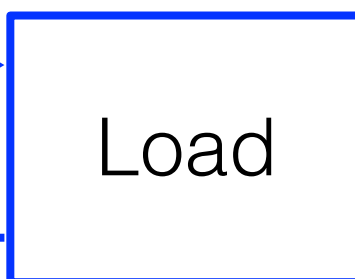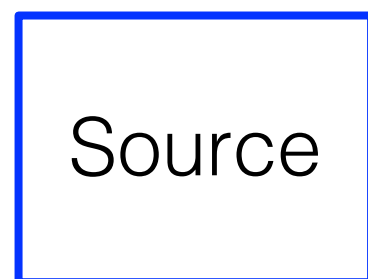

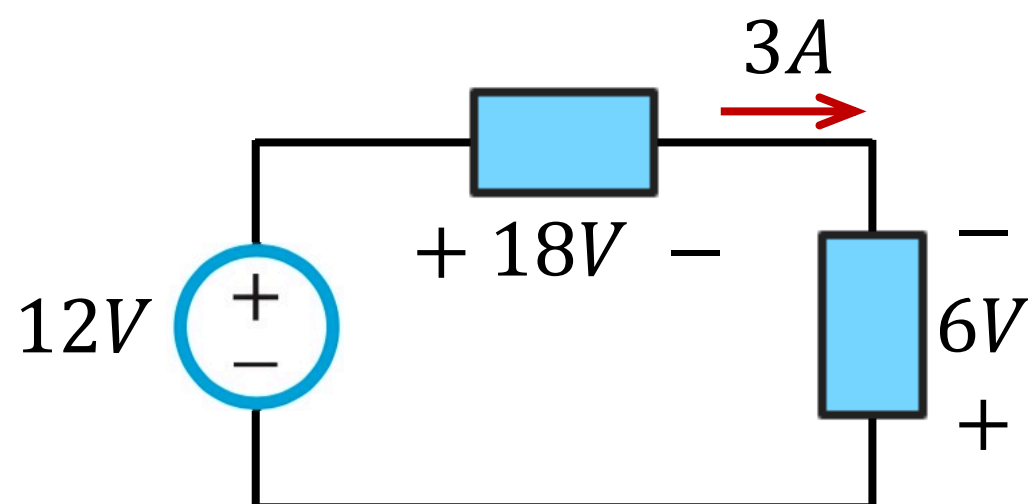Dissipate Power  
Mostly dissipated  
as heat.





For each circuit below, find the power consumed or dissipated by each of the components. Show that conservation of power is satisfied.

