



Reminders to self:

- ☐ Turn on lecture recording to Cloud
- ☐ Turn on Zoom microphone

- Last Lecture

- Finished full-adder
- Ripple carry adder and subtracter
- Adder with carry look ahead

- Today's Lecture

- A couple more slides on adders with carry look ahead
- A bit more on K-maps
- Start multi-level logic



Handouts and Announcements

- Announcements
 - Homework Problems – no new assignment
 - Homework Reminders
 - Problems 5-1 and 5-2
 - Due: 11:25am Monday 2/6
 - Participation Quiz 5
 - Based on today's lecture. 15min limit after you start.
 - Available 12:25pm today, due 12:25pm tomorrow, but also available 24hrs more with late penalty
 - Read for Monday: pages 204-214



Handouts and Announcements

- Announcements

- Mini-Exam 2 Reminder

- Available 5pm Monday 2/6 through 5:00pm Tuesday 2/7
- Due in Carmen PROMPTLY at 5:00pm on 2/7
- Designed to be completed in ~36 min, but you may use more
- When planning your schedule:
 - I recommend building in 10-15 min extra
 - To allow for downloading exam, signing and dating honor pledge, saving solution as pdf, and uploading to Carmen
- I also recommend not procrastinating

- Exam review topics available on Carmen

- Sample Mini-Exams 1 and 2 from Au20 also available




16-bit Carry-Lookahead Adder

- If more than four bits need to be added
 - In principle the carry-lookahead circuit can be expanded
 - But each additional bit means number of inputs to AND and OR gates increases
 - Number of inputs is known as “fan-in”
 - Practical limits (from transistor-level design of gates) set a maximum fan-in
 - In practice, can cascade the 4-bit carry-lookahead circuits
 - A 16-bit adder shown here

Where we left
off last lecture


Group of wires = Bus

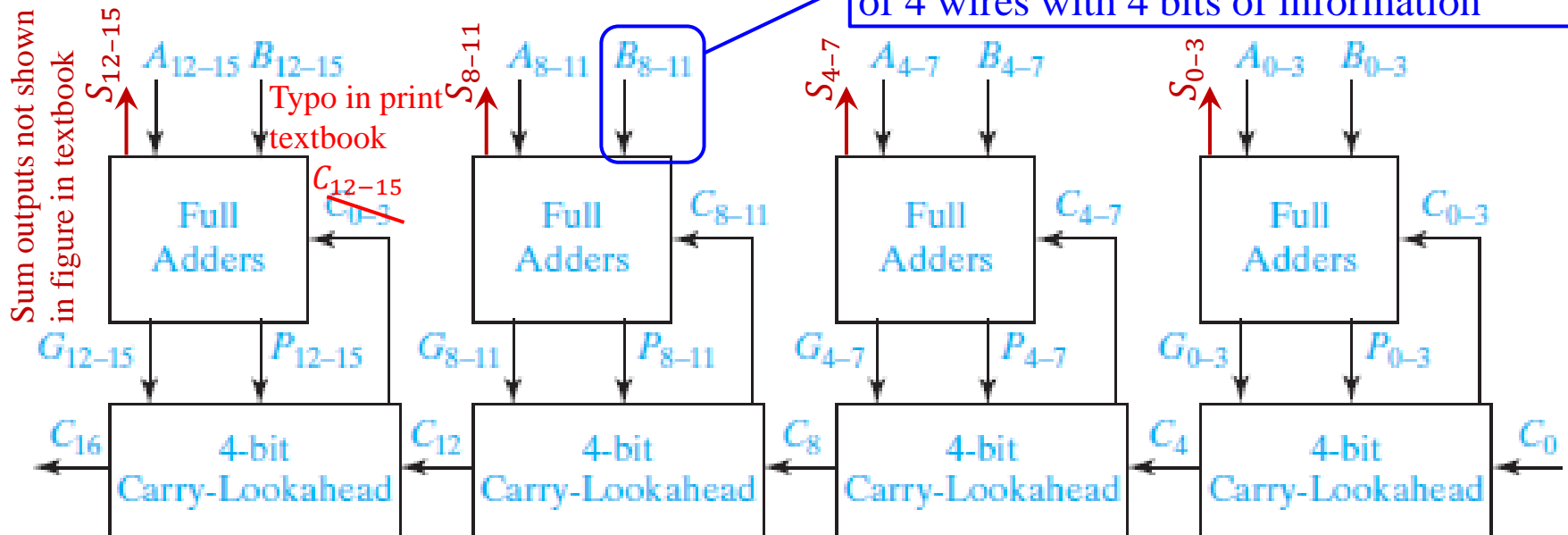Observe notation: Now represents a “bus”
of 4 wires with 4 bits of information





16-bit Carry-Lookahead Adder

 


- But now there is ripple delay cascading through the Carry-Lookahead circuits: $C_0 \Rightarrow C_4 \Rightarrow C_8 \Rightarrow C_{12} \Rightarrow C_{16}$
- It is still an improvement over brute force 16 bit ripple adder
 - Brute force 16 bit ripple adder: 32 gate delays for C_{16} to settle
 - 16 bit adder shown here: 8 gate delays
- Additional improvement possible: additional level of Carry-Lookahead



16-bit Carry-Lookahead Adder

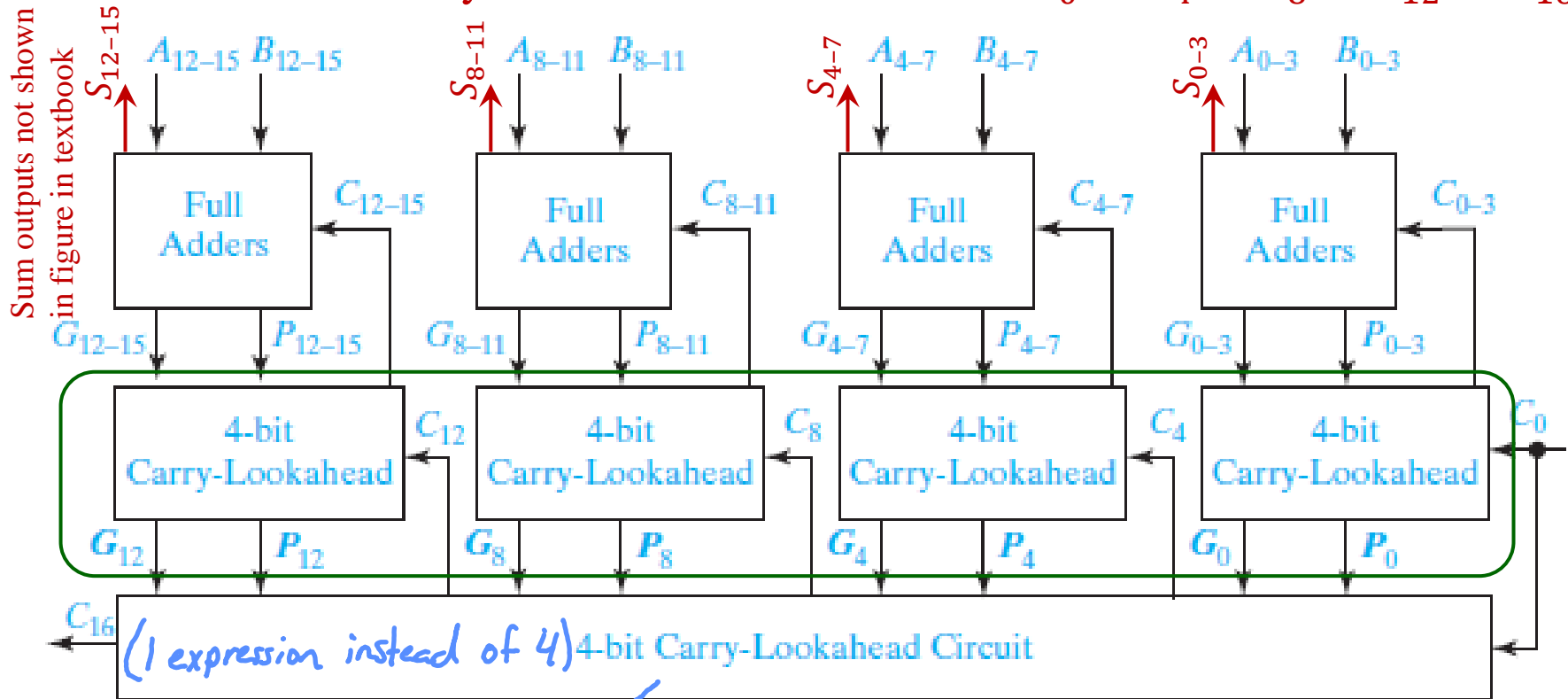Additional level of Carry-Lookahead added to handle $C_0 \Rightarrow C_4 \Rightarrow C_8 \Rightarrow C_{12} \Rightarrow C_{16}$



This is same Carry-Lookahead circuit as before

But first level of Carry-Lookahead modified to output G , P and C_i as shown, but not the carries to pass forward



POS from K-Map

ECE2060

To get reduced POS form of function F from K-Map

1. Group the zeros (Maxterms) in K-Map
2. Use those groups to write \bar{F} in SOP form
3. Use DeMorgan's to convert to F in POS form

Example: $F(a, b, c) = \sum m(0, 1, 6, 7)$

Find reduced POS form of F

$a \backslash bc$	0	1
00	1	0
01	1	0
11	0	1
10	0	1

$a=1, b=0$ (for the red group)
 $a=0, b=1$ (for the green group)

$$\bar{F} = a\bar{b} + \bar{a}b$$

$$F = \overline{a\bar{b} + \bar{a}b} = (\overline{a\bar{b}})(\overline{\bar{a}b}) = (\bar{a} + b)(a + \bar{b})$$



POS from K-Map

ECE2060

Example: $F(a, b, c, d) = \sum m(0, 1, 2, 3, 4, 5, 6, 7, 10, 11, 12, 14, 15)$

Find reduced POS form of F

$ab \backslash cd$	00	01	11	10
00	1	1	1	0
01	1	1	0	0
11	1	1	1	1
10	1	1	1	1

$a=1$
 $b=0$
 $c=0$

$$F' = ab'c' + ac'd$$

$a=1$
 $c=0$
 $d=1$

$$F = (a' + b + c)(a' + c + d')$$


$$F = [ab'c' + ac'd]' = (ab'c')'(ac'd)' = (a' + b + c)(a' + c + d')$$



Prime Implicants

ECE2060

 - The product terms that result from groups in K-maps are known as “*implicants*” of the function
- An implicant is also a “*prime*” implicant if it cannot be combined with another term to eliminate a variable




- $a'b'c$, $a'cd'$, and ac' are prime implicants
- Not prime implicants:
 - $a'b'c'd' \rightarrow$ can be grouped into $a'b'd'$ or $b'c'd'$ *prime*
 - abc' and $ab'c' \rightarrow$ can be grouped into ac' *prime*
- A SOP expression containing a term that is not a **prime** implicant is not minimal



Prime Implicants

ECE2060

 - A SOP expression containing a term that is not a prime implicant is not minimal
- Redundant terms: It is possible for all terms to be prime implicants but the function to not be minimal




- bc' , ac , and ab are prime implicants
- But $F = bc' + ac + ab$ is not minimal
- Prime implicant ab is redundant
- Minimal $F = bc' + ac$



Essential Prime Implicants

ECE2060

 - If a minterm is covered by only one prime implicant, that prime implicant is an “*essential*” prime implicant
- Essential prime implicants must be included in the minimal SOP expression



- All prime implicants drawn
- Red 1s covered by more than one prime implicant → *not all of those implicants are essential*
- Green 1s covered by only one prime implicant → those prime implicants are *essential*
- Essential prime implicants, drawn as green groups, must be included in SOP expression
- Only one of the two magenta groups should be included (*either one is Ok - expression not unique*)

$$F = a'c' + acd + a'b'd' + a'bd$$

$$F = a'c' + acd + a'b'd' + bcd$$



Essential Prime Implicants

Single Output

ECE2060

Procedure

1. Choose a minterm (a 1, not an x) that has not yet been covered
2. Find all 1's and X's adjacent to that minterm (check the n adjacent squares on an n-variable k-map
3. If a single prime implicant covers the minterm and all adjacent 1's and X's then that term is an essential prime implicant → include it
4. Repeat steps 1, 2, and 3 until all essential prime implicants have been included
5. For the remaining 1's
 - Find a minimum set of prime implicants that covers them
 - If there is more than one such set, choose a set with a minimum number of literals (minimize number of gate inputs)



More about Don't Cares

ECE2060

$$F(A, B, C) = \sum m(2, 4, 5, 7) + \sum d(1, 3, 6)$$

A	B	C	Optimal	Ignoring X	Grouping all X
0	0	0	0	0	0
0	0	1	X	0	1
0	1	0	1	1	1
0	1	1	X	0	1
1	0	0	1	1	1
1	0	1	1	1	1
1	1	0	X	0	1
1	1	1	1	1	1

Ignoring don't cares: $F = AB' + AC + A'BC'$ 4 gates, 10 inputs

Optimal: $F = A + B$ 1 gate, 2 inputs

Grouping all X. $F = A + B + C$ 1 gate, 3 inputs

A \ BC	0	1
00	0	1
01	X	1
11	X	1
10	1	X


A \ BC	0	1
00	0	1
01	0	1
11	0	1
10	1	0

A \ BC	0	1
00	0	1
01	1	1
11	1	1
10	1	1



Multi-Level Logic

 
- Also known as Multi-*Stage* Logic
- Two-level logic
 - Sum of Products, or
 - Product of Sums
- SOP: Inputs \rightarrow AND \rightarrow OR \rightarrow Output





Two-level Logic

 - POS: Inputs \rightarrow OR \rightarrow AND \rightarrow Output



- K-Maps \rightarrow SOP \rightarrow 2-stage AND \rightarrow OR




Two-level Logic

Primary reasons for SOP 2-Stage Design

 1. Speed

- Each “stage” has a delay (*gate-delay*)



- 2-stage is the shortest for AND/OR/NOT implementation of “arbitrary” logic functions



Primary reasons for SOP 2-Stage Design

2. Regularization

- All inputs into AND gates
- All AND gates go into OR gates
- All outputs come from OR gates
- On an IC, can make:
 - An array of AND gates with possible connections
 - Another array of OR gates with possible connections from AND array
- Make input & AND-OR connections to create a logic function
- **PLA** : Programmable Logic Array
- **FPGA** : Field Programmable Gate Array



Multi-Level Logic

Terminology:

- **Number of levels:** *maximum* number of gates cascaded in series between input and output
- **AND-OR circuit:** a two-level circuit composed of a level of AND gates followed by an OR gate output (*SOP form*)
- **OR-AND circuit:** a two-level circuit composed of a level of OR gates followed by an AND gate output (*POS form*)
- **OR-AND-OR circuit:** a three-level circuit composed of
 - a level of OR gates
 - followed by a level of AND gates
 - followed by an OR gate output
- ETC.
- “*Circuit of AND and OR gates*” implies no particular ordering of the gates or number of levels; the output gate may be either AND or OR



Multi-Level Logic

Changing the numbers of levels:

- **AND-OR:** number of levels can usually be *increased* by *factoring* SOP expression
- **OR-AND:** number of levels can usually be *increased* by *multiplying out* some of the terms in POS expression
- **Why increase numbers of levels?**
 - There may be constraints on fan-in (*num of inputs to a gate*)
 - Can reduce fan-in at expense of adding levels
 - May also be able to reduce total number of gates by adding levels
 - Trade-off: More levels \rightarrow longer overall gate-delay \rightarrow slower digital system



Multi-Level Logic

FIGURE 7-1


Four-Level
Realization of Z

© Cengage Learning 2014

Tree diagram


- Each gate shown as node (6 gates)
- Nodes labeled with # gate inputs
- Total of 13 gate inputs

$$Z = (AB + C)(D + E + FG) + H$$

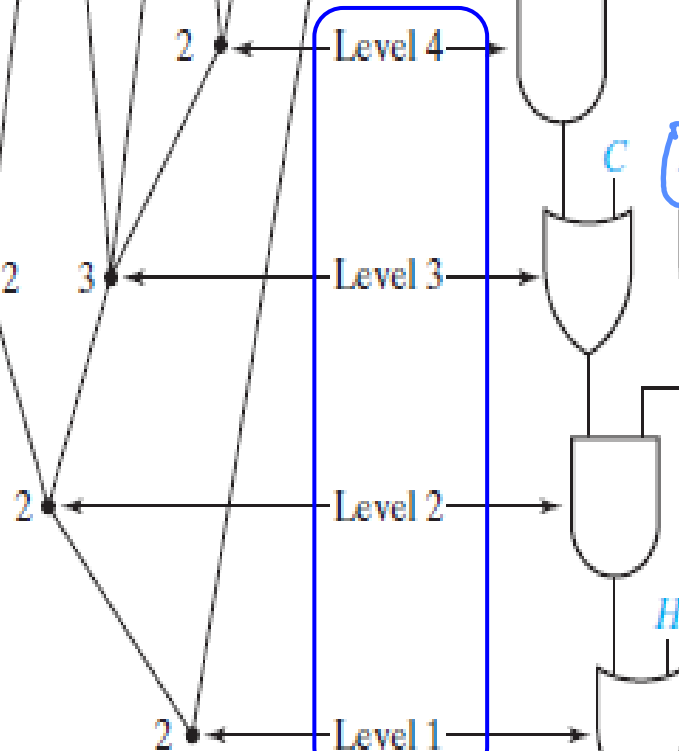

AND - OR - AND - OR

(a)

 



Multi-Level Logic

FIGURE 7-2

Three-Level
Realization of Z

© Cengage Learning 2014

Tree diagram

- Still 6 gates
- Total of 19 gate inputs
- Maximum fan-in = 5
- But shorter overall gate delay


Less gates
Higher fan-in

$$Z = AB(D + E) + C(D + E) + ABFG + CFG + H$$

* The same gate can be used for both appearances of $(D + E)$.

OR-AND-OR

(a)

 

(b)