

### Chapter 3. Pipelining and Parallel Processing

#### Exercise Solution

Exercise 1. (a) Sample period  $T_{sample}$  of the given DFG is

$$T_{sample} = 4T \quad (3.1)$$

So the maximum achievable sample rate is

$$f_{sample} = \frac{1}{T_{sample}} = \frac{1}{4T} \quad (3.2)$$

(b) The pipelining levels are shown by the dashed lines in Figure 3.1. 9 registers are required.

 


Fig. 3.1 Pipelining levels for Exercise 1(b)

### Chapter 3. Pipelining and Parallel Processing

Exercise Solution

Problem2. (a). The critical path is  $M_1 - A_2 - M_2 - A_1 - M_3 - A_3 - A_4$  as shown by the dashed line in Figure 3.1(a). The latency is one clock cycle=10u.t

 


Fig. 3.1 (a). Critical Path Illustration for Exercise 1 (b). Pipelined IIR filter for Exercise 2

(b). Pipelining latches are placed on the dotted lines in Figure 3.1(b). As can be seen, the critical path is one multiply and one add, which is 3 time units. The latency is four clock cycles= $4 \times 3 = 12$ u.t

■

Problem5 (a). The pipelining cutset is shown by the dashed line in Figure 3.2(a). Number of delays needed for pipelining= $n + 2n + 1 = 3n + 1$

(b). The block filter architecture is illustrated in Figure 3.2(b). Sample period= $T/3$ . Sample rate  $f_{sample}=3/T$ . Number of delays needed for pipelining= $9n + 3$

$$y(3k) = ax(3k) + bx(3k - 2) + cx(3k - 3) \quad (3.1)$$

2

$$y(3k+1) = ax(3k+1) + bx(3k-1) + cx(3k-2)$$

$$y(3k+2) = ax(3k+2) + bx(3k) + cx(3k-1)$$

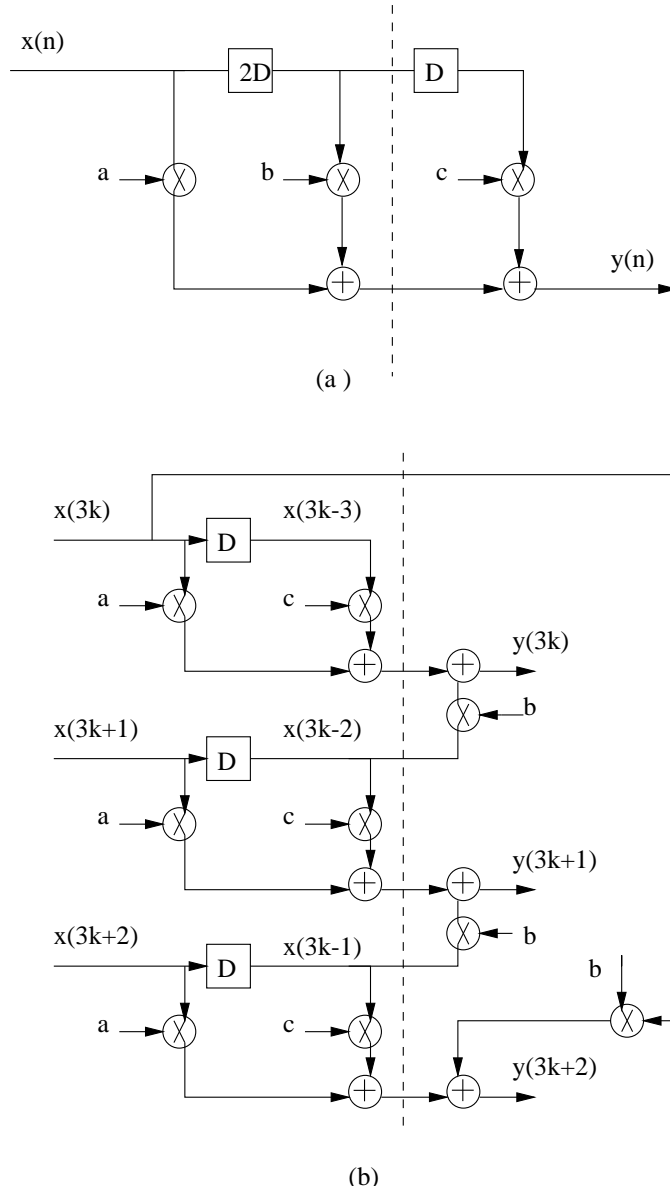


Fig. 3.2 (a):Pipeline of direct-form; (b):Block filter architecture for Exercise 5

Exercise 9. Suppose  $M$  level pipelining is needed. Let  $\beta$  be the supply voltage reduction factor, i.e., the supply voltage can be reduced to  $\beta V_0$  for the pipelined system. From text, the power reduction factor is  $\beta^2$ . Therefore, we have

$$\beta^2 \leq \frac{1}{5}. \quad (3.2)$$

Suppose that the pipelined system and the original system have the same sample rate, we have

$$M = \frac{\beta(V_0 - V_t)^2}{(\beta V_0 - V_t)^2}. \quad (3.3)$$

Take  $\beta = \sqrt[3]{0.2} = 0.447$ , then

$$M = \lceil \frac{0.447(5 - 0.4)^2}{(0.447 \times 5 - 0.4)^2} \rceil = \lceil 2.8 \rceil = 3. \quad (3.4)$$

Therefore, the system should be pipelined at 3 level. Substitute  $M = 3$  into (3.3) and solve for  $\beta = 0.427$ . The supply voltage for pipelined system is  $\beta V_0 = 2.14$  Volts. ■

Exercise 12. Since pipelining level  $M=4$  and block size  $L=4$ , we have

$$16(\beta V_0 - V_t)^2 = \beta(V_0 - V_t)^2 \quad (3.5)$$

Substitute  $V_0=5$  Volts and  $V_t=0.4$  Volts in to (3.5), we have

$$\beta^2 - 0.2129\beta + 0.0064 = 0. \quad (3.6)$$

Solving for  $\beta$ , we get

$$\beta = 0.176675, \text{ or } \beta = 0.03622. \quad (3.7)$$

$\beta = 0.03622$  is disgarded since  $0.03622V_0 = 0.181$  Volts, which is less than the threshold voltage. Therefore, the supply voltage for the parallel pipelined system is  $\beta V_0 = 0.883$  Volts. The power ratio is

$$Ratio = \beta^2 = 3.12\%. \quad (3.8)$$