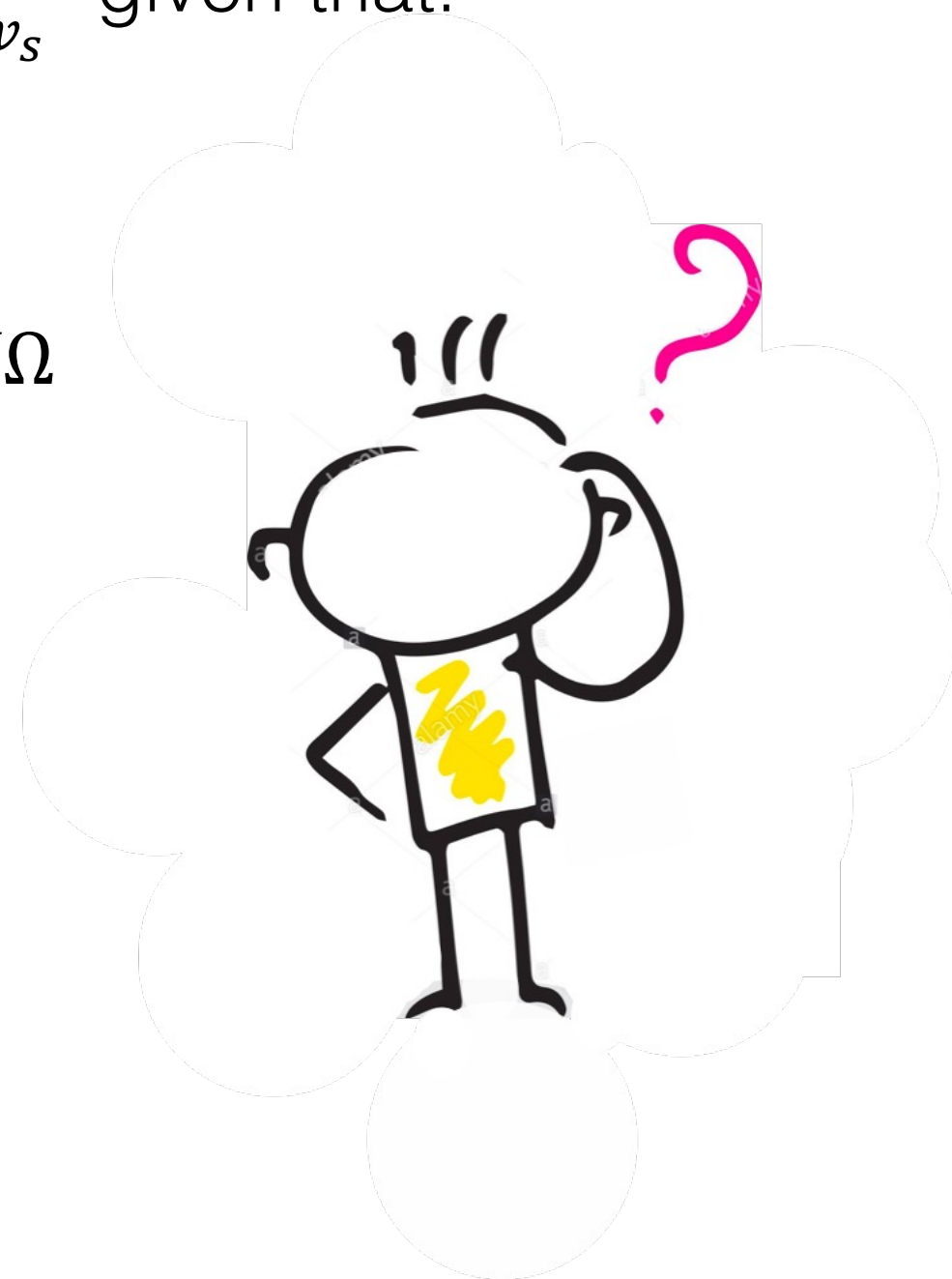


Find $\frac{v_{out}}{v_s}$ given that:

$$R_{in} = 10^6 \Omega$$

$$R_{out} = 100 \Omega$$

$$A_{vol} = 10^6$$





THE OHIO STATE UNIVERSITY


COLLEGE OF ENGINEERING

Op-amp models



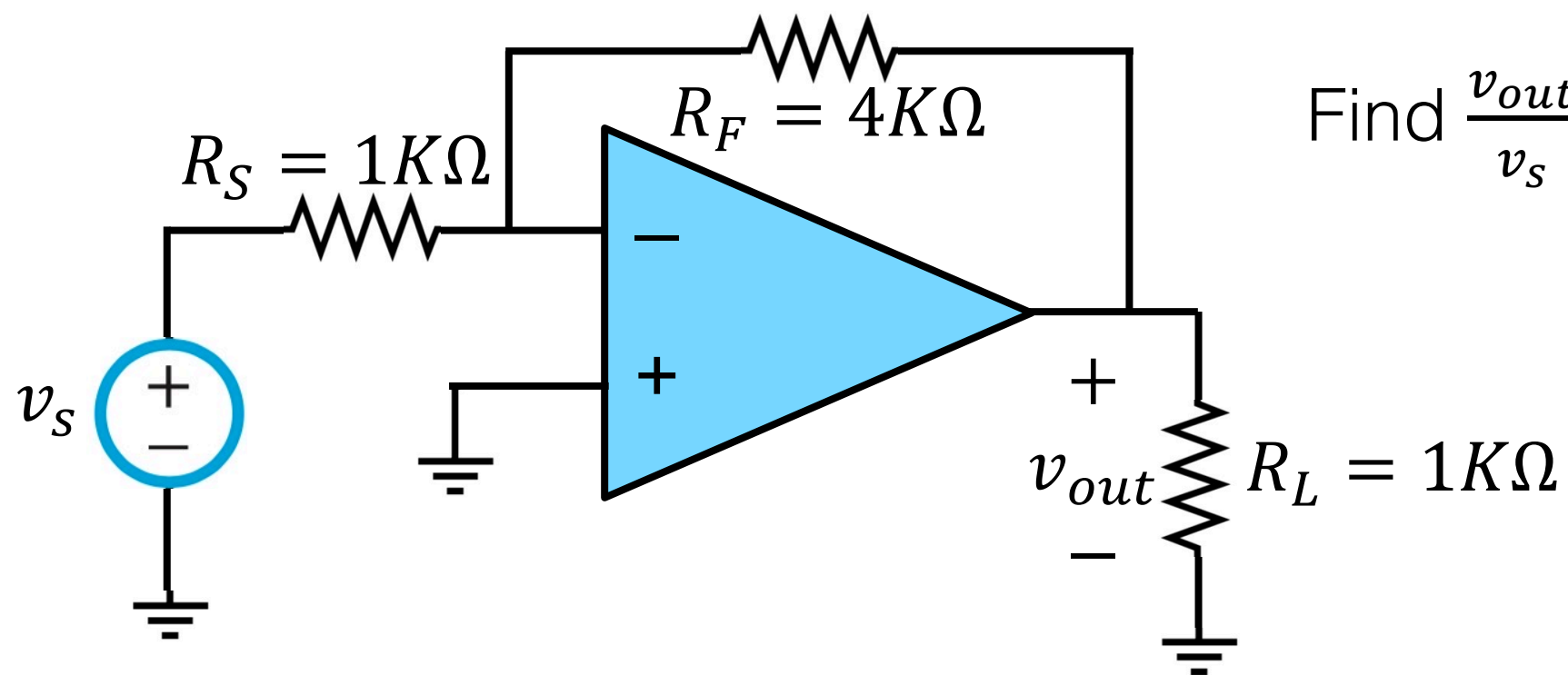
- Learning Objectives:
 - Analyze a circuit using the behavioral and ideal model of the op-amp.
 - Identify the voltage gain of a non-inverting and an inverting amplifier.





Find $\frac{v_{out}}{v_s}$ given that:

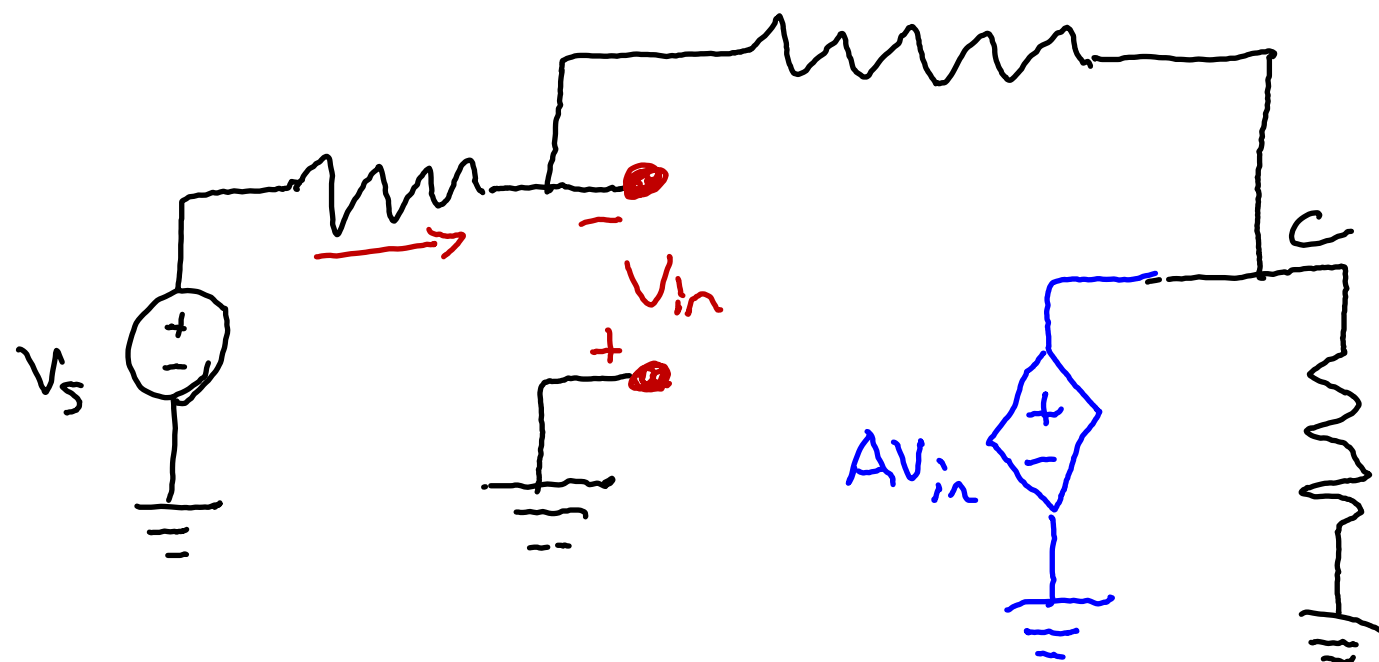$R_{in} = \infty\Omega$
open circuit
 $R_{out} = 0\Omega$
 $A_{vol} = \infty$
short circuit
Behavioral Model



Node Voltage Analysis (4 nodes)

$$V_O = 0V$$

$$V_C = AV_{in} = A(V_O - V_B)$$

$$V_A = V_S$$

$$V_C = -AV_B$$

KCL @ B:

$$i_{R_S} = i_{R_F}$$

$$\frac{V_S - V_B}{R_S} = \frac{V_B - V_C}{R_F}$$

$$R_F V_S - R_F V_B = R_S V_B - R_S V_C$$

$$R_F V_S + R_S V_C = (R_S + R_F) V_B$$

$$V_B = \frac{R_F V_S + R_S V_C}{R_S + R_F} \quad (2)$$

(2) in (1)

$$V_C = -A \cdot \frac{R_F V_S + R_S V_C}{R_S + R_F}$$

$$(R_S + R_F) V_C = -A R_F V_S - A R_S V_C$$


$$(R_S + R_F + A R_S) V_C = -A R_F V_S$$

$$\frac{V_c}{V_s} = \frac{-AR_F}{R_s + R_F + AR_s} \quad A \rightarrow \infty$$

$$\frac{V_c}{V_s} = \lim_{A \rightarrow \infty} \frac{-AR_F}{R_s + R_F + AR_s}$$


$$\frac{V_c}{V_s} = \frac{-R_F}{R_s} = -\frac{4000}{1000} = -4$$

This is an inverting amplifier

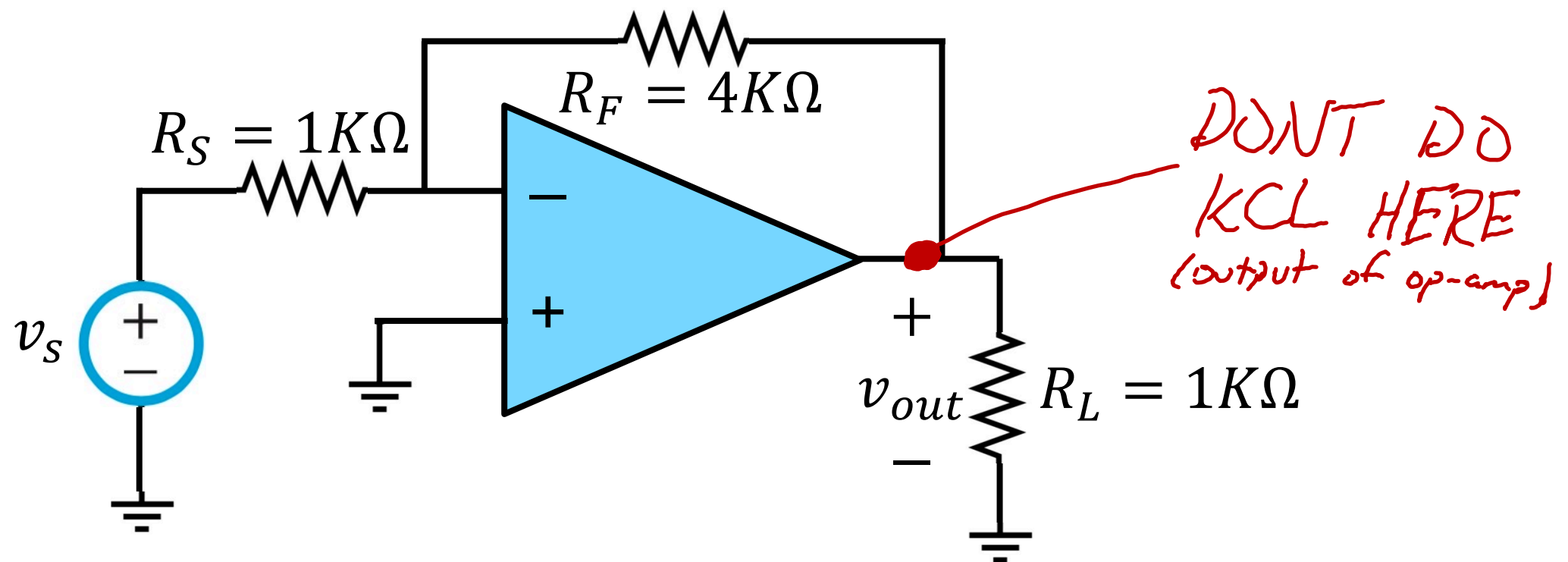

Assumptions

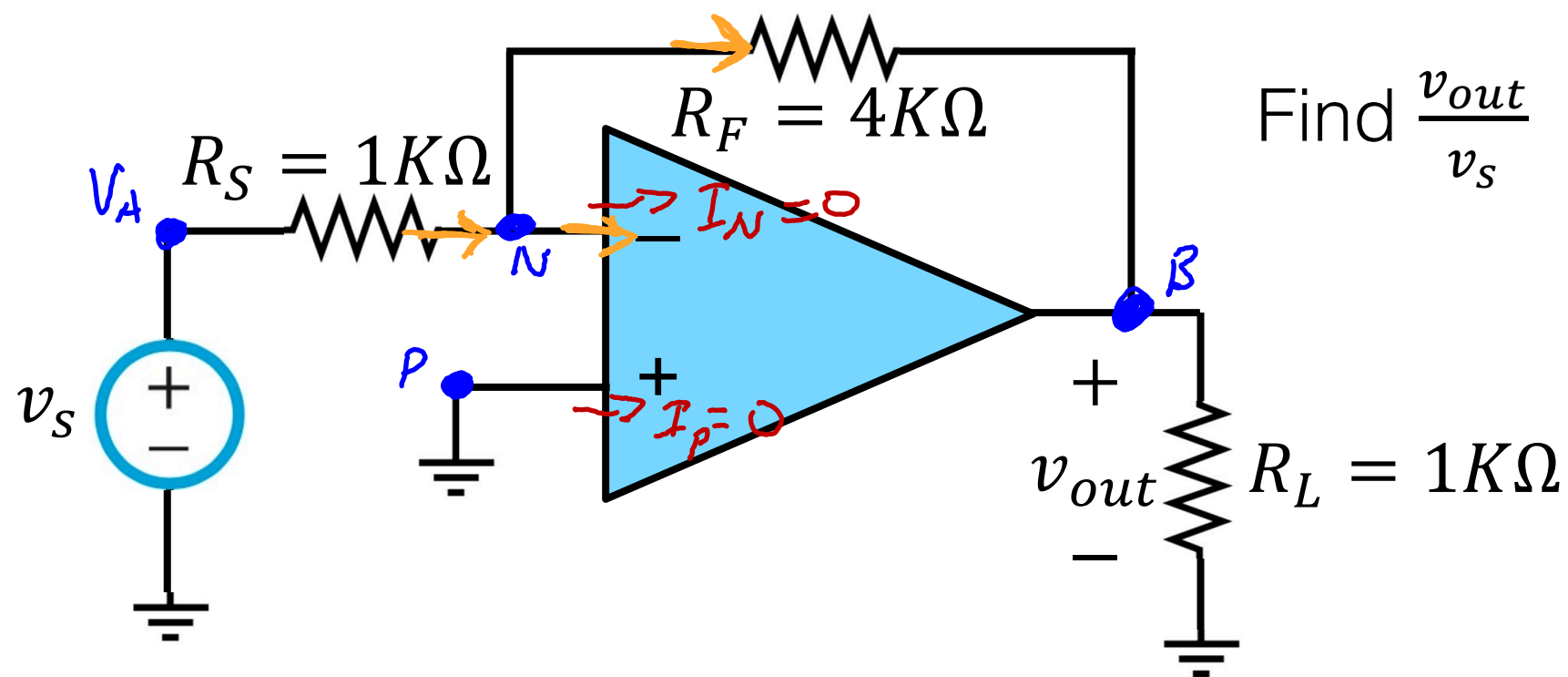1. $i_p = i_n = 0A$
 2. $v_p = v_n$ (voltage is the same, different node).
- Use nodal analysis as before, but with using the conditions stated above.
 - Do not apply KCL at op-amp output unless calculating i_o .



Ideal Model

1. $i_p = i_n = 0$
2. $V_p = V_n = 0$ ← For this example

Node Voltage Analysis 4 nodes

$$V_p = 0$$

$$V_A = V_s$$

DO NOT DO KCL @ B BASED ON IDEAL MODEL

KCL @ N

$$i_{R_S} = i_{R_F} + 0$$

$$\frac{V_A - V_N}{R_S} = \frac{V_N - V_B}{R_F}$$


ideal model $V_N = V_p = 0$

$$\frac{V_S}{R_S} = \frac{-V_B}{R_F}$$

$$\frac{V_B}{V_S} = \frac{-R_F}{R_S}$$



Non-Inverting Amplifier

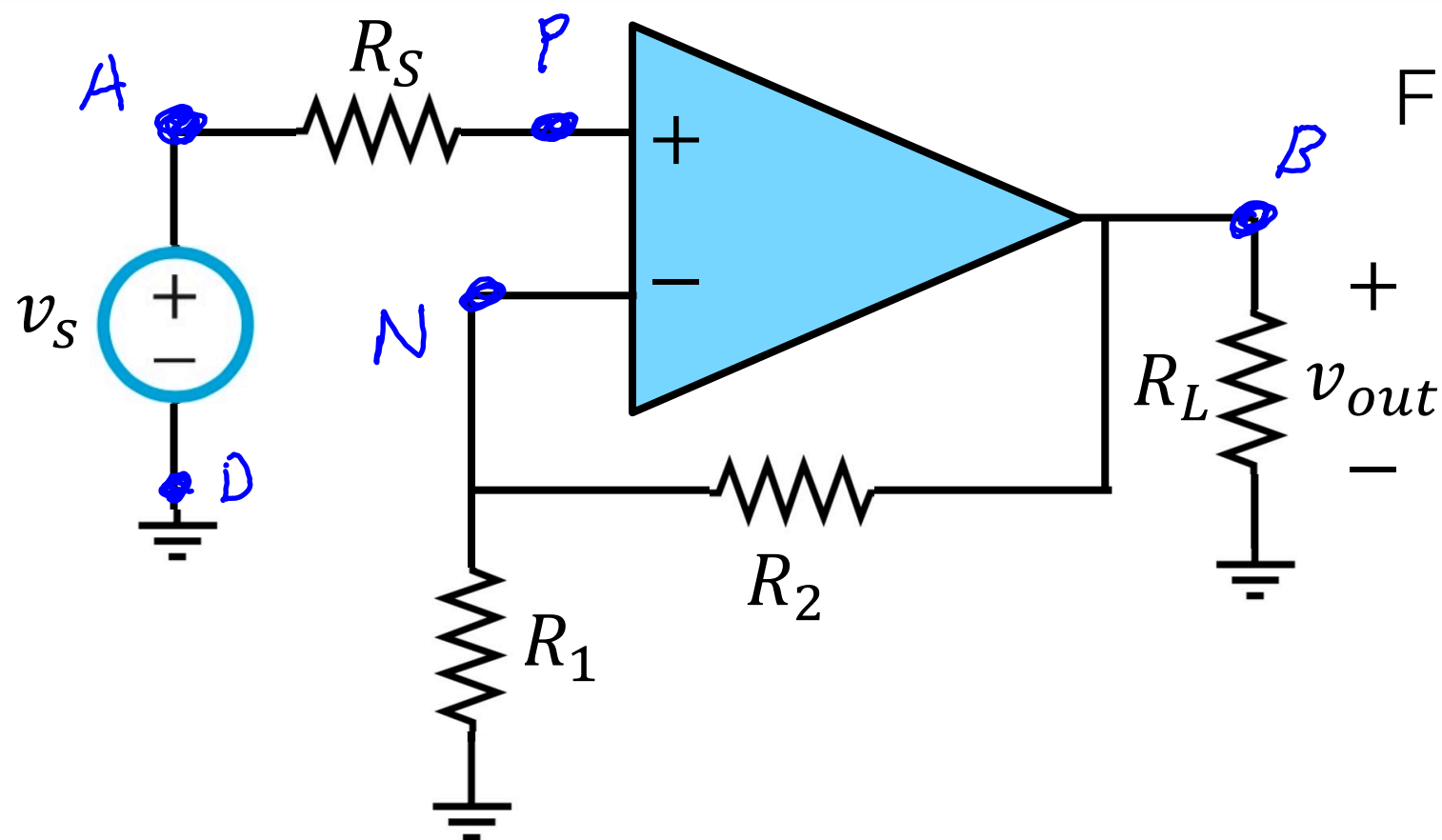

Find $\frac{v_{out}}{v_s}$


ideal model

1. $i_p = i_n = 0$
2. $V_p = V_n$

NVA

$V_D = 0$
 $V_A = V_S$

Don't do KCL @ B

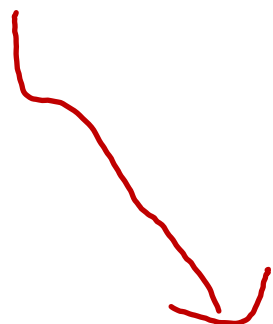

KCL @ P


$$i_{RS} = 0$$

$$\frac{V_S - V_P}{R_S} = 0$$


$$V_S - V_P = 0$$

$$V_S = V_P = V_N$$


KCL @ N

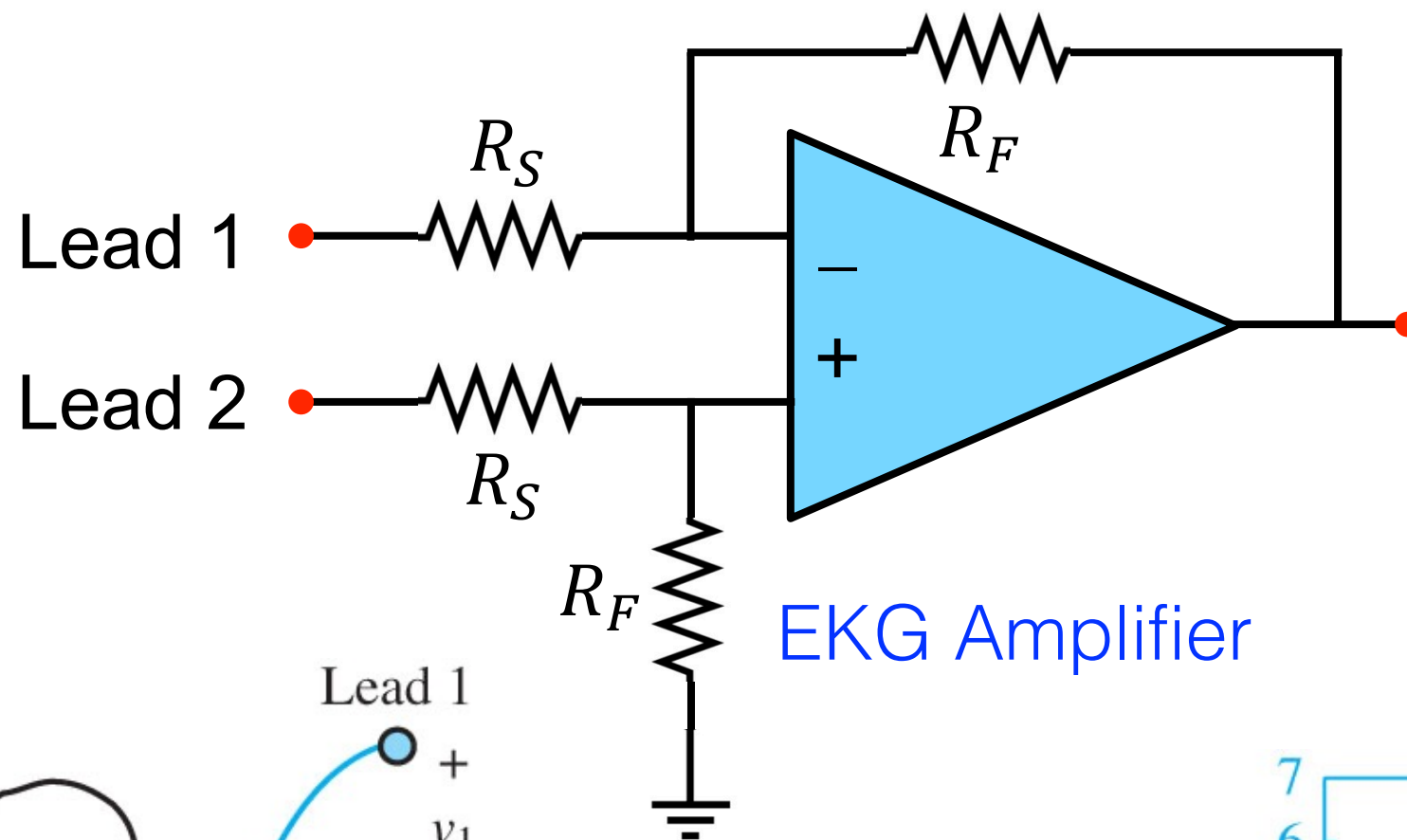

EKG Amplifier

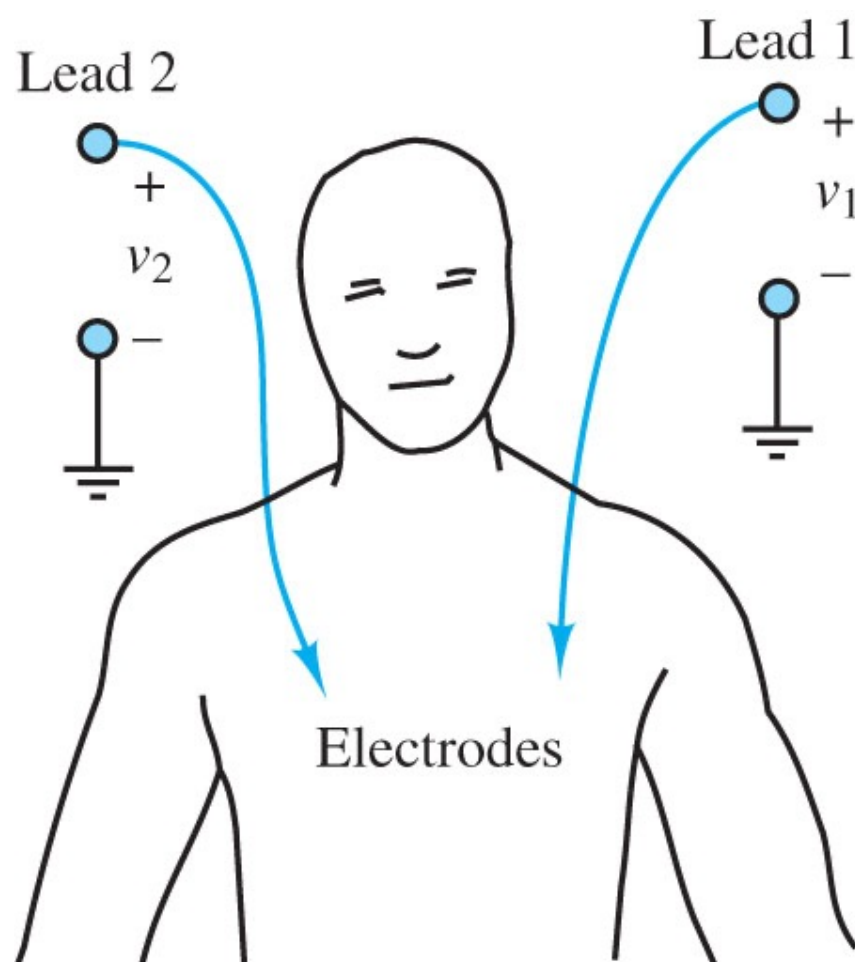

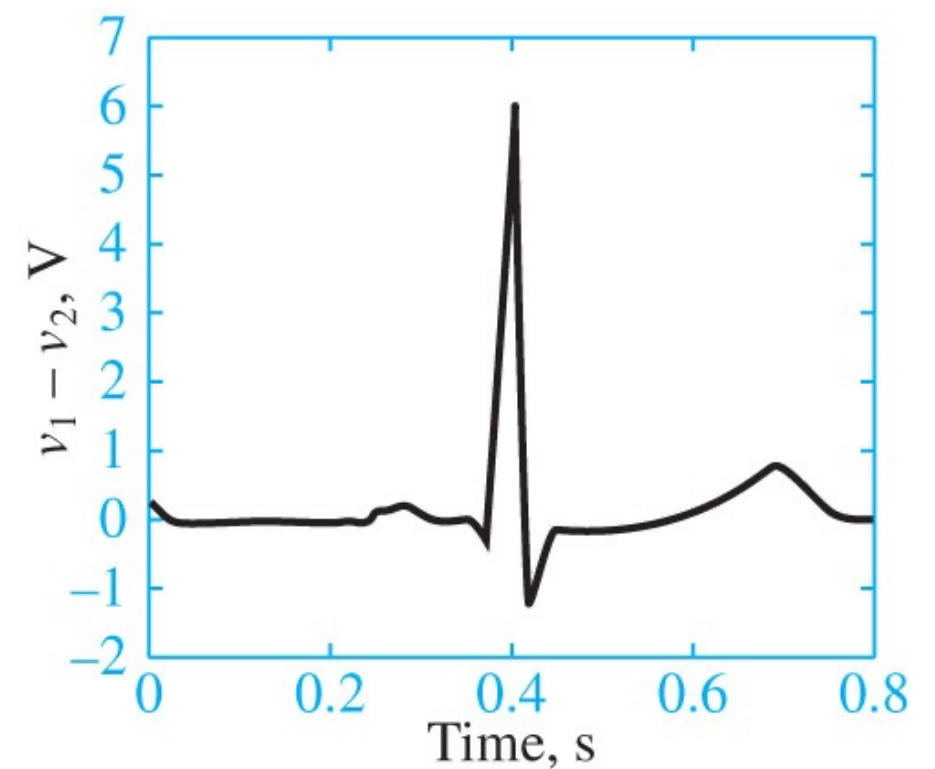Better version:
Instrumentation
Amplifier





Instrumentation Amplifier

