

**Due: 09/18/2024 Please submit online via CarmenCanvas.**


Consider the following two inverter types shown below and assume that each inverter has a fan-out of 2 (i.e. it drives a load of 2x its own size).

**Static Analysis:**


- i. Simulate in Cadence the VTC of each inverter. Plot the results
- ii. What is the swing range of each inverter?
- iii. From the figure, calculate (approximately)  $V_{IH}$ ,  $V_{IL}$ ,  $NM_H$ ,  $NM_L$  and  $V_M$  of each inverter.
- iv. Plot the gain vs. input voltage of each inverter and calculate the max gain.
- v. Given the results in i-iii, comment on advantage/disadvantage of one inverter design vs. another.

**Transient Analysis:**

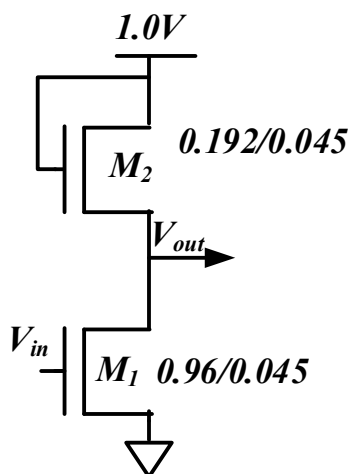- vi. Assume a 1GHz input square wave signal with an 8ps rise and fall time is applied to each of the inverters. Simulate the output transient signal and measure the circuit rise/fall times as well as the  $t_{PHL}$ ,  $t_{PLH}$  and  $t_P$ .
- vii. Plot the instantaneous power and measure the average power consumed over one cycle in each inverter.
- viii. Given the results in v-vi, comment on advantage/disadvantage of one inverter design vs. the other.



***NMOS Only Inv.***

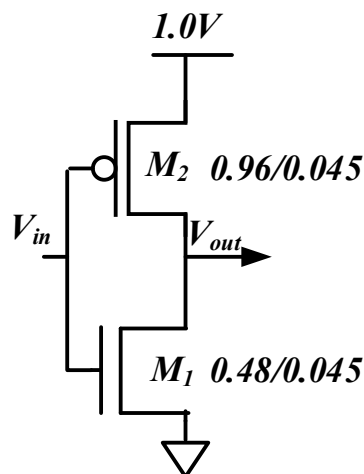

***CMOS Inv.***

Note: 0.48/0.045 means  $W = 0.48\mu\text{m} = 480\text{nm}$  and  $L = 0.045\mu\text{m} = 45\text{nm}$ .