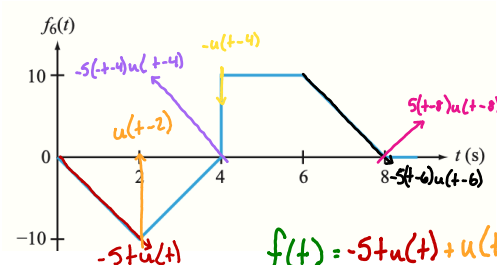


Homework 10

Due: Tuesday, April 25th, 2023 by 7PM.

Note: In order to receive full credit, you must show your work and carefully justify your answers. The correct answer without any work will receive little or no credit.

- Use step functions to write the expression for the function below, then find the Laplace transform.



$$f(t) = -5u(t) + u(t-2) - 5(-t+4)u(t-4) - u(t-4) - 5(t-6)u(t-6) + 5(t-8)u(t-8)$$

$$\downarrow \quad \downarrow \quad \downarrow \quad \downarrow \quad \downarrow \quad \downarrow$$

$$\frac{-5}{s} \quad \frac{e^{-2s}}{s} \quad \frac{-5e^{4s}}{s^2} \quad \frac{-e^{-4s}}{s} \quad \frac{-5e^{-6s}}{s^2} \quad \frac{5e^{-8s}}{s^2}$$

$$f(s) = \frac{-5}{s} + \frac{e^{-2s}}{s} - \frac{5e^{4s}}{s^2} - \frac{e^{-4s}}{s} - \frac{5e^{-6s}}{s^2} + \frac{5e^{-8s}}{s^2}$$

- Obtain the inverse Laplace transform by hand.

$$\frac{100}{s^2(s+5)}$$

$$-\frac{4}{s} + \frac{20}{s^2} + \frac{4}{s+5} \quad \leftarrow \text{partial}$$


$$-L^{-1}\left(\frac{4}{s}\right) = -4u(t)$$

$$L^{-1}\left(\frac{20}{s^2}\right) = 20t$$

$$L^{-1}\left(\frac{4}{s+5}\right) = 4e^{-5t}$$



$$L^{-1}\left(\frac{100}{s^2(s+5)}\right) = -4u(t) + 20t + 4e^{-5t}$$

3. For the circuit below,

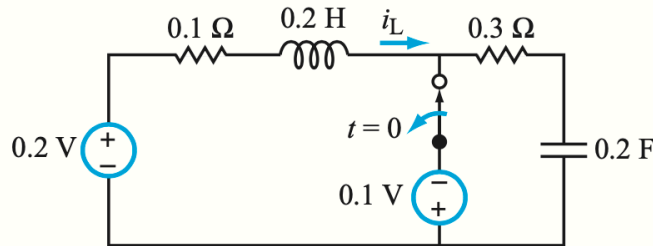

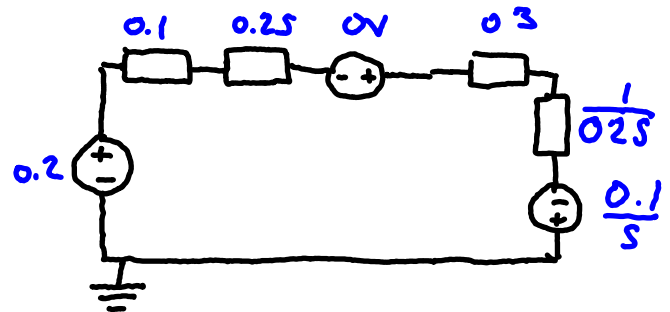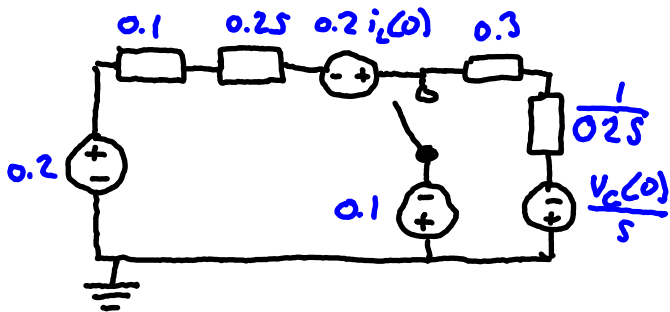0.1 V (to -0.1V) 0 A (max 3A)

- Find the initial voltage for the capacitor and the initial current for the inductor.
- Find the s-domain circuit equivalent.
- Find $I_L(s)$.
- Find $i_L(t)$.



$$0.1 + 0.2s + 0.3 + \frac{5}{s}$$

$$0.4 + 0.2s + \frac{5}{s}$$


$$I_L(s) = \frac{0.2}{0.4 + 0.2s + \frac{5}{s}}$$

$$\frac{0.2}{((0.2s^2 + 0.8s + 5s)/s)} \rightarrow \frac{0.2s}{0.2s^2 + 5.8s} \rightarrow \frac{0.0345}{s + 2.708} + \frac{0.1655}{0.2s + 0.85}$$

\downarrow \downarrow
 $0.0345e^{-2.708t}$ $0.8275e^{-4.25t}$

$$I_L(t) = 0.0345e^{-2.708t} + 0.8275e^{-4.25t}$$

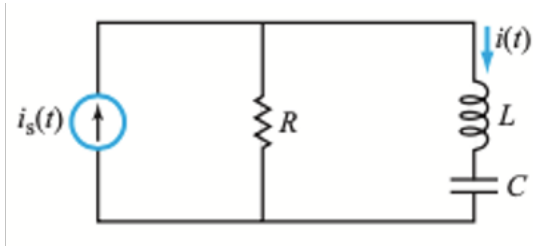
4. On the circuit below, assume all initial conditions are 0 and that $R = 1\text{k}\Omega$, $L = 1\text{mH}$, and $C = 1\mu\text{F}$.
- Find the transfer function $I(s)/I_s(s)$.
 - Assume $s = j\omega$. What type of filter is it?
 - Sketch by hand the magnitude bode plot of the system. Clearly explain your reasoning.



$$L = SL = 0.001\text{ s}$$

$$C = \frac{1}{Sc} = \frac{1}{.000001\text{ s}} = \frac{1e6}{s}$$

$$R =$$

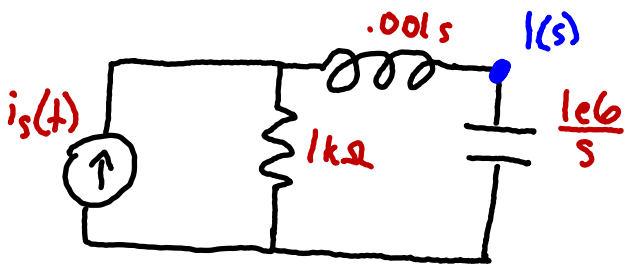

KCL @ $i(s)$

$$\frac{i_s(s) - i(s)}{.001\text{ s} - 1000} = \frac{1e6}{s}$$

$$\frac{i_s(s)}{.001\text{ s} - 1000} = i(s) \left(\frac{s}{1e6} + \frac{1}{.001\text{ s} - 1000} \right)$$

$$\frac{i_s(s)}{.001\text{ s} - 1000} = i(s) \left(\frac{.001\text{ s}^2 - 1000\text{ s} + 1e6}{1e6 (.001\text{ s} - 1000)} \right)$$

$$i_s(s) = i(s) \left(\frac{.001\text{ s}^2 - 1000\text{ s} + 1e6}{1e6} \right)$$

$$\frac{i_s(s)}{i(s)} = \left(\frac{.001\text{ s}^2 - 1000\text{ s} + 1e6}{1e6} \right) \rightarrow \frac{i(s)}{i_s(s)} = \frac{1e6}{.001\text{ s}^2 - 1000\text{ s} + 1e6} \times 1000$$

$$\frac{i(s)}{i_s(s)} = \frac{1e9\text{ s}}{s^2 - 1e6\text{ s} + 1e9}$$

Band Pass Filter

Zeros: 0

Poles: 998999 , 1001
(via quadratic formula)

