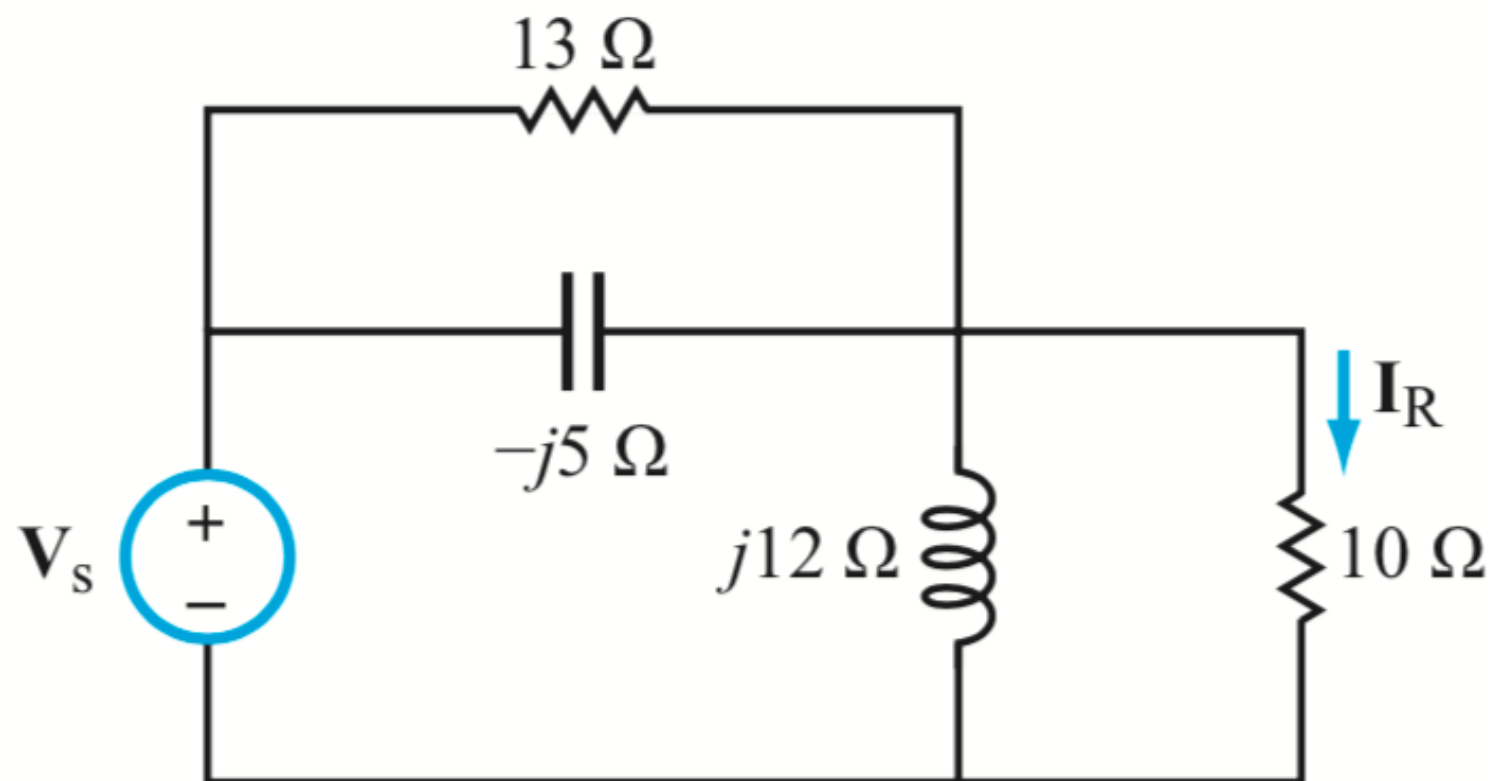





- Find  $I_R$ , given that  $V_s = 25V$ .





Your objective is to obtain a Thevenin, given that  $i_s(t) = 3\cos(4 \times 10^4 t)$ , then:

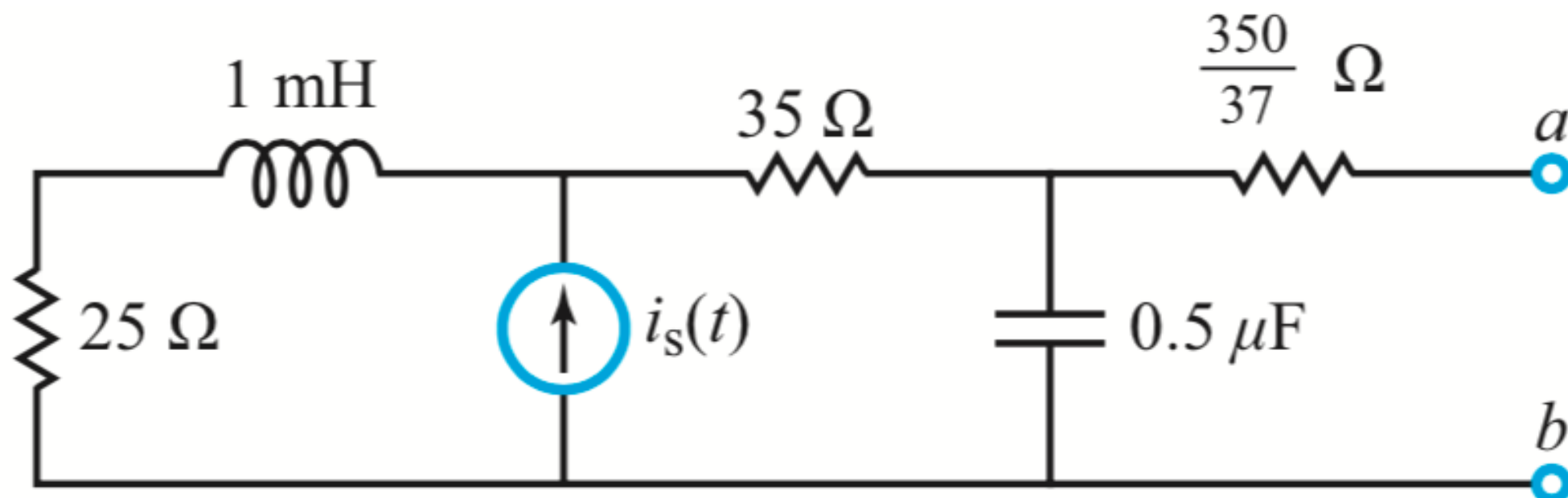
- Transform the circuit to the phasor domain.
- Apply the source-transformation technique to obtain the Thevenin equivalent circuit at terminals (a, b).
- Transform the phasor-domain Thevenin circuit back to the time domain.









$$\omega = 40k$$

$$j\omega L = 40k \cdot 1m \cdot j = 40j$$
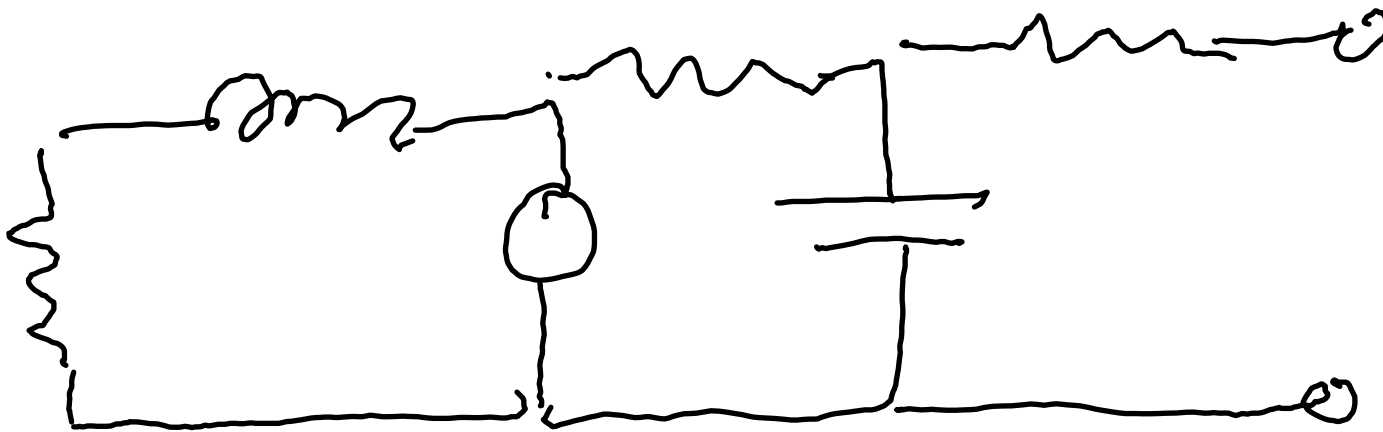
$$\frac{-j}{\omega F} = \frac{-j}{40k \cdot .5\mu} = -50j$$



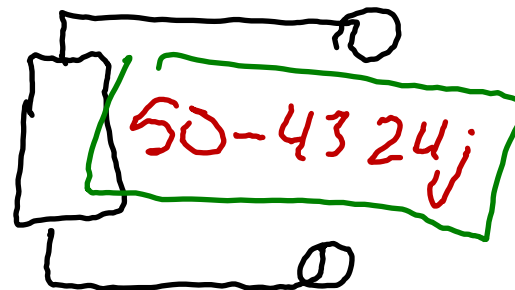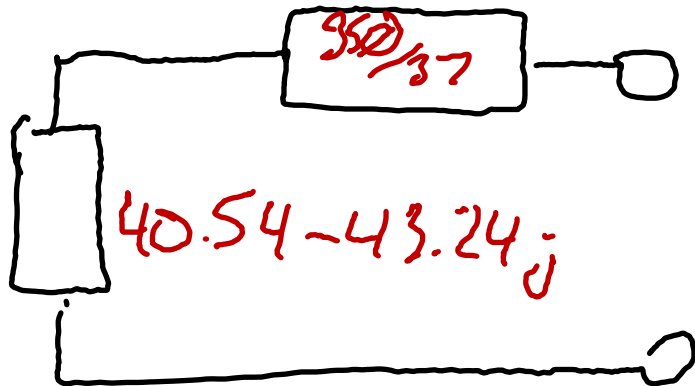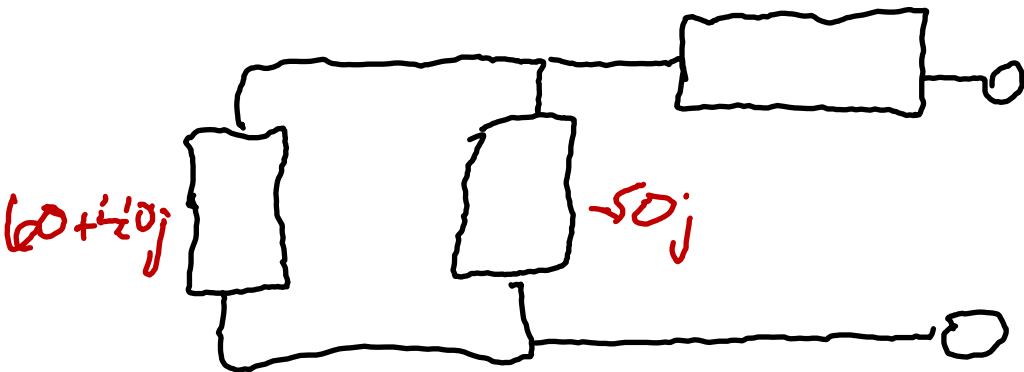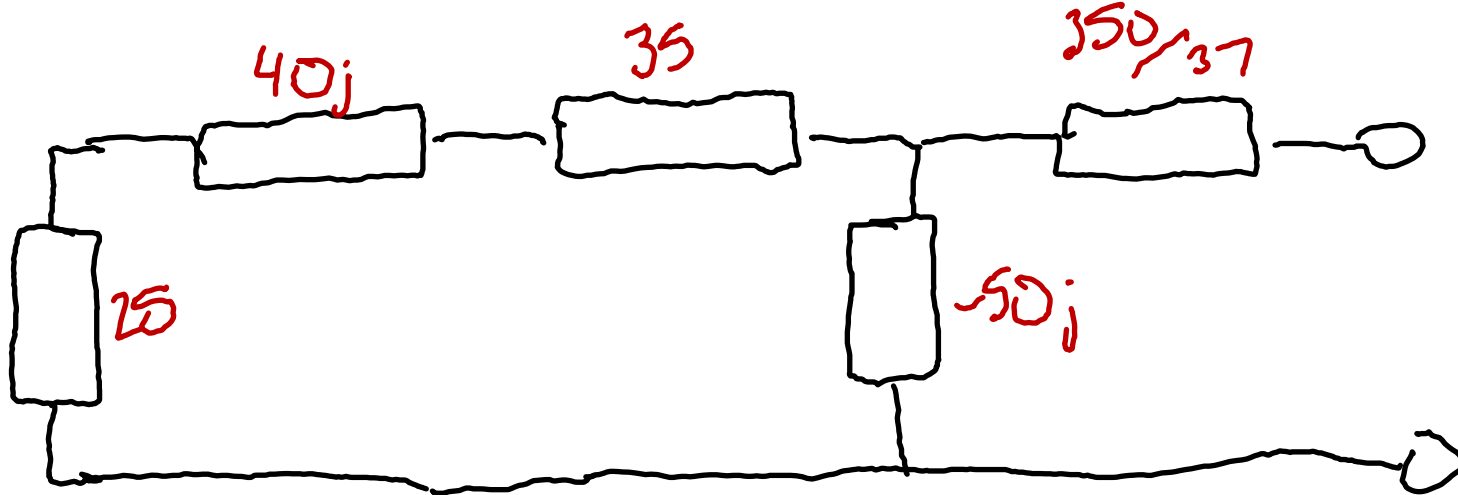

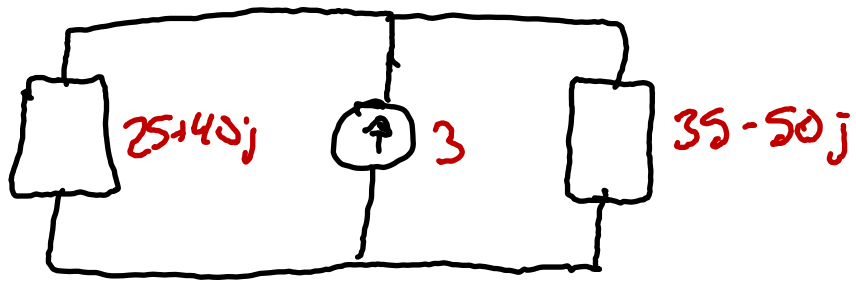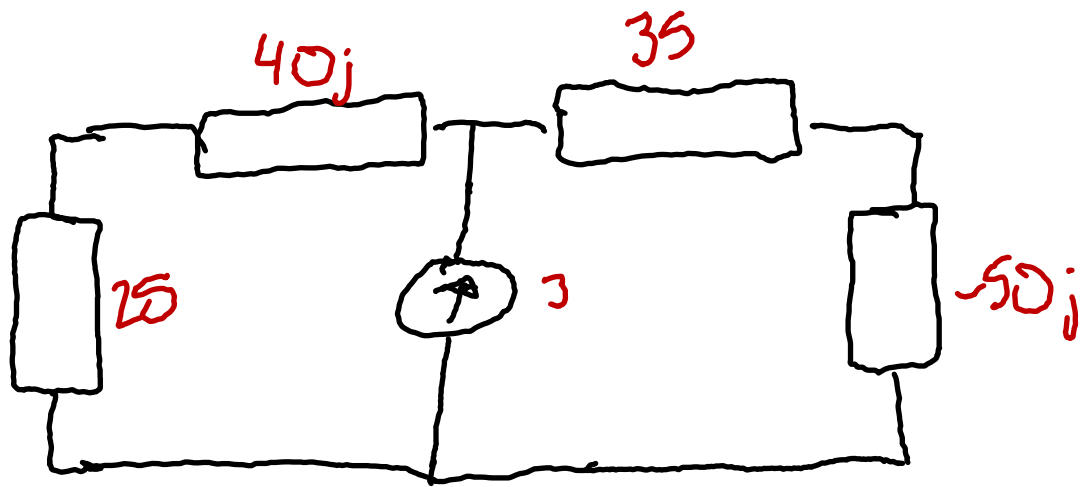

$$V_{TH} = -50j I_1$$

$$Z_{eq} = \frac{(25 + 40j)(35 - 50j)}{60 - 10j}$$

$$I_1 = \frac{Z_{eq}}{R_1} \cdot I_s$$

$$= \frac{25 + 40j}{60 - 10j} \cdot 3 = 2.326 \angle 67.45^\circ$$

$$V_{TH} = -50j ($$





- Determine the complex power, apparent power, average power absorbed, reactive power, and power factor for a load circuit whose voltage and current at its input terminals are given by:
  - $v(t) = 100\cos(377t - 30^\circ) V$ ,  $i(t) = 2.5\cos(377t - 60^\circ) A$ .
  - $v(t) = 25 \cos(2\pi \times 10^3 t + 40^\circ) V$ ,  
 $i(t) = 0.2 \cos(2\pi \times 10^3 t - 10^\circ) A$ .
  - $V = 110 \angle 60^\circ V$ ,  $I = 3 \angle 45^\circ A$ .
  - $V = 440 \angle 0^\circ V$ ,  $I = 0.5 \angle 75^\circ A$ .



- In the circuit below,  $v(t) = 40 \cos(105t) \text{ V}$ ,  $R_1 = 100 \Omega$ ,  $R_2 = 500 \Omega$ ,  $C = 0.1 \mu\text{F}$ , and  $L = 0.5 \text{ mH}$ . Determine the complex power for each passive element, and verify that conservation of energy is satisfied.

