

When is it filtering enough??

$$P_{out} < \frac{1}{2} P_{in}$$

Corner frequency or half-power frequency is the point where more signal is being filtered out than let through.


$$V_{out}^2 < \frac{1}{2} V_{in}^2$$

$$\frac{V_{out}^2}{V_{in}^2} < \frac{1}{2}$$

$$\frac{V_{out}}{V_{in}} < \frac{1}{\sqrt{2}}$$

$$\left. \frac{V_{out}}{V_{in}} \right|_{dB} < 20 \log_{10} \left(\frac{1}{\sqrt{2}} \right) < -3dB$$

LPF

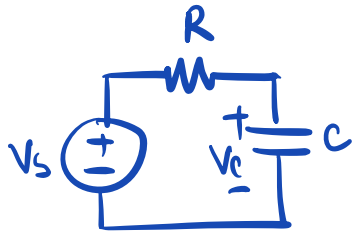

$$\frac{V_c}{V_s} = \frac{1}{1 + j\omega CR}$$

$$\left| \frac{V_c}{V_s} \right| = \frac{1}{\sqrt{1 + (\omega CR)^2}} < \frac{1}{\sqrt{2}}$$

$$\sqrt{2} < \sqrt{1 + (\omega CR)^2}$$

$$2 < 1 + (\omega CR)^2$$

$$1 < (\omega CR)^2$$

$$1 < \omega CR$$

all 1st order
RC circuits

$$\left[\frac{1}{CR} < \omega \right]$$

$$\omega_c = \frac{1}{CR}$$



Poles: are values that make
your denominator = 0

$$\frac{1}{1+x} \rightarrow x+1=0 \Rightarrow x=-1 \leftarrow \text{pole}$$

Zeros: are values that make
your numerator = 0

$$\frac{x}{1+x} \rightarrow x=0 \leftarrow \text{zero}$$

$$\frac{1}{x^2 + 2x + 4} \quad \begin{cases} \text{zeros} = \text{none} \\ x^2 + 2x + 4 = 0 \end{cases}$$

quadratic equation

$$\frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

HPF $\frac{j\omega CR}{1 + j\omega CR}$

\rightarrow zeros $\cancel{j\omega CR} = 0$
 $x = 0 \leftarrow 1 \text{ zero}$

\hookrightarrow poles $1 + \cancel{j\omega CR} = 0$
 $x CR = -1$
 $x = -\frac{1}{CR}$

$j\omega = x$

LPF $\frac{1}{1 + j\omega CR}$

\rightarrow zeros = none

\hookrightarrow poles $\Rightarrow 1 + \cancel{j\omega CR} = 0$
 $x CR = -1$
 $x = -\frac{1}{CR} \leftarrow \text{cut off frequency.}$

$1 + \frac{j\omega}{\omega_c}$
 $\leftarrow \text{cut off frequency.}$

$$\cancel{x} + j\omega CR = \cancel{x} + \frac{j\omega}{\omega_c}$$

$$\cancel{j\omega CR} = \cancel{j\omega} / \omega_c$$

$$CR = \frac{1}{\omega_c} \Rightarrow \omega_c = \frac{1}{CR}$$



THE OHIO STATE UNIVERSITY

COLLEGE OF ENGINEERING

Bode Plot



- Learning Objectives:
 - Generate magnitude frequency plots for high and low pass-filters.






Sketch a Bode Plot



Simple Transfer Function (constant):

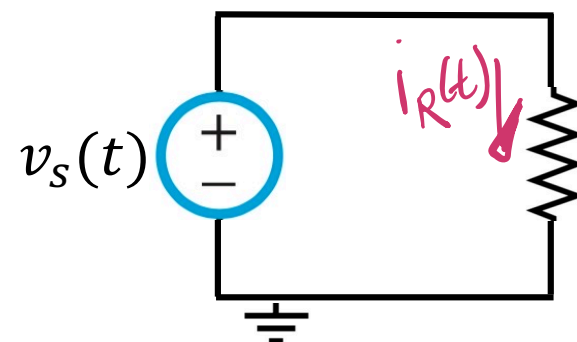- $H(s) = K = \frac{1}{R} \angle 0^\circ$



$$I_R = \frac{V_s}{R}$$

$$\frac{I_R}{V_s} = \frac{1}{R}$$

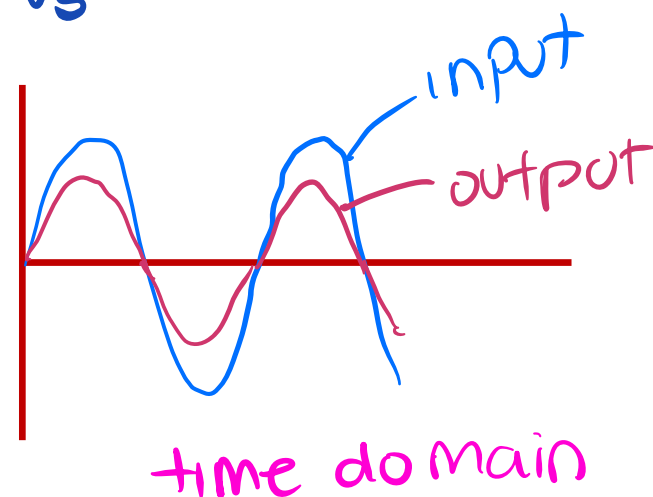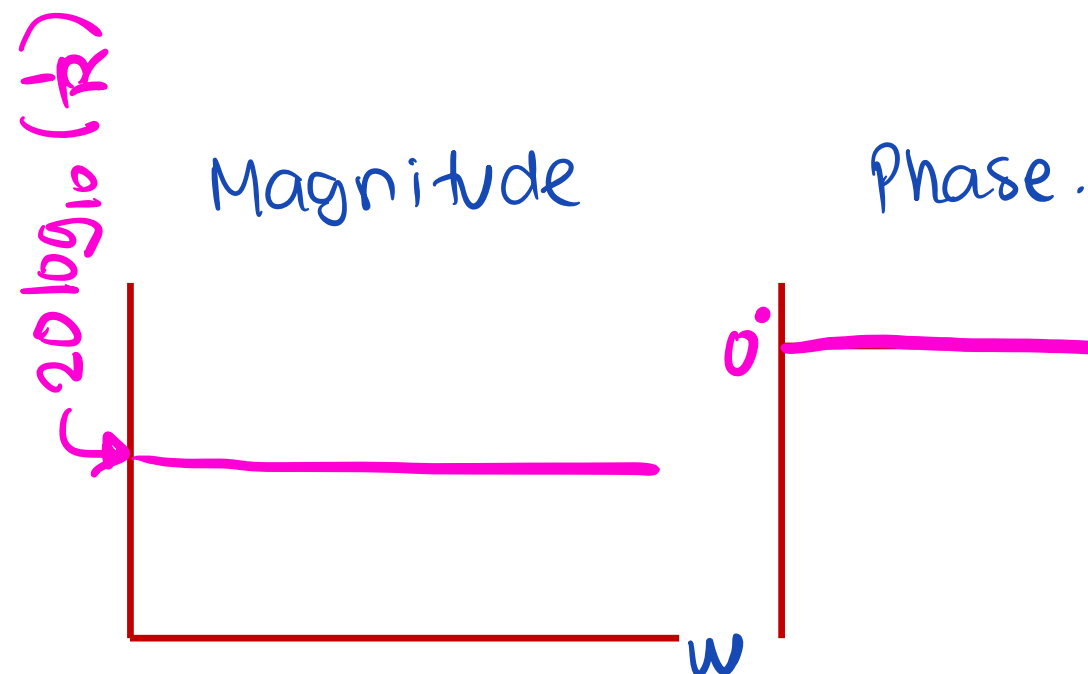







Sketch a Bode Plot

Pole @ the origin:
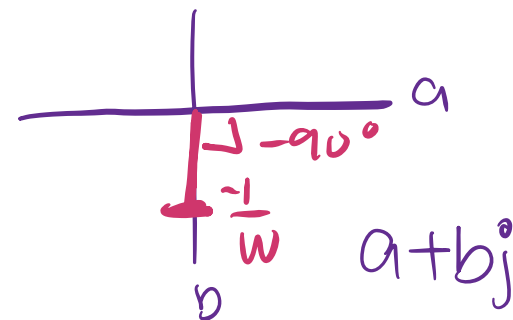
$$\bullet H(s) = \frac{1}{j\omega} = \frac{-j}{\omega} = \frac{1}{\omega} \angle -90^\circ$$


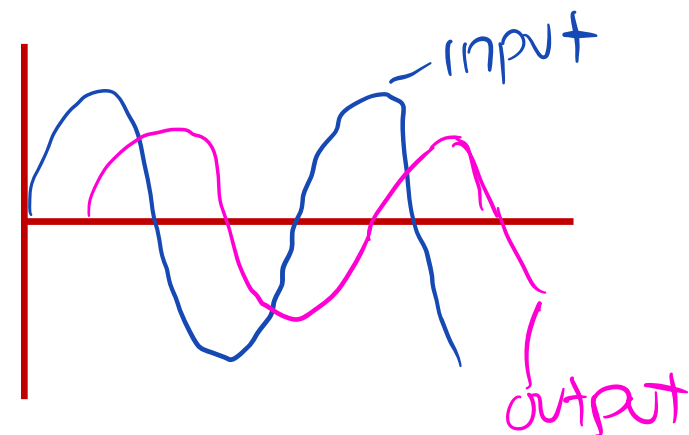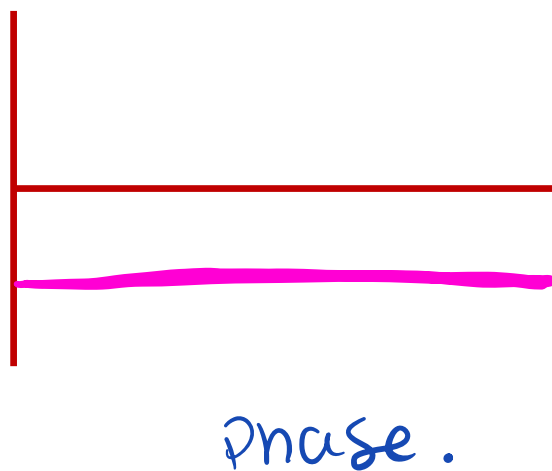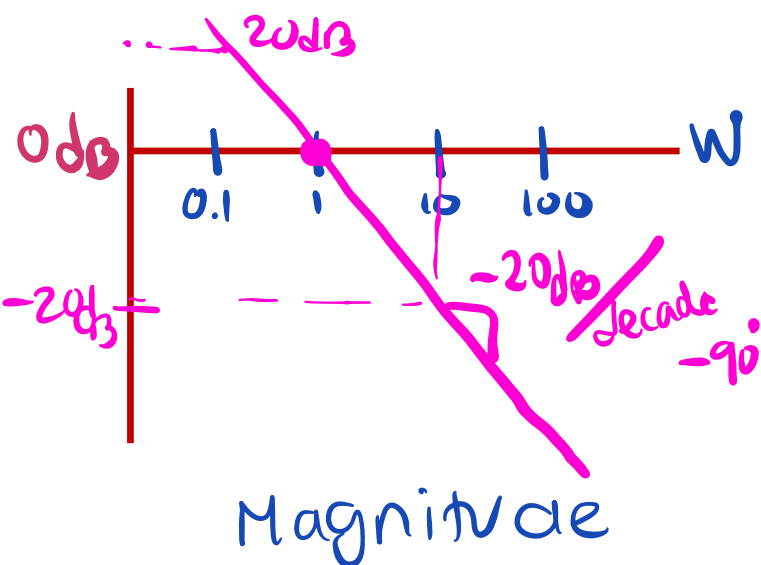
$$20 \log_{10} \left(\frac{1}{\omega} \right) \begin{cases} \nearrow \omega = 0.1 \rightarrow 20 \log_{10}(10) = 20 \text{ dB} \\ \rightarrow \omega = 1 \rightarrow 20 \log_{10}(1) = 0 \text{ dB} \\ \searrow \omega = 10 \rightarrow 20 \log_{10}(0.1) = -20 \text{ dB} \end{cases}$$






Pole @ the origin:

$$H(s) = \frac{K}{j\omega} = K \cdot \frac{1}{j\omega}$$

Annotations: A pink arrow points from the K to a circled 1. A blue arrow points from the $\frac{1}{j\omega}$ to a circled 2.

$$G(s) = \frac{K}{(j\omega)^2} = K \cdot \frac{1}{j\omega} \cdot \frac{1}{j\omega}$$

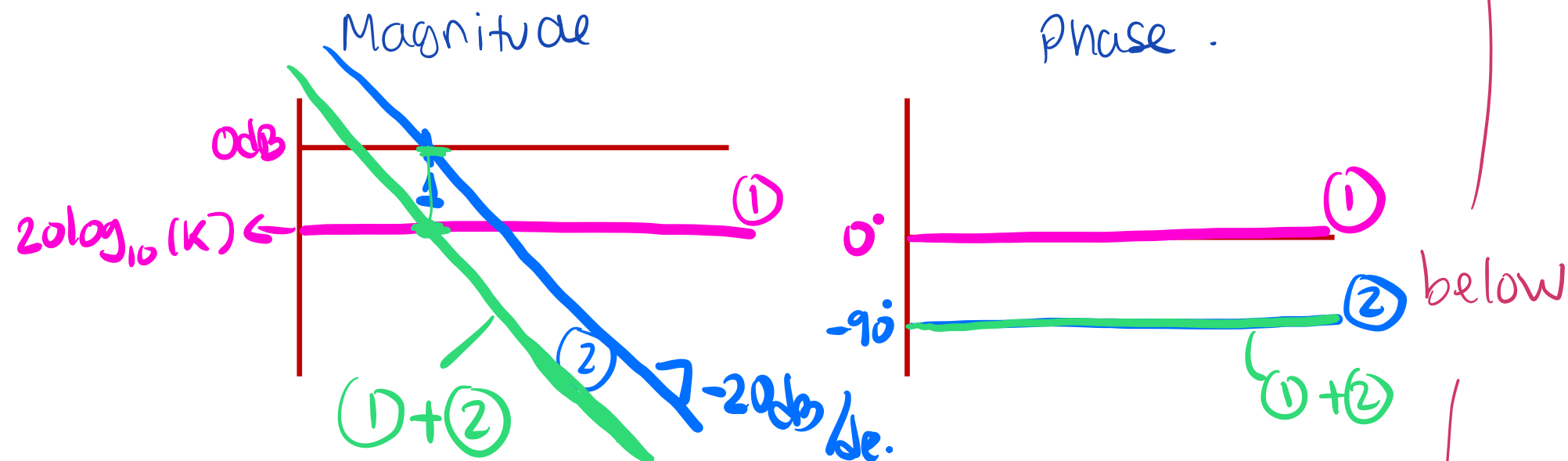Annotation: A pink arrow points from the K to a circled 1. A blue arrow points from the $\frac{1}{j\omega}$ to a circled 2.



$$z_1 = A \angle \alpha \quad z_2 = B \angle \beta$$

$$P(s) = z_1 z_2 = \underbrace{AB}_{\text{magnitude}} \underbrace{\angle \alpha + \beta}_{\text{phase}}$$

$$20 \log_{10} (A \cdot B) = 20 \log_{10} (A) + 20 \log_{10} (B)$$

