

Use the 3 to 8 decoder with inverting outputs shown below, along with NAND gates, to implement the following functions:

$$F(A, B, C) = \sum m(0, 2, 5)$$

$$G(A, B, C) = \sum m(0, 4, 5, 6)$$

