ECE2060 (9487) Homework Problem 9-4 Due 11:25am M 2/27

Complete a PLA table for implementing the following expressions.

$$F(A,B,C) = \sum m(3,4,5)$$
$$G(A,B,C) = \sum m(3,4,5,7)$$

$$G(A, B, C) = \sum m(3,4,5,7)$$

Then draw the corresponding PLA structure diagram with dots (not Xs) marked at the appropriate intersections in the AND-array and OR-array.