
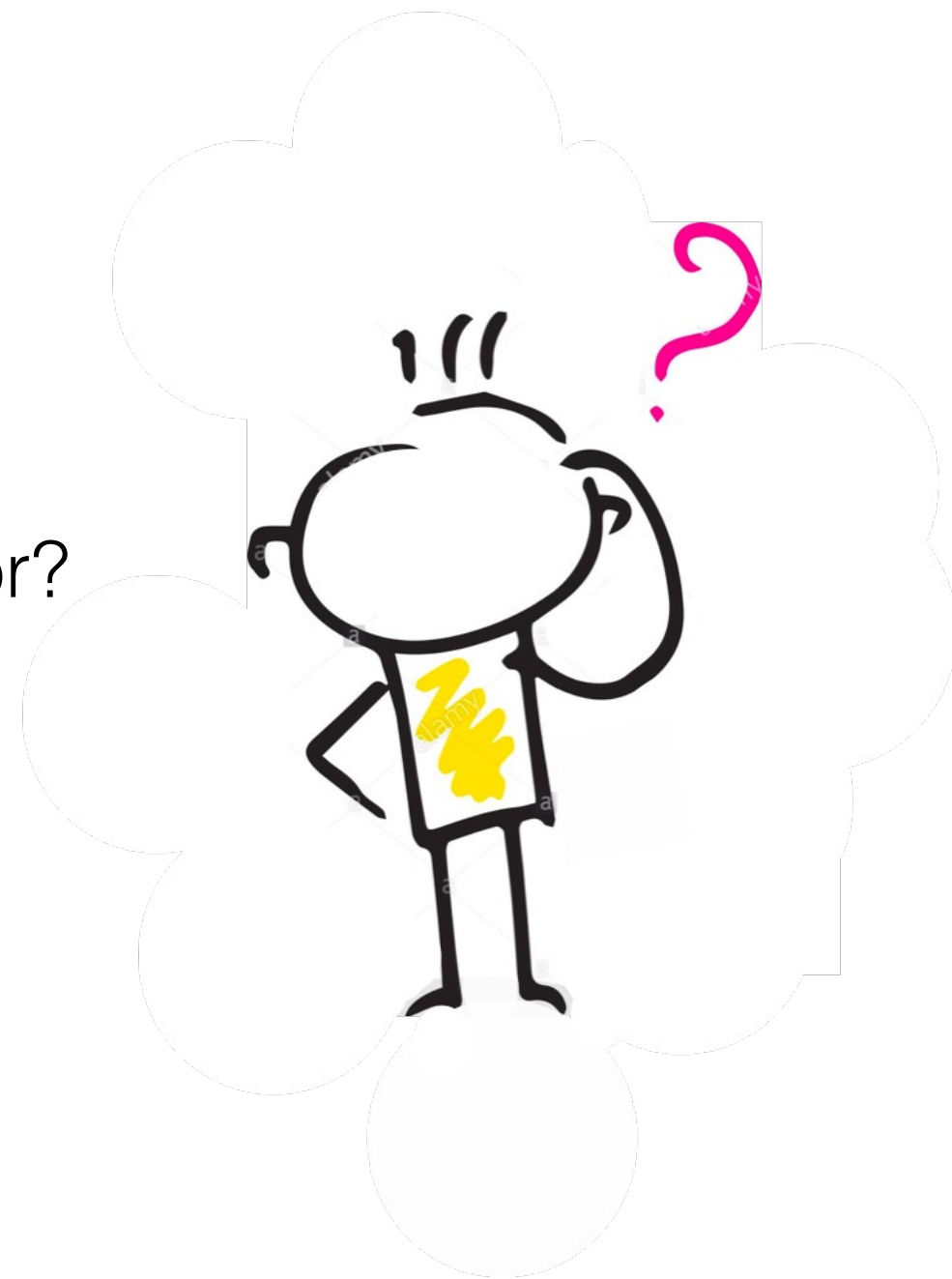


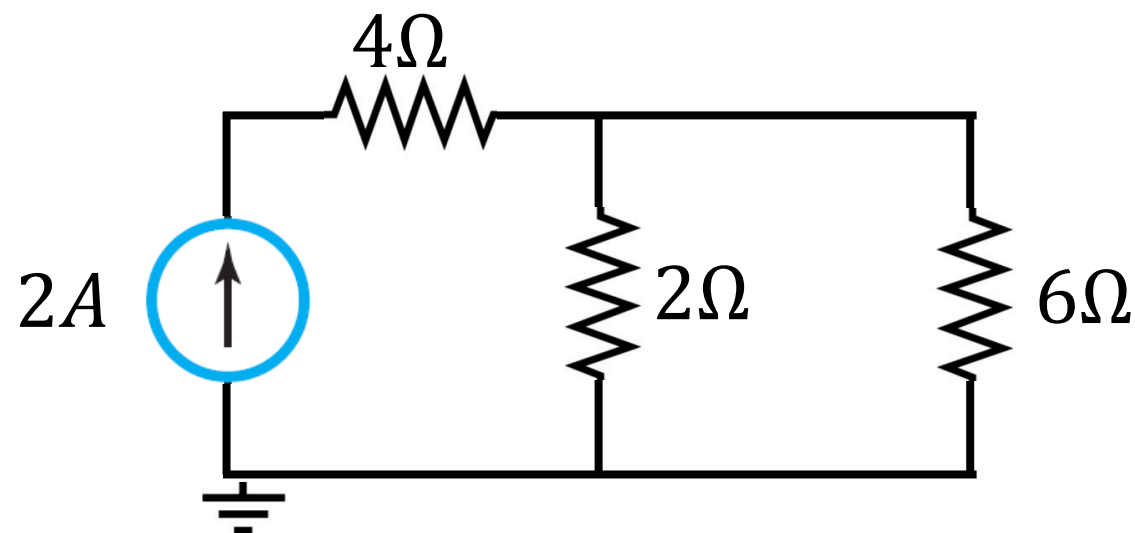

1. What is a voltage divider and what is a current divider?

2. What is the current across the 2Ω resistor?






THE OHIO STATE UNIVERSITY

COLLEGE OF ENGINEERING

Node Voltage Analysis




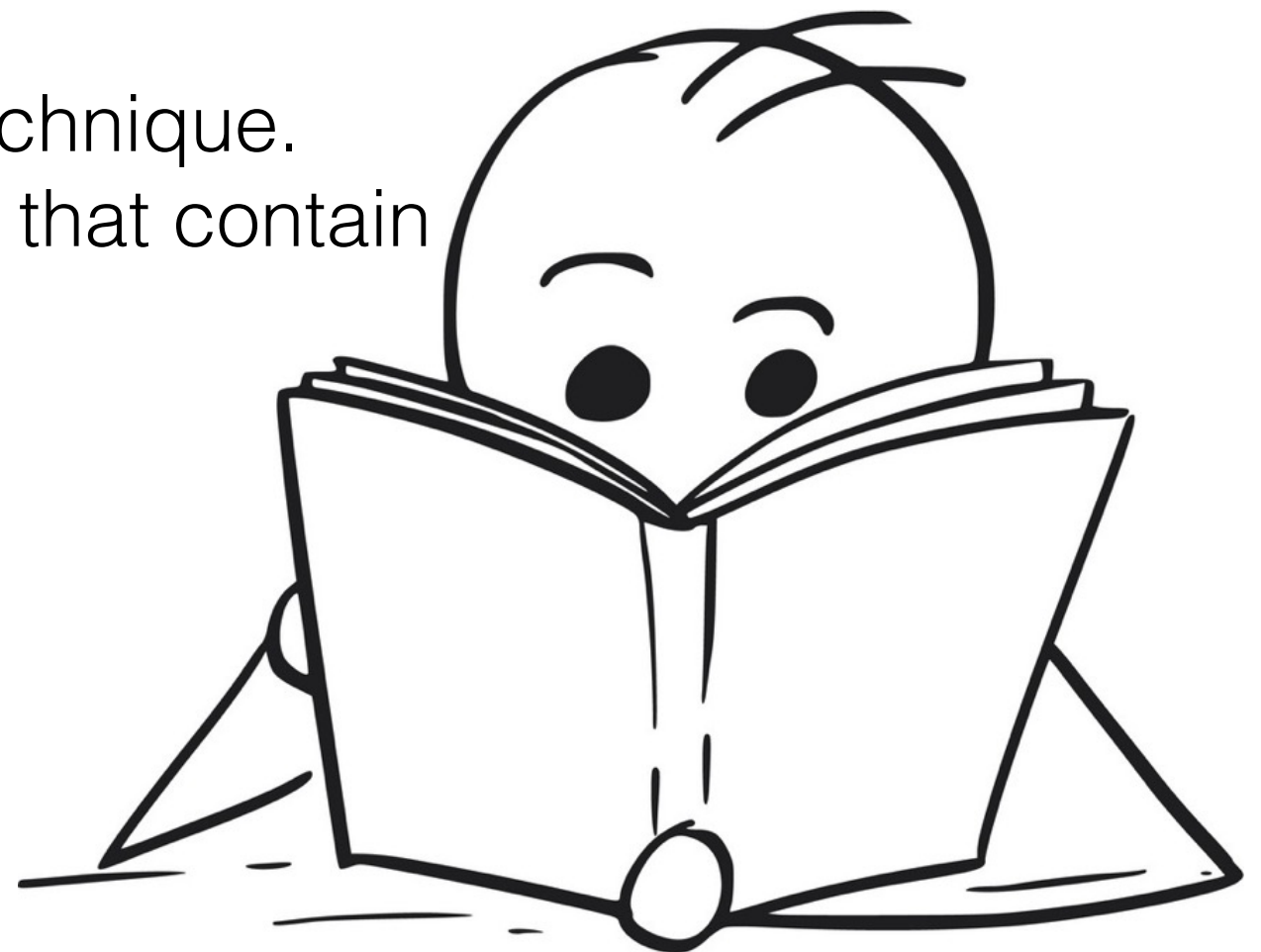
- Learning Objectives:
 - Apply the node-voltage analysis technique to linear electric circuits.
 - Identify a super-node.
 - Apply the node-voltage technique to analyze electric circuits that contain super-nodes.






Node Voltage Method

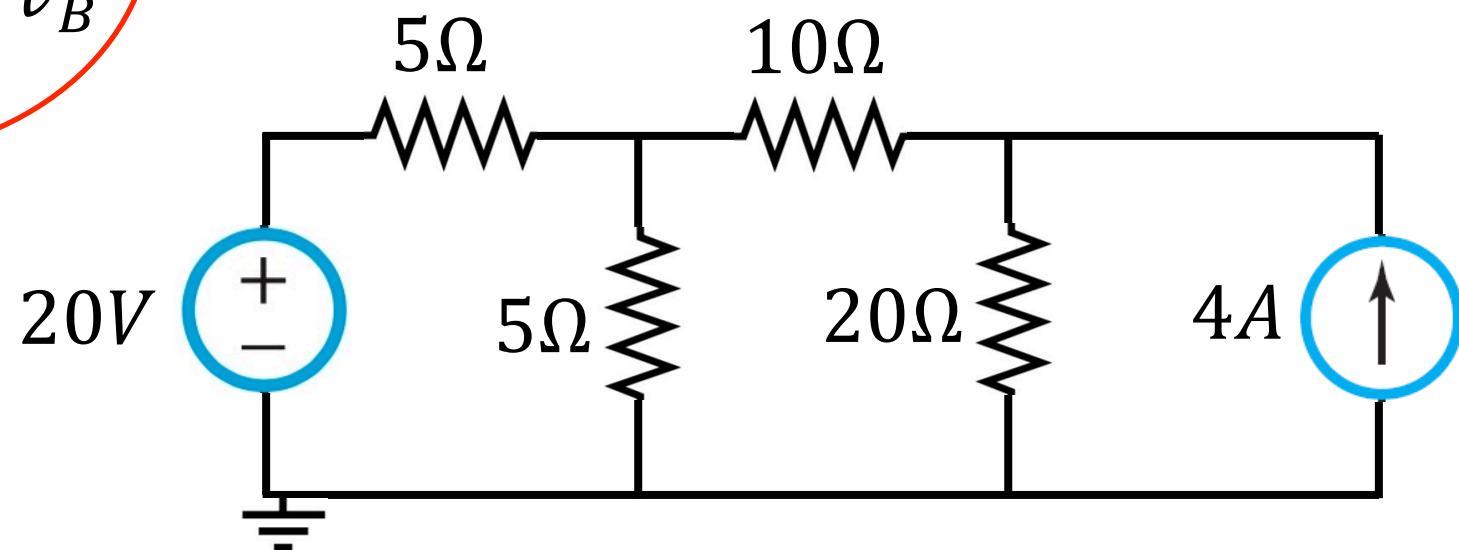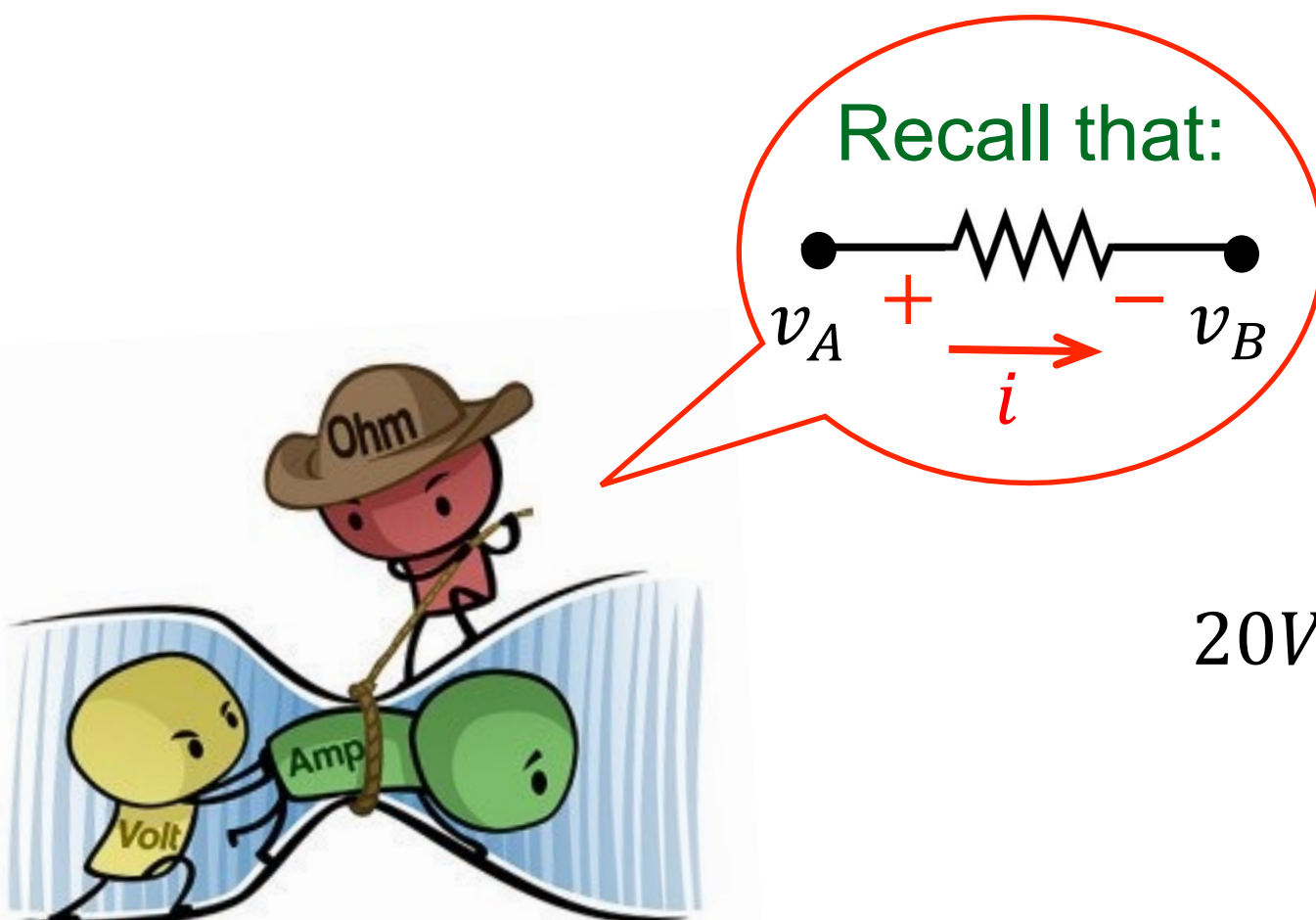1. Identify how many nodes there are and assign variables to each of them. Mainly used to solve for node voltages.
2. Select a reference node.
3. Identify if the voltage on any of the nodes is known.
4. Assume a direction for the current on each of the elements.






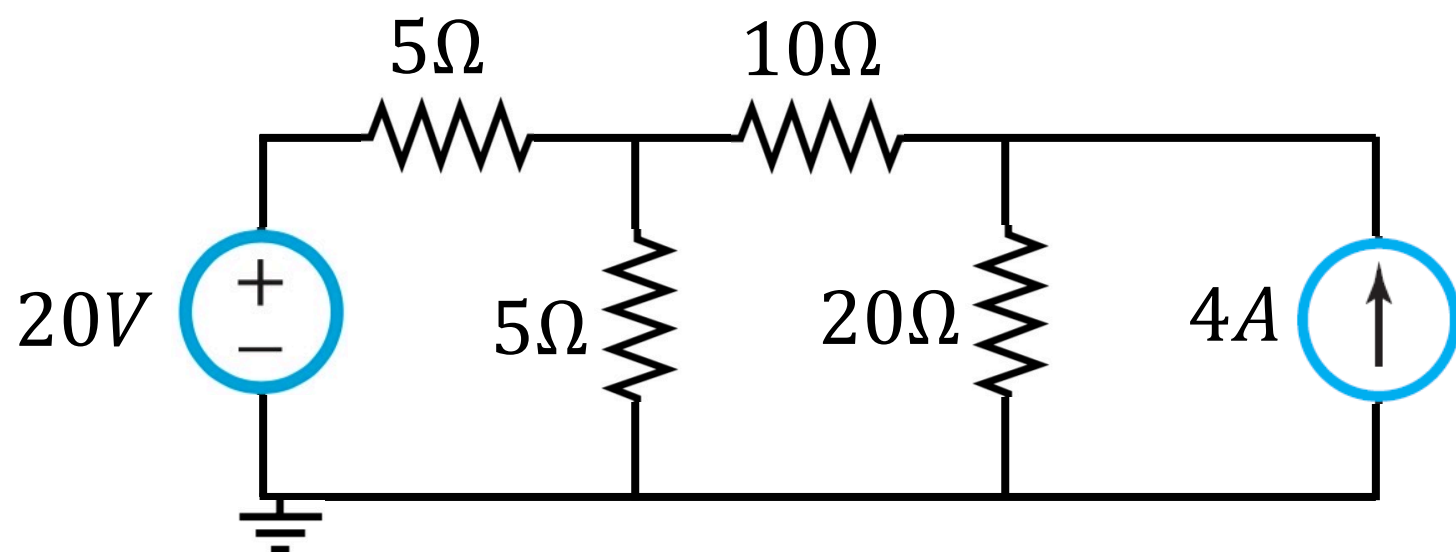1. Identify how many nodes there are and assign variables to each of them.
2. Select a reference node.
3. Identify if the voltage on any of the nodes is known.
4. Assume a direction for the current on each of the elements.
5. Apply KCL to all remaining nodes.
6. Solve.






- Non-grounded voltage source.

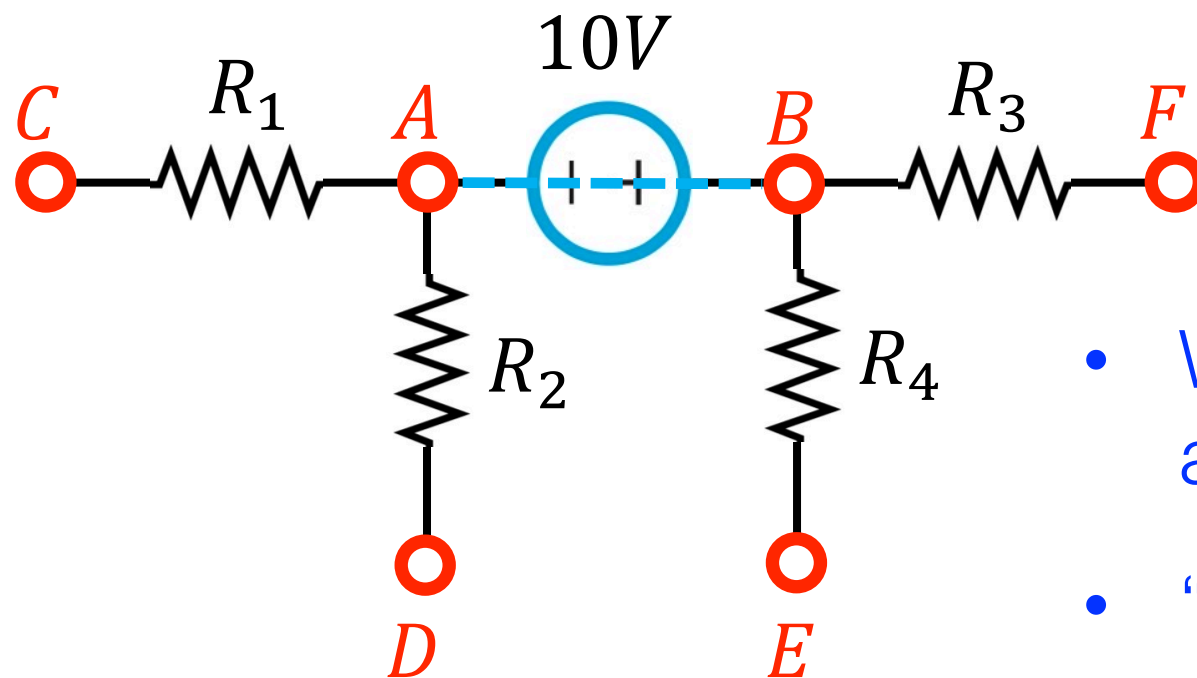

- We do not know the current flowing across the voltage source.
- “Remove the voltage source.”



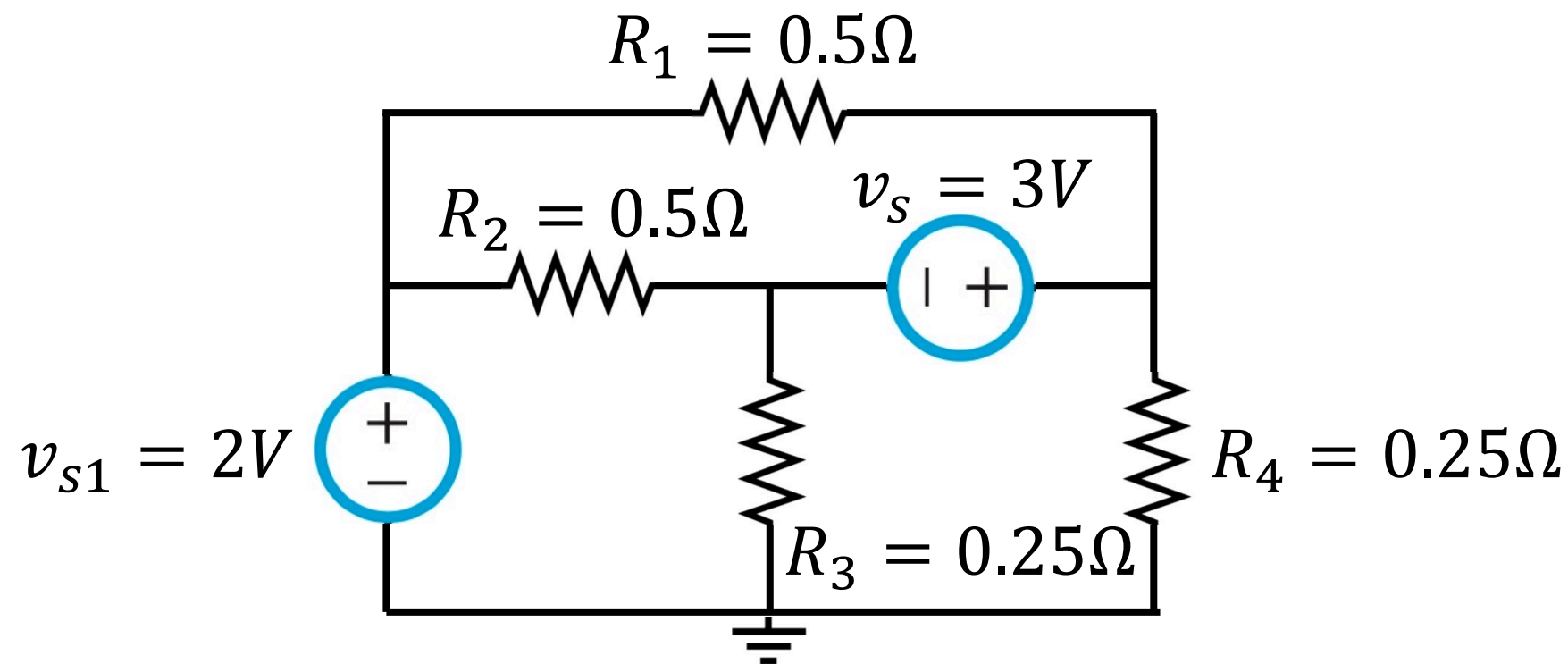Using node voltage analysis, find the voltage across R_4 .



$$V_D = 0V$$

$$2 = V_A - V_D$$

$$V_A = 2V$$

Auxiliary Equation

$$3 = V_C - V_B$$

KCL @ Super Node

$$i_2 = i_3 + i_4 + i_1$$

KCL @ super node

$$2 - V_B = 2V_B + 2V_C + V_C - 2$$

$$4 = 3V_B + 3V_C$$

$$V_1$$

$$V_2$$

$$V_3$$

$$V_4 = V_C - V_D = V_C$$

$$4 = 3(V_C - 3) + 3V_C$$

↓

$$13 = 6V_C$$

$$V_C = \frac{13}{6} V$$

Aux Eq.

$$3 = V_C - V_B$$

$$V_B = V_C - 3$$