



Find  $f(t)$

$$F(s) = \frac{4}{(s+1)(s+2)^2}$$

$$\downarrow$$
$$s_1 = -1$$

$$\downarrow$$
$$s_2 = -2$$
$$s_3 = -2$$

$$F(s) = \frac{A}{s+1} + \frac{B}{s+2} + \frac{C}{(s+2)^2}$$

$$A = F(s) \cdot (s+1) \Big|_{s=-1}$$

$$= \frac{4}{(s+2)^2} \Big|_{s=-1}$$

$$= \frac{4}{1} = 4$$

$$A = 4$$

$$C = F(s) \cdot (s+2)^2 \Big|_{s=-2}$$

$$= \frac{4}{s+1}$$

$$= \frac{4}{-1} = -4$$

$$C = -4$$



$$F(s) = \frac{4}{s+1} + \frac{B}{s+2} - \frac{4}{(s+2)^2} = \frac{4}{(s+1)(s+2)^2}$$

$$4(s+2)^2 + B(s+1)(s+2) - 4(s+1) = 4$$

$$4(s^2 + 4s + 4) + B(s^2 + 2s + 2) - 4s - 4 = 4$$

$$\underbrace{s^2(4+B)}_{=0} + \underbrace{s(16+2B-4)}_{=0} + \underbrace{16+2B-4}_{=4} = 0s^2 + 0s + 4$$

$$4+B=0 \\ \hookrightarrow B=-4$$

$$F(s) = \frac{4}{s+1} + \frac{-4}{s+2} + \frac{-4}{(s+2)^2}$$

$$F(t) = [4e^{-t} - 4e^{-2t} - 4te^{-2t}] u(t)$$



**THE OHIO STATE UNIVERSITY**

---

COLLEGE OF ENGINEERING

# s-Domain Circuit Elements Model



- Learning Objectives:
  - Use the Laplace transform for circuit analysis.



## Phasor Domain

- Cosine
- move  $V_s / i_s \rightarrow$  complex number
- Find impedances
- Solve circuit
- Go back to time domain

## S-Domain

- Laplace transfer  
 $V_s / i_s \rightarrow$  S-Domain
- How capacitors, inductors, resistors look like in S-domain
- Solving circuit using DC analysis
- Partial fraction expansion
- Inverse Laplace transfer to go back to time domain



Time Domain

$$i_c(t) = C \cdot \frac{dv_c(t)}{dt}$$


Frequency Domain

$$I_c(s) = C \left[ sV_c(s) - \underbrace{v_c(0)}_{\text{Initial condition}} \right]$$


$$I_c(s) + CV_c(0) = CSV_c(s)$$

$$V_c(s) = \underbrace{\frac{I_c(s)}{CS}}_{\text{Voltage}} + \underbrace{\frac{\cancel{C}V_c(0)}{\cancel{C}S}}_{\text{Voltage}}$$
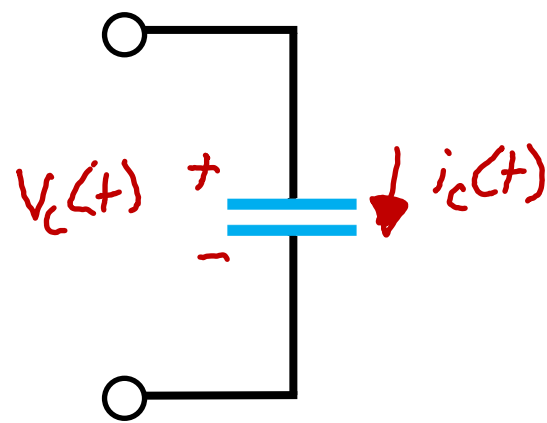
$$= \underbrace{\frac{1}{sC}}_{Z_c(s)} \cdot I_c(s)$$



Capacitor  
in S-Domain

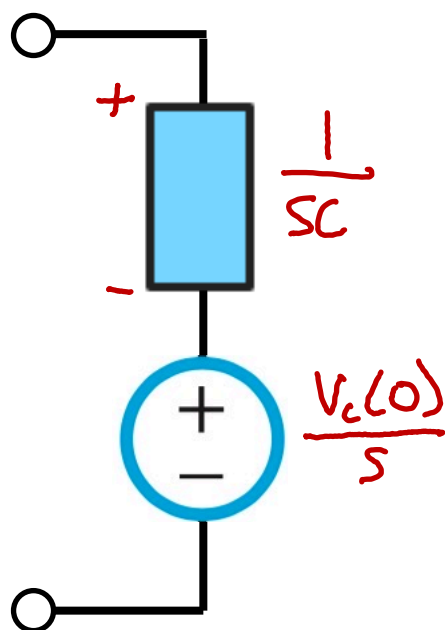



Time Domain

$$V_L(t) = L \cdot \frac{dI_L(t)}{dt}$$



Frequency Domain

$$V_L(s) = L \cdot [sI_L(s) - i_L(0)]$$

$$V_L(s) = \underbrace{LSI_L(s)}_{\text{Voltage}} - \underbrace{Li_L(0)}_{\text{Voltage}}$$

↓


$$\frac{LS \cdot I_L(s)}{I_L(s)} \rightarrow Z_L(s)$$

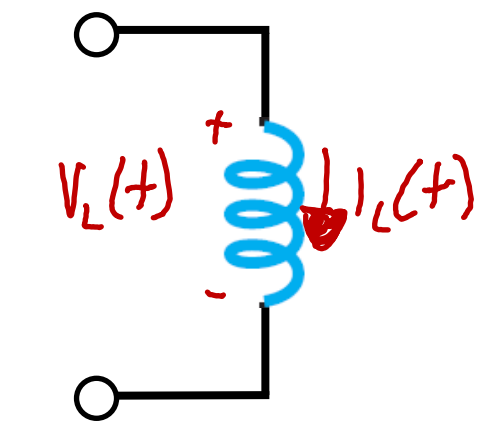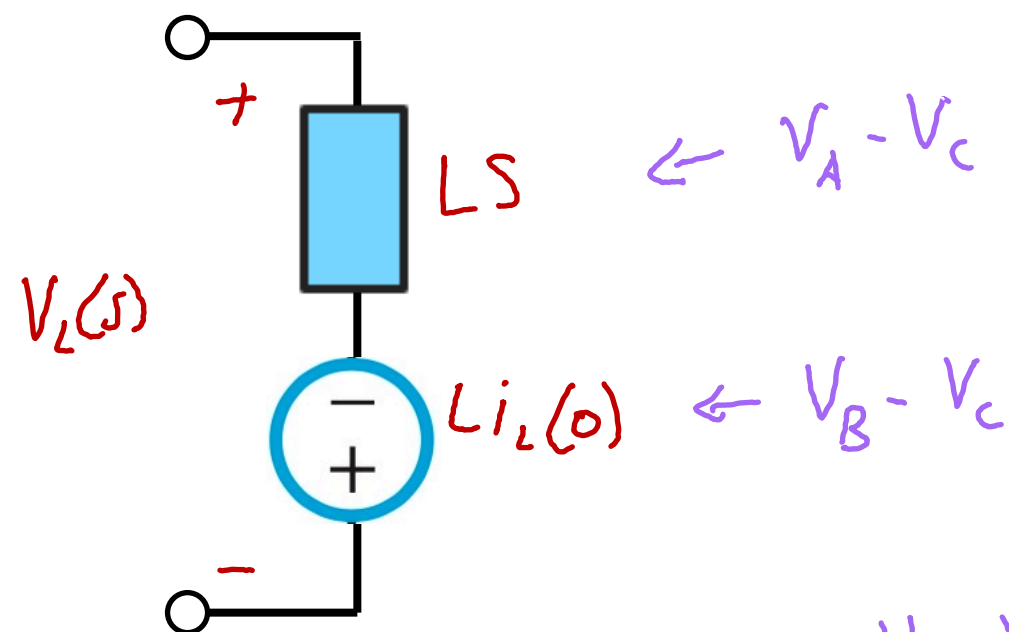Inductor in  
S-Domain


$$V_A - \cancel{V_C} - (V_B - \cancel{V_C}) = V_A - V_B$$




Capacitor

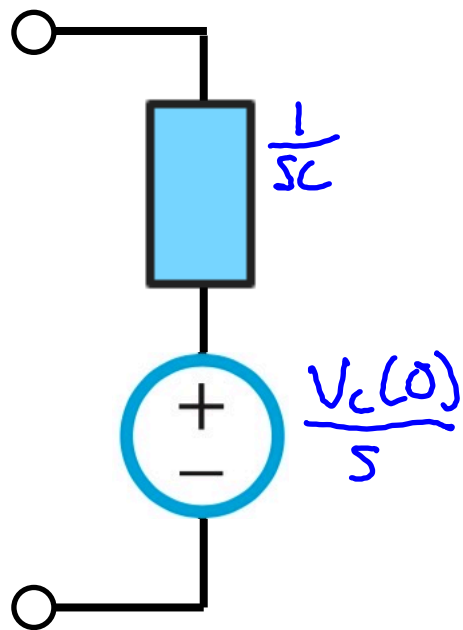


Same thing

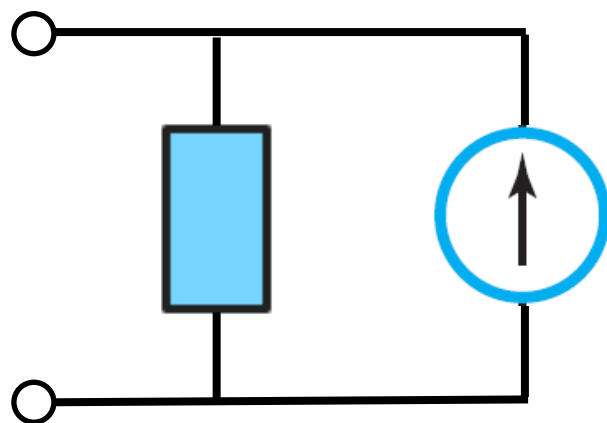



Inductor

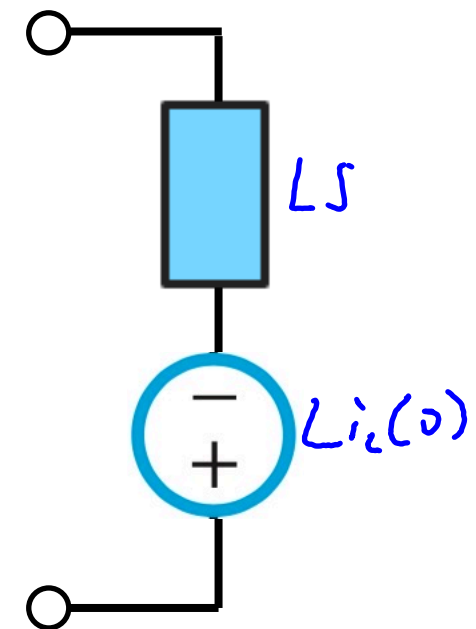

Same thing

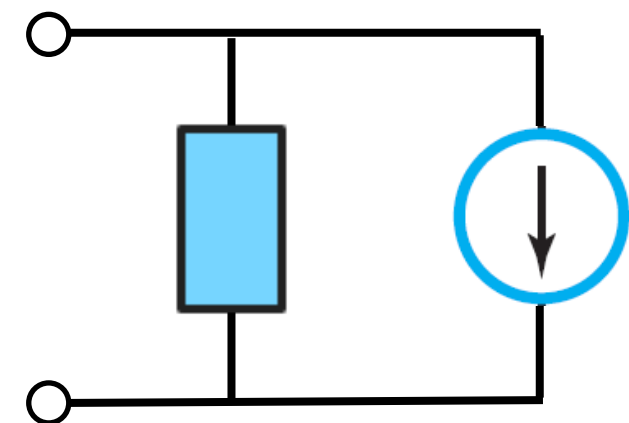




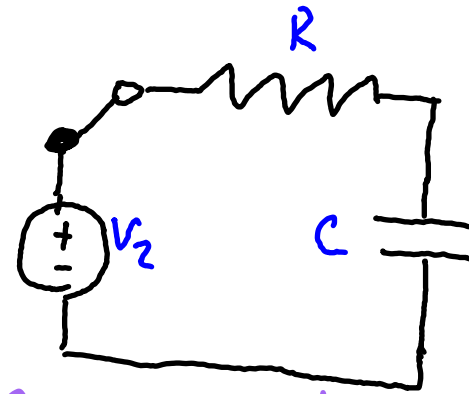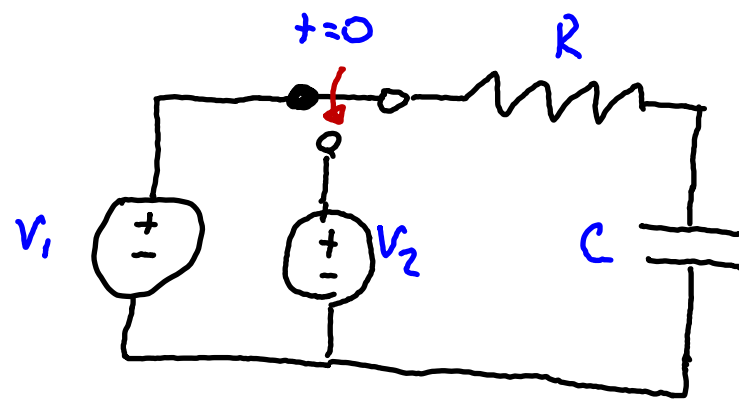

Can only do  
S-domain for  $t > 0$

S-Domain

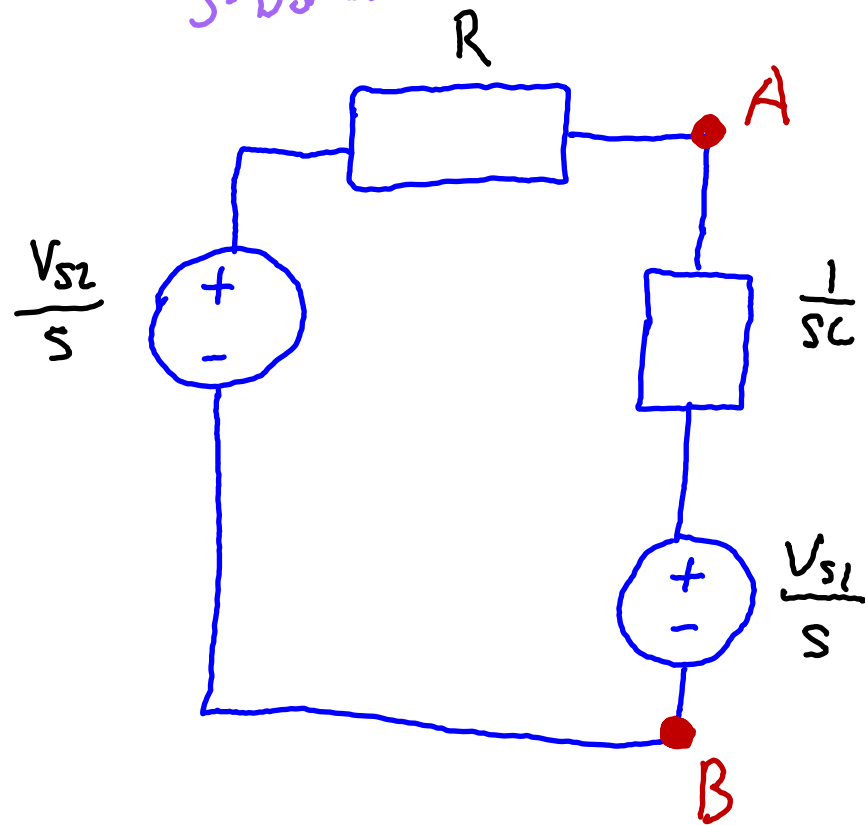

$$V_C(0) = V_{s1}$$