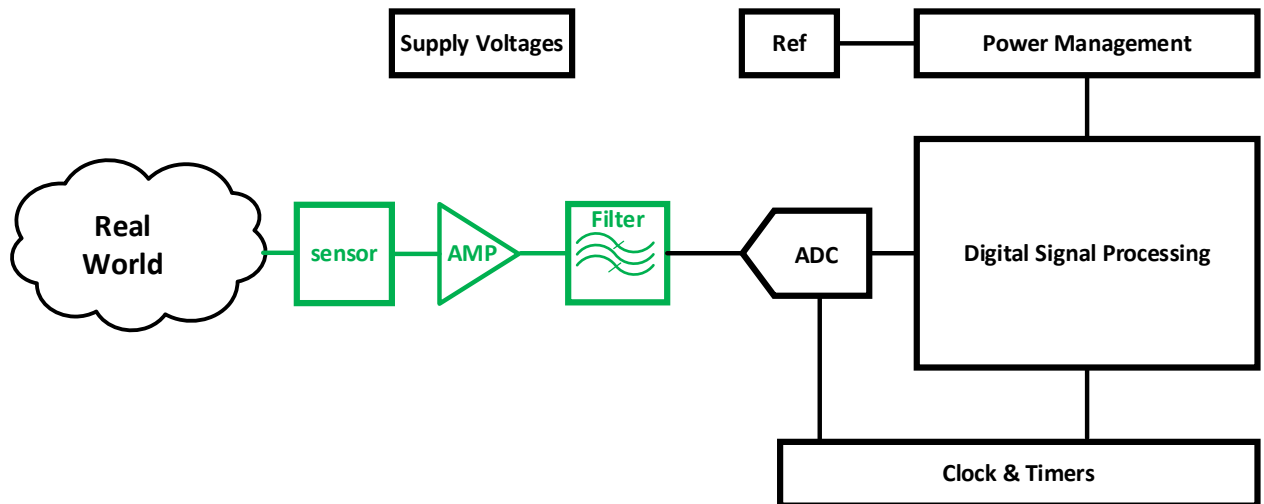


Spring 2024 – ECE 3020


Homework 6

Due: 02/21/2024


1. An electronics design engineer is tasked with building the analog front end (highlighted green) of an ECG system shown below:



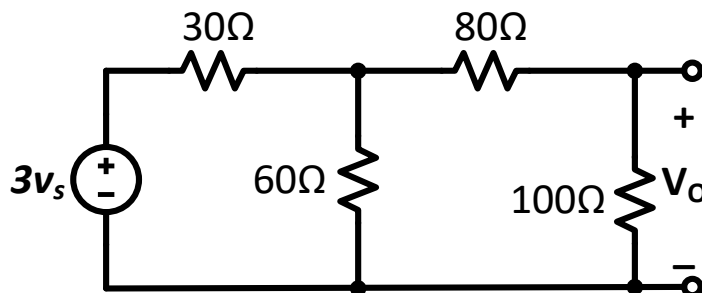
- a. If the sensor interface looks the circuits below, convert it into a Thevenin source.



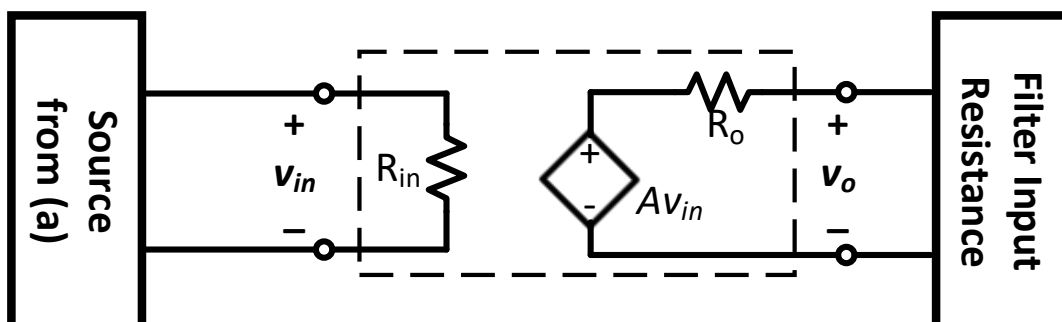- b. Use the Thevenin source derived in a), to source the voltage amplifier model below. Assuming the filter has an input resistance of R_L ($10\text{k}\Omega$), what is the expression for the amplifier gain (v_o/v_s)? What should R_{in} and R_o be for maximum gain?



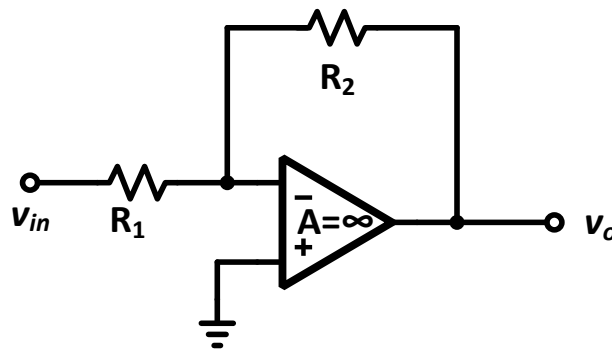- c. Now replace the amplifier model with an inverting op-amp based amplifier. Choose the resistor ratios to obtain a nominal gain of -10V/V . If the loss from the Thevenin source to the inverting amplifier is to be 1%, what should the value of R_1 be?



- d. If the op-amp has an input offset of 3mV , Calculate the output offset.
- e. Now, consider the op-amp having finite gain and bandwidth such that $A = A_0/(1+s/w_p)$. If $A_0 = 1000\text{V/V}$ and $w_p = 2\pi \cdot f_p$ where $f_p = 435.2\text{ Hz}$. What is the new closed-loop gain and bandwidth?
- f. Plot the open-loop and closed-loop gains from (e) using Bode plots. Annotate the DC gains, corner frequencies and unity gain frequencies of the open and closed loop gains?
- g. What is the maximum usable frequency of the analog front-end?